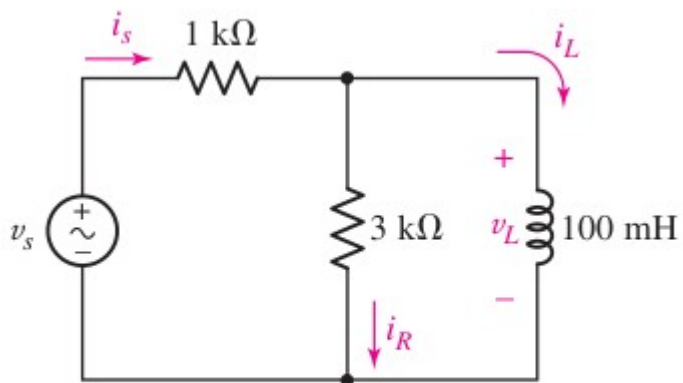


NeSS Tutorial-8


Sinusoidal excitation

Q1. Let $v_s = 40 \cos 8000t$ V in the circuit of Fig. 10.7. Use Thévenin's theorem where it will do the most good, and find the value at $t = 0$ for (a) i_L ; (b) v_L ; (c) i_R ; (d) i_s .



■ FIGURE 10.7

Q2. Find $V_C(t)$ in below figure

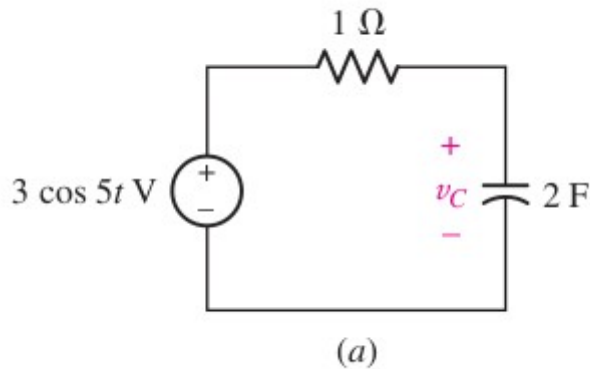

Phasor representation:

Q3. Let $\omega = 2000 \text{ rad/s}$ and $t = 1 \text{ ms}$. Find the instantaneous value of each of the currents given here in phasor form: (a) $j10 \text{ A}$; (b) $20 + j10 \text{ A}$; (c) $20 + j(10/20^\circ) \text{ A}$.

Reactance of R,L and C

Q4. Apply the voltage $8/\underline{-50^\circ}$ V at a frequency $\omega = 100$ rad/s to a 4 H inductor, and determine the phasor current and the time-domain current.

Q5. In the circuit of Fig. 10.17, both sources operate at $\omega = 1$ rad/s. If $I_C = 2/28^\circ$ A and $I_L = 3/53^\circ$ A, calculate (a) I_s ; (b) V_s ; (c) $i_{R1}(t)$.



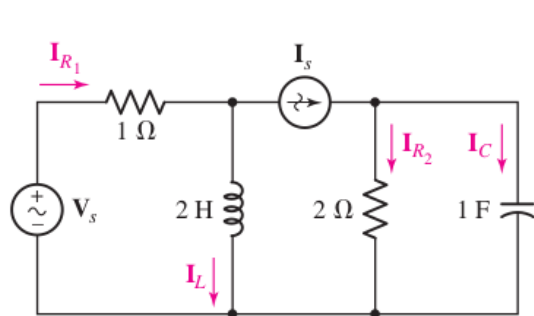


FIGURE 10.17 A three-mesh circuit. Each source operates at the same frequency ω .

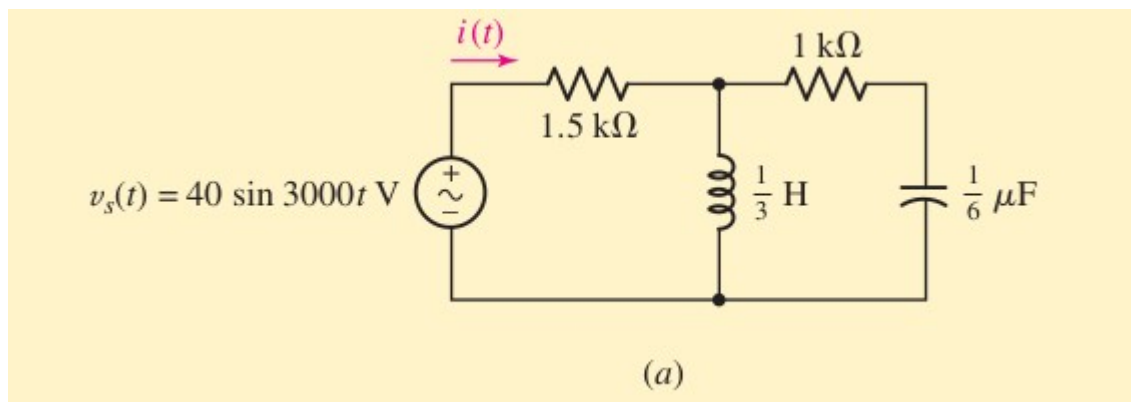Q6. Find the current $i(t)$ in the circuit shown in Fig. 10.20a.




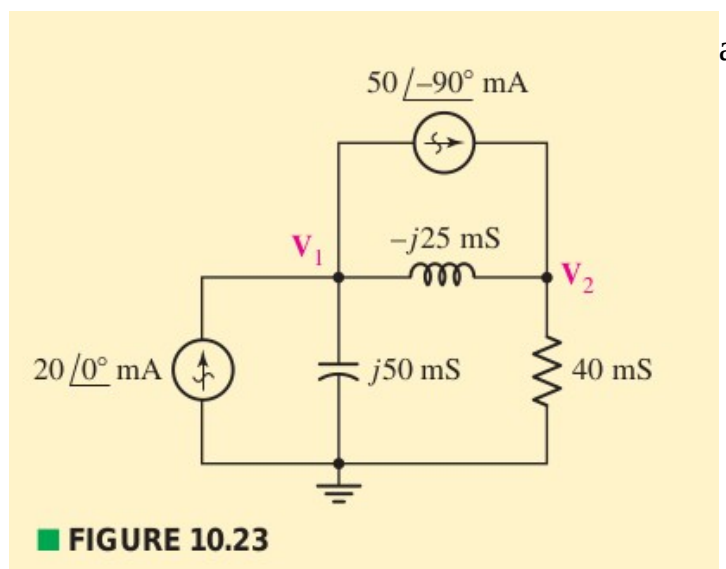Q7. Use nodal analysis on the circuit of Fig. 10.23 to find V_1 and V_2 .



Superposition:

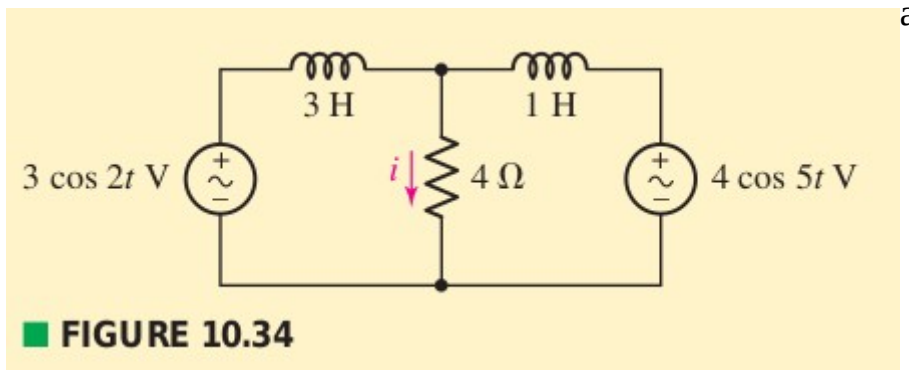Q8. Determine the current i through the 4Ω resistor of Fig. 10.34.



Thevenin, nortal equivalents:

Q9. For the circuit of Fig. 10.32, find the (a) open-circuit voltage V_{ab} ; (b) downward current in a short circuit between a and b ; (c) Thévenin equivalent impedance Z_{ab} in parallel with the current source.

