

Voltage Regulator

Zener Diode Shunt Voltage Regulator

When an ideal diode is reverse biased, it conducts no current. The depletion layer at the reverse biased pn junction acts like an insulator. Like any real insulator, it can suffer breakdown when the applied potential is sufficiently high. A Zener diode has been specially built so that its depletion layer breaks down (safely) at low voltages. At breakdown, the diode presents very little incremental resistance to current flow, and so it can act like a good voltage reference.

Simple Zener Regulator Circuit

The circuit in Figure below maintains $\sim V_Z$ on its output by reverse biasing the Zener diode with $\sim I_Z$ current.

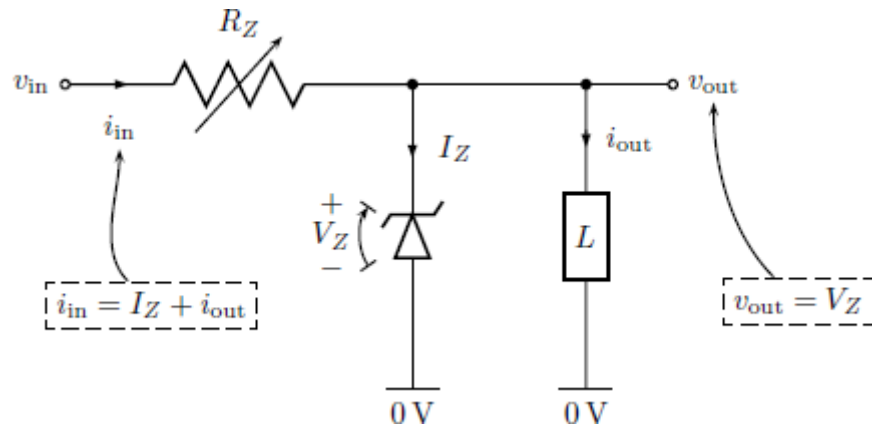


Figure 1: Zener diode shunt voltage regulator with load L.

Typical V_Z , I_Z , and “on” resistance R_{on} for Zener diodes can be noted from datasheet.

The resistor R_Z both biases the Zener diode and limits the output current i_{out} . That is,

$$v_{out} = v_{in} - (I_Z + i_{out})R_Z = v_{in} - \left(I_Z + \frac{v_{out}}{L}\right)R_Z, \dots\dots\dots(1)$$

and so, for $v_{out} = V_Z$, R_Z must be chosen so that

$$R_Z = \frac{v_{in} - V_Z}{I_Z + i_{out}} = \frac{v_{in} - V_Z}{I_Z + \frac{v_{out}}{L}} = \frac{v_{in} - V_Z}{I_Z + \frac{V_Z}{L}} \dots\dots\dots(2)$$


where L is the typical load (e.g., $\sim 10\text{ k}$) and v_{out} is the desired output. As the load L moves off the typical load, the current through the Zener diode will change. A very small L will rob the Zener of so much current that it will move out of its Zener operation range. At that point, the output v_{out} will drop far below V_Z as the circuit reduces to a R_Z -L voltage divider.

Zener Regulator Laboratory Procedure:

1. Design (i.e., choose components for desired output) and build the regulator.
 - Lookup your Zener diode's I_Z and V_Z in the datasheet
 - Using a 4.3V Zener diode will simplify later calculations.
 - Make sure you have the right Zener diode.
 - * Diode part numbers (e.g., 1N5229) are written in very small text that is “word-wrapped” around the outside of the glass diode package. Rotate diode to read the text.
 - Use input $v_{in} = 15V$.
 - Use output $v_{out} = V_Z$.
 - Using equation 2, calculate the R_Z needed to properly bias your Zener diode.
 - Use I_Z from datasheet
 - Assume a typical load of 10 k.
2. Verify proper regulator output, but DO NOT TUNE the regulator.
 - Use a 10 k load.
 - Use your digital multimeter to measure the output.
 - If output is far from expected V_Z , make sure you calculated biasing resistor R_Z correctly.
 - For your report, refer to equation 1 and discuss how R_Z should be changed to tune the output (e.g., increase it or decrease it).
3. With no load (i.e., $L = \infty$, an open circuit), record the i_{in} current measured by the power supply as the no-load quiescent current, which is the additional current required to operate the regulator with no load.

$L(\text{Load})\Omega$	$v_{out}(V)$	$i_{in}(mA)$

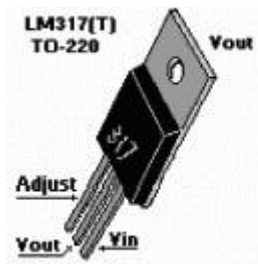
LM317 Adjustable Positive Series Voltage Regulator



The LM317 maintains 1.25V potential difference between its “Out” and “Adjust” pins, and the voltage divider acts as a lever propping V_{out} above the ground reference.

In Figure 2, the (temperature-independent) output is given by
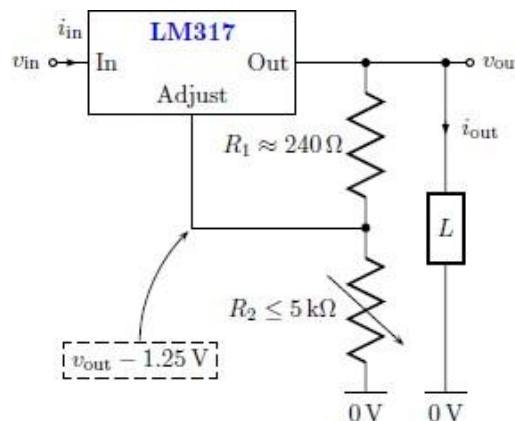
$$v_{out} = (1.25) * \left(1 + \frac{R_2}{R_1}\right) \dots \dots \dots (3)$$



(a) Using variable-resistor divider.

Figure 2: LM317 adjustable series voltage regulator with load L. Use $40V > (v_{in} - v_{out}) > 3V$.


LM317 IC Regulator Laboratory Procedure:

1. Design (i.e., choose components for desired output) and build the regulator in Figure 2(a).
 - RESISTOR VALUES SHOWN in schematics reflect nominal potentiometer sizes.
 - Again, use input $v_{in} = 15V$.
 - Use equation 3 to calculate the proper R_2/R_1 ratio.
 - From Figure 2(a), set $R_1 \approx 240$ and calculate R_2 . Implement R_2 with a variable resistor made from adjacent legs of a 2 k or 5 k potentiometer.
2. Tune regulator output by adjusting the R_1 – R_2 divider (or potentiometer) until measured $v_{out} \approx 10V$.
 - Use a 10k load.
 - Use your digital multimeter (DMM) to measure the output voltage.

3. Use your DMM to measure (and RECORD) the potential between the Output and Adjust pins. What is expected?
4. Vary the load resistance and note the output voltage values.
5. With no load (i.e., $L = \infty$, an open circuit), record the i_{in} current measured by the power supply as the no-load quiescent current, which is the additional current required to operate the regulator with no load.

$L(\text{Load})\Omega$	$v_{out}(V)$

LM7805 Voltage Regulator

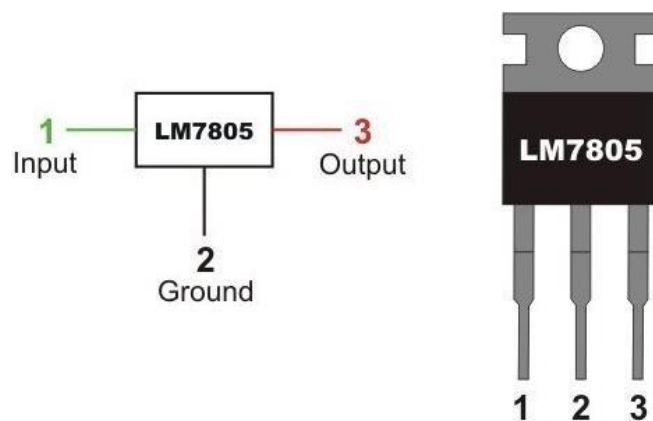

Line Regulation:

Line regulation refers to the ability of a circuit to maintain constant (regulated) output voltage with change in the input voltage.

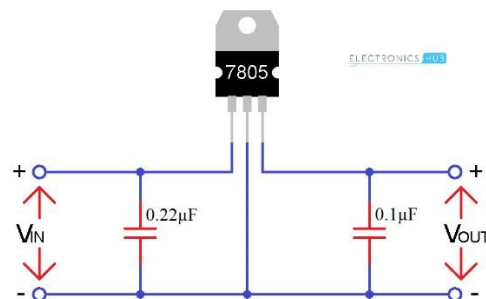


Figure 3: LM7805 voltage regulator

1. Design and build the circuit given in fig 3.
2. Apply a DC input voltage ranging from 0 volts to 15 volts in steps (at least 5) and measure the output voltage using your DMM.
3. Note the results and present them as a table.

V_{in} (v)	V_{out} (v)
...	...
...	...

Load Regulation:

Load regulation refers to the ability of a circuit to maintain constant (regulated) output voltage with change in the load resistance.

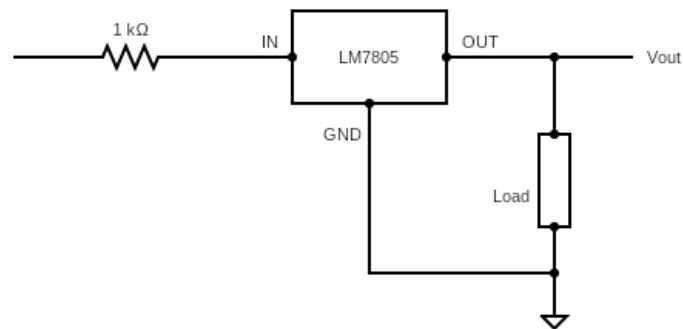


Figure 4: LM7805 voltage regulator

1. Design and build the circuit given in fig 4.
2. Apply a DC input of 15 volts and vary the load resistance in steps (at least 5) and measure the output voltage using your DMM.
3. Note the results and present them as a table.

V_{in} (v)	V_{out} (v)
...	...
...	...