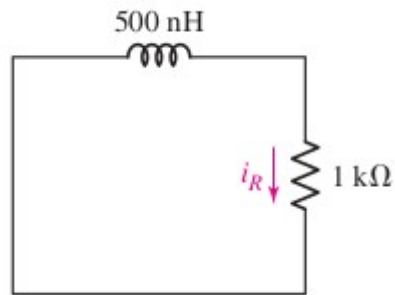



NeSS
Tut-6
RL and RC circuits

RL source free model:

Q1. Determine the current i_R through the resistor of Fig. 8.3 at $t = 1 \text{ ns}$ if $i_R(0) = 6 \text{ A}$.




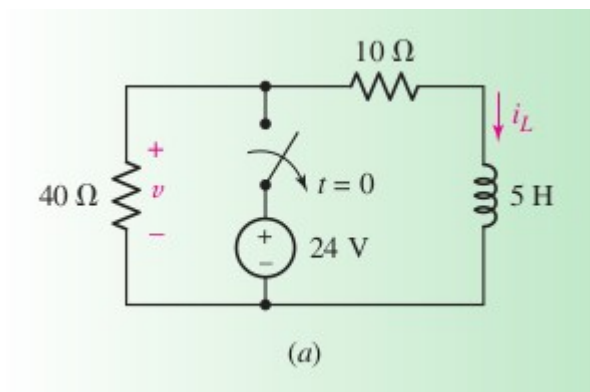Q2. For the circuit of Fig. 8.5a, find the voltage labeled v at $t = 200 \text{ ms}$.




RC source free model:

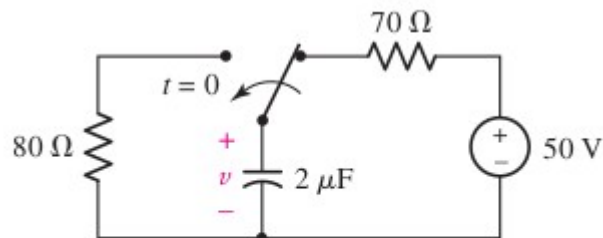Q3. Noting carefully how the circuit changes once the switch in the circuit of Fig. 8.18 is thrown, determine $v(t)$ at $t = 0$ and at $t = 160 \text{ μs}$.




■ FIGURE 8.18

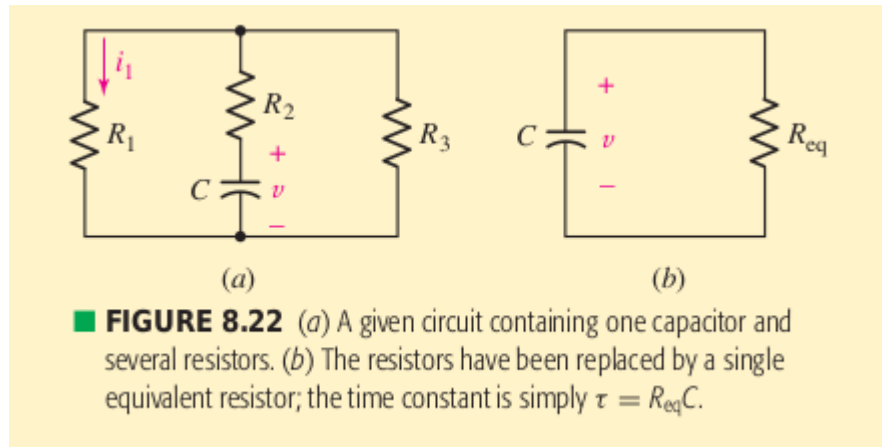Q4. Find $v(0)$ and $i_1(0)$ for the circuit shown in Fig. 8.22a if $v(0) = V_0$.



Driven RC and RL models

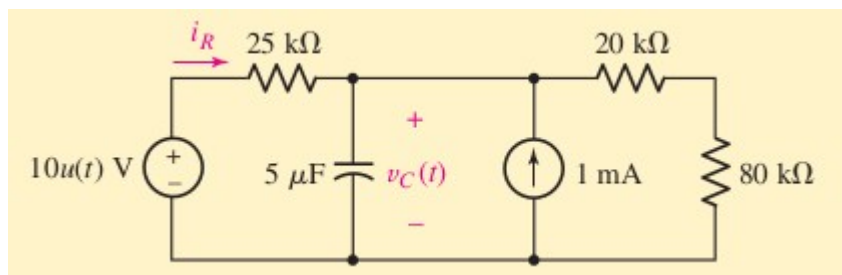Q5. For the circuit of Fig. 8.44, find $v_C(t)$ at t equal to (a) 0^- ; (b) 0^+ ; (c) ∞ ; (d) 0.08 s.



Q6. Determine $i(t)$ for all values of time in the circuit of Fig. 8.37.

