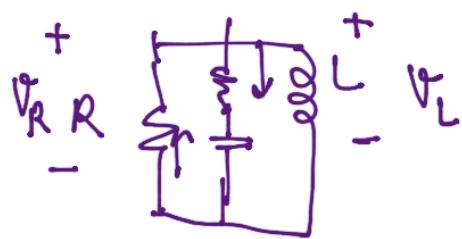


# Chapter 8



$[i, v \rightarrow (t)] \rightarrow$  transient response  
 $[t \rightarrow \infty \quad i_\infty, v_\infty] \rightarrow$  steady state value.

Natural response ( $R, L, C \dots$ )

Response : Natural (source-free) + Forced response (external stimulation  $i, v$ )  
Transient response

Complementary function

(1) Source free R-L

$$KVL \quad -iR + V_L = 0$$

$$\Rightarrow -iR - L \frac{di}{dt} = 0$$


$$\Rightarrow \int_{i_0}^{i(t)} \frac{di}{i} = - \int_{t=0}^t \frac{R}{L} dt$$

$$\left[ \ln i \right]_{i_0}^{i(t)} = -\frac{R}{L} (t - 0)$$

$$\ln \frac{i(t)}{i_0} = -\frac{R}{L} t$$


$i(t) = i_0 e^{-\frac{R}{L} t}$

$$t=1 \quad e^{-R/L}$$

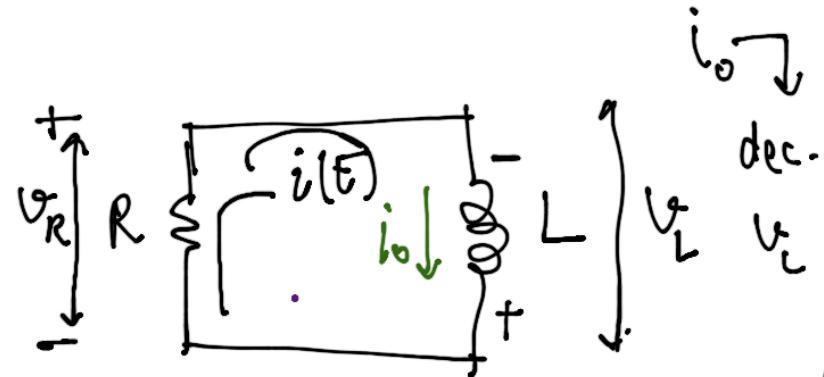

$i(t) \Rightarrow$  instantaneous current.
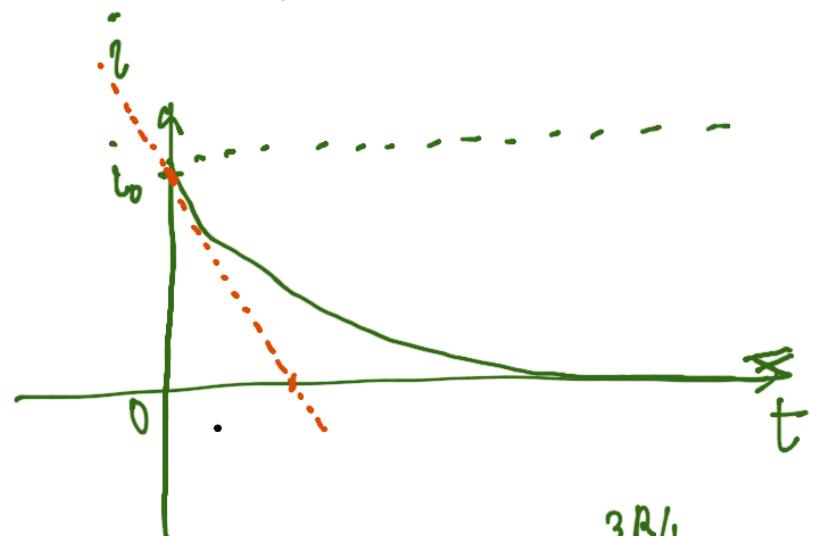
$$i : i(t=0) \xrightarrow{\text{!}} i_0 \xrightarrow{\text{!}} i(t)$$



$$e^{-\infty} = \frac{1}{\infty} \rightarrow 0$$

Another form of  
solution.

$$\frac{di}{i} = -\frac{R}{L} dt$$

$$\ln i = -\frac{R}{L} t + \text{constant}$$

$$t=0 \quad i=i_0$$

$$\ln i_0 = \text{constant}$$

$$\ln i = -\frac{R}{L} t + \ln i_0 \Rightarrow i = i_0 e^{-\frac{R}{L} t}$$

General Solution

$v, i \rightarrow$  exponential  $\underbrace{(\sin \omega t + i \cos \omega t)}$   
st

$$\rightarrow i(t) = A e^{st} : \text{general solution}$$

$$\rightarrow \frac{di(t)}{dt} = A s e^{st}$$

$$\left\{ \begin{array}{l} \text{slope for } S = S_1, S_2, \dots \\ A_1, A_2, \dots \end{array} \right.$$

$$\frac{di}{dt} = -\frac{R}{L} \dot{i}(t)$$

$$sA e^{st} = -\frac{R}{L} A e^{st}$$

$$sA = -\frac{R}{L} A$$

$$\text{Solution : } s_1 = -\frac{R}{L}$$

$$i(t) = A e^{-\frac{R}{L} t} \quad : \text{ general solution.}$$

$i(t=0) \rightarrow \text{solve for } A$

General case.

$$f = A e^{st}$$

$$f' = A s e^{st}$$

$$a \frac{df}{dt} + bf = 0$$

$$a As e^{st} + b A e^{st} = 0 \Rightarrow As + b = 0$$

$$s = -\frac{b}{A}$$

where  $f$  is changing  
with time

$$\text{Energy} \quad i_L = i_R = i_0 e^{-\frac{R}{L}t}$$

$$P_R(t) = i^2 R = \left( i_0 e^{-\frac{R}{L}t} \right)^2 \cdot R$$


$$P_R(t) = i_0^2 R e^{-\frac{2Rt}{L}}$$

$$\text{Energy}_R = \int_0^t P_R(t) \cdot dt = i_0^2 R \int_0^t e^{-\frac{2Rt}{L}} dt$$

$$= i_0^2 R \left( \frac{1}{-\frac{2R}{L}} \right) \left[ e^{-\frac{2Rt}{L}} \right]_0^t$$

$$= -\frac{1}{2} i_0^2 L \left[ e^{-\frac{2Rt}{L}} - 1 \right]$$
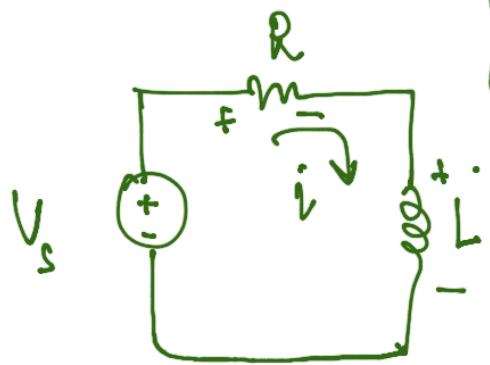
$$t \rightarrow \infty \quad \text{Energy}_R = -\frac{1}{2} i_0^2 L \left( \cancel{\frac{1}{L}} - 1 \right) = \frac{1}{2} i_0^2 L$$



L-R circuit with  $V_s$

$$V_s - iR - V_L = 0$$

$L \rightarrow \infty$  s.c.  $t \rightarrow \infty$

$$V_L = L \frac{di}{dt}$$

$$V_s - iR - L \frac{di}{dt} = 0$$

$$\frac{di}{dt} > 0$$

$$i = A e^{st} \quad (I)$$

$$V_s - iR - L A s e^{st} = 0$$

(II)

$$(V_s - iR) = +L \frac{di}{dt}$$

$$\int \frac{di}{V_s - iR} = + \int \frac{dt}{L} \Rightarrow \left[ \frac{-1}{R} \ln(V_s - iR) \right]_{i_0}^i = + \left[ \frac{t}{L} \right]_0^t$$

$$\Rightarrow \left[ \ln(V_s - iR) \right]_{i_0}^i = - \frac{R}{L} t$$

$$\ln \frac{V_s - iR}{V_s - i_0 R} = - \frac{R}{L} t \Rightarrow \frac{V_s - iR}{V_s - i_0 R} = e^{-\frac{R}{L} t}$$

$$V_s - iR = (V_s - i_0 R) e^{-\frac{R}{L}t}$$

$t = \infty$

~~incorrect response due to incorrect assumption of sign~~

~~$i(t) = \frac{1}{R} (V_s - (V_s - i_0 R) e^{-\frac{R}{L}t})$~~

~~$(V_s - i_0 R) e^{-\frac{R}{L}t}$~~

~~$\oplus$   $Rt/L$~~

~~Blows up. Does not satisfy  $i = \frac{V_s}{R}$~~

$L \rightarrow S.C$

$i_\infty = \boxed{\frac{V_s}{R}} = i_{\max}$

$t \rightarrow \infty$

Checking

$$i(\infty) = \frac{1}{R} V_s \Rightarrow (V_s - i_0 R) e^{\infty} \rightarrow 0$$

$X + V_L$        $i \rightarrow \infty \rightarrow$  we go back to starting equation & change sign of  $V_L$

$i \rightarrow \text{dissipating}$

$i(t) = \frac{1}{R} \left[ V_s - (V_s - i_0 R) e^{-\frac{Rt}{L}} \right]$


if  $i_0 = 0$

$i(t) = \boxed{\frac{V_s}{R} \left( 1 - e^{-\frac{Rt}{L}} \right)}$

$$V_L = L \frac{di}{dt}$$

$$= V_s \cdot \left( 0 + \left( + \frac{R}{L} \right) e^{-\frac{Rt}{L}} \right)$$

$$V_L = V_s e^{-\frac{Rt}{L}}$$

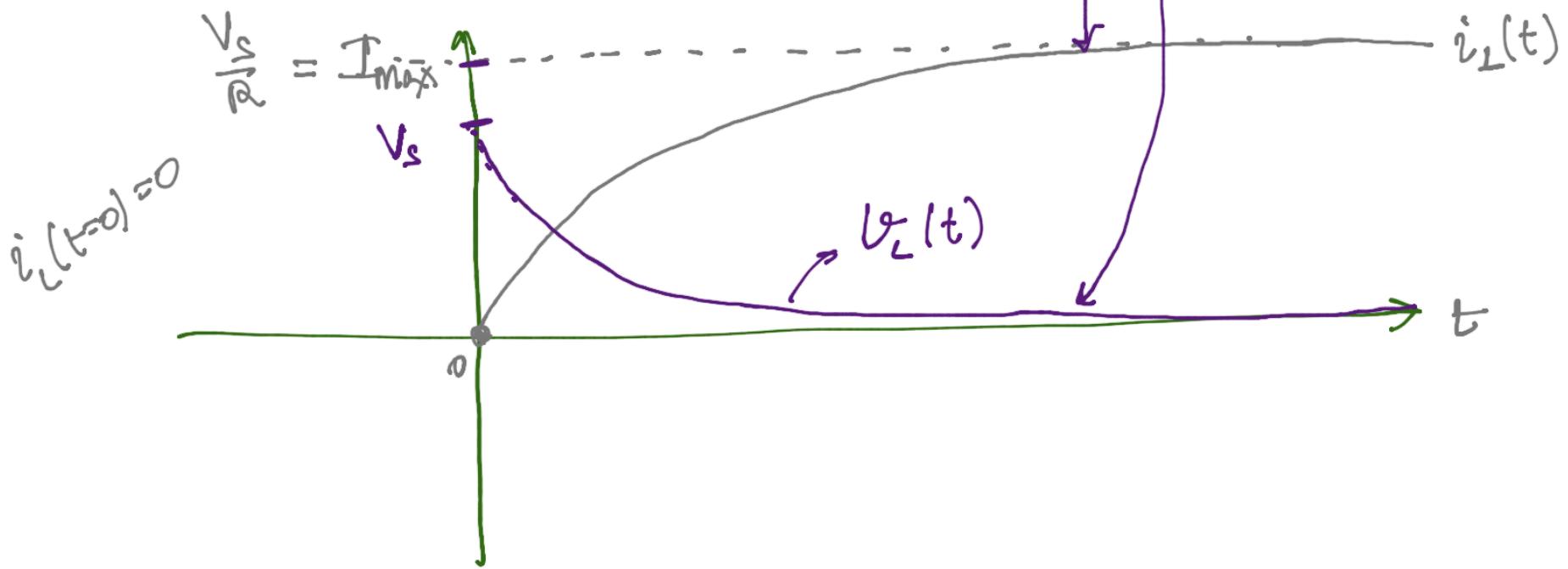



$$i_L = \frac{V_s}{R} \left( 1 - e^{-\frac{Rt}{L}} \right)$$

$$V_L(t) = V_s e^{-\frac{Rt}{L}}$$

Slope at initial point  $t=0$

R-L Series free
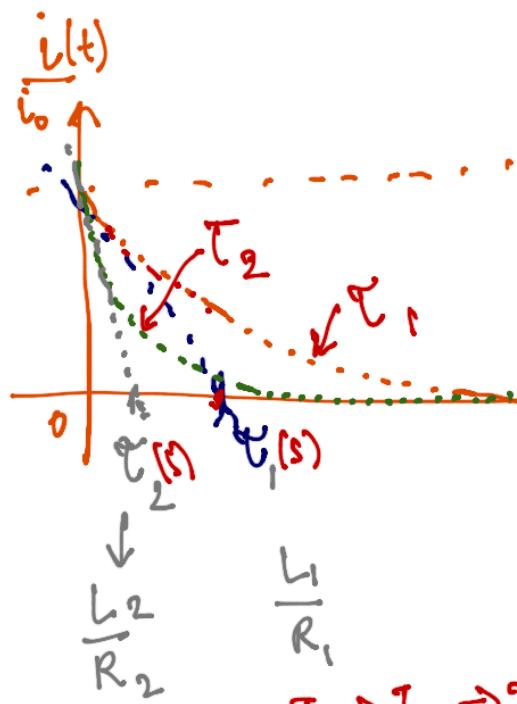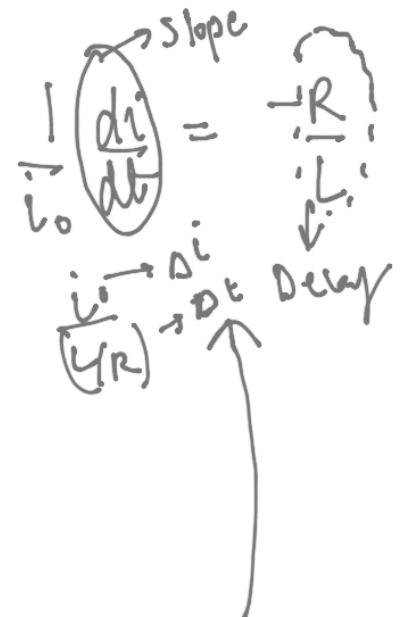
$$i = i_0 e^{-\left(\frac{R}{L}\right)t}$$



Slope  $\frac{di}{dt} = -i_0 \frac{R}{L} e^{-\frac{Rt}{L}}$

$$\left. \frac{di}{dt} \right|_{t=0} = -i_0 \left( \frac{R}{L} \right) = \frac{i_0}{\tau}$$

Slope at  $t=0$

$\tau = \text{time constant : Units of time (Seconds or ms)}$   
 $\tau = \frac{L}{R} : \text{how fast changing}$   
 $\tau = -t / (\ln i)$   
 $i = i_0 e^{-t/\tau}$

$L$  is small or  $R$  is large  $\tau \rightarrow$  small  $\Rightarrow$  faster decay

$R$  is small or  $L$  is large  $\tau \rightarrow$  large  $\Rightarrow$  slower decay.  $i = i_0 e^{-t/\tau}$

$\tau$  is large.  $i$  is large  $\rightarrow$  decay slow  
 $\tau$  is small.  $i$  is small  $\rightarrow$  decay fast.

General

$$\text{Gain} = \frac{V_{\text{Output}}}{V_{\text{Input}}}$$

Gain  
(mini-project)

$V_s$  → input

$$V_o(t) = [\text{function}] V_s(t)$$

$$\text{Gain} = \frac{V_o(t)}{V_s(t)}$$

Time constant


$$\frac{L}{R} \cdot t = \text{unit is of time}$$

$\tau$  → determines speed of response. Larger  $\tau \Rightarrow$  faster response.

## Practice 8.2

Given circuit →

Find  $v$  for  $t > 0$ .

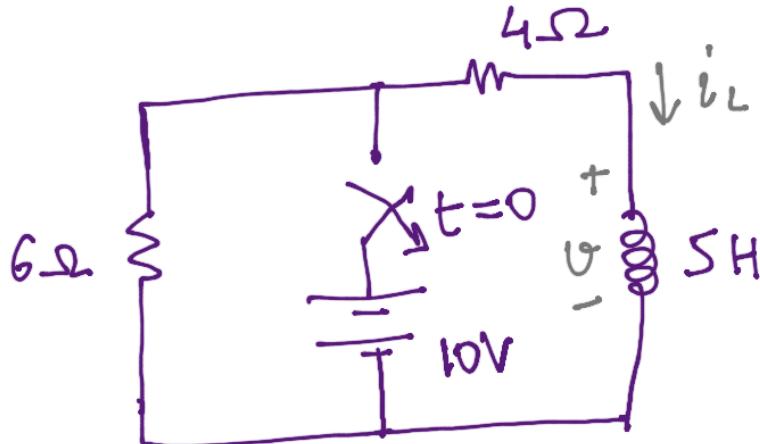

Facts: Switch is opened at  $t=0$  : Battery removed

For  $t < 0$ , { the circuit was operating with battery  
circuit was at steady state (unless mentioned)



Part 1 Find steady state  $v$  &  $i_L$  (for  $t < 0$ )

Part 2 Find solution to  $v$  &  $i_L$  (for  $t > 0$ )


Part 1 ( $t < 0$ ) Circuit is given by  
Inductor is short circuit at steady state.

$$\Rightarrow i_L = \frac{10}{4} = 2.5A$$

$$v_L = 0$$

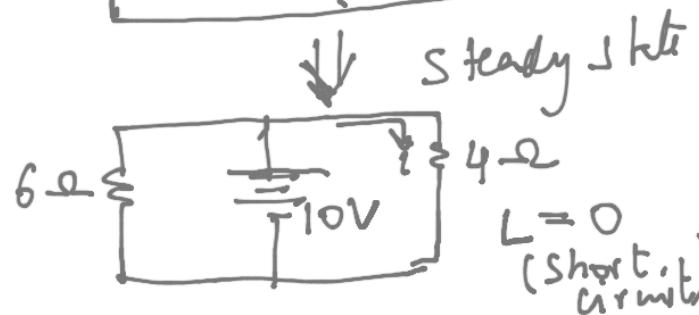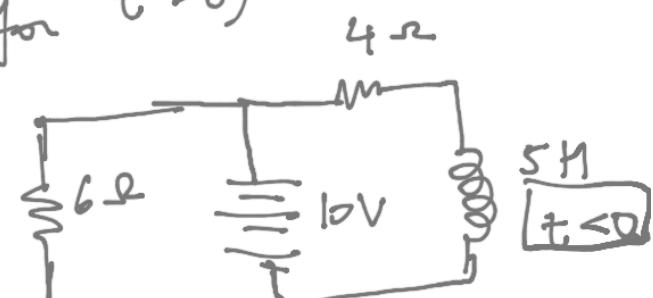

Part 2 ( $t \geq 0$ )

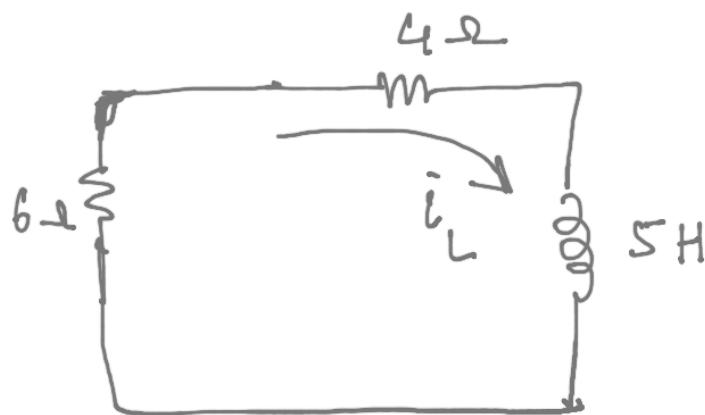

Voltage Source disconnected  
Circuit will be driven  
by inductor energy.

Now  $i_L(0) = 2.5A$  (calculated from part I)

$$V_L(0) = 0$$

Write KVL

$$6i_L + 4i_L - 5\frac{di_L}{dt} = 0$$

$\underbrace{6i_L + 4i_L}_{V_R}$        $\underbrace{- 5\frac{di_L}{dt}}_{V_L} = 0$

$$V_L(t) = 5 \frac{di_L}{dt}$$

$$V_R = 10 i_L \quad (V_R = V_L)$$

$$\Rightarrow 5 \frac{di}{dt} - 10 i_L = 0 \quad \left\{ \begin{array}{l} \text{Let, } i = A e^{st} \\ \Rightarrow \frac{di}{dt} = A s e^{st} \end{array} \right.$$

Using General solution  $s i - 2 i = 0$

$$s = 2$$

$$-2t$$

$$\Rightarrow i_L(t) = A e^{-2t} \Rightarrow t=0 \quad i_L = 2.5 = A$$

$$V_L = 5 \frac{d}{dt} (A e^{-2t}) = 5 * (-2) * (2.5) e^{-2t}$$

$$V_L = 25 e^{-2t}$$

from Part 1  
(initial condition)