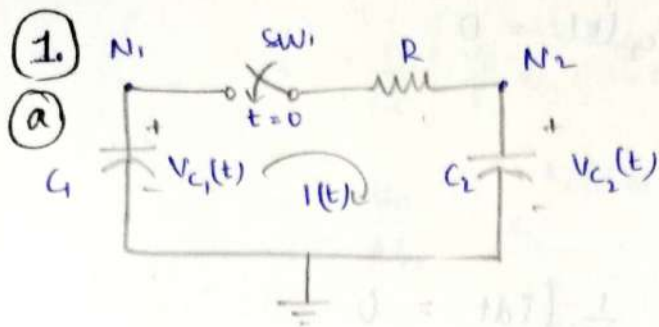


AEC Assignment - 2



Given, $V_{C_1}(0^-) = V_0$

$$V_{C_2}(0^-) = 0.$$

Let us come up with general conditions,

$$i(t) \rightarrow t = 0^+ \rightarrow 0$$

$$t = 0^+ \rightarrow \frac{V_0}{R}$$

$$t = \infty \rightarrow 0$$

$$V_{C_1}(t) \rightarrow t = 0^+ \rightarrow V_0$$

$$t = 0^+ \rightarrow V_0$$

$$t = \infty \rightarrow \frac{C_1}{C_1 + C_2} V_0$$

$$V_{C_2}(t) \rightarrow t = 0^+ \rightarrow 0$$

$$t = 0^+ \rightarrow 0$$

$$t = \infty \rightarrow \frac{C_1}{C_1 + C_2} V_0$$

At $t = \infty$

charge must be conserved,

$$C_1 V_0 + C_2(0) = (C_1 + C_2) V_\infty$$

$$V_\infty = \frac{C_1}{C_1 + C_2} V_0$$

Now, apply KVL in the loop.

$$V_{C_1}(t) - IR - V_{C_2}(t) = 0$$

w.k.t $V_C = \frac{1}{C} \int i dt$

$$\Rightarrow -\frac{1}{C_1} \int I dt - IR - \frac{1}{C_2} \int I dt = 0$$

differentiate on both sides.

$$-I \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = R \frac{dI}{dt}$$

$$\frac{I}{C_{eq}} = -R \frac{dI}{dt}$$


$$\int_0^t \frac{dt}{-RC_{eq}} = \int_{I_0}^{I(t)} \frac{dI}{I}$$

$$\ln \frac{I(t)}{I_0} = -\frac{t}{RC_{eq}}$$

$$\therefore \boxed{I(t) = I_0 e^{-t/RC_{eq}}}$$

where,
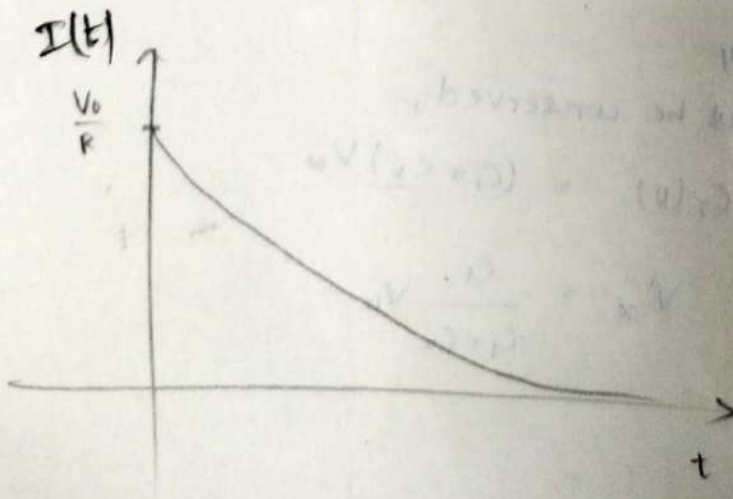
$$I_0 = \frac{V_0}{R}; \quad C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$



$$V_C(t) = -\frac{1}{C_1} \int I(t) dt$$

$$= -\frac{1}{C_1} \int \frac{V_0}{R} e^{-t/RC_{eq}} dt$$

$$= -\frac{V_0}{RC_1} \left[\frac{e^{-t/RC_{eq}}}{-\frac{1}{RC_{eq}}} \right] + k$$


$$= \frac{V_0 C_2}{C_1 + C_2} \left[e^{-t/RC_{eq}} \right] + k$$

At $t = 0$

$$V_0 = \frac{V_0 C_2}{C_1 + C_2} + k$$

$$k = \frac{C_1 V_0}{C_1 + C_2}$$
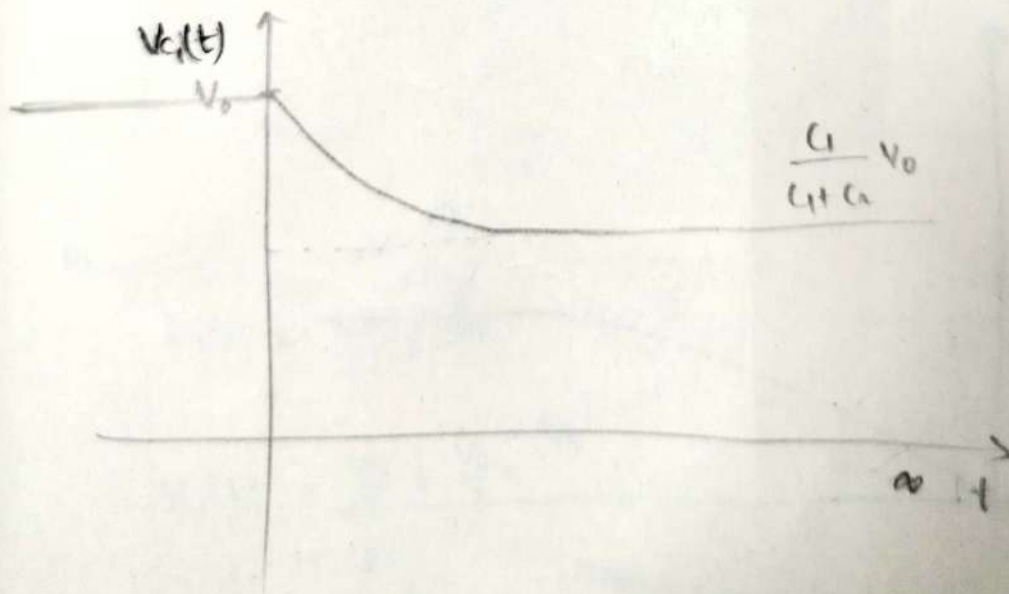
$$\therefore V_C(t) = \frac{C_1}{C_1 + C_2} V_0 + \frac{C_2}{C_1 + C_2} V_0 e^{-t/\tau}$$



$$V_{C_2}(t) = \frac{1}{C_2} \int I(t) dt$$

$$= \frac{1}{C_2} \int \frac{V_0}{R} e^{-t/RC_{eq}} dt$$

$$= \frac{V_0}{C_2 R} \left[\frac{e^{-t/RC_{eq}}}{-\frac{1}{RC_{eq}}} \right] + k$$


$$= -\frac{C_1 V_0}{C_1 + C_2} \left[e^{-t/RC_{eq}} \right] + k$$

at $t = 0$

$$0 = -\frac{C_1 V_0}{C_1 + C_2} + k$$

$$k = +\frac{C_1 V_0}{C_1 + C_2}$$

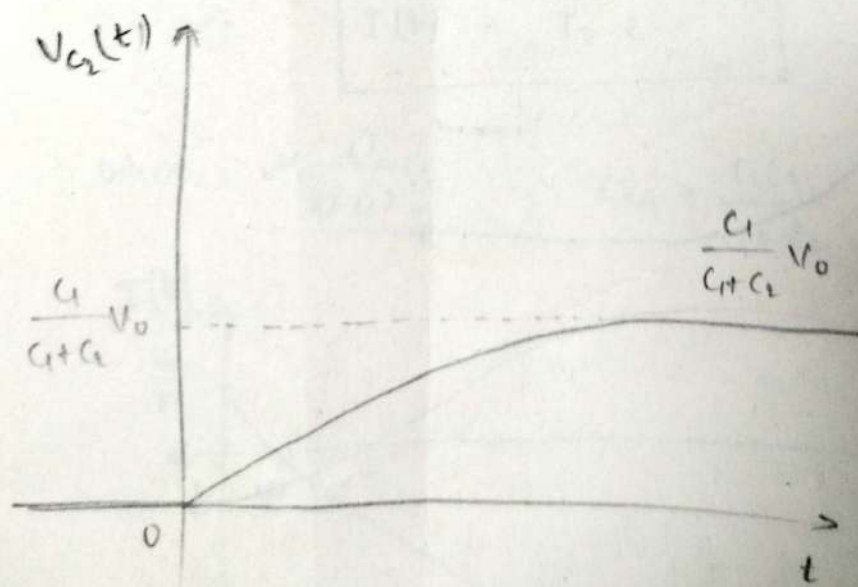
$$\Rightarrow V_{C_2}(t) = \frac{C_1}{C_1 + C_2} V_0 \left[1 - e^{-t/RC_{eq}} \right]$$



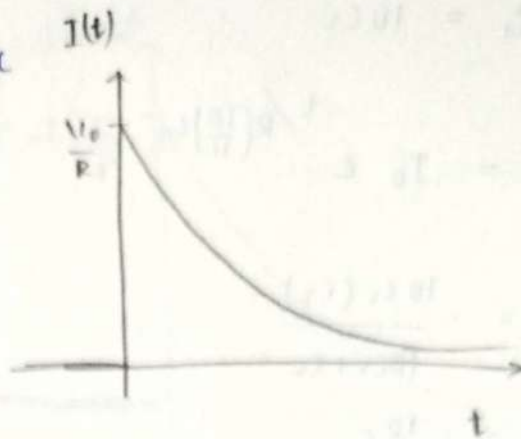(i) $C_1 = C_2$

$$I(t) = I_0 e^{-t/2RC}$$

$$C_{eq} = \frac{C \times C}{C + C} = C/2$$





$$V_{C_1}(t)$$

$$V_{\infty} = \frac{C_1}{C_1 + C_2} V_0 = \frac{V_0}{2}$$

$$V_{C_2}(t)$$

$$V_{\infty} = \frac{C_1}{C_1 + C_2} V_0 = \frac{V_0}{2}$$

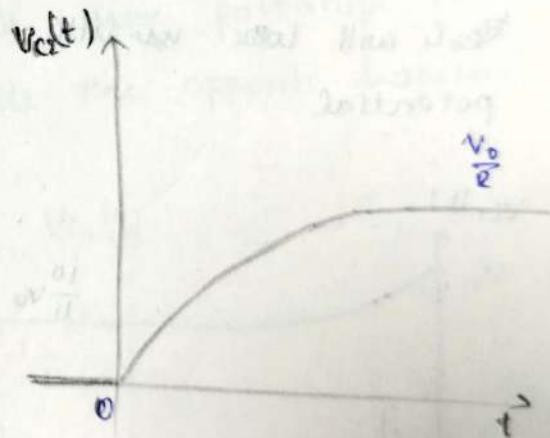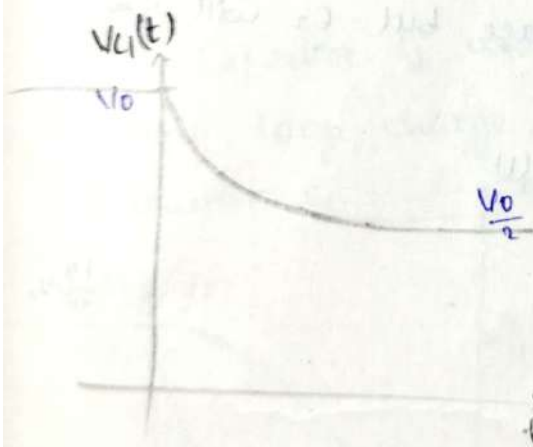Since, the value of C is equal, the voltage gets equally divided when capacitor is fully charged.



Here,

$$I(t) = \frac{V_0}{R} e^{-\frac{2t}{RC}}$$

$$V_{C_1}(t) = \frac{V_0}{2} + \frac{V_0}{2} e^{-t/\tau}$$


$$V_{C_2}(t) = \frac{V_0}{2} [1 - e^{-2t/RC}]$$

$$(ii) \quad C_1 = 10 C_2$$

$$I(t) = I_0 e^{-t / R \left(\frac{10}{11} \right) C_2} \quad \frac{V_0}{R} = I_0$$

$$C_{eq} = \frac{10 C_1 (C_2)}{10 C_1 + C_2}$$

$$= \frac{10}{11} C_2$$

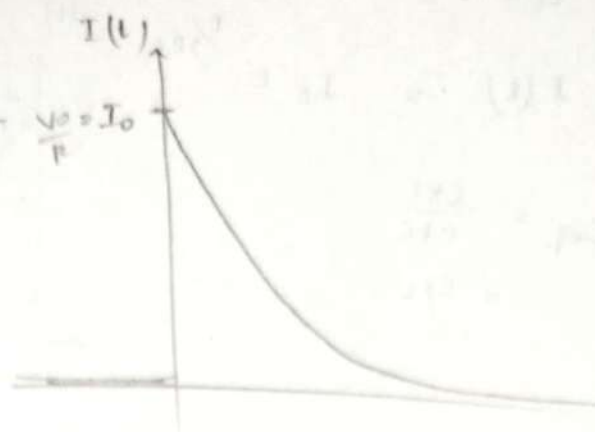

The maximum & min value of $I(t)$ remain same, but the curve might be bend.



wk.t

$$V_{\infty} = \frac{C_1}{C_1 + C_2} V_0$$

$$V_{\infty} = \frac{10}{11} V_0$$

As $C_1 > C_2$, the V_{∞} will be almost to V_0

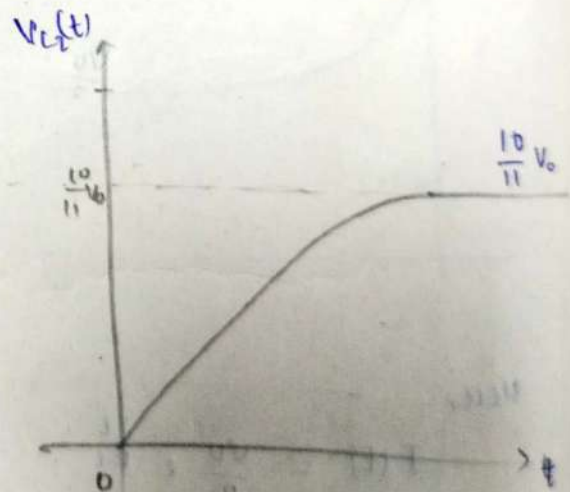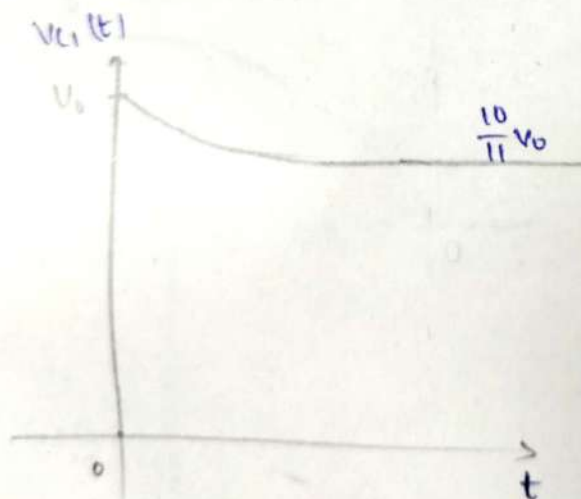C_1 will lose ~~very~~ little voltage but C_2 will gain potential



Here,

$$I(t) = \frac{V_0}{R} e^{-\frac{11t}{10RC_2}}$$

$$V_{C1}(t) = \frac{10}{11} V_0 + \frac{V_0}{11} e^{-\frac{11t}{10RC_2}}$$


$$V_{C2}(t) = \frac{10}{11} V_0 \left[1 - e^{-\frac{11t}{10RC_2}} \right]$$

$$(iii) \quad C_1 = \frac{1}{10} C_2$$

$$I(t) = I_0 e^{-t/R(11)C_1}$$

$$C_{eq} = \frac{(C_1)(10C_1)}{11C_1}$$

$$= \frac{10}{11} C_1$$

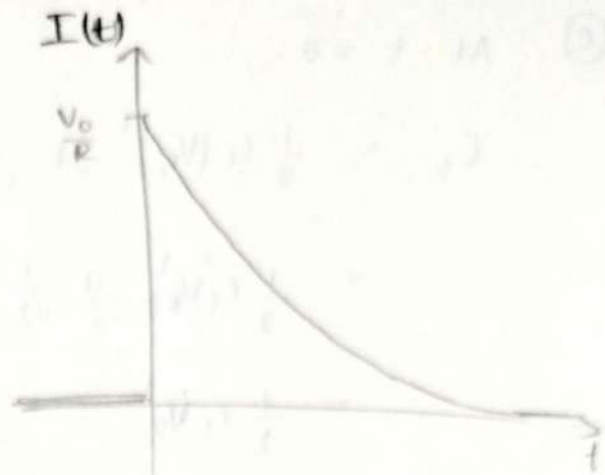



The max & min values of I_{eq} are same but the slope of curve changes acc to C values.

w.k.t

$$V_{\infty} = \frac{C_1}{C_1 + C_2} V_0$$

$$V_{\infty} = \frac{1}{11} V_0$$

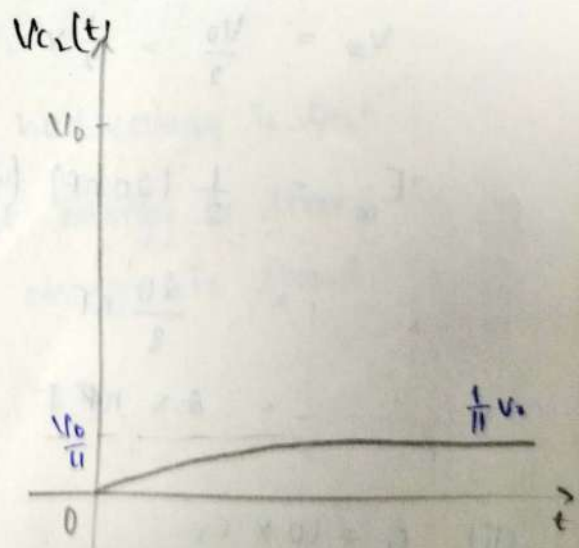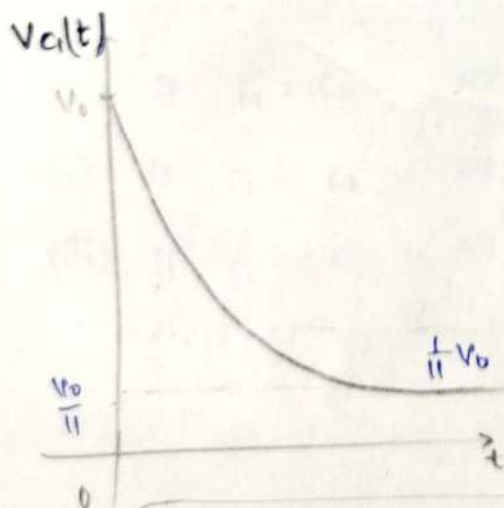As $C_1 < C_2$, the V_{∞} will be closer to 0.
i.e. Capacitor C_2 will lose more potential i.e. gain large charge, while the opposite happens capacitor C_1



Here, $I(t) = \frac{V_0}{R} e^{-\frac{11t}{10RC_1}}$

$$V_{C_1}(t) = \frac{V_0}{11} + \frac{10}{11} V_0 e^{-\frac{11t}{10RC_1}}$$

$$V_{C_2}(t) = \frac{V_0}{11} [1 - e^{-\frac{11t}{10RC_1}}]$$

(b) Ltspice commands

.model swl swl (Ron = 1m Roff = 1Meg Vt = .5 Vh = 0)

here sw — name of the switch.

Ron → this is the resistance when switch is closed, ~~its~~ value.

— its value must be very low for current to completely flow.


Roff → resistance when switch is open.

— its value must be high so no current passes.

Vt → min threshold voltage for switch to change


Vh → = 0 show purely dependent circuit.

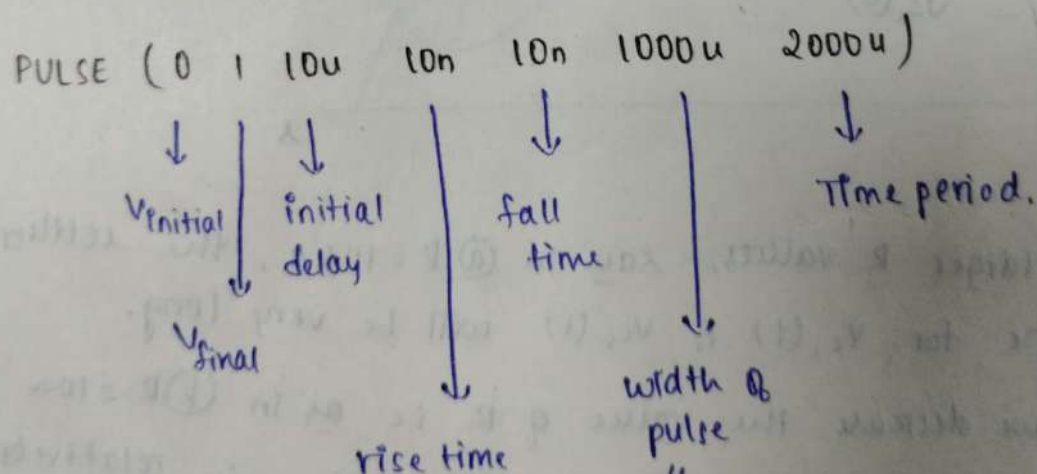Hence, this explains the mechanism in which switch will be working, basing on the ~~inp~~ voltage inflow





during this span
the pulse will be at
Vfinal

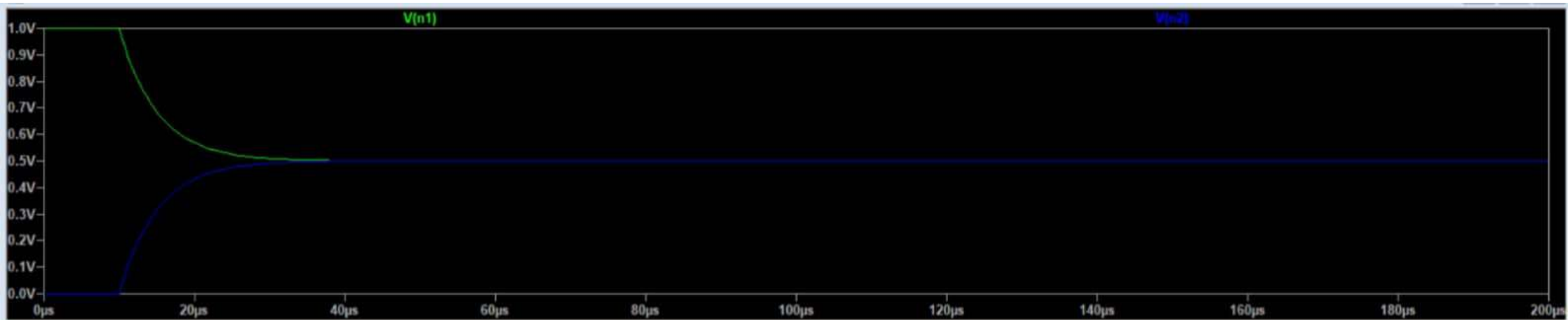With these values, we can generate a pulse of voltage input that keeps changing periodically.





Q1.b.asc

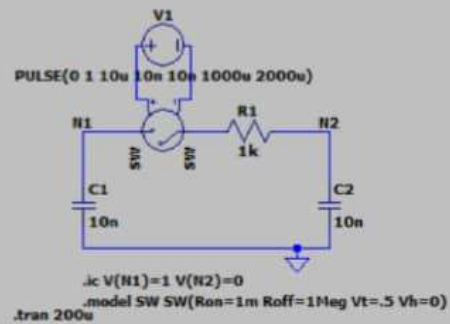

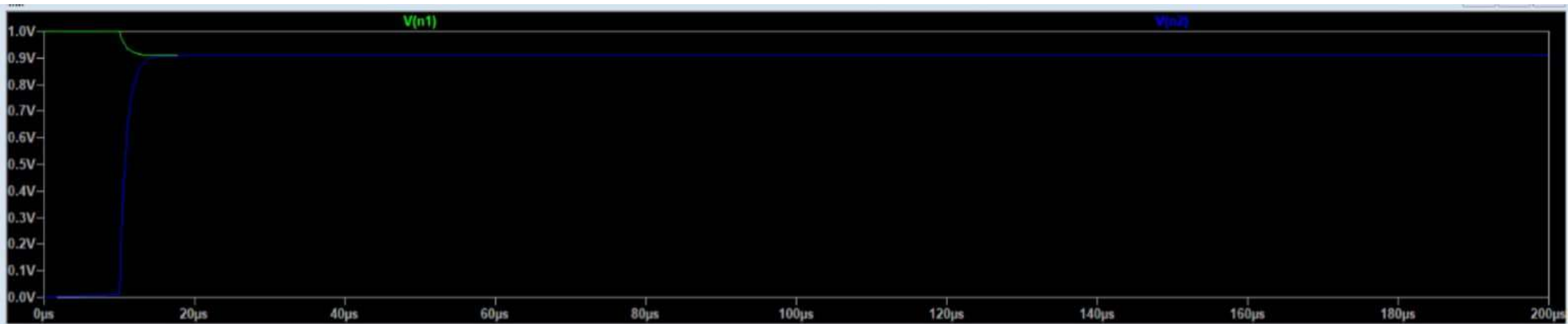


Q1.b.asc

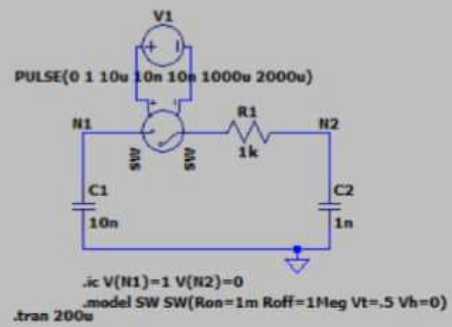

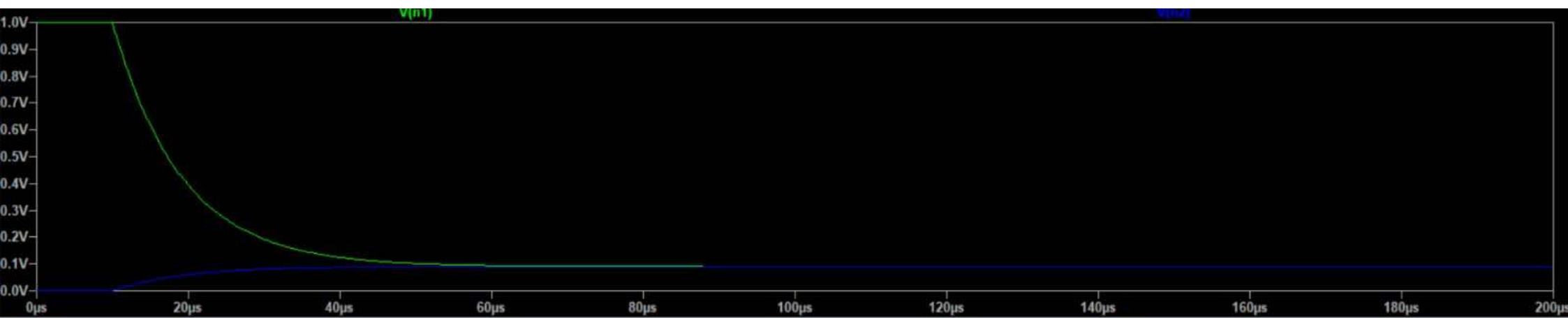

Q1.b.asc

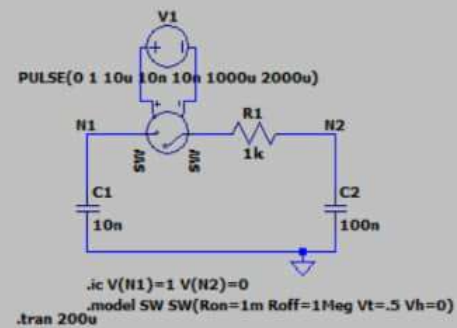

(c) At $t = 0$

$$\begin{aligned} E_0 &= \frac{1}{2} C_1 (V_0)^2 + \frac{1}{2} C_2 (V_0(t=0))^2 \\ &= \frac{1}{2} C_1 V_0^2 + \frac{1}{2} C_2 (0)^2 \\ &= \frac{1}{2} C_1 V_0^2 \end{aligned}$$

$$\begin{aligned} E_\infty &= \frac{1}{2} C_1 (V_\infty)^2 + \frac{1}{2} C_2 (V_\infty)^2 \\ &= \frac{1}{2} (C_1 + C_2) (V_\infty)^2 = \frac{C_1}{C_1 + C_2} (E_0) \end{aligned}$$

From part (b)

$$C_1 = 10 \text{ nF}$$

$$V_0 = 1 \text{ V}$$

$$V_\infty = \frac{C_1}{C_1 + C_2} V_0$$

(i) $C_1 = C_2 = 10 \text{ nF}$

$$V_\infty = \frac{V_0}{2} = \frac{1}{2} \text{ V}$$

$$\begin{aligned} E_\infty &= \frac{1}{2} (20 \text{ nF}) \left(\frac{1}{2}\right)^2 \\ &= \frac{20}{8} \text{ nJ} \\ &= 2.5 \text{ nJ} \end{aligned}$$

(ii) $C_1 = 10 \times C_2$

$$C_2 = \frac{10 \text{ n}}{10} = 1 \text{ nF}$$

$$V_\infty = 0.9090 \text{ V}$$

$$\begin{aligned} E_\infty &= \frac{1}{2} (10 \text{ n} + 1 \text{ n}) (0.909)^2 \\ &= \frac{1}{2} (11) (0.826) \text{ n} \\ &= 4.54 \text{ nJ} \end{aligned}$$

$$(iii) \quad C_1 = \frac{1}{10} C_2$$

$$C_2 = 100 \text{ nF}$$

$$V_{\infty} = 0.0909 \text{ V}$$

$$E_{\infty} = \frac{1}{2} (10+100) \text{ n} \times (0.09)^2$$

$$= 0.45 \text{ nJ}$$


Relation of C_1 & C_2	E_{∞}	E_{∞} interms of E_0
(i) $C_1 = C_2$	2.5 nJ	$E_0/2$
(ii) $C_1 = 10 \times C_2$	4.54 nJ	$\frac{10}{11} E_0$
(iii) $C_1 = \frac{C_2}{10}$	0.45 nJ	$\frac{1}{11} E_0$

Conclusions:

- (i) if $C_1 = C_2 \Rightarrow$ only half energy is lost
- (ii) if $C_1 \gg C_2 \Rightarrow$ most energy is stored
- (iii) if $C_1 \ll C_2 \Rightarrow$ less energy is stored

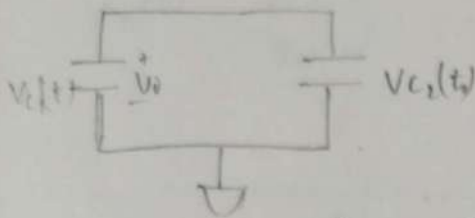(C) Two capacitor Paradox


Generally, when two capacitors are connected as shown below and when they reach their steady state, the final energy isn't conserved



i.e. $E_{\text{initial}} > E_{\infty}$

The best possible sol:

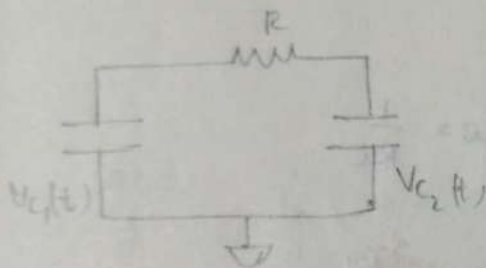However, this ~~lost~~ energy can be shown to be present by placing a resistor between them,



i.e., the resistor dissipates that rest energy.

$$E_{\text{initial}} = \frac{1}{2} C_1 V_0^2 + \frac{1}{2} C_2 V_0^2$$

$$= \frac{1}{2} C_1 V_0^2$$

$$E_{\infty} = \frac{1}{2} C_1 V_{\infty}^2 + \frac{1}{2} C_2 V_{\infty}^2$$

$$= \frac{1}{2} (C_1 + C_2) V_{\infty}^2$$


$$= \frac{1}{2} (C_1 + C_2) \left(\frac{C_1 V_0}{C_1 + C_2} \right)^2$$

$$= \frac{1}{2} C_1 V_0^2 \left(\frac{C_1}{C_1 + C_2} \right)$$

$$= E_0 \left(\frac{C_1}{C_1 + C_2} \right)$$

$$E_{\text{dissipated by } R} = \int i^2 R dt = \frac{C_2}{C_1 + C_2} E_0$$

But for this case ~~where~~

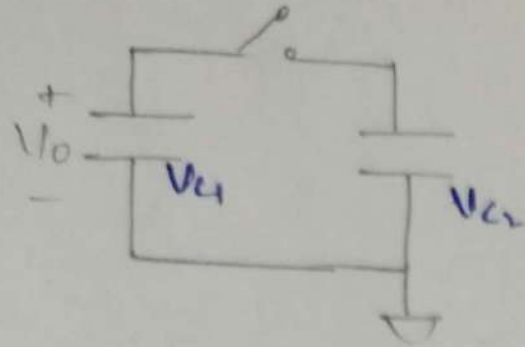

The initial and final energy is lost similar to as where resistor is placed.

In that case the difference can be explained as the heat dissipated by the resistor.

However, in this case,

as the energy isn't conserved, the most probable case is that the resistance in the connecting wires can dissipate that ~~lost~~ energy in the form of heat / radiation.

(d) Effect of reducing R on settling time.

When there is a change in R, the time constant is differed and hence, settling time is altered.

$$\tau = RC$$

$$\text{if } R \downarrow \Rightarrow \tau = \downarrow$$

\Rightarrow if time constant is \downarrow , then steady state is achieved faster.

\therefore Reducing the value of R decreases the settling time and steady state is obtained faster.

Given, — $C_1 = C_2 = 10 \text{ nF}$

$$V_{C_1}(0^-) = V_0 = 1 \text{ V}$$


$$V_{C_2}(0^-) = 0 \text{ V}$$

Equations


$$V_{C_1}(t) = \frac{C_1}{C_1 + C_2} V_0 + \frac{C_2}{C_1 + C_2} V_0 e^{-t/\tau}$$

$$V_{C_2}(t) = \frac{C_1}{C_1 + C_2} V_0 \left[1 - e^{-t/RC} \right]$$


(a) $R = 10 \text{ k}\Omega$

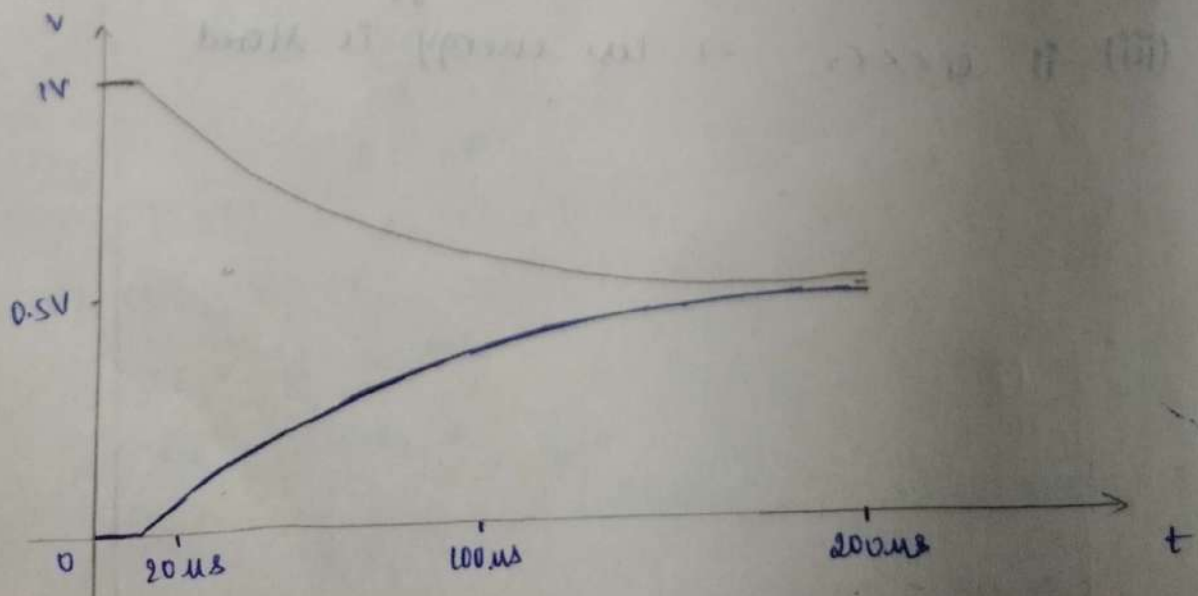

(b) $R = 10\Omega$

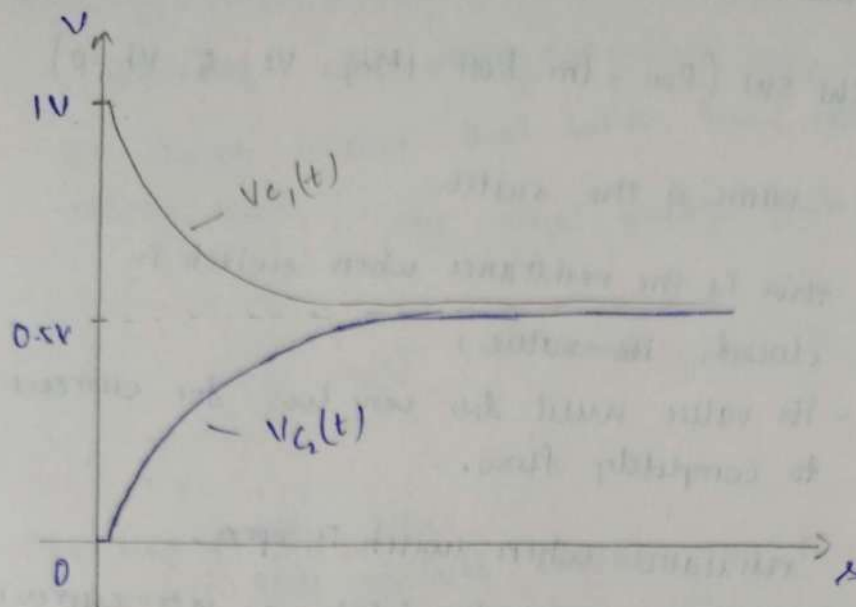

(c) $R = 1m\Omega$

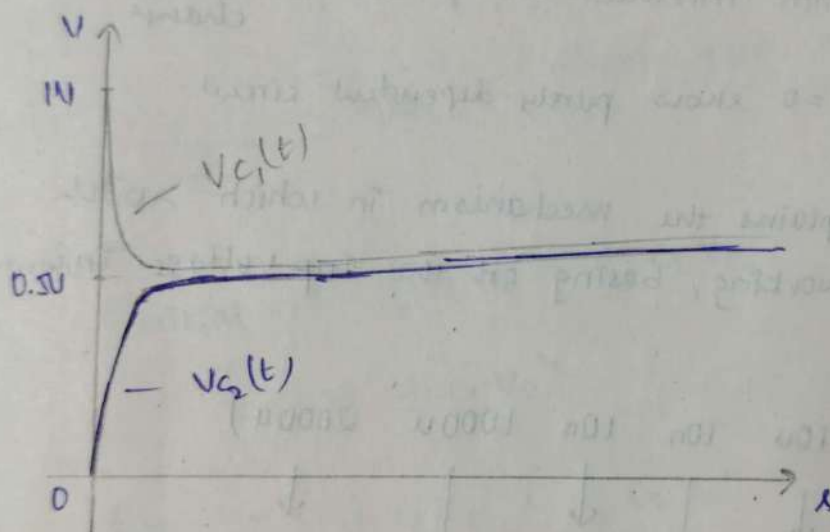


For larger R values, say in (a) $R = 10k\Omega$, the settling time for $V_{c1}(t)$ & $V_{c2}(t)$ will be very long.

As we decrease the value of R i.e. as in (b) $R = 10\Omega$ and (c) $R = 1m\Omega$, the settling time is relatively shorter and faster.

\therefore The effect of reducing R value is the reducing of settling time of $V_{c1}(t)$ & $V_{c2}(t)$.

Also, if $R \downarrow$, then current flowing in circuit will ~~decrease~~ increase

2. RC circuits as filters

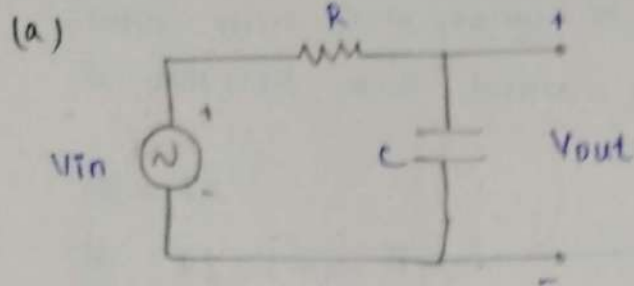

Given

$$R = 20\text{ k}\Omega$$

$$C = 10\text{ pF}$$

$$V_C(0^-) = 0\text{ V}$$

(i)



also, $V_{in} = V_0 u(t)$
step func.

$$V_{out}(t) \xrightarrow{t=0^-} 0$$

$$t=0^+ \rightarrow 0 \quad \text{— since } R \text{ is in series}$$

$$t=\infty \rightarrow V_0 \quad \text{— fully charged}$$

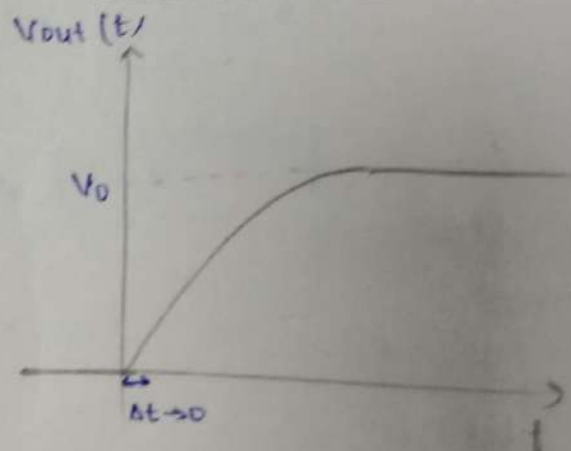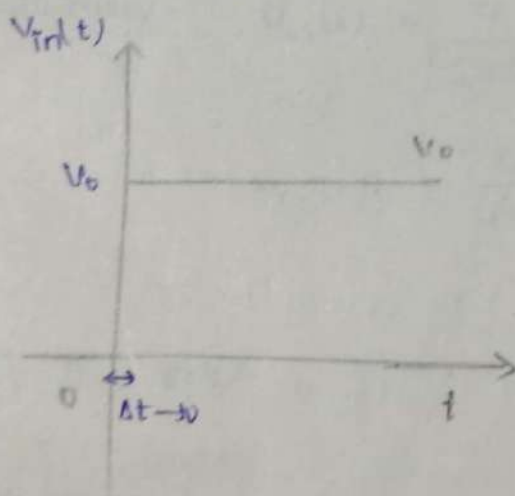* The curve of V_{out} is expected to rise exponentially (non-linear)




Here in $V_{in}(t)$, just after a very small time Δt , the value of V_0 immediately went to V_0 without any delay.

— But this transition is not being seen in $V_{out}(t)$ graph. After small time Δt , $V_{out}(t)$ is still $< V_0$. After some visible time, it changes to V_0 .

This is because the RC combination in the circuit acts as a filter and filters out all of the fast transitions and also a delay occurs.

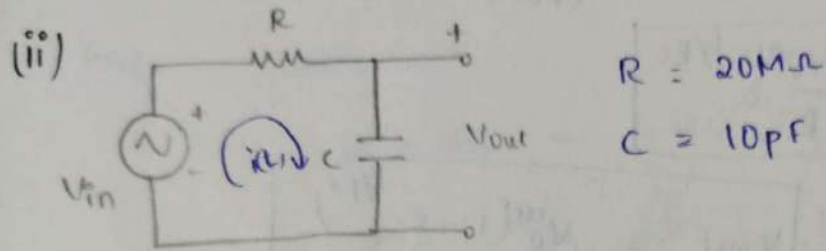Hence, this RC circuit acts as a "low pass filter."



$$V_c(0^-) = 0 \text{ V}$$

$$V_c(0^+) = 0 \text{ V} \quad [\because \text{resistor is in series}]$$

$$V_c(\infty) = V_0$$

Apply KVL

$$V_0 - iR - V_c(t) = 0.$$

~~$$V_0 - iR - V_c(t) = 0.$$~~

$$V_0 - RC \frac{dV_c}{dt} - V_c(t) = 0.$$

$$V_0 - V_c = RC \frac{dV_c}{dt}$$

$$\int \frac{dt}{RC} = \int \frac{dV_c}{V_0 - V_c}$$

$$\frac{t}{RC} = - \left[\ln(V_0 - V_c) \right]_0^{V_0}$$

$$-\frac{t}{RC} = \ln(V_0 - V_c) - \ln V_0$$

$$-\frac{t}{RC} = \ln \left(\frac{V_0 - V_c}{V_0} \right)$$



$$e^{-t/RC} = 1 - \frac{V_c}{V_0}$$

$$V_c(t) = V_0^{ult} (1 - e^{-t/RC})$$

$$i(t) = C \frac{dV_c}{dt} = C \left(-V_0 e^{-t/RC} \cdot \left(-\frac{1}{RC} \right) \right)$$

$$i(t) = \frac{V_0^{ult}}{R} e^{-t/RC}$$
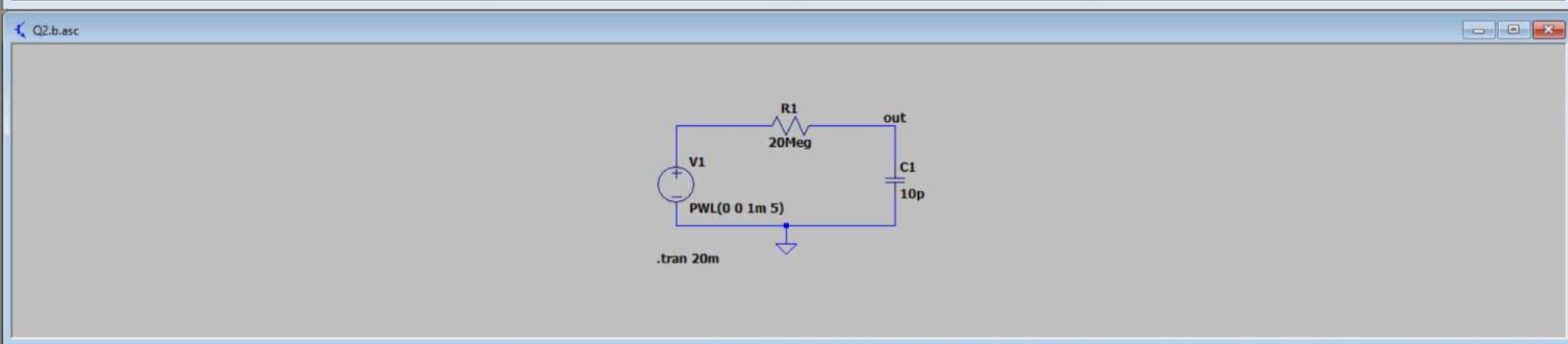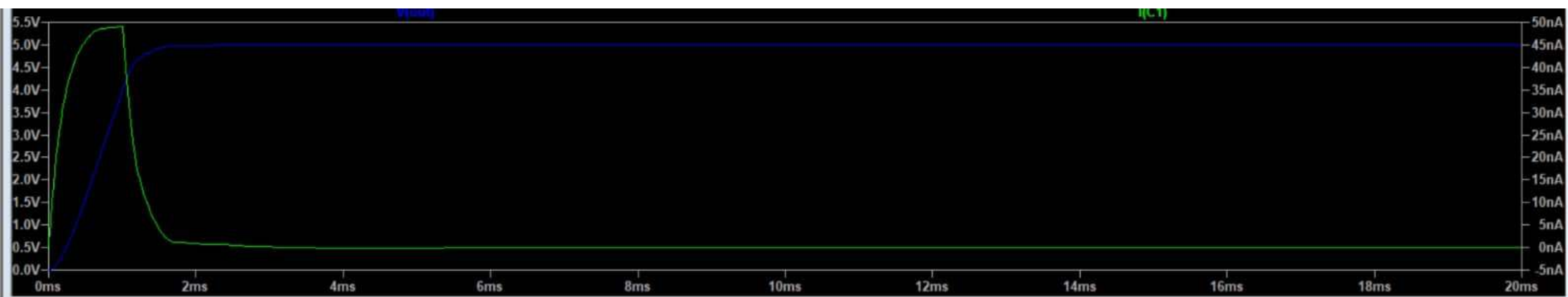
$$V_c = V_{out} \Rightarrow V_{out} = V_0^{ult} (1 - e^{-t/RC})$$



(iii)

Transfer Function

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{Z_c}{Z_R + Z_c}$$

$$Z_c = \frac{1}{sC}$$

$$= \frac{1/sC}{1/sC + R}$$

$$\boxed{\frac{V_{out}}{V_{in}} = \frac{1}{1 + sCR}}$$

$$\left| \frac{V_{out}(j\omega)}{V_{in}(j\omega)} \right| = \left| \frac{1}{1 + j\omega CR} \right|$$

$$= \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$\phi = -\tan^{-1}(\omega RC)$$

Take

$$20 \log \left| \frac{V_o}{V_i}(\omega) \right| = 20 \left(\log \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} \right)$$
$$= -20 \log \sqrt{1 + \omega^2 R^2 C^2}$$

3dB frequency is the frequency at which

$$|H(j\omega)| = \frac{1}{\sqrt{2}} |H(s)|$$

$$\frac{1}{\sqrt{1+\omega^2 R^2 C^2}} = \frac{1}{\sqrt{2}} \frac{1}{\sqrt{1+0}}$$

$$\sqrt{1+\omega^2 R^2 C^2} = \sqrt{2}$$

$$\omega^2 R^2 C^2 = 1$$

$$\omega = \frac{1}{RC}$$

$$f_c = \frac{1}{2\pi RC}$$

\therefore 3dB cutoff frequency is $\omega = \frac{1}{RC}$

~~(10)~~



$$\text{Gain} = 20 \log |H(s)|$$

$$= 20 \log \left| \frac{1}{\sqrt{1+\omega^2 R^2 C^2}} \right|$$


$$= -20 \log \sqrt{1+\omega^2 R^2 C^2}$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{1}{1+sRC}$$
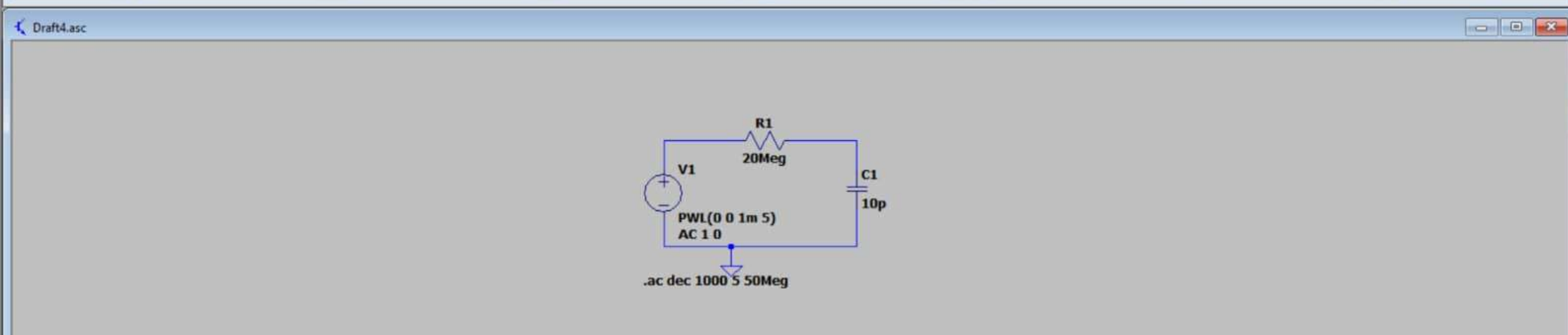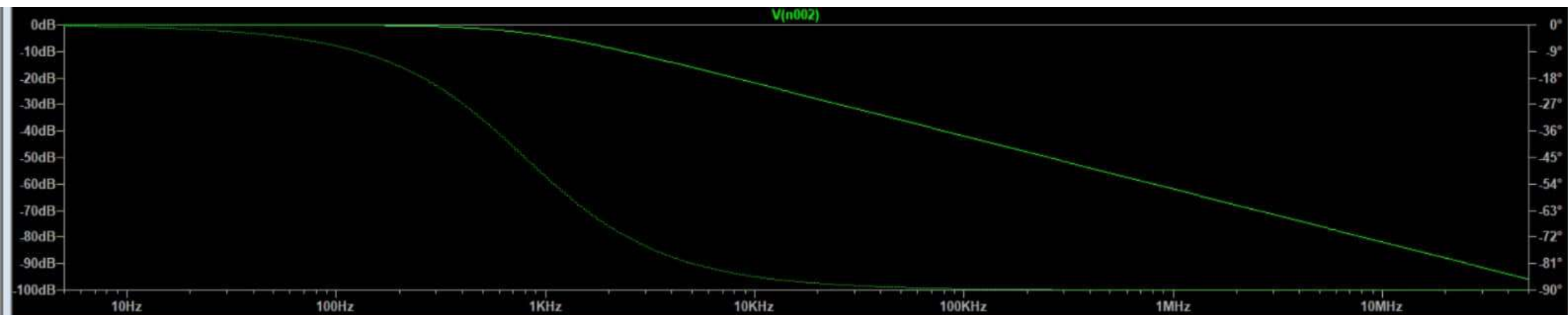
$$\text{Phase } (\phi) = -\tan^{-1}(\omega RC)$$



(b)

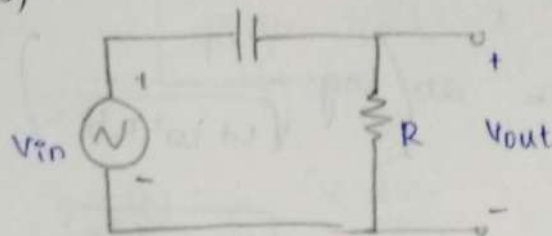

$$R = 20k\Omega$$

$$C = 10pF$$

$$V_c(0^-) = 0$$

(i)


on analysing $V_c(t)$

$$V_c(0^-) = 0$$

$$V_c(0^+) = V_0$$

$$V_c(\infty) = 0$$

$$V_{in} = V_0 u(t)$$

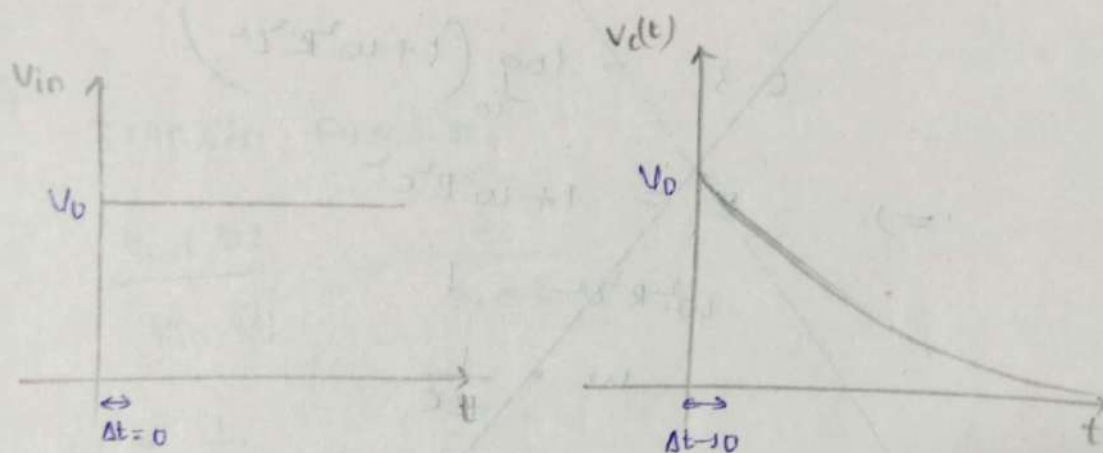


* The curve of V_{out} is expected to fall exponentially (non-linear)

Here also, in $V_{in}(t)$, just after a very small time Δt , the value of V_0 immediately went to V_0 without any delay.

And in $V_{out}(t)$ for a same Δt , we are able to achieve a ~~sa~~ similar transition and jump to V_0 and slowly reduces.

\therefore This is a High-Pass Filter.

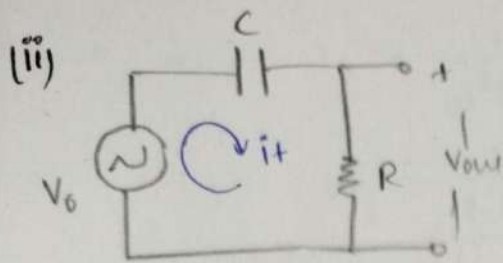\rightarrow A low pass filter attenuates ~~low~~ low f and passes high frequencies.



Apply KVL

$$V_C(0^-) = 0$$

$$V_C(0^+) = V_0$$

$$V_C(\infty) = 0$$

$$V_0 - V_C(t) - iR = 0$$

$$V_0 - V_C - RC \frac{dV_C}{dt} = 0$$

$$V_0 - V_C = RC \frac{dV_C}{dt}$$

$$\int \frac{dt}{RC} = \int \frac{dV_C}{V_0 - V_C}$$

$$-\frac{t}{RC} = -\ln(V_0 - V_C) \Big|_0^{V_C}$$

$$-\frac{t}{RC} = \ln\left(\frac{V_0 - V_C}{V_0}\right)$$

$$V_C = V_0 (1 - e^{-t/RC})$$

$$i_C(t) = C \frac{dV_C}{dt}$$

$$= -C(V_0) \left(\frac{-1}{RC}\right) e^{-t/RC}$$

$$i_C(t) = \frac{V_0}{R} e^{-t/RC} \quad \text{--- current across capacitor}$$


$$V_{out} = iR$$


$$= \frac{V_0}{R} e^{-t/RC} \times R$$

$$V_{out} = V_0 e^{-t/RC}$$




Q2high.asc

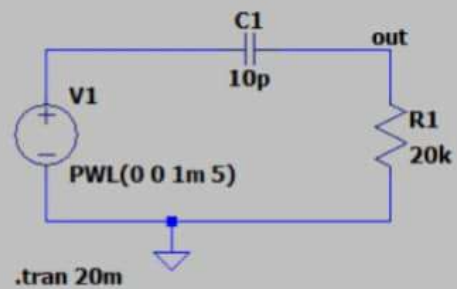

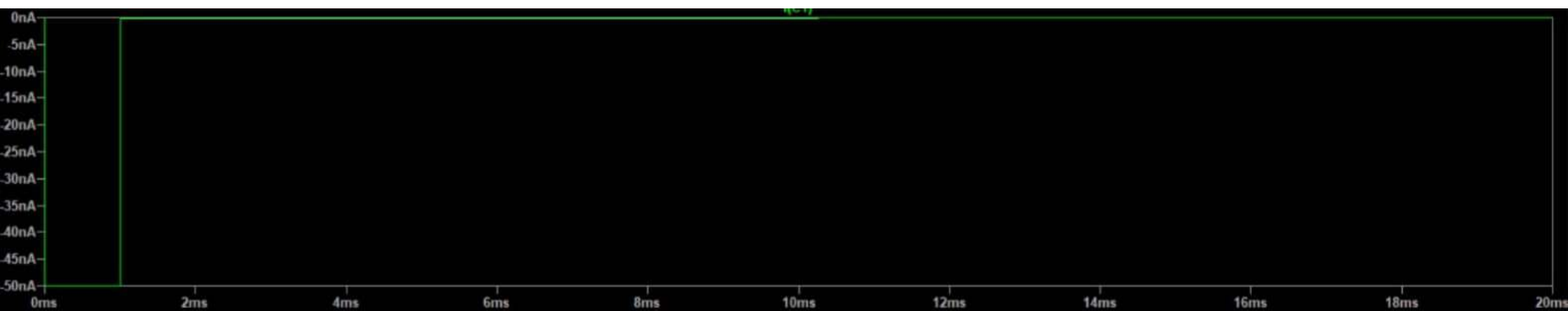

Q2high.asc

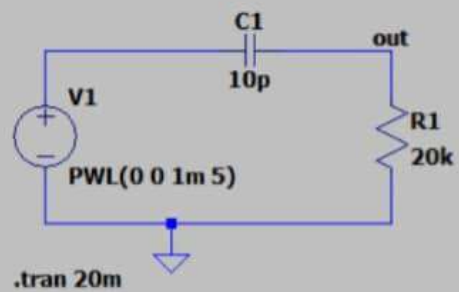

(iii)

Transfer Function

$$\frac{V_{out}(s)}{V_{in}} = \frac{R}{R + \frac{1}{sC}}$$
$$= \frac{sCR}{1 + sCR}$$

$$20 \log \left| \frac{V_{out}}{V_{in}} \omega \right| = 20 \log \left| \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}} \right|$$

$$\left| \frac{V_{out}}{V_{in}} \omega \right| = \left| \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}} \right|$$

$$H(j\omega) = 20 \log |\omega RC| - 20 \log \sqrt{1 + \omega^2 R^2 C^2}$$

(i) $\omega < \frac{1}{RC}$ $H(j\omega) = 20 \log \omega RC$

(ii) $\omega = \frac{1}{RC}$ $H(j\omega) = -3 \text{ dB}$

(iii) $\omega \gg \frac{1}{RC}$ $H(j\omega) = 0$

3dB cut-off frequency is the frequency at which

$$|H(\omega)| = \frac{1}{\sqrt{2}} |H(0)|$$

$$\frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}} = \frac{1}{\sqrt{2}} \Rightarrow \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$\frac{\omega^2 R^2 C^2}{1 + \omega^2 R^2 C^2} = \frac{1}{2}$$

$$\omega^2 R^2 C^2 = 1$$

$$\boxed{\omega = \frac{1}{RC}}$$



~~Find~~


$$\text{Gain} = 20 \log |H(\omega)|$$

$$= 20 \log \left| \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}} \right|$$

$$= 20 \log |\omega RC| - 20 \log \sqrt{1 + \omega^2 R^2 C^2}$$
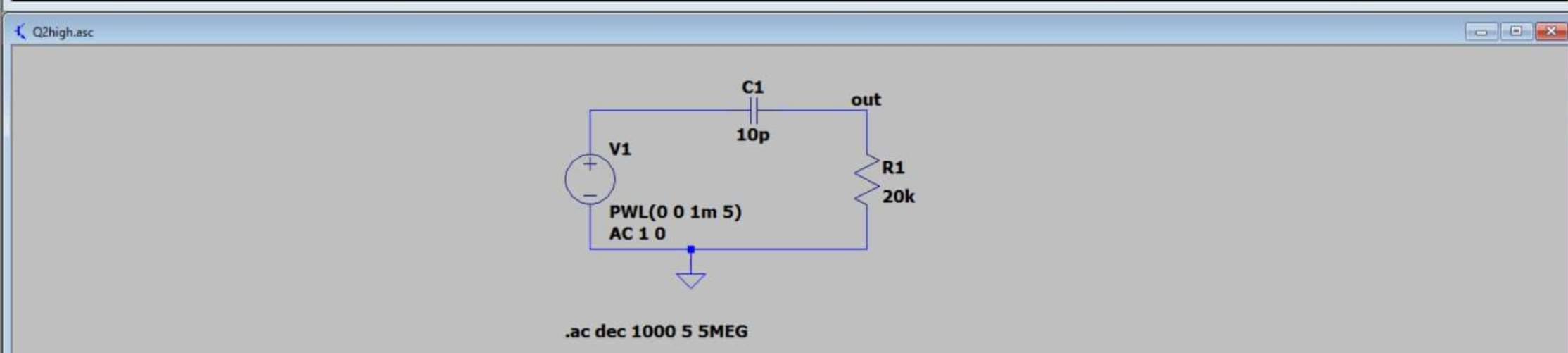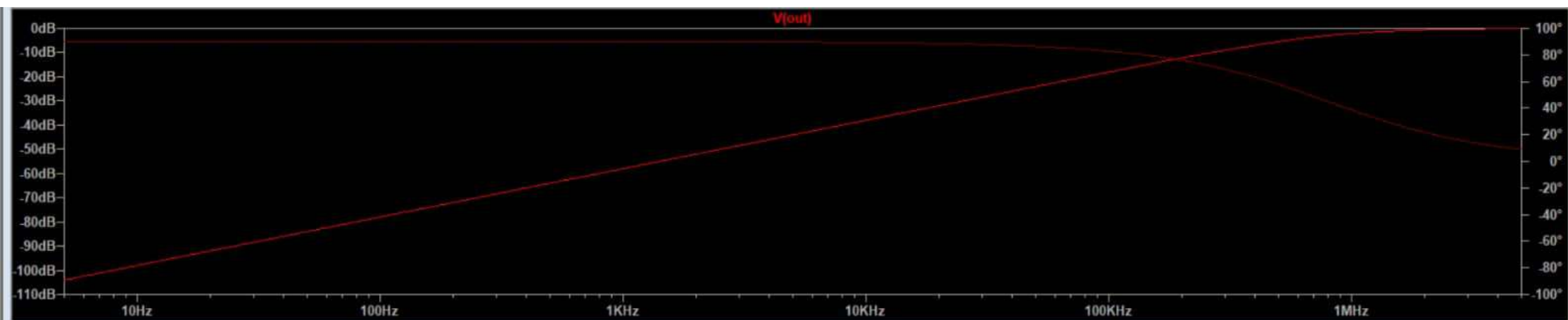
$$\text{Phase } \phi = \cancel{\tan^{-1}} \pi/2 - \tan^{-1}(\omega RC)$$



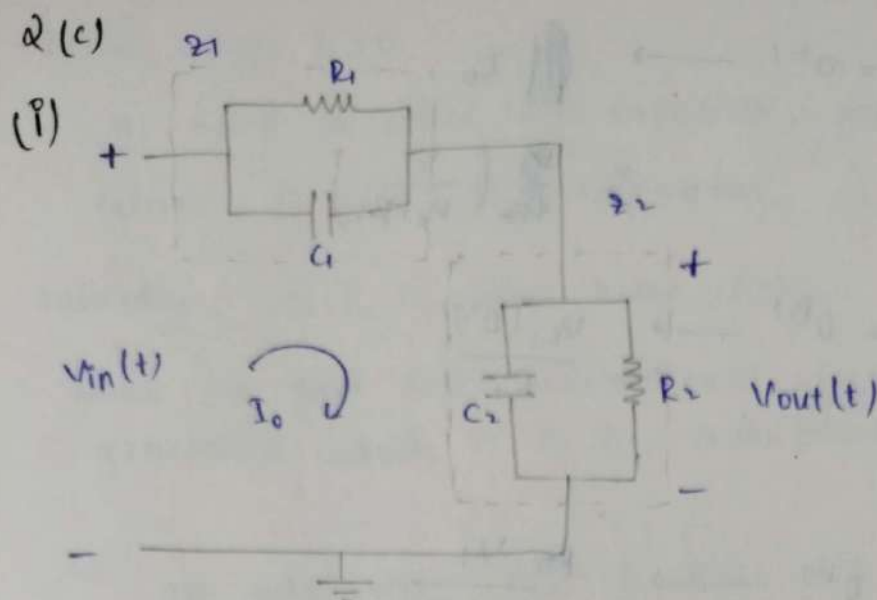

Given

$$V_{in}(t) = \begin{cases} V_1 & t \leq 0 \\ V_2 & 0 \leq t \leq T_b \quad (V_2 \geq V_1) \\ V_1 & t \geq T_b \end{cases}$$

and, $T_b \gg R_1 C_1$

Initially,

$$I_0(0^-) = \frac{V_0}{R_1 + R_2}$$

Here

$$\Delta V = V_2 - V_1$$

$$V_{C_1}(t) \quad t = 0^- \longrightarrow \frac{R_1 V_1}{R_1 + R_2}$$

$$t = 0^+ \longrightarrow V_{C_1}(0^-) + \Delta V_{C_1}$$

$$= \frac{R_1 V_1}{R_1 + R_2} + \frac{C_2}{C_1 + C_2} \Delta V$$

[ΔV is shown in next page]

$$V_{C_2}(t) \quad t = 0^- \longrightarrow \frac{R_2 V_1}{R_1 + R_2}$$

$$t = 0^+ \longrightarrow V_{C_2}(0^-) + \Delta V_{C_2}$$

$$= \frac{R_2 V_1}{R_1 + R_2} + \frac{C_1}{C_1 + C_2} \Delta V$$

$$I_{R_1}(t)$$

$$t = 0^{(-)} \longrightarrow I_0$$

$$= \left(\frac{V_1}{R_1 + R_2} \right)$$

$$t = 0^{(+)} \longrightarrow \frac{V_{C_1}(0^+)}{R_1}$$

$$I_{R_2}(t)$$

$$t = 0^{(-)} \longrightarrow \frac{V_1}{R_1 + R_2}$$

$$t = 0^{(+)} \longrightarrow \frac{V_{C_2}(0^+)}{R_2}$$

$$I_{C_1}(t)$$

$$t = 0^{(-)} \longrightarrow 0$$

$t = 0^{(+)} \longrightarrow$ Impulsive current for $\Delta t \rightarrow 0$
and again reaches steady state

$$I_{C_2}(t)$$

$$t = 0^{(-)} \longrightarrow 0$$

$t = 0^{(+)} \longrightarrow$ Impulsive current for small t and then steady state is obtained.

For $t < 0$,

the capacitors are completely charged, hence no current flows into them. $I_{C_1}(0^-) = I_{C_1}(0^+) = 0$.

to All the current flows into resistors and is equal in both of them

Now, when $t > 0$


as no R in series with Capacitor, an impulsive current I flows into capacitor.

Initially, C_1 & C_2 have some charge

Now, we give some additional charge is generated which is to be redistributed.

So, an additional ΔV_{C_1} & ΔV_{C_2} are generated at $t = 0^+$.

at $t=0$, equivalent circuit,

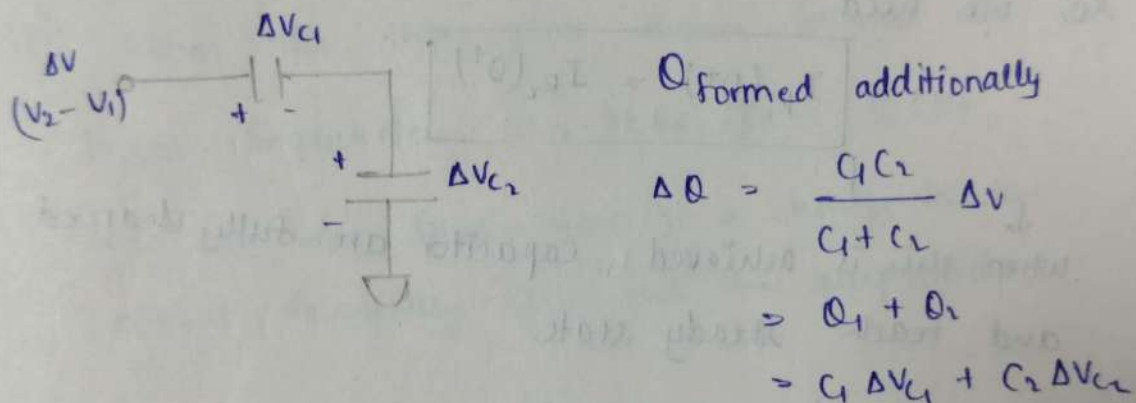

and $\Delta V = \Delta V_{C_1} + \Delta V_{C_2}$ — (1)

Since charge must be conserved

$$C_1 \Delta V_{C_1} = C_2 \Delta V_{C_2}$$
 — (2)

On solving (1), (2)

$$\Delta V_{C_1} = \frac{C_2}{C_1 + C_2} \Delta V$$

$$\Delta V_{C_2} = \frac{C_1}{C_1 + C_2} \Delta V$$

After $t > 0$,

Impulsive current goes into capacitors.

But still small amount of I goes into the resistor

i.e

$$I_{R_1}(0^+) = \frac{V_{C_1}(0^+)}{R_1}$$

$$I_{R_2}(0^+) = \frac{V_{C_2}(0^+)}{R_2}$$

Because of this there are small transient changes in capacitor and is not constant.



So, we need



$$I_{R_1}(0^+) = I_{R_2}(0^+)$$



when this is achieved, capacitors are fully charged and reach steady state



$$\Rightarrow R_1 C_1 = R_2 C_2$$

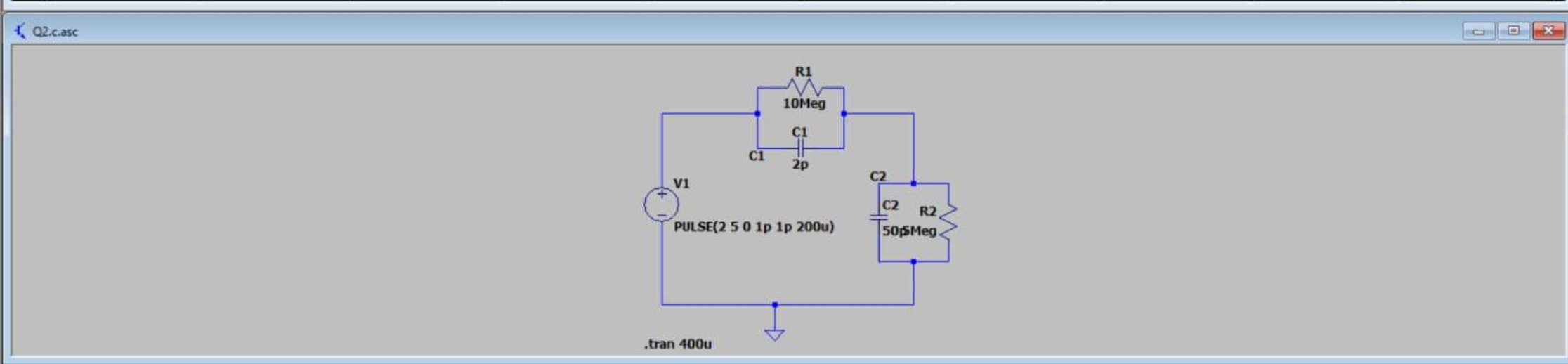
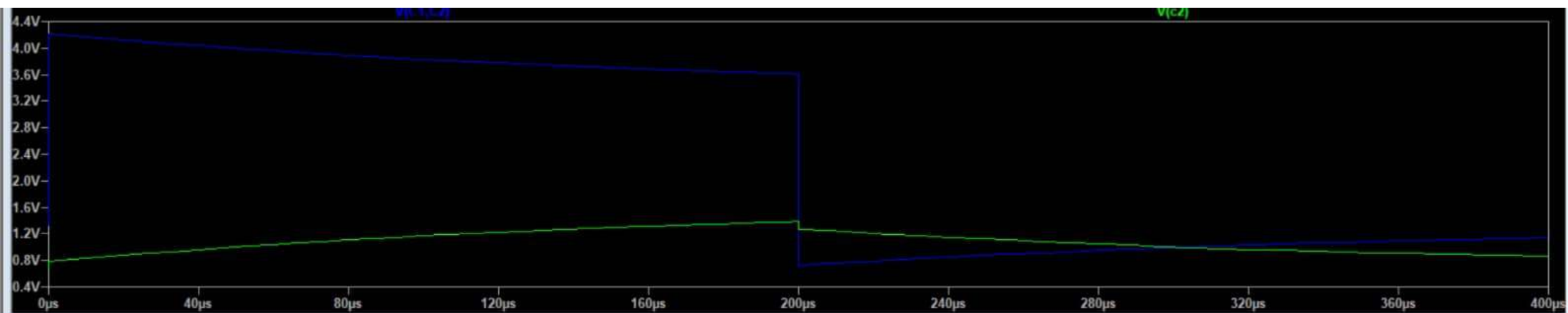
if this is possible, then $V_{C_1}(0^+)$ & $V_{C_2}(0^+)$ will remain fixed without transient changes.





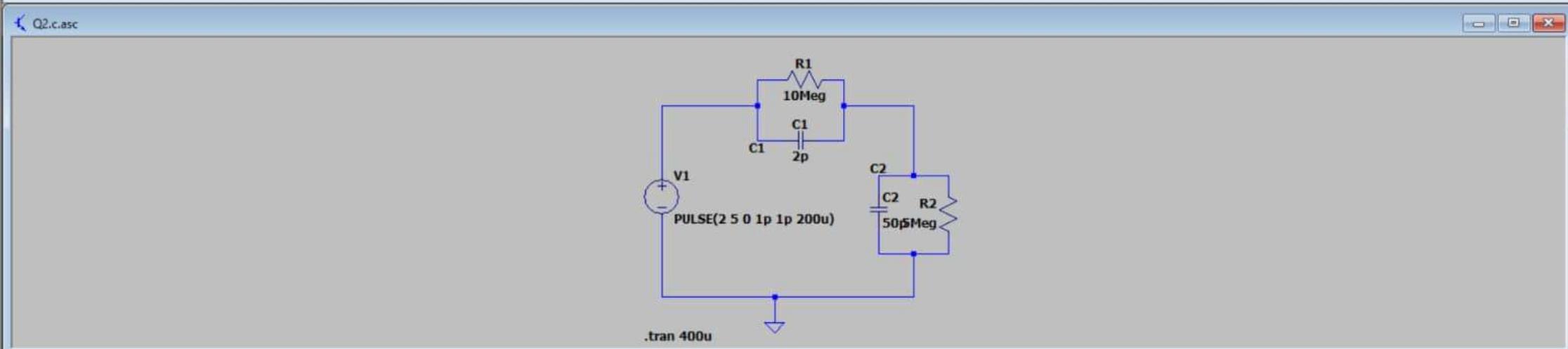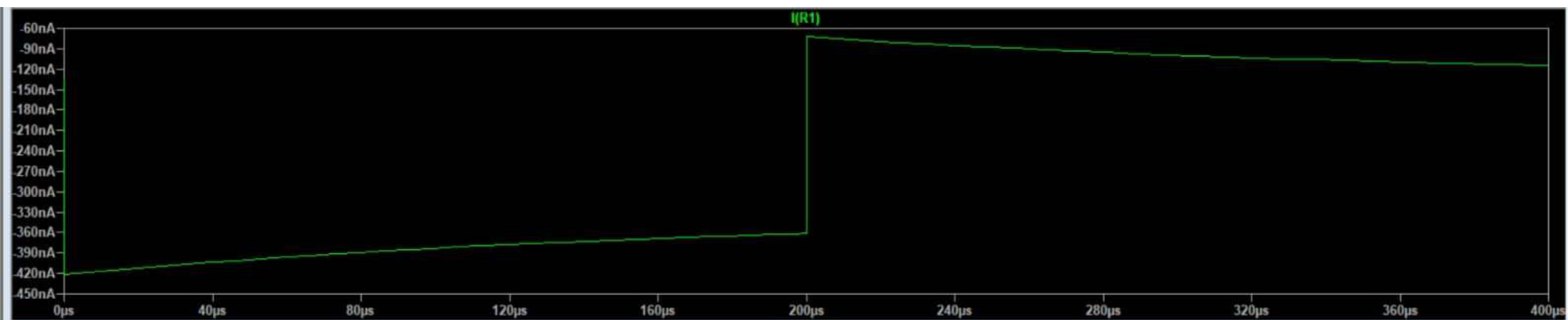


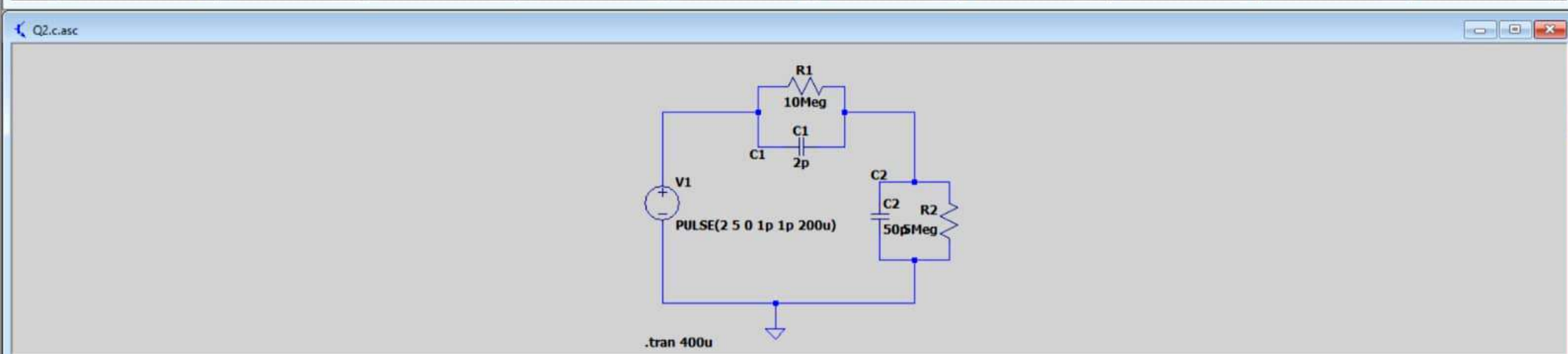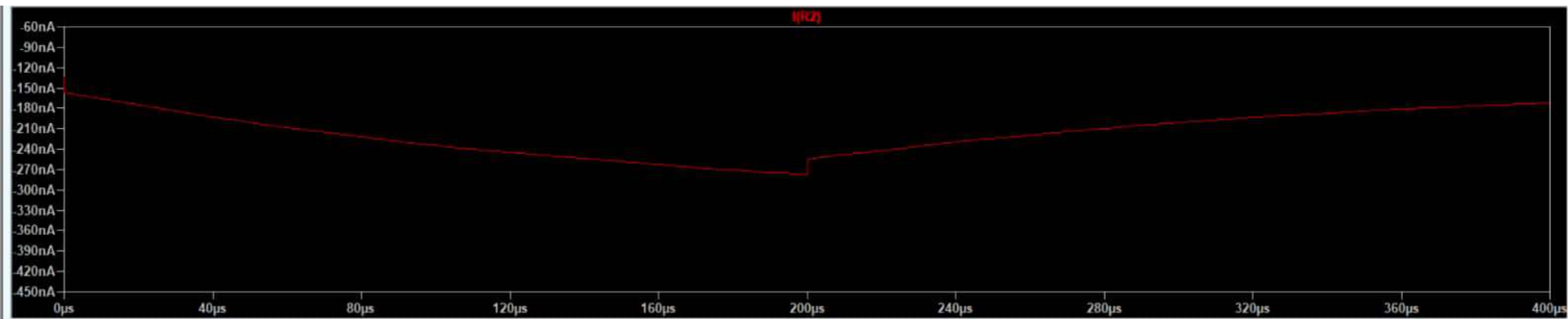


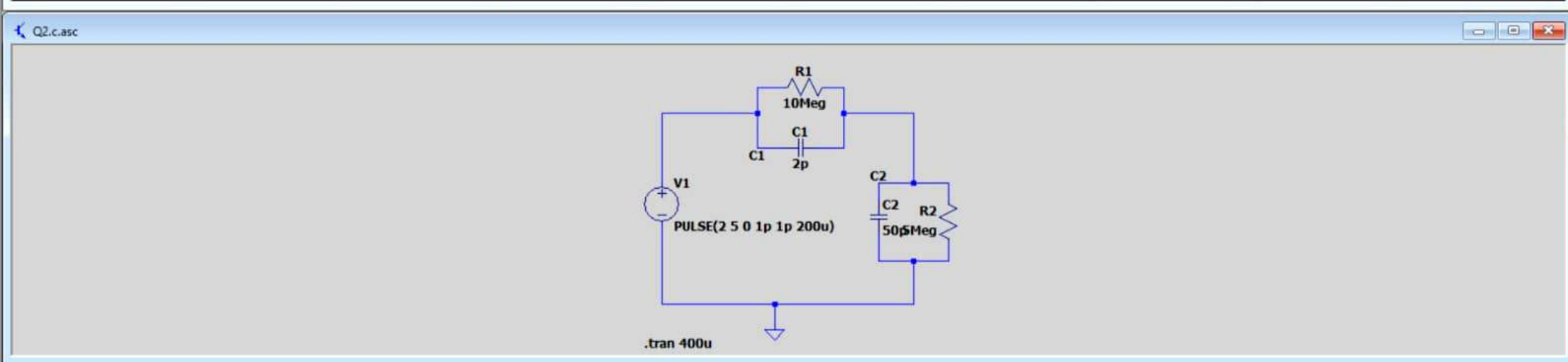
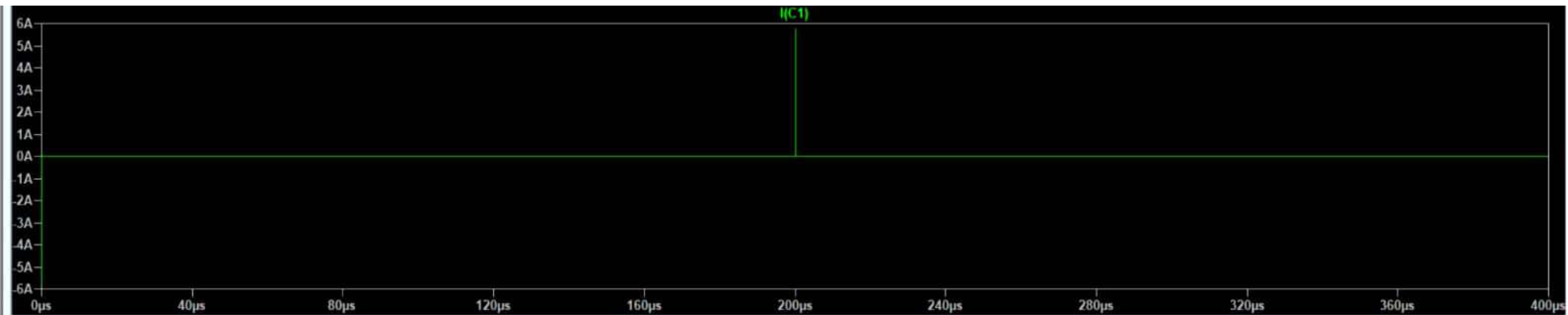


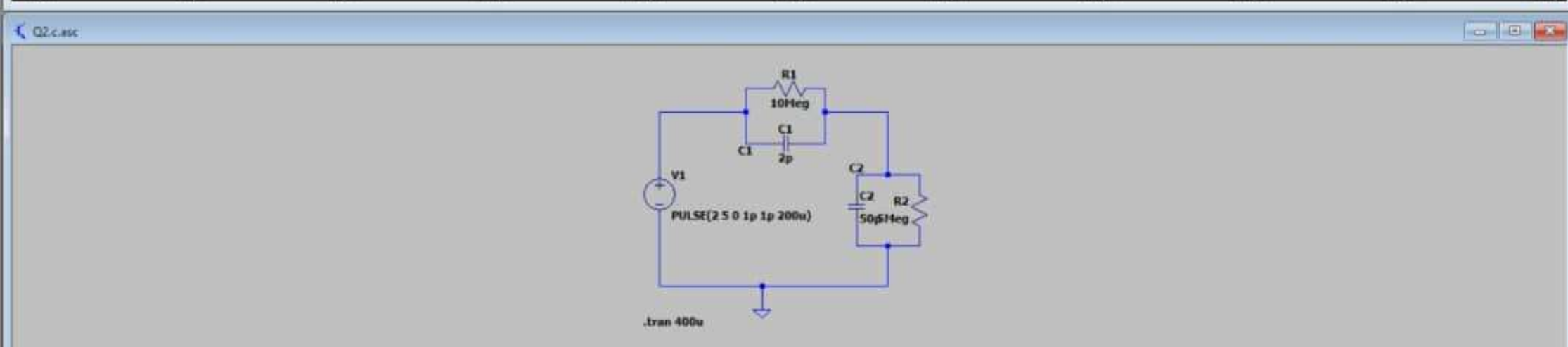
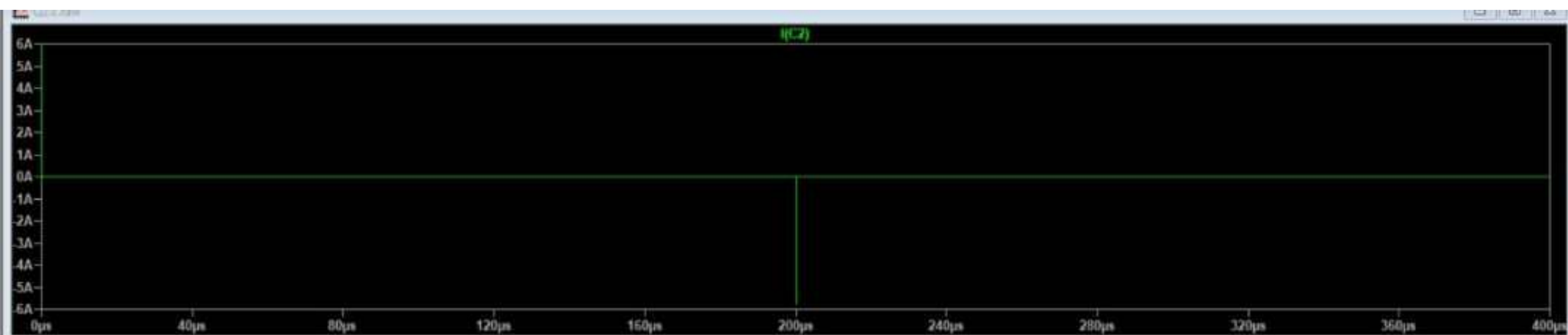


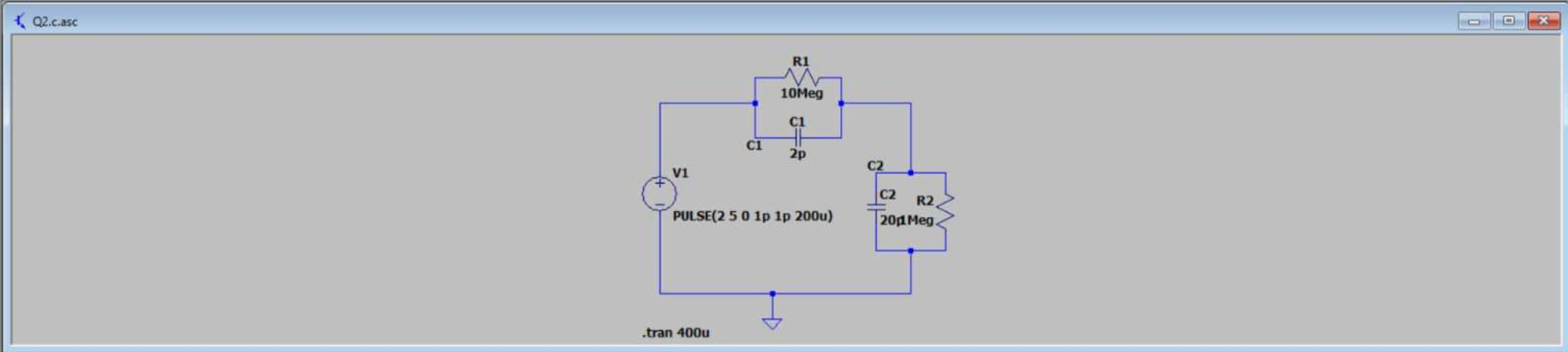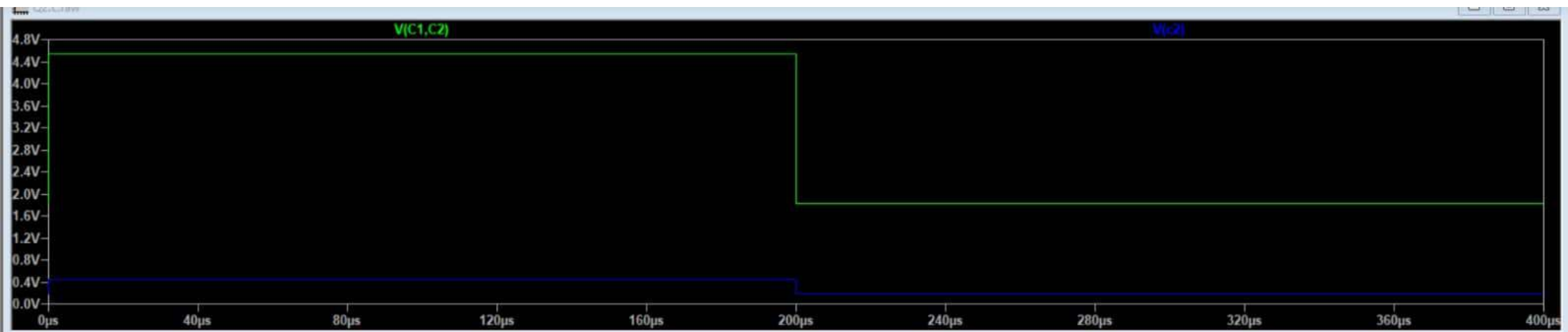

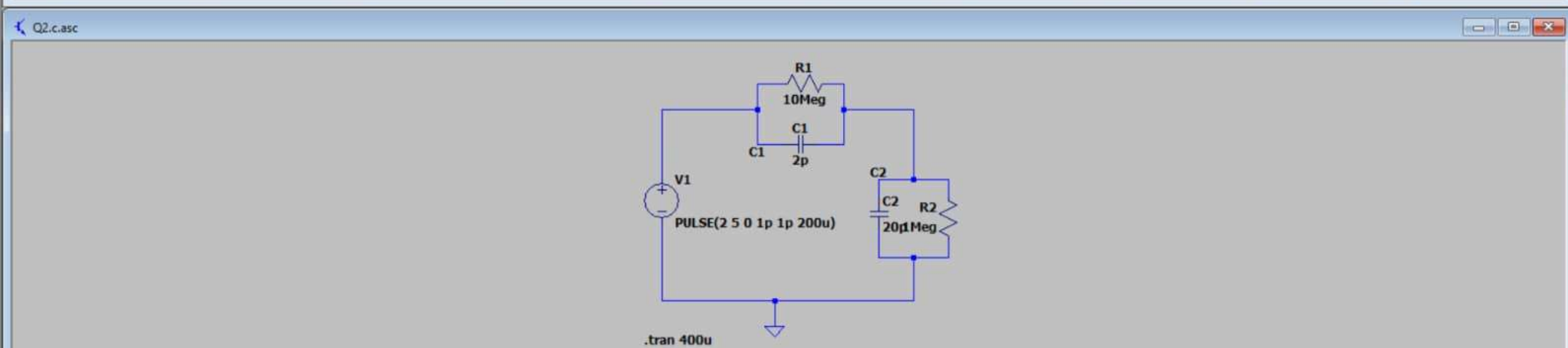

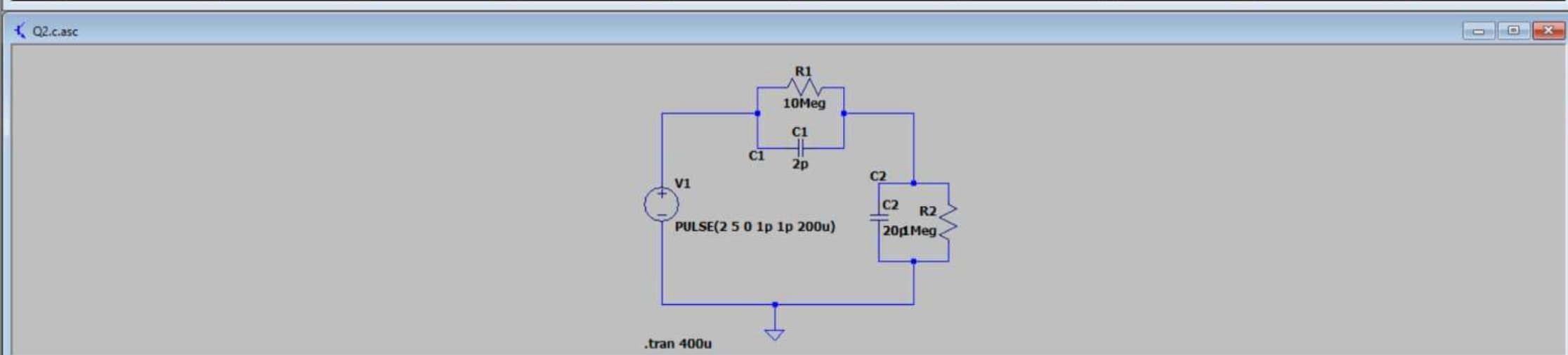

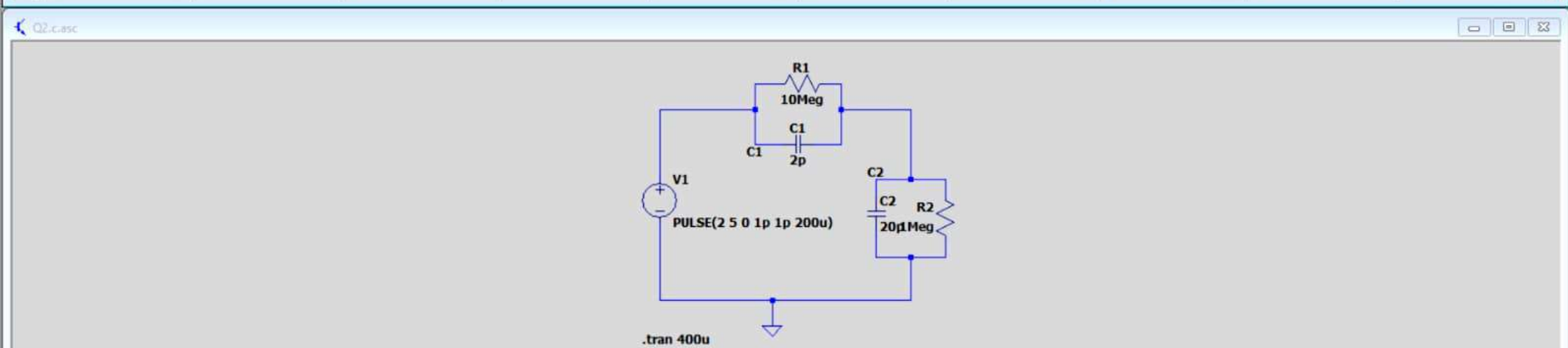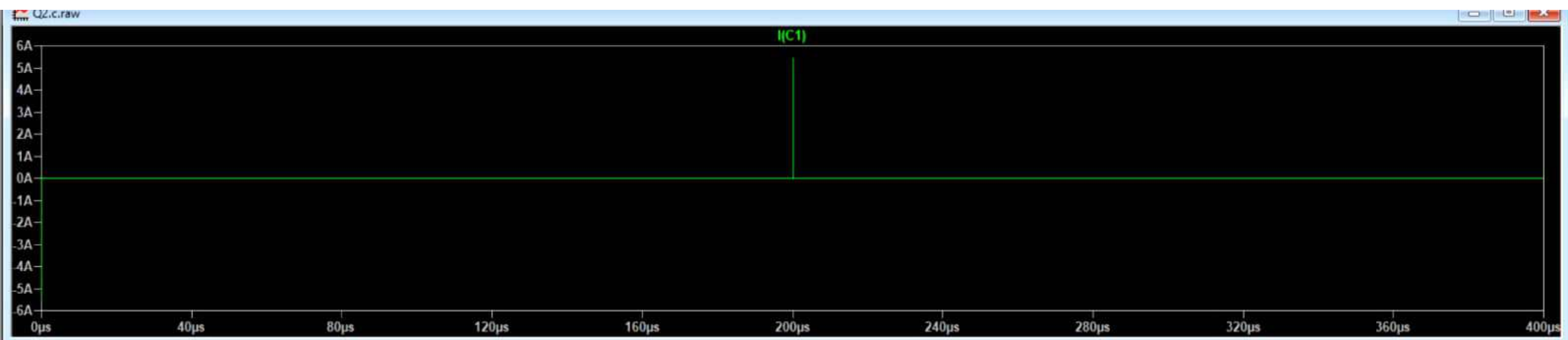

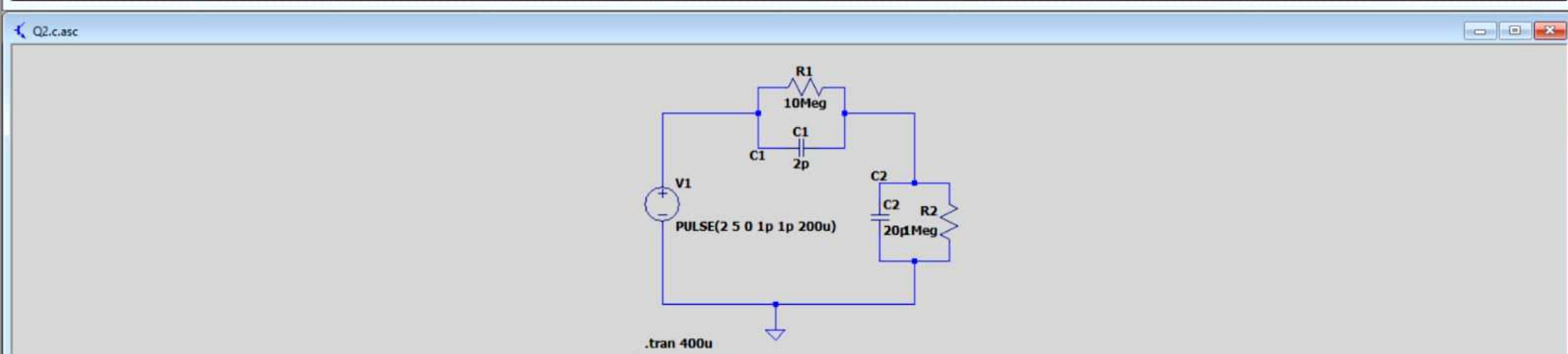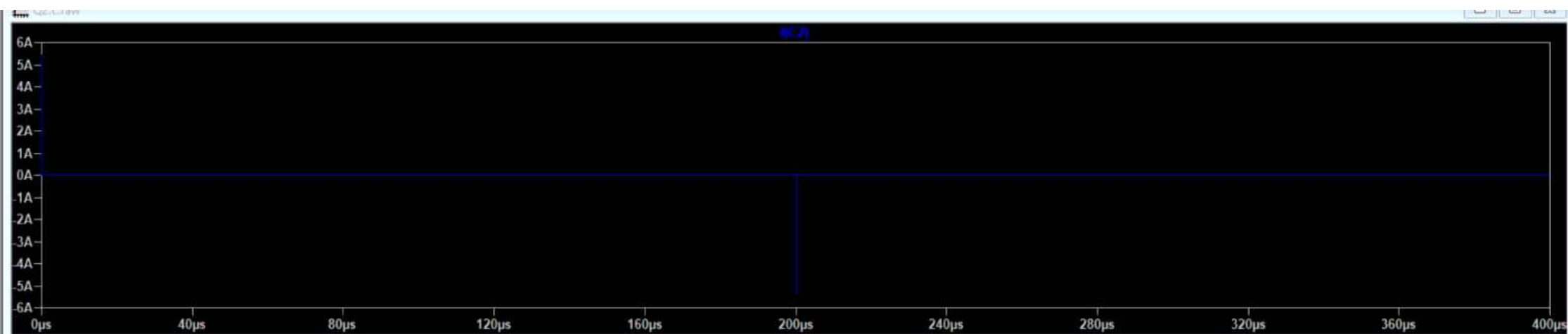

(iv)

Transfer Function :

$$\begin{aligned}
 \frac{V_{out}(s)}{V_{in}(s)} &= \frac{Z_2}{Z_1 + Z_2} \\
 &= \frac{\frac{R_2}{1 + sC_2R_2}}{\frac{R_2}{1 + sC_2R_2} + \frac{R_1}{1 + sC_1R_1}} \\
 &= \frac{R_2 (1 + sC_1R_1)}{R_1 + R_2 + R_1R_2s(C_1 + C_2)} \\
 &= \frac{R_2}{(R_1 + R_2)} \left(\frac{1 + sC_1R_1}{1 + sC_{eq}R_{eq}} \right) \\
 R_{eq} &= \frac{R_1R_2}{R_1 + R_2} ; C_{eq} = C_1 + C_2
 \end{aligned}$$

When,

$$R_1C_1 = R_2C_2$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{R_2}{R_1 + R_2}$$

Transfer function is constant.

Hence, it allows all the frequencies to pass through it.

∴ It is called an "ALL PASS FILTER".

Now,

$$\text{if } R_1 C_1 > R_2 C_2$$

$$\frac{R_1}{R_2} > \frac{C_2}{C_1}$$

in this case

$$\text{as } \omega \uparrow \Rightarrow \frac{V_{out}}{V_{in}} \uparrow \Rightarrow \text{High pass filter}$$

$$\text{if } R_1 C_1 < R_2 C_2$$

here,

$$\text{as } \omega \uparrow \Rightarrow \frac{V_{out}}{V_{in}} \downarrow \Rightarrow \text{Low pass filter.}$$

∴ When

Nature of circuit

$$R_1 C_1 = R_2 C_2 \rightarrow \text{All Pass circuit}$$

$$R_1 C_1 > R_2 C_2 \rightarrow \text{High pass}$$

$$R_1 C_1 < R_2 C_2 \rightarrow \text{Low pass}$$

(ii)

Yes, the circuit allows to pass quick transitions in input to the output in the cases where $R_1 C_1 > R_2 C_2$ [High pass]



And, it allows the slow transitions in input to output when $R_1 C_1 < R_2 C_2$ [Low Pass]

(iii)



(v) By observing the ~~transfer function~~ Bode ~~plot~~ plot below, we can clearly tell that transfer function of this circuit is constant when $R_1 C_1 = R_2 C_2$ at -20dB (approx).



Hence, there doesn't exist a -3dB bandwidth in the circuit.



plots shown below at

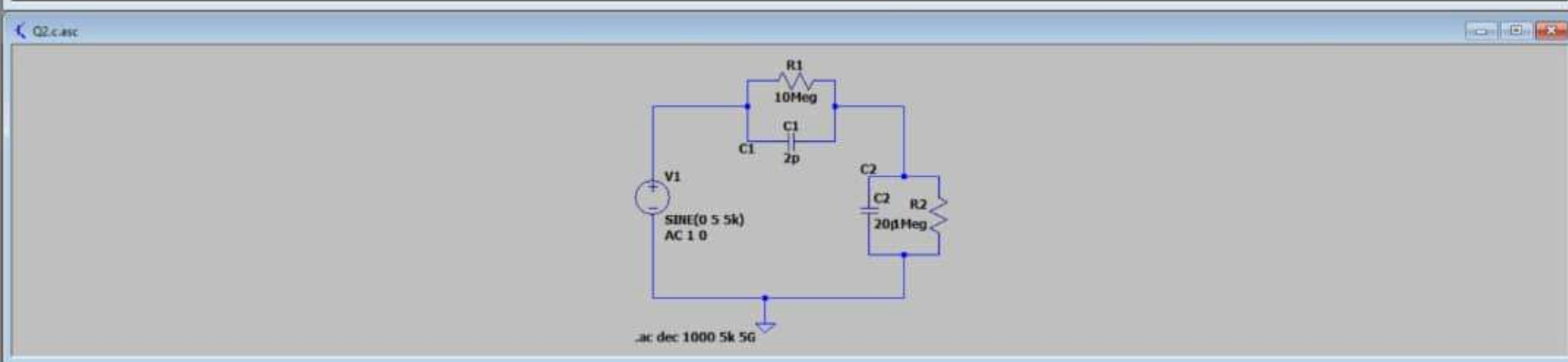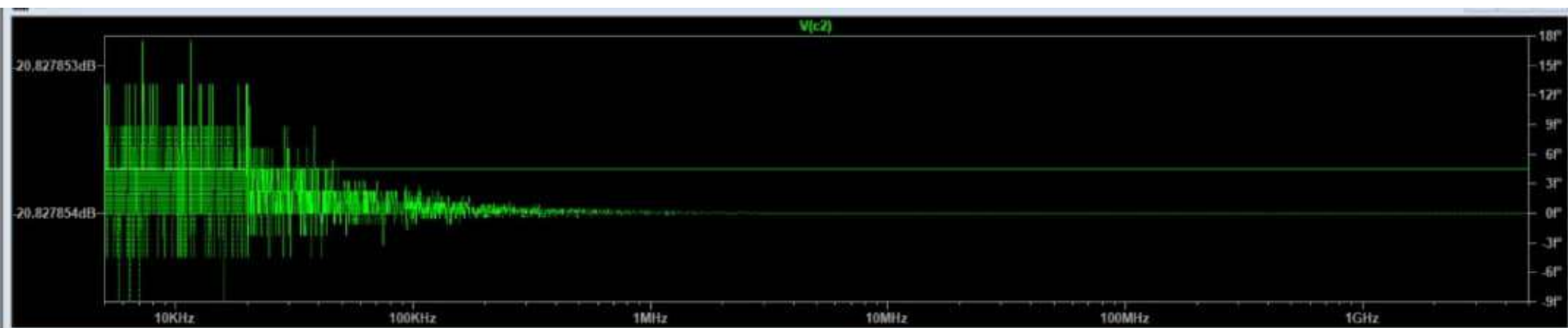

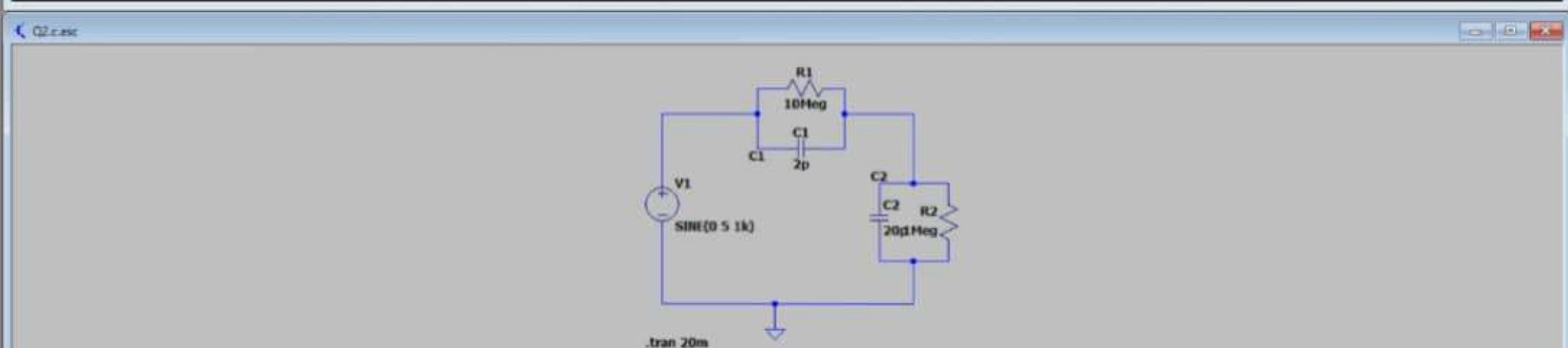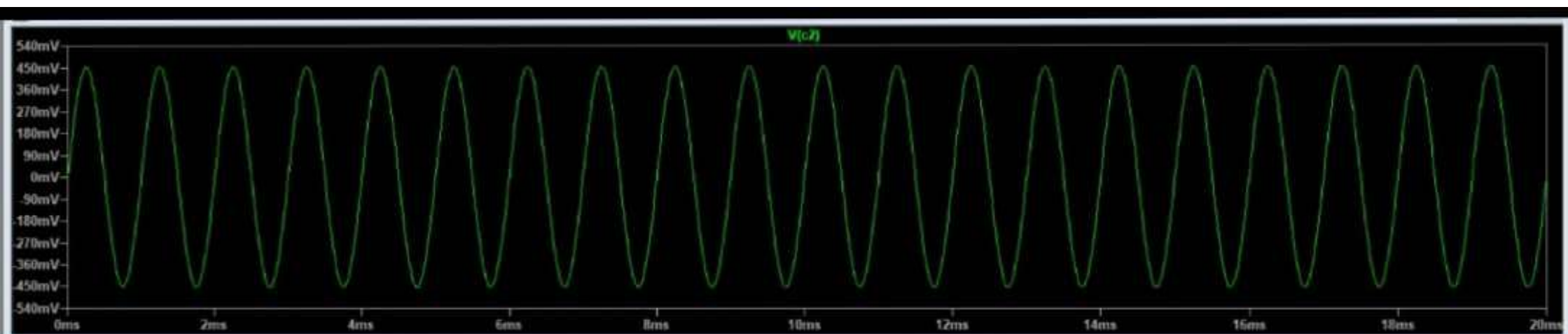(vi) From the three plots shown below at input frequencies $f = 1\text{ kHz}, 5\text{ kHz}, 10\text{ kHz}$, we can see that there is a change in the output frequency but not the amplitude.



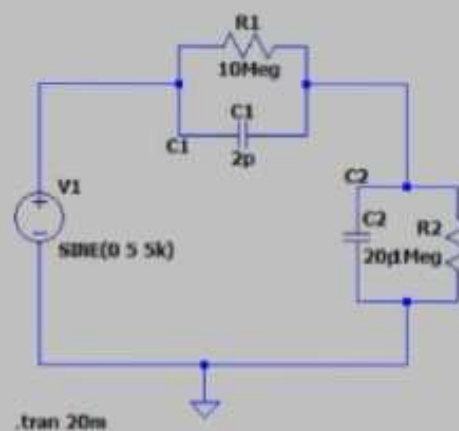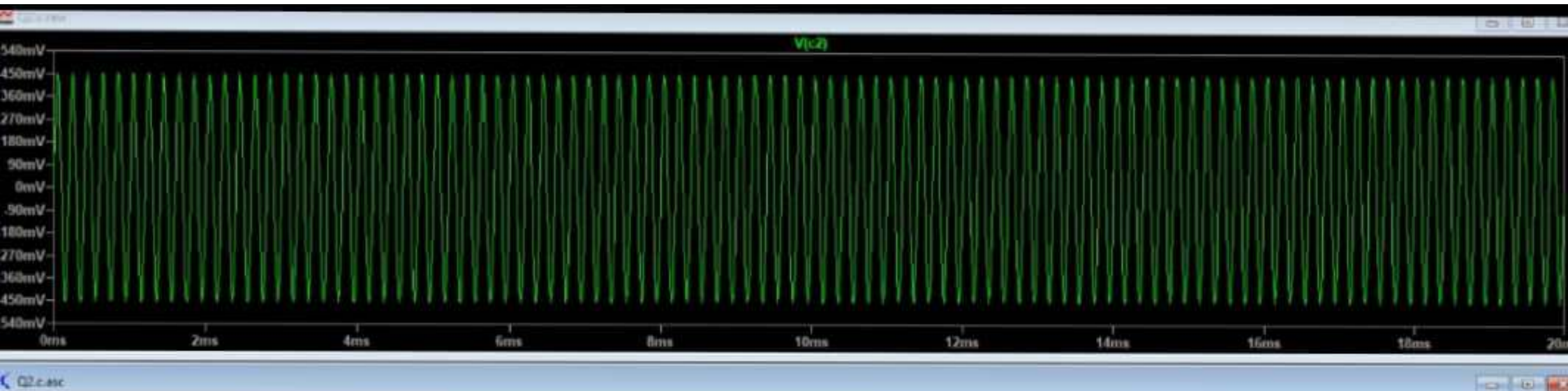

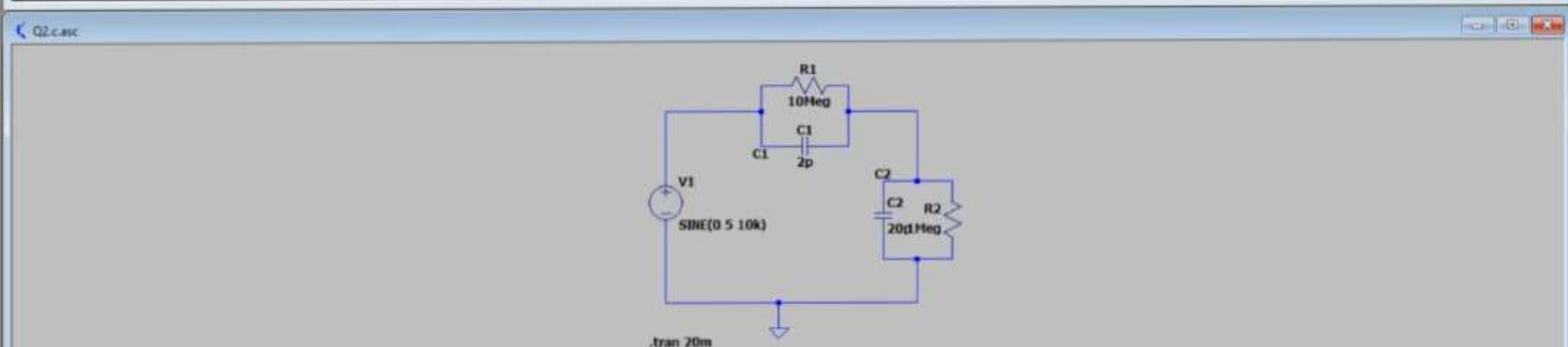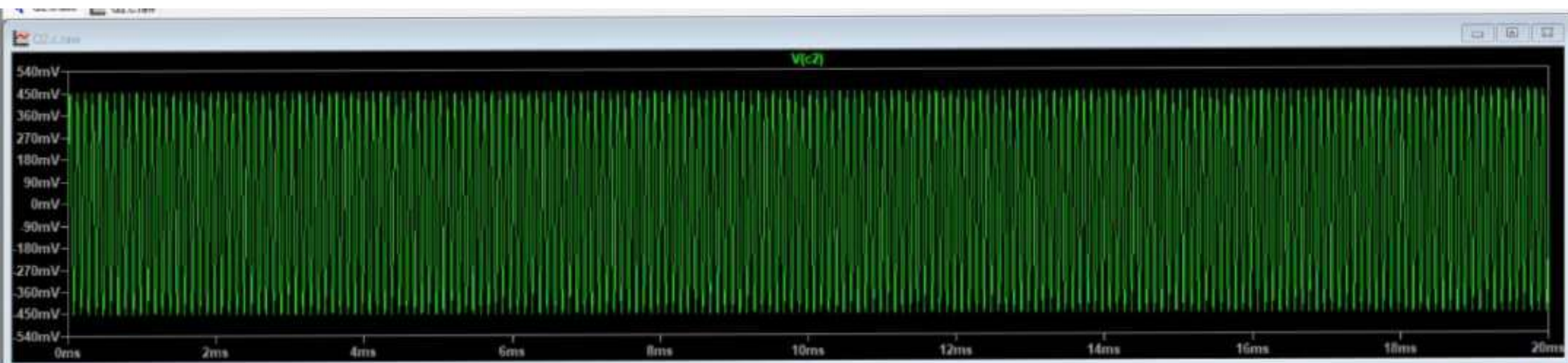

3) Bode Plots

$$(a) \quad H(j\omega) = 1 + j\omega T$$

$$|H(j\omega)| = \sqrt{1 + \omega^2 T^2}$$

$$\phi = \tan^{-1}(\omega T)$$

Take

$$20 \log |H(j\omega)| = 20 \log \sqrt{1 + \omega^2 T^2}$$


$$(i) \quad \omega \ll \frac{1}{T} \quad H(j\omega) = 0 \text{ dB}$$

$$(ii) \quad \omega = \frac{1}{T} \quad H(j\omega) = 3 \text{ dB}$$


$$(iii) \quad \omega \gg \frac{1}{T} \quad H(j\omega) = 20 \log(\omega T)$$

Magnitude Plot

$$20 \log |H(j\omega)|$$

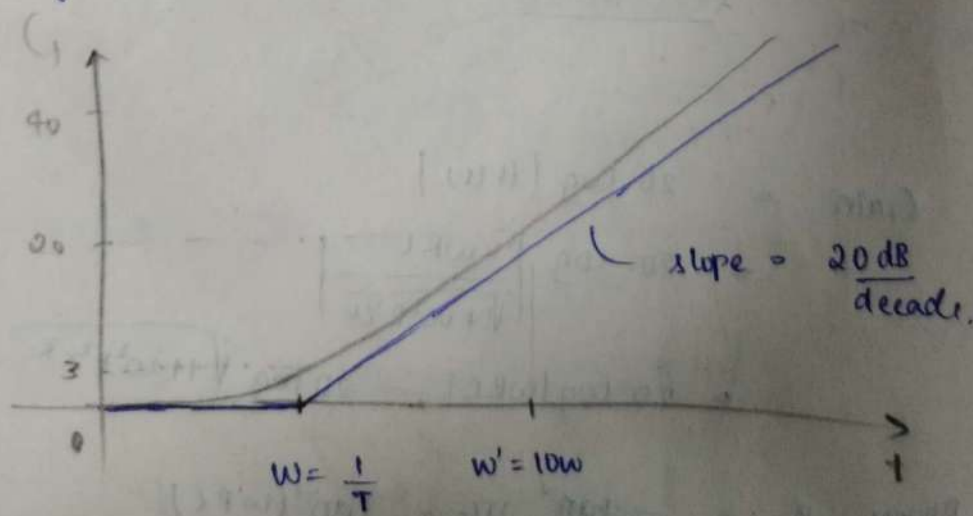

Phase Plot
 $\phi = \tan^{-1}(\omega T)$

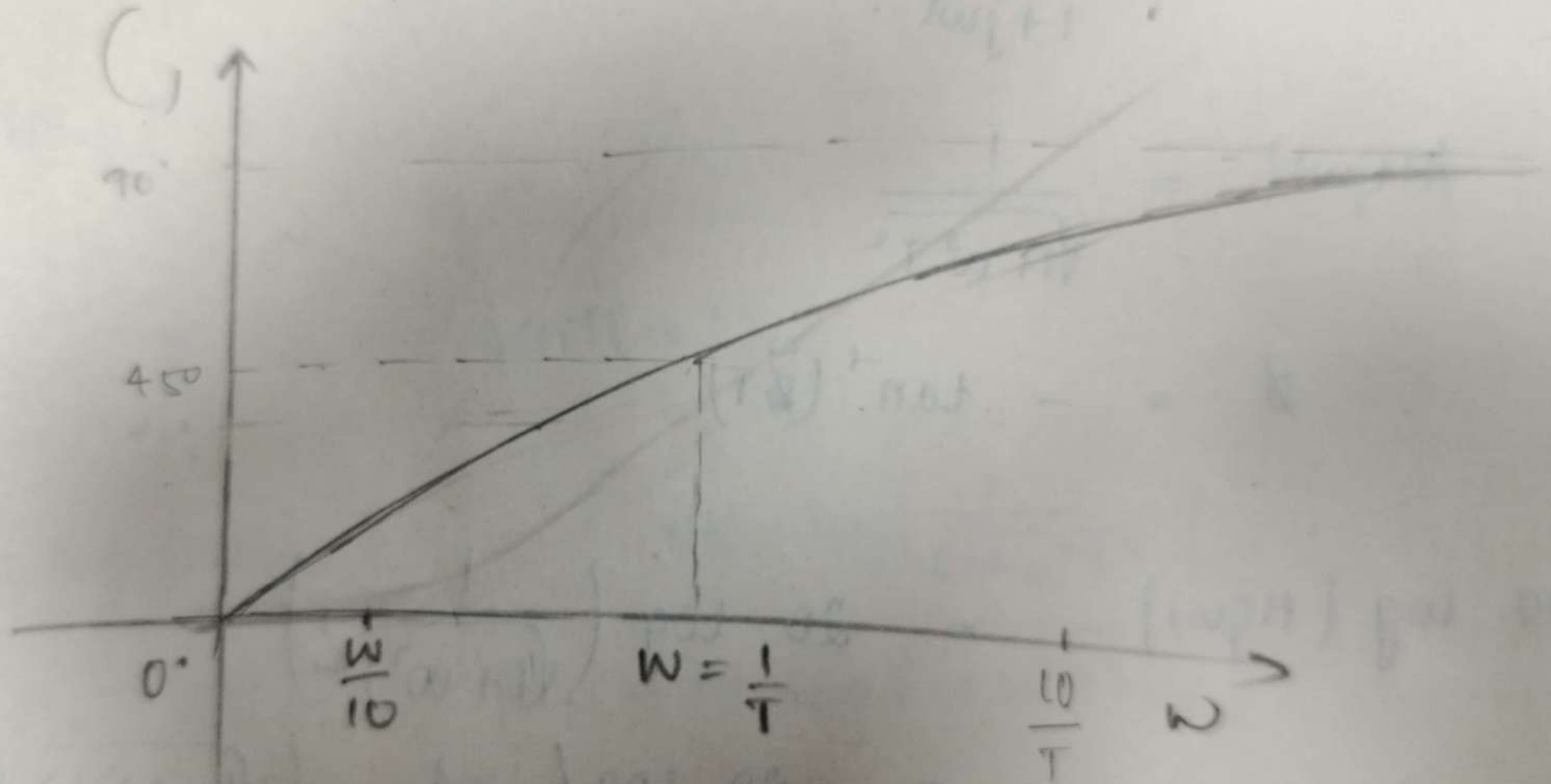

$$(b) \quad H(j\omega) = \frac{1}{1+j\omega T}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1+\omega^2 T^2}}$$


$$\phi = -\tan^{-1}(\omega T)$$

$$\begin{aligned} 20 \log |H(j\omega)| &= 20 \log \left(\frac{1}{\sqrt{1+\omega^2 T^2}} \right) \\ &= -20 \log \sqrt{1+\omega^2 T^2} \end{aligned}$$


$$(i) \quad \omega T \ll 1 \quad \Rightarrow \quad 0 \text{ dB}$$

$$(ii) \quad \omega T \approx 1 \quad \Rightarrow \quad -20 - 10 \log 2 = -3 \text{ dB}$$
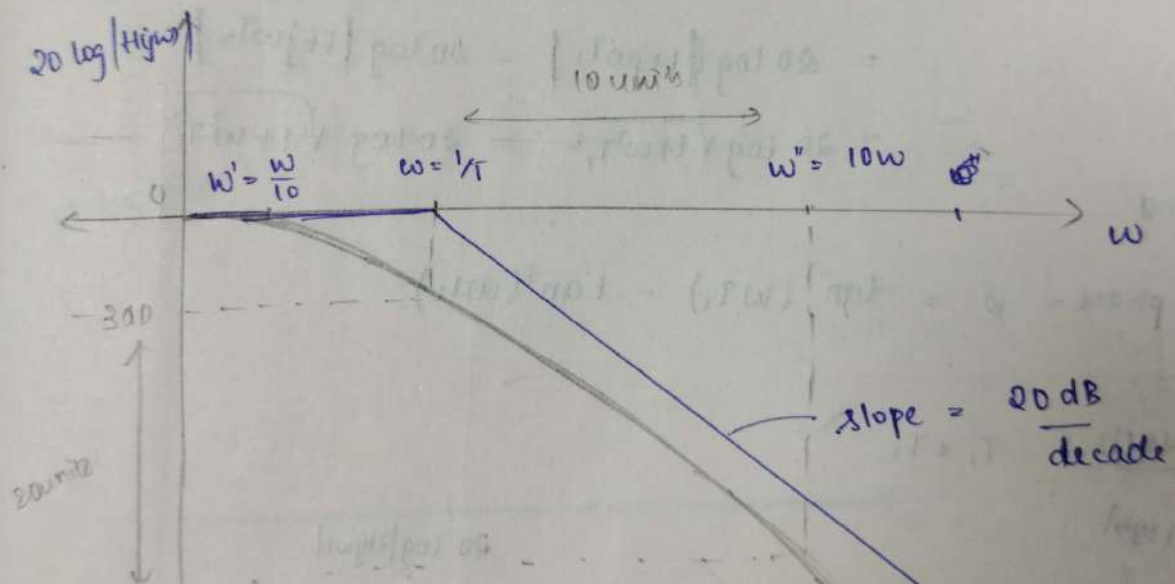
$$(iii) \quad \omega T \gg 1 \quad \Rightarrow \quad -20 \log(\omega T)$$



For every 10x change, $20 \log |H(j\omega)|$ changes by 20 units.

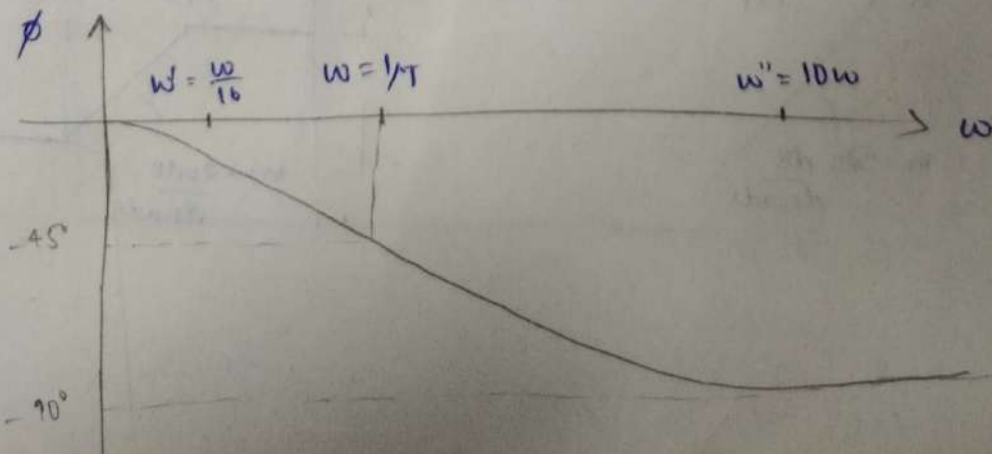



$$(c) \quad H(j\omega) = \frac{1+j\omega T_1}{1+j\omega T_2}$$

$$\begin{aligned} 20 \log |H(j\omega)| &= 20 \log \left| \frac{1+j\omega T_1}{1+j\omega T_2} \right| \\ &= 20 \log |1+j\omega T_1| - 20 \log |1+j\omega T_2| \\ &= 20 \log \sqrt{1+\omega^2 T_1^2} - 20 \log \sqrt{1+\omega^2 T_2^2} \end{aligned}$$


and

$$\text{phase} = \phi = \tan^{-1}(\omega T_1) - \tan^{-1}(\omega T_2)$$

Case (i) : $T_1 < T_2$

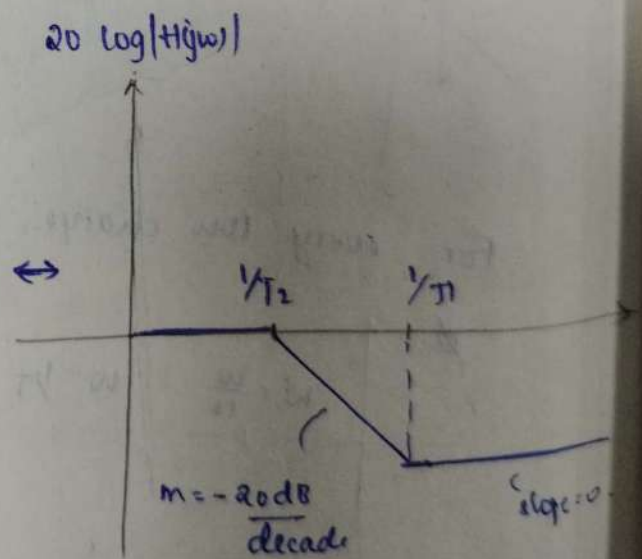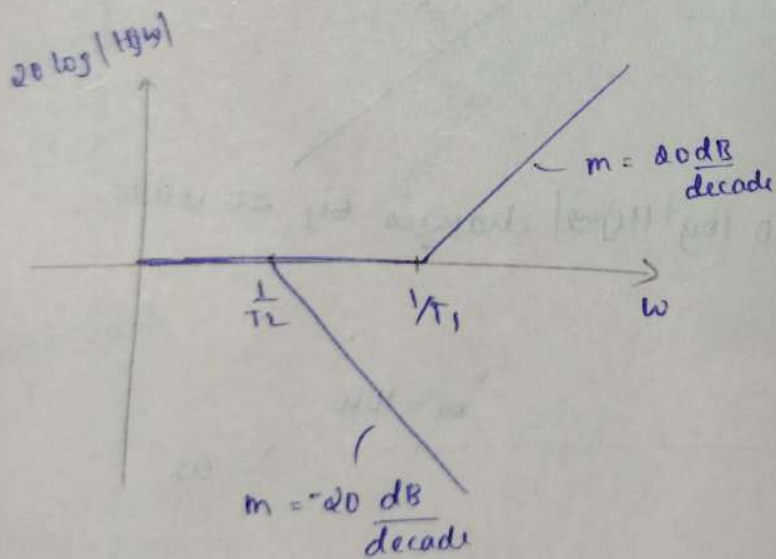


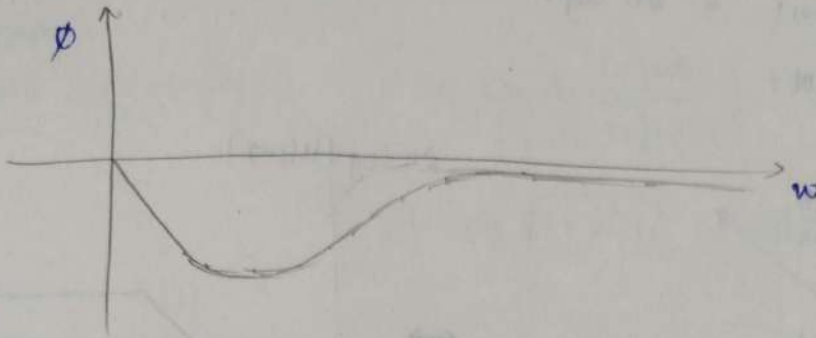
$$\phi = \tan^{-1}(\omega T_1) - \tan^{-1}(\omega T_2)$$



Case (ii) - $T_1 = T_2$

$$20 \log |H(j\omega)| = 20 \log \sqrt{1 + \omega^2 T_1^2} - 20 \log \sqrt{1 + \omega^2 T_2^2} = 0.$$
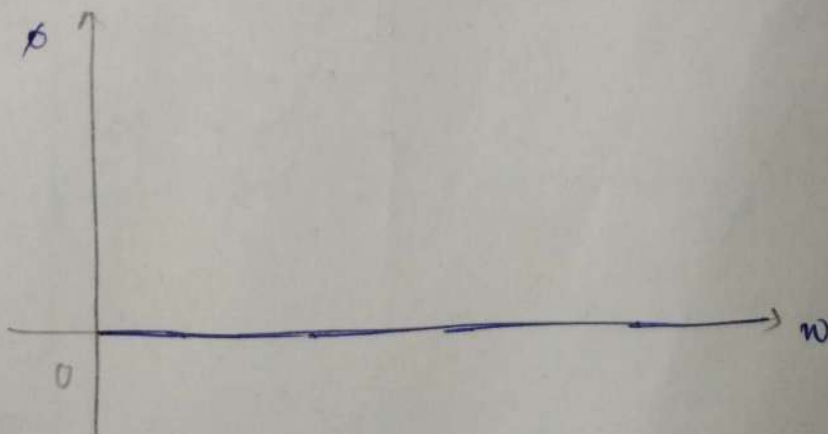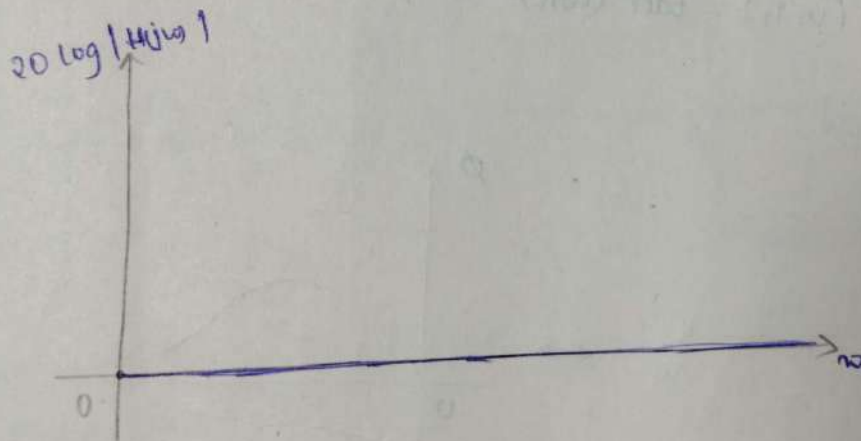
$$\phi = \tan^{-1}(\omega T_1) - \tan^{-1}(\omega T_2) = 0.$$




slope = 0.

Case (iii) $T_1 > T_2$


$$20 \log |H(j\omega)| = 20 \log \sqrt{1 + \omega^2 T_1^2} - 20 \log \sqrt{1 + \omega^2 T_2^2}$$

Magnitude Plot:

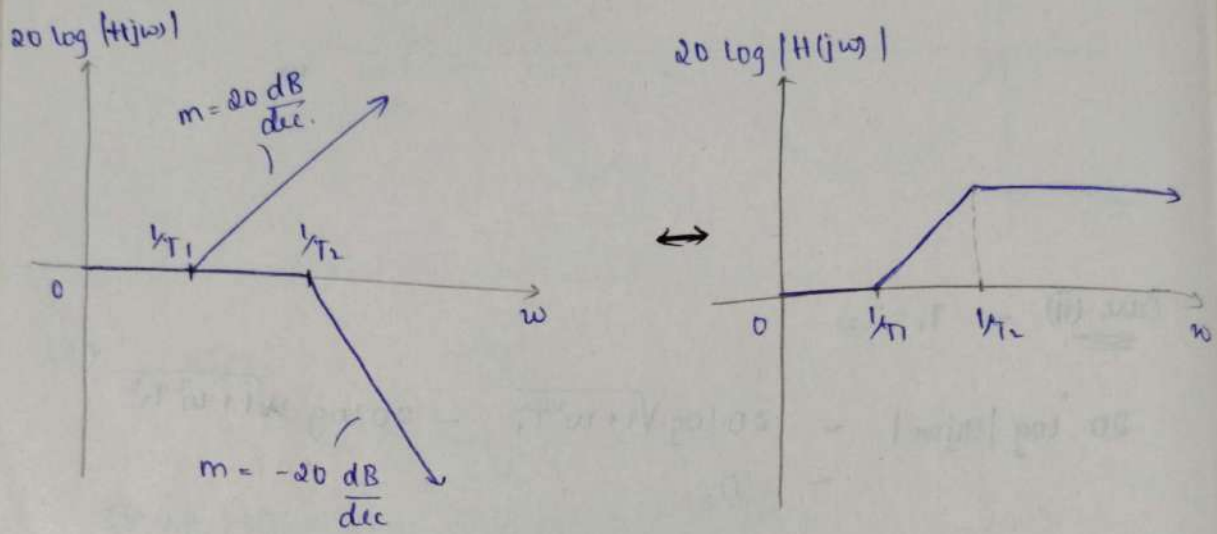

Phase Plot:
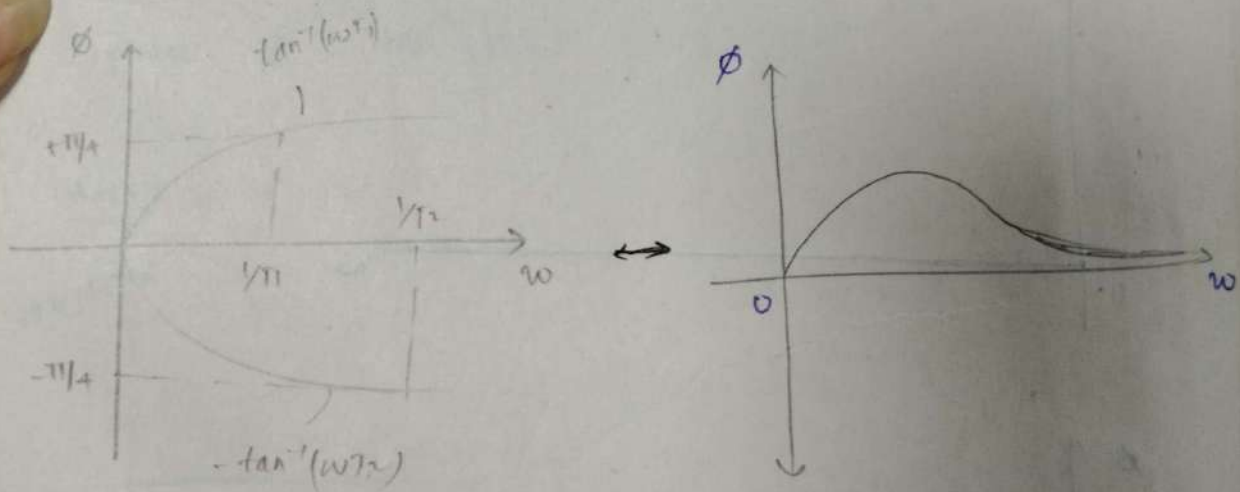
$$\phi = \tan^{-1}(\omega T_1) - \tan^{-1}(\omega T_2)$$



$$(d) \quad H(j\omega) = \frac{1 - j\omega T_1}{1 + j\omega T_2}$$

magnitude

$$20 \log |H(j\omega)| = 20 \log \left| \frac{1 - j\omega T_1}{1 + j\omega T_2} \right|$$


$$= 20 \log \sqrt{1 + \omega^2 T_1^2} - 20 \log \sqrt{1 + \omega^2 T_2^2}$$

$$\text{Phase, } \phi = \tan^{-1}(-\omega T_1) - \tan^{-1}(\omega T_2)$$


$$= -[\tan^{-1}(\omega T_1) + \tan^{-1}(\omega T_2)]$$

Case (i): $T_1 < T_2$

Magnitude Plot:

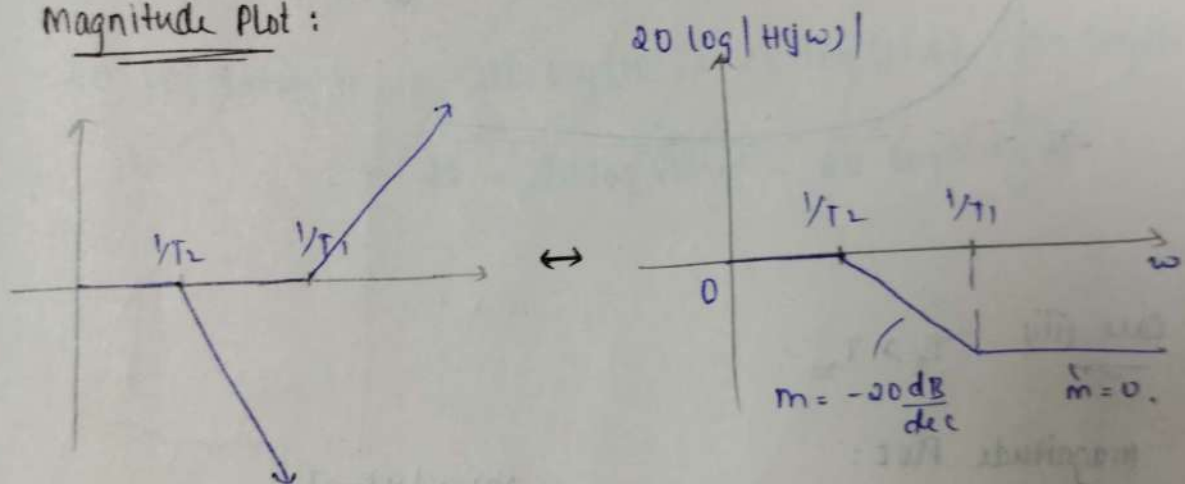


Phase Plot

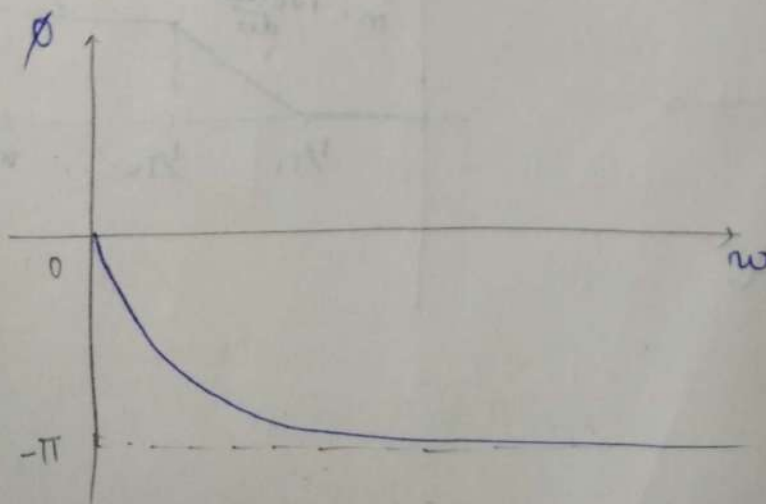

Case (ii) - $T_1 = T_2$


Magnitude = 0

Magnitude Plot

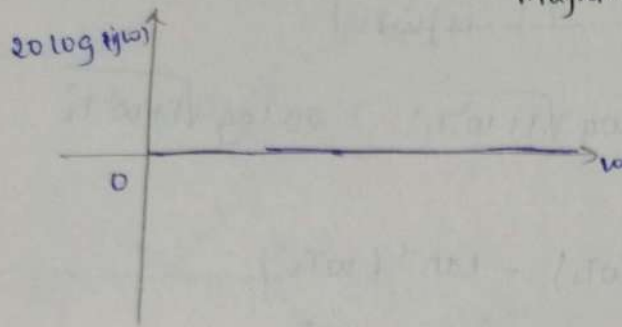



$$\phi = -2 \tan^{-1}(\omega T_1)$$

Phase Plot.

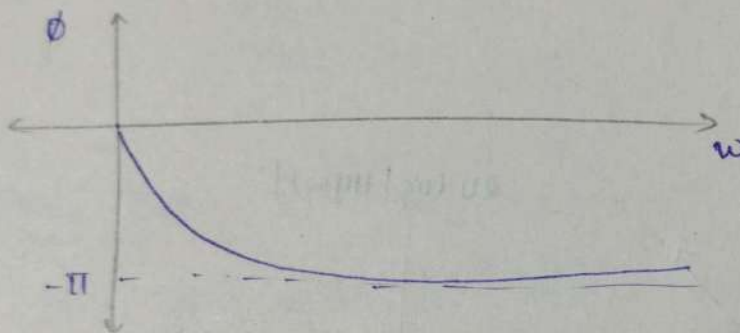


Case (iii) $T_1 > T_2$

Magnitude Plot:

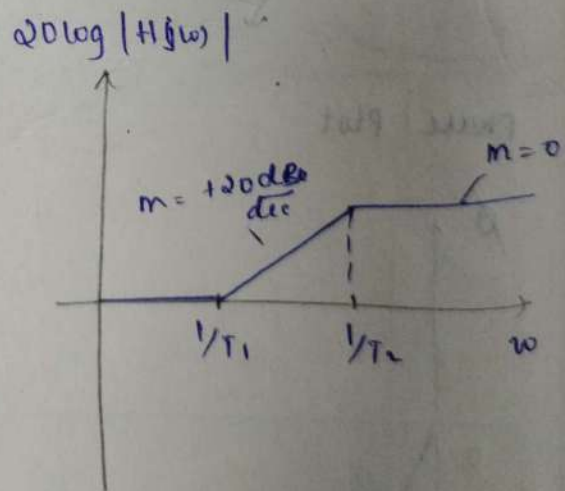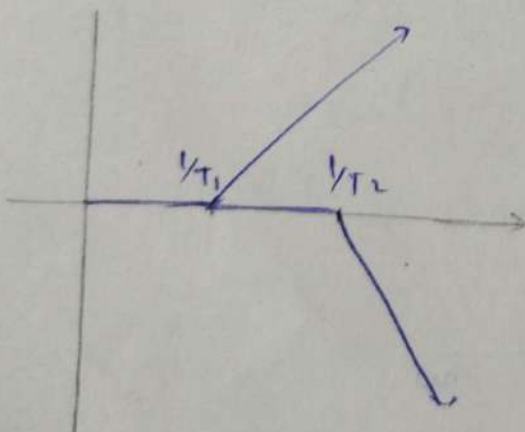


Phase plot:

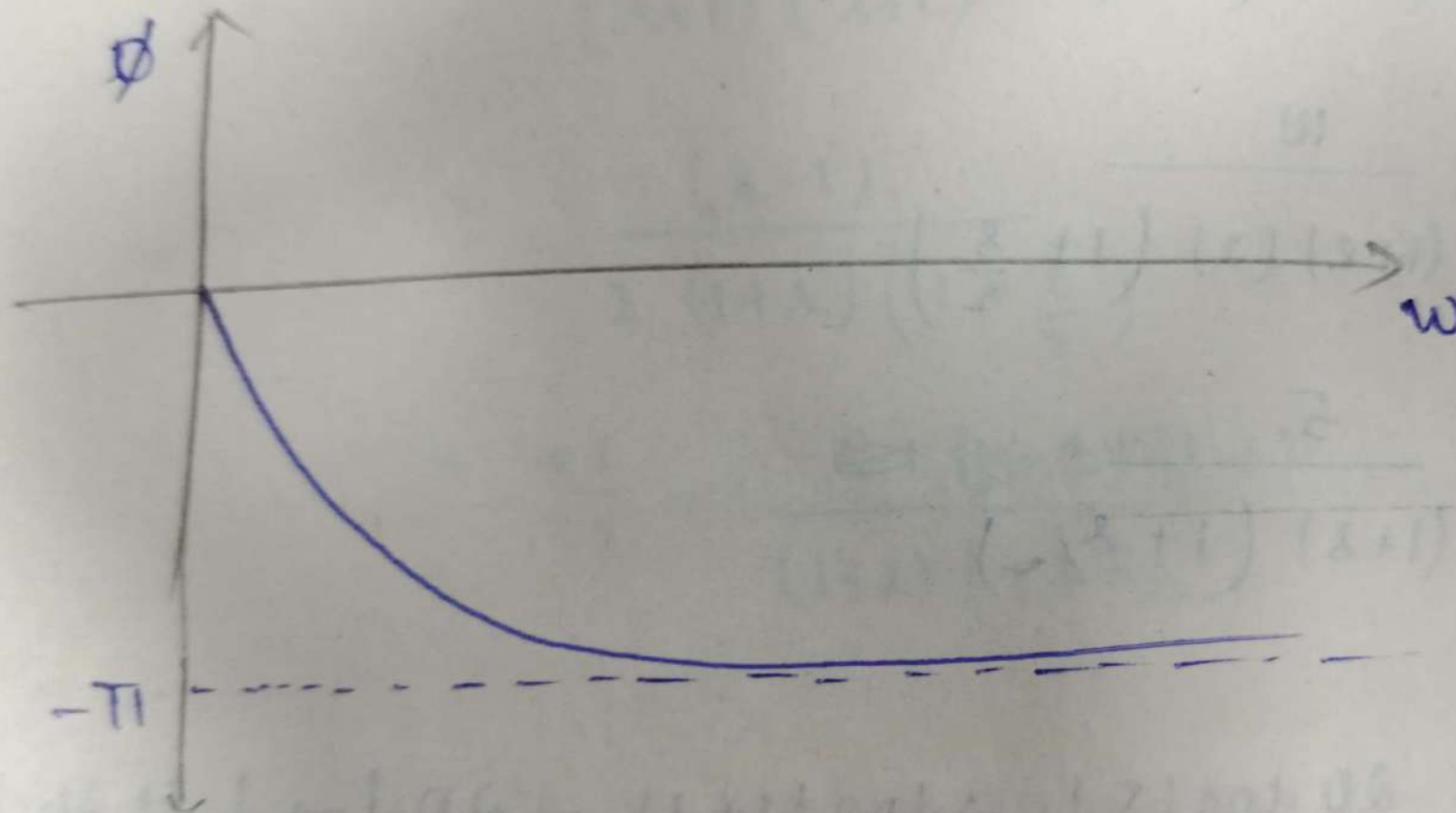


$$\begin{aligned}
 (e) \quad H(s) &= \frac{10}{(s+1)(s+2)} \\
 &= \frac{10}{(1+s)(2)(1+\frac{s}{2})} \\
 &= \frac{5}{(1+s)(1+\frac{s}{2})}
 \end{aligned}$$

$$\begin{aligned}
 20 \log |H(s)| &= 20 \log(5) - 20 \log |1+s| - 20 \log |1+\frac{s}{2}| \\
 &= 14 - 20 \log \sqrt{1+\omega^2} - 20 \log \sqrt{1+\frac{\omega^2}{4}} \\
 &= 14 - 20 \log \sqrt{1+\omega^2} - 20 \log \sqrt{1+\omega^2(\frac{1}{2})^2}
 \end{aligned}$$

Magnitude Plot:

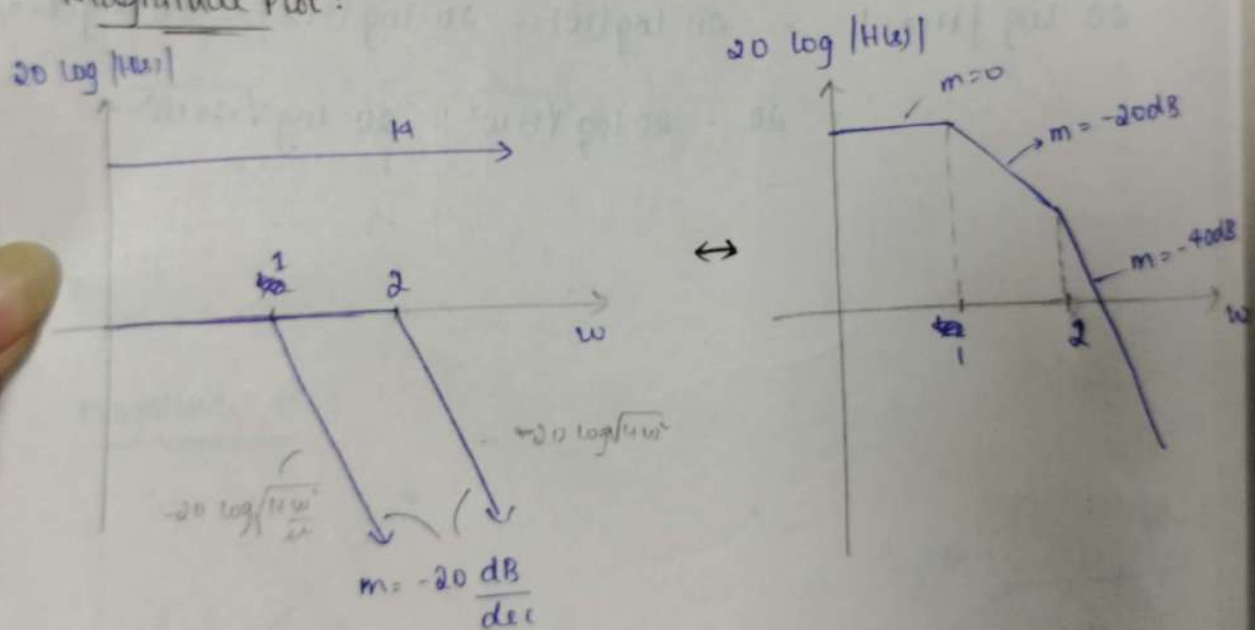


Phase Plot:

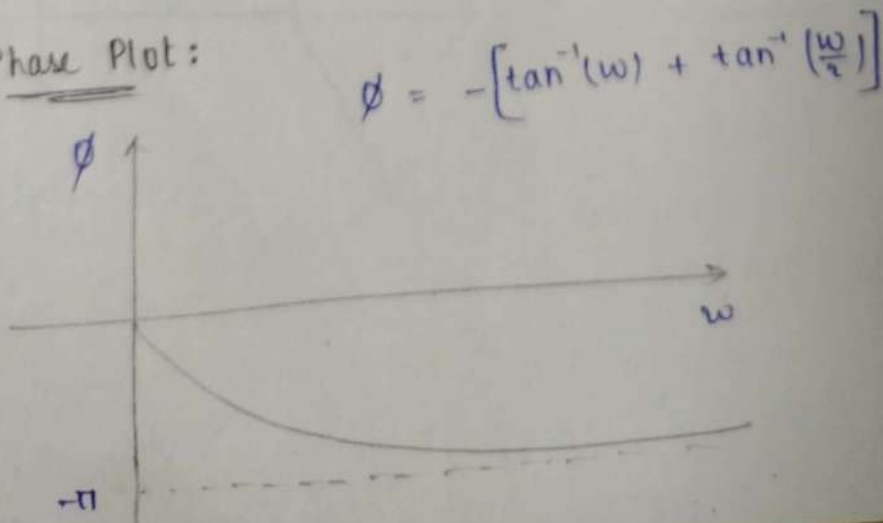


$$\begin{aligned}
 (f) \quad H(s) &= \frac{(s-1)}{(s+1)(s+2)} \\
 &= \frac{(s-1)}{2(1+s)\left(1+\frac{s}{2}\right)} \\
 &= +\frac{1}{2} \frac{(s-1)}{(1+s)(1+s/2)}
 \end{aligned}$$

$$\begin{aligned}
 20 \log |H(j\omega)| &= 20 \log |s-1| - 20 \log |1+s| - 20 \log \left|1+\frac{s}{2}\right| - 20 \log 2 \\
 &= 20 \log \sqrt{1+\omega^2} - 20 \log \sqrt{1+\omega^2} - 20 \log \sqrt{1+\omega^2/4} - 6 \\
 &= -6 - 20 \log \sqrt{1+\omega^2/4}
 \end{aligned}$$

Magnitude Plot:

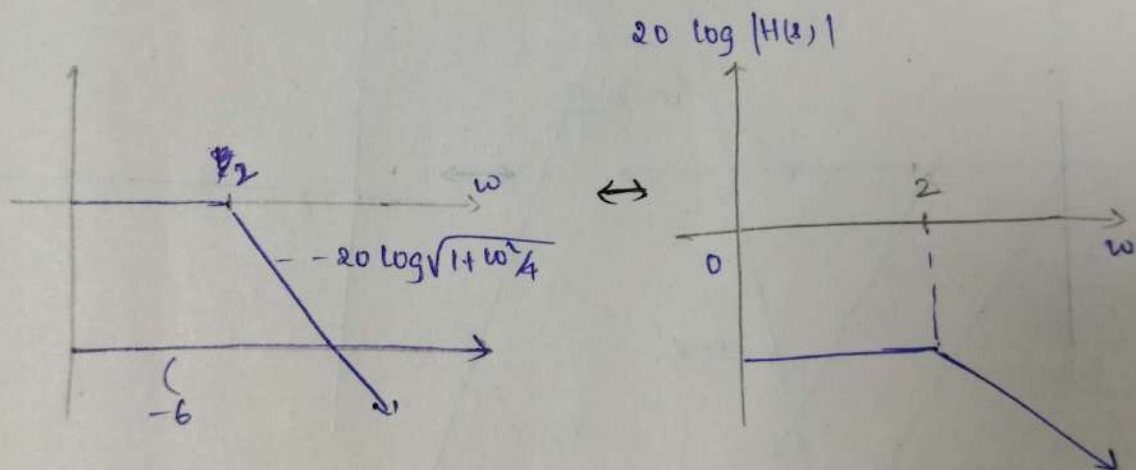

Phase Plot:

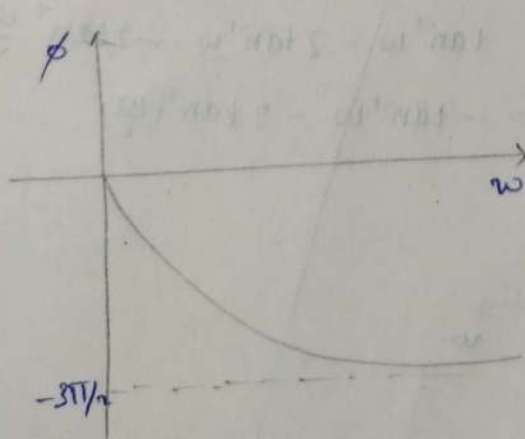

$$\begin{aligned}
 \phi &= \tan^{-1}(-\omega) - \tan^{-1}(\omega) - \tan^{-1}(\omega/2) \\
 &= -2 \tan^{-1} \omega - \tan^{-1}(\omega/2)
 \end{aligned}$$

$$(g) \quad H(s) = \frac{2(s+1)}{s^2(s+2)(s+0.5)}$$

$$= \frac{2(s+1)}{(s)(s)(s) \left(1+\frac{s}{2}\right) \left(1+\frac{s}{0.5}\right)}$$

$$= \frac{2(s+1)}{(s)(s) \left(1+\frac{s}{2}\right) (1+2s)}$$



$$20 \log |H(s)| = 20 \log 2 + 20 \log |s+1| - 2(20) \log |s|$$

$$- 20 \log \left|1+\frac{s}{2}\right| - 20 \log |1+2s|$$

$$= 6 + 20 \log \sqrt{1+\omega^2} - 40 \log \omega$$


$$- 20 \log \sqrt{1+\frac{\omega^2}{4}} - 20 \log \sqrt{1+4\omega^2}$$

Magnitude Plot :

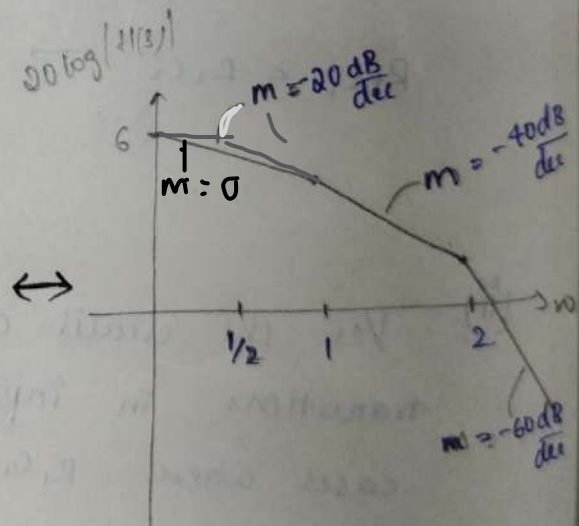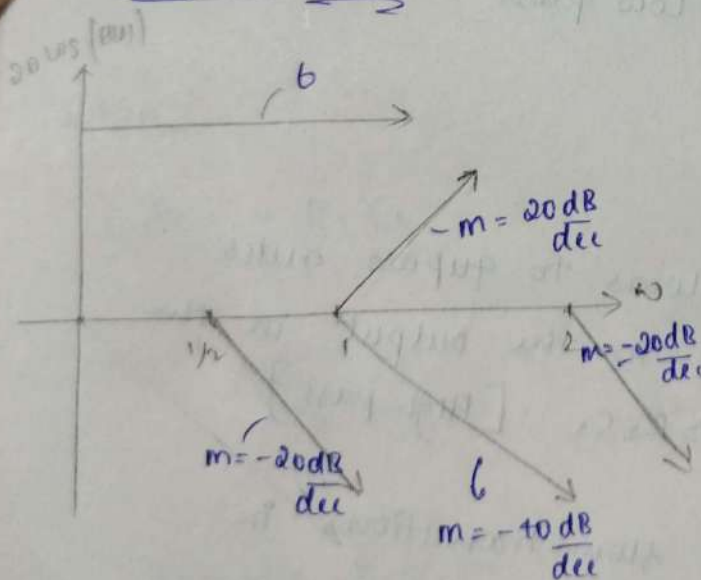

Phase Plot:
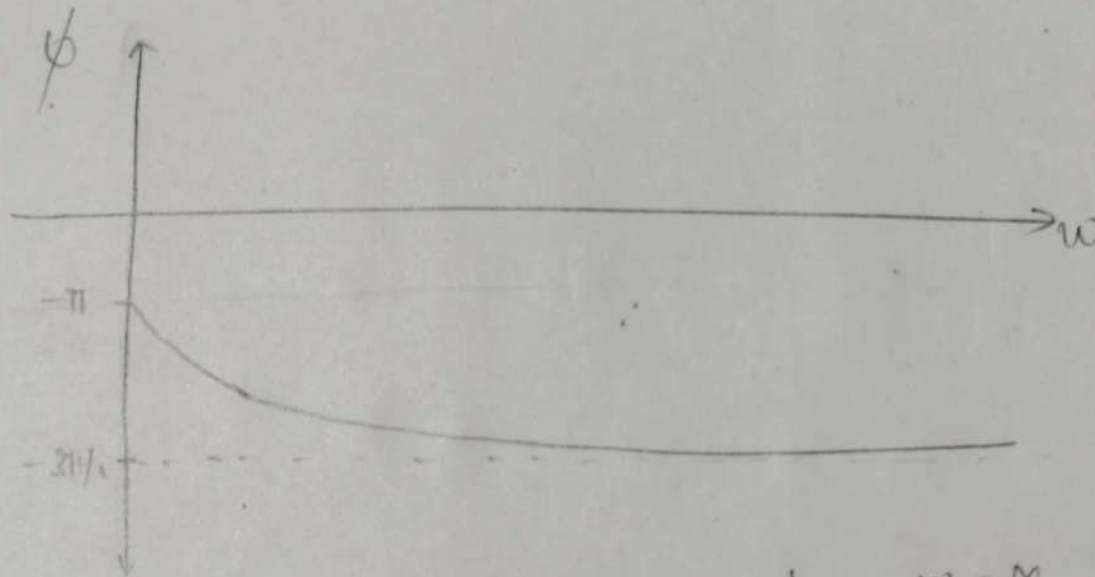
$$\phi = \tan^{-1} \omega - \pi/2 - \tan^{-1} \left(\frac{\omega}{2} \right) - \tan^{-1} (2\omega)$$



$$\begin{aligned} \text{when } \omega = \infty & \quad \phi = -3\pi/2 \\ \omega = 0 & \quad \phi = -\pi \end{aligned}$$