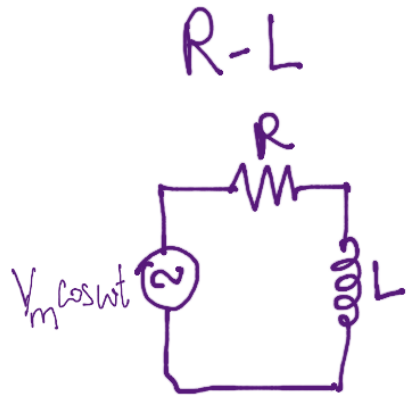


Sinusoid Response



KVL

$$L \frac{di}{dt} + iR = V_m \cos \omega t$$

①

input angular freq: (rad/s)

freq. of input sig.

$\pi \text{ rad} = 180^\circ$

Solution i will be form of $\sin \omega t$ and $\cos \omega t$

$$i = I_1 \cos \omega t + I_2 \sin \omega t$$

Substitute i in ① and separate $\cos \omega t$ & $\sin \omega t$ terms & = 0.

\Rightarrow Solve I_1 & I_2 (constants)


$(-e^{at}) \rightarrow \text{avg}$

$$i = \frac{RV_m}{(R^2 + \omega^2 L^2)} \cos \omega t + \frac{\omega L V_m}{(R^2 + \omega^2 L^2)} \sin \omega t$$

$$i = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \left[\frac{R}{\sqrt{R^2 + \omega^2 L^2}} \cos \omega t + \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} \sin \omega t \right]$$

$\cos \theta$

$\sin \theta$

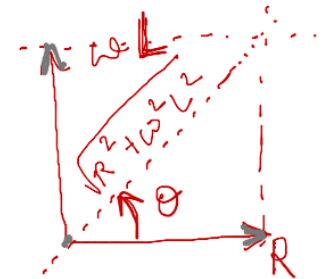

S.S after
Nat. response
decay \therefore

$$i = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos \left(\omega t - \tan^{-1} \frac{\omega L}{R} \right) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \text{Re} \left(e^{j(\omega t - \theta)} \right)$$

Observations (L-R)

- i LAGS behind V_s by $\tan^{-1} \frac{\omega L}{R}$ [if $R \rightarrow 0$ $\text{lag} = 90^\circ$]

- $i \propto V_s \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}}$

- $j\omega L$ is called INDUCTIVE REACTANCE (X_L)

Forced response: Steady State response (here) is time varying but does not decay. (we allow the transient natural response to die)

Complex Forcing Function (easy method to solve)

$$(j = i = \sqrt{-1})$$

- Replace $V_m \cos \omega t$ supply $\rightarrow V_m e^{j\omega t}$ (Real)

- Let us assume a solution of form $I_m e^{j(\omega t + \phi)}$ ϕ - phase shift.

$$\rightarrow L \frac{di}{dt} + iR = L I_m j\omega e^{j(\omega t + \phi)} + R I_m e^{j(\omega t + \phi)} = V_m e^{j\omega t}$$
$$\Rightarrow \underline{I_m (j\omega L + R) e^{j\phi}} = V_m \Rightarrow \underline{I_m e^{j\phi}} = \frac{V_m}{(j\omega L + R)}$$

$$\underline{I}_m \frac{e^{j\phi}}{(\cos\phi + j\sin\phi)} = \frac{V_m}{R^2 + \omega^2 L^2} (R - j\omega L)$$

Real LHS = Real RHS

Im LHS = Im RHS

$$\underline{I}_m \cos\phi = \frac{V_m}{R^2 + \omega^2 L^2} \cdot R \quad \text{--- ①}$$

$$\underline{I}_m \sin\phi = \frac{V_m}{R^2 + \omega^2 L^2} \omega L \quad \text{--- ②}$$

$$\phi = \tan^{-1} \frac{②}{①} = -\tan^{-1} \frac{\omega L}{R} \quad \checkmark$$

$$\underline{I}_m = \sqrt{①^2 + ②^2} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \quad \checkmark$$

$$\begin{aligned} V \cos(\omega t) &\rightarrow V_m e^{j\omega t} \\ I \cos(\omega t - \phi) &\rightarrow I_m e^{j(\omega t - \phi)} \end{aligned}$$

Ans: Real part of $\underline{I}_m e^{j(\omega t - \phi)}$

$$\Rightarrow i = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right)$$

* Super position theorem: Real forcing function \rightarrow real part of response
 Imaginary forcing function \rightarrow imaginary part of response.

$$I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos \left(\omega t - \underbrace{\tan^{-1} \frac{\omega L}{R}}_{\phi} \right) \rightarrow$$

Polar notation : $\left[\underbrace{I_m}_{\substack{\downarrow \\ \text{Magnitude}}} \angle \underbrace{\phi}_{\substack{\downarrow \\ \text{Phase difference}}} \right] \equiv \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \angle -\tan^{-1} \frac{\omega L}{R}$


$\omega = \boxed{}$

Hw: Solve R-C circuit S.S solution using (complex forced function)

Show : (i) Current leads the voltage

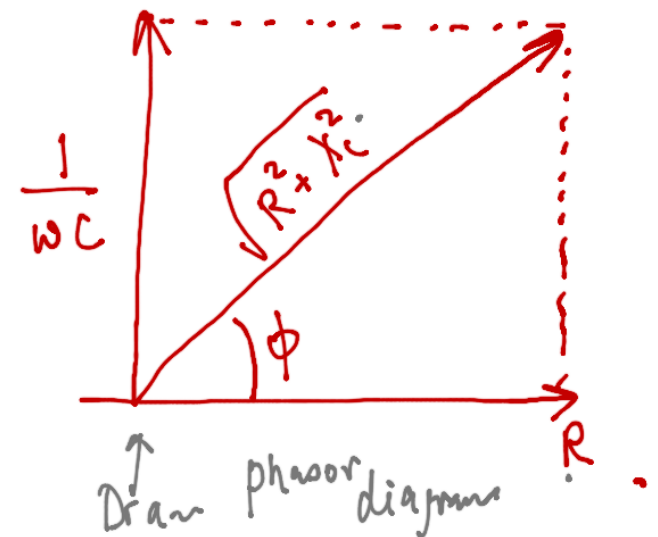(ii) $I_m = \frac{V_m}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}}$ and $\angle \phi = \tan^{-1} \left(\frac{1}{\omega R C} \right)$

$X_C = \frac{1}{j\omega C}$: Capacitive Reactance



Phasors

$$i(t) = I_m \cos(\omega t + \phi) \quad : \text{Time domain}$$

$$\Downarrow$$

$$i(t) = \text{Re} \left[I_m e^{j(\omega t + \phi)} \right]$$

$$\Downarrow$$

$$\underline{I} = I_m e^{j\phi}$$

$$\Rightarrow \underline{I_m} \angle \phi$$

: Frequency Domain.
(polar form)

$$\left. \begin{array}{l} \omega \rightarrow \text{ang. freq. (rad/s)} \\ \omega = \frac{2\pi}{T} = 2\pi f \quad \text{freq. (Hz)} \\ T \rightarrow \text{Time period} \end{array} \right\}$$

Eg $V = 115 \angle -45^\circ \text{ V}, \omega = 500 \text{ rad/s}$
 $v(t) = 115 \sin(500t - 45^\circ)$

Simple solution using phasors



$$\text{Impedance } Z = R + j\omega L$$

$$V_{\text{supply}} = V_s \cos \omega t = V_s \angle 0^\circ$$

$$\therefore \underline{I} = \frac{V_{\text{supply}}}{Z} = \frac{V_s \angle 0^\circ}{R + j\omega L}$$

$$\rightarrow |\underline{I}| = \frac{V_s}{\sqrt{R^2 + \omega^2 L^2}} \quad \phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$$



time	phasor
R	$\rightarrow R$
L	$\rightarrow j\omega L = X_L$ (Ind. Reactance)
C	$\rightarrow \frac{1}{j\omega C} = \frac{-j}{\omega C}$ $= X_C = \text{Cap. Reactance}$

Similarly for R-C



$$I = \frac{V_s \angle 0^\circ}{R + \frac{1}{j\omega C}} \rightarrow Z \Omega$$
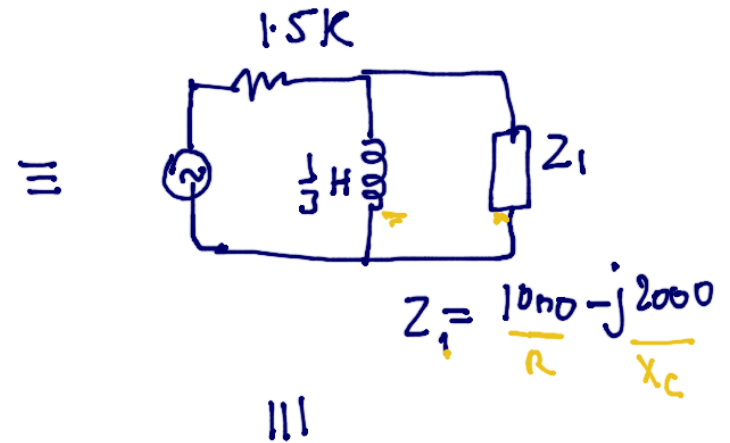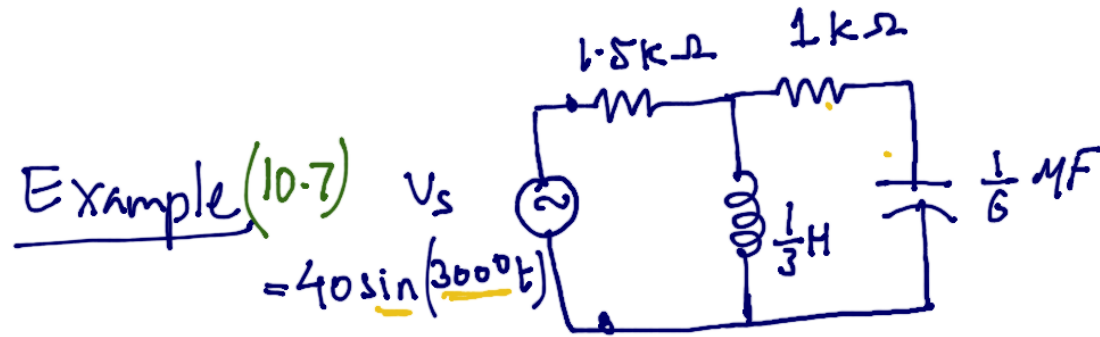
$$(s.s) \quad \underline{I} = \frac{V_s}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \angle \tan^{-1} \left(\frac{1}{\omega RC} \right)$$



$$\omega = 3000 \text{ rad/s}$$

$$V_s = 40 \cos(3000t - 90^\circ) \rightarrow \phi$$

$$Z_L = j\omega L = j 3000 * \frac{1}{3} = j 1k \Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j 3000 * \frac{10^{-6}}{6}} = -j 2000 \Omega$$

$$Z = 1.5k + \left(\frac{j1000}{x_L} \parallel Z_1 \right)$$

$$= \frac{1.5k}{R} + \frac{(j1k * (1k - j2k))}{(1k + 1k - j1k)}$$

$$I = \frac{V \angle \phi}{Z} = \frac{40 e}{(3-j) \times 1000 \times 1.5k} = \frac{40 e^\phi}{k e^\theta} = \left(\frac{40}{k} \right) e^{(\phi-\theta)}$$

$$Z = 1.5k * \frac{(j+2)k(1-j)}{(1-j)(1+j)}$$

$$Z = \left(\frac{3-j}{2} \right) k * 1.5k$$