

CHAPTER 11

POWER

inst. volt inst. curr.

$$p(t) = v(t) i(t)$$

Instantaneous power:

$$P_R(t) = v(t) i(t) = i^2(t) R = \frac{v^2(t)}{R}$$

$$P_L(t) = L \frac{di(t)}{dt} = \frac{1}{L} v(t) \int_0^t v(t) dt$$

$$P_C(t) = C v(t) \frac{dv(t)}{dt} = \frac{1}{C} i(t) \int i(t) dt$$

$$(v_i = L \cdot \frac{di(t)}{dt})$$

$$(i_C(t) \propto \frac{dv(t)}{dt})$$


Sinusoids: $p(t) = (V_m \cos(\omega t)) (I_m \cos(\omega t + \phi))$ ($\omega = \frac{2\pi}{T}$)

$$= \underbrace{\frac{V_m I_m}{2} \cos\phi}_{\text{constant}} + \underbrace{\frac{V_m I_m}{2} (\cos 2\omega t + \phi)}_{\text{Time varying (period } = \frac{2\pi}{\omega} \text{) } \frac{1}{2T} \text{ Hz}}$$

Average Power

$$P_{\text{avg}} = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} p(t) dt$$

(t₁ to t₂) energy

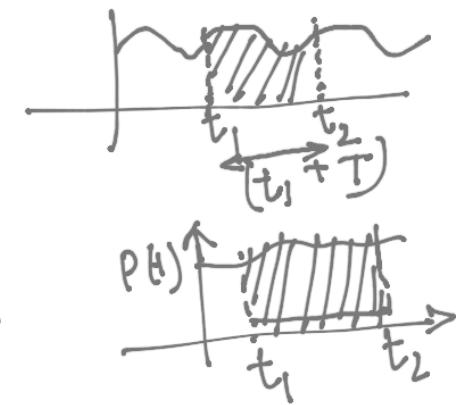

for periodic waveforms $t_2 = T + t_1$

$$P_{\text{avg}} = \frac{1}{T} \int_{t_1}^{t_1+T} p(t) dt = \frac{1}{T} \int_{-T/2}^{T/2} p(t) dt$$

Time period of waveform


(a) $P = \frac{1}{nT} \int_{t_1}^{t_1+nT} p(t) dt$ $n = 1, 2, 3, \dots$

$$(t_2 = t_1 + nT)$$

$$P_{\text{avg}} (\text{sin.}) = \frac{1}{nT} \int_{-nT/2}^{nT/2} p(t) dt$$

In some cases $T \rightarrow \infty$ (specific case)
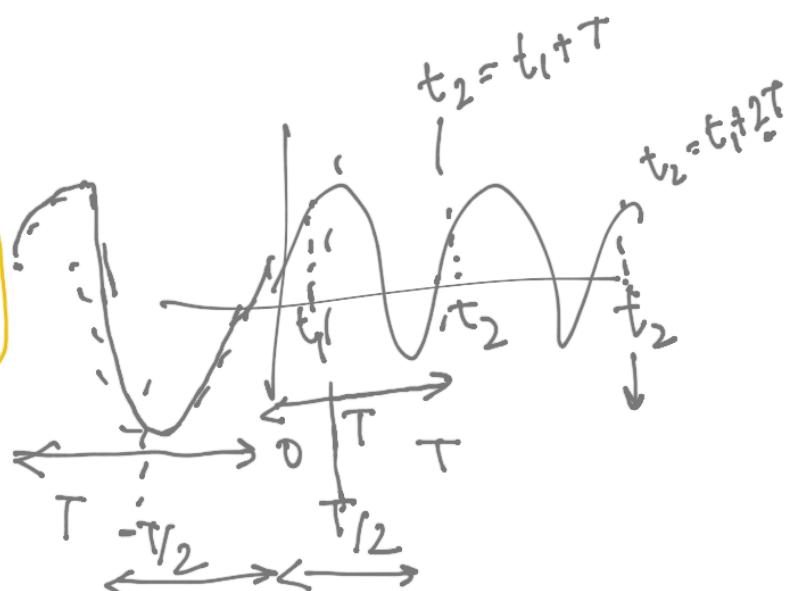
$$P_{\text{avg}} = \lim_{T \rightarrow \infty} \frac{1}{nT} \int_{-nT/2}^{nT/2} p(t) dt$$



~~Final~~

Avg. of Sin. power

$$P_{\text{avg}} = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \left[\frac{V_m I_m}{2} \cos \phi + \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(2\omega t + \phi) dt \right]$$

On taking average over $T = \frac{2\pi}{\omega}$

$$P_{\text{avg}} (\text{sin}) = \frac{V_m I_m}{2} \cos \phi$$

General case if forcing voltage $V = V_m \cos(\omega t + \theta)$

$$P_{\text{avg}} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

I_m & V_m are in same phase (or in phase with each other)

Resistor
 $(\phi = 0^\circ)$

$$P_{\text{avg}, R} = \frac{V_m I_m}{2}$$

→ Power absorbed (or dissipated)
by resistor

Ideal L or C (no R)

$\phi = 90^\circ$ (-90° for L & $+90^\circ$ for C)

$$\therefore P_{\text{avg}, L} = 0$$

&

$$P_{\text{avg}, C} = 0$$

Max. Power Transfer



if Z_L is eq. (thermin) impedance, max. power delivered to load is when

$$Z_L = Z_{th}^*$$

Proof
Hw 5
 $P = ?$
 $\angle \phi$

$$\rightarrow Z_{th} = R + jX$$

Z_{th}

$$= R - jX$$

Conjugate

Average power due to multiple currents :-

$$i(t) = I_{m_1} \cos \omega_1 t + I_{m_2} \cos \omega_2 t + \dots + I_{m_N} \cos(\omega_N t)$$

$$P_{avg} = \frac{1}{2} \left(I_{m_1}^2 + I_{m_2}^2 + \dots + I_{m_N}^2 \right) R$$



$I_{m_1} \cos \omega_1 t$
 $I_{m_2} \cos \omega_2 t$

$I_{m_N} \cos \omega_N t$

Effective Value

Eff. value of a periodic current is equal to D.C value of current which delivers same power to 'R' (resistor) when flowing through it.

$$\text{Power absorbed} = I_{\text{eff}}^2 R = \frac{1}{T} \int_0^T i^2 R dt$$

($I_{\text{eff}} = \text{D.C value}$)

sinusoidal power dissipated

$$\Rightarrow I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

For Sinusoidal wave form

$$I_{\text{eff}}^2 = \frac{1}{T} \int_0^T (I_m \cos^2(\omega t + \phi)) dt$$

$$I_{\text{eff.}} = I_m \cdot \frac{1}{\sqrt{2}}$$

RMS value current
(Root Mean Square)

$$V_{\text{rms}}^2 = \frac{V_m^2}{2}$$

$$\therefore P = \frac{I_m^2}{2} R = \frac{I_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} R$$

$$P_{avg} = I_{eff}^2 R$$

$$P = \frac{V_{eff}^2}{R}$$

$$I_{eff} = I_{rms}$$

$$V_{eff} = V_{rms}$$

For multiple pf. circuits

$$I_{eff} = \sqrt{I_{1pf}^2 + I_{2pf}^2 + I_{3pf}^2 + \dots + I_{Npf}^2}$$

$$I_{eff}^2 = \frac{1}{2} (I_{m1}^2 + I_{m2}^2 + \dots + I_{mN}^2)$$

$$I_{rms}^2 = I_{eff}^2 = (I_{eff1}^2 + I_{eff2}^2 + \dots + I_{effN}^2)$$

(L, C, R)

For Resistive Circuits

(L & C) Due to Ckt. elements

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta - \phi)$$


$$P_{avg} = V_{eff} I_{eff} \cos(\theta - \phi)$$

Apparent Power

$$\cos(\theta - \phi) = \frac{P_{avg}}{V_{eff} I_{eff}} = \frac{\text{Power Factor}}{(\text{PF})}$$

$\theta - \phi$ = Power factor angle

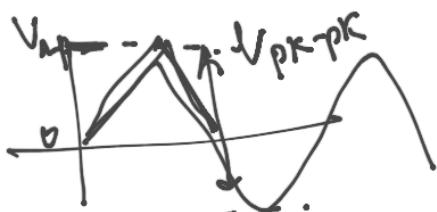$\text{PF} = 0$ (for L & C only circuits)



Complex Power

$$\underline{V}_{\text{eff}} = V_{\text{eff}} \angle \theta$$

$$\underline{I}_{\text{eff}} = I_{\text{eff}} \angle \phi$$

$$P_{\text{avg}} = V_{\text{eff}} I_{\text{eff}} \operatorname{Re}(e^{j(\theta-\phi)}) \rightarrow \text{Coming from discussion earlier.}$$

$$= \operatorname{Re} \left[\underline{V}_{\text{eff}} \underline{I}_{\text{eff}} \left(e^{j\theta} \cdot e^{-j\phi} \right) \right]$$

$$= \operatorname{Re} \left[\underline{V}_{\text{eff}} e^{j\theta} \underline{I}_{\text{eff}}^* e^{-j\phi} \right]$$

$$P_{\text{avg}} = \operatorname{Re} \left(\underline{V}_{\text{eff}} \underline{I}_{\text{eff}}^* \right)$$

complex conjugate

$$S = A + jB$$

$$S^* = A - jB$$

$$= \underline{V}_{\text{eff}}^* \underline{I}_{\text{eff}} = S$$

Complex power

Complex Power

$$(VA) \leftarrow S = P + jQ$$


Real power
(W)

Reactive power

Units: Volt * Amp Reactive

(VAR)
No energy transfer
= Wattless power

Phasor diagram

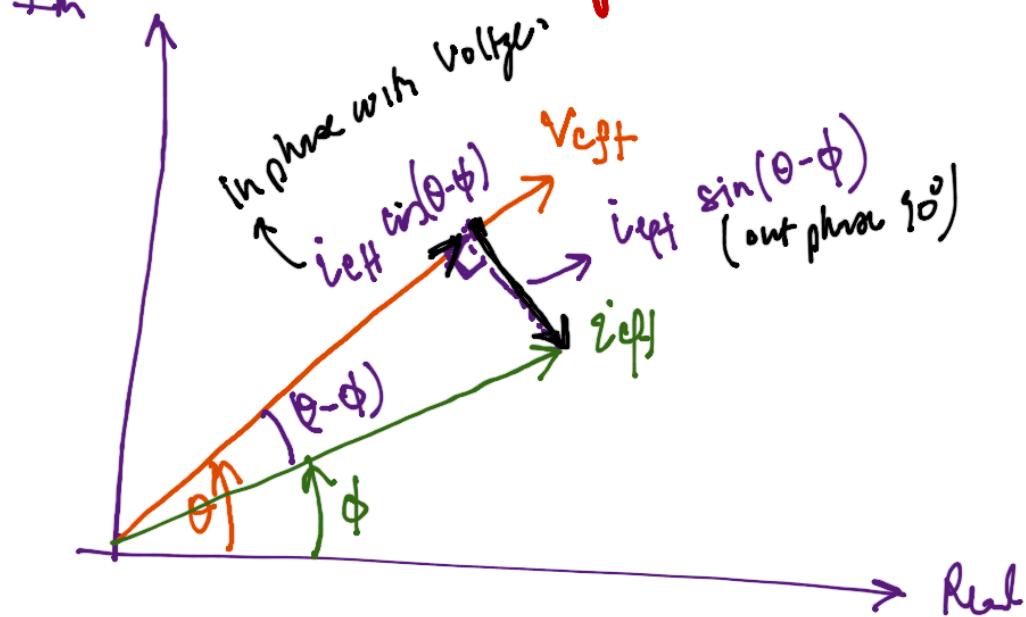


$$V_{\text{eff}} = V_{\text{eff}} \angle \theta$$

$$I_{\text{eff}} = i_{\text{eff}} \angle \phi$$

Real Power
(W) \leftarrow
 $V_{\text{eff}} * i_{\text{eff}} \cos(\theta - \phi)$

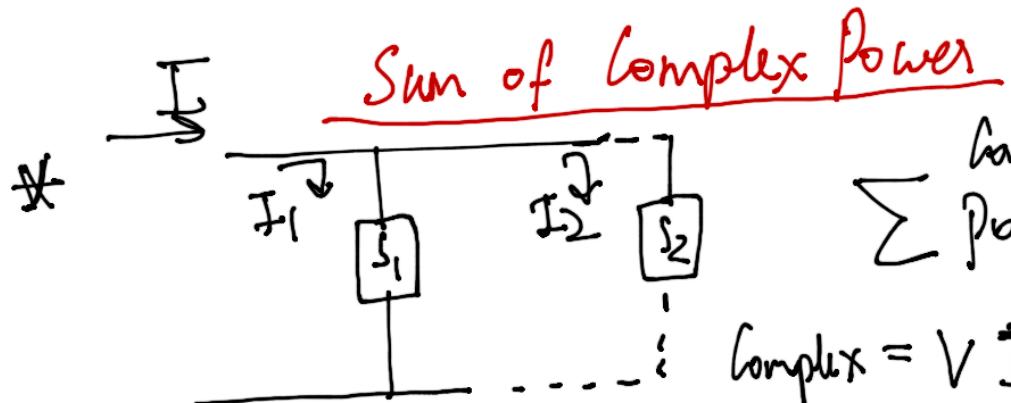$V_{\text{eff}} i_{\text{eff}} \sin(\theta - \phi)$
Reactive part (VAR)
 90° out of phase with V_{m}



$$\sum \text{Power} = S_1 + S_2 + \dots$$


$$\begin{aligned} \text{Complex} &= V I^* = S \\ &= V \left(I_1^* + I_2^* + \dots \right) . \end{aligned}$$

$$= V I_1^* + V I_2^* + \dots$$

$$= S_1 + S_2$$

CHAPTER 13

One Port Network

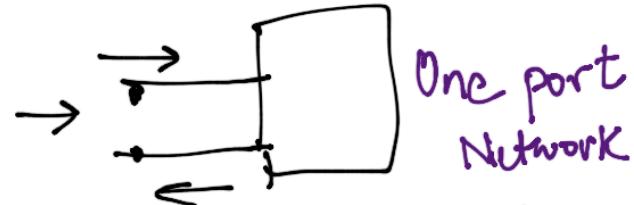

One port
Network

1 port.

Node voltage

$$\left. \begin{array}{l} V_1 = Z_{11} I_1 + Z_{12} E_2 + \dots + Z_{1N} I_N \\ V_2 = \\ \vdots \\ V_N = Z_{N1} I_1 + \dots + Z_{NN} I_N \end{array} \right\}$$

currents

$$\left[\begin{array}{c} V_1 \\ \vdots \\ V_N \end{array} \right] = \left[\begin{array}{cccc} Z_{11} & Z_{12} & \dots & Z_{1N} \\ \vdots & & & \\ Z_{N1} & Z_{N2} & & Z_{NN} \end{array} \right] \left[\begin{array}{c} I_1 \\ I_2 \\ \vdots \\ I_N \end{array} \right]$$

\downarrow
Input V

Δ_2

Impedance Matrix

\downarrow
Current I

$$I = V / \Delta_2 \Leftarrow$$

$$\frac{I}{\Delta_Z} = \text{Admittance Matrix } Y$$

$$\left. \begin{array}{l} V_1 = Z_{11} I_1 + Z_{12} I_2 \\ V_2 = Z_{21} I_1 + Z_{22} I_2 \end{array} \right\} \text{Simple case example.}$$

$$V_I = Z I$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \quad V_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

Impedance Parameter (Z)

$$Y = \frac{I}{V}$$

$$I_1 = Y_{11} V_1 + \dots + Y_{1N} V_N$$

$$I_2 = Y_{21} V_1 + \dots + Y_{2N} V_N$$

.

$$I_N = Y_{N1} V_1 + \dots + Y_{NN} V_N$$

$$\underbrace{I}_{\mathbb{I}}$$


$$Y = \begin{bmatrix} Y_{11} & \dots & Y_{1N} \\ \vdots & & \vdots \\ Y_{N1} & \dots & Y_{NN} \end{bmatrix} \quad V = \begin{bmatrix} V_1 \\ \vdots \\ V_N \end{bmatrix}$$

Admittance matrix

$$Y_{11} = \frac{I}{V}$$

\vdots
 $V_2 = V_3 = \dots = V_N = 0$
 \vdots

Hybrid

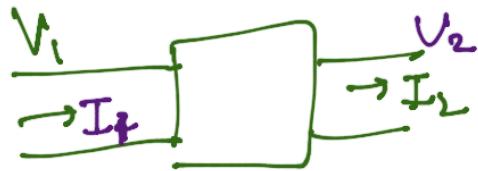

$V_1, I_2 \rightarrow$ Outputs

$I_1, V_2 \rightarrow$ Feeding

HYBRID PARAMETER & MATRIX

$$\left\{ \begin{array}{l} V_1 = h_{11} I_1 + h_{12} V_2 \\ I_2 = h_{21} I_1 + h_{22} V_2 \end{array} \right.$$

H matrix $\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \rightarrow$ Hybrid parameter

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = H \text{ matrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

\uparrow

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

Transmission Matrix




$$V_1 = t_{11} V_2 - t_{12} I_2$$

$$I_1 = t_{21} V_2 - t_{22} I_2$$

$$t = \begin{bmatrix} t_{11} & -t_{12} \\ t_{21} & -t_{22} \end{bmatrix}$$

Transmission Parameters.

Example

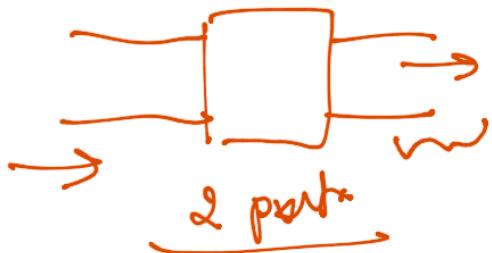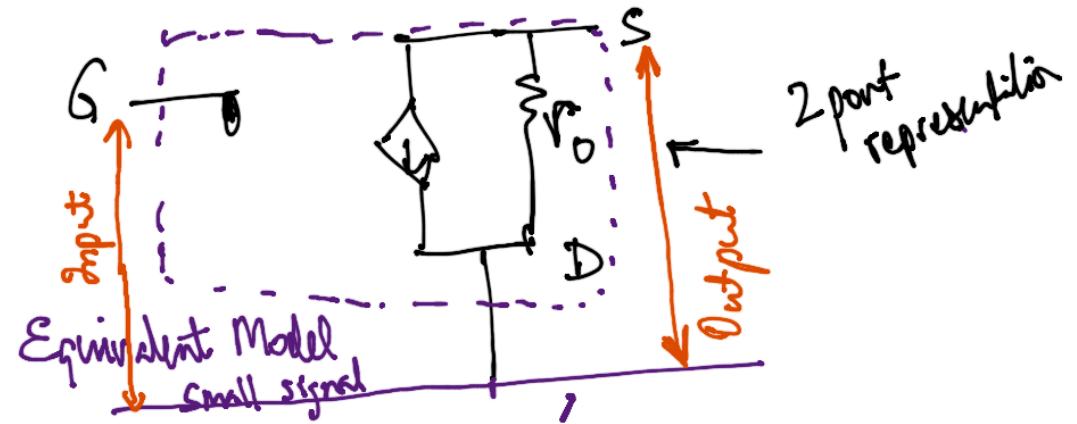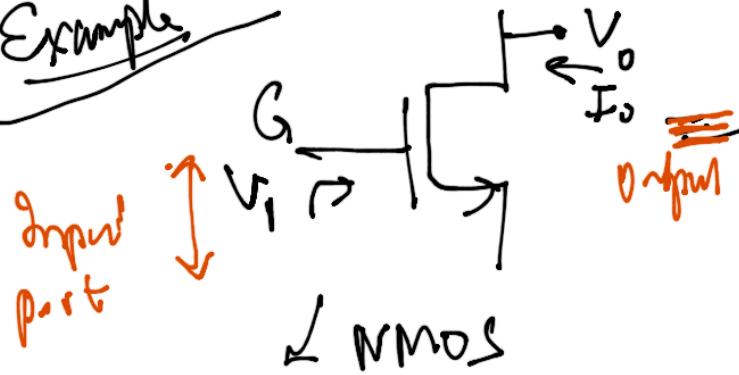


$$\begin{bmatrix} V_o \\ I_o \end{bmatrix} = \begin{bmatrix} & \\ & \end{bmatrix}_{\text{Parameters}} \begin{bmatrix} V_i \\ I_i \end{bmatrix}_{\text{Inputs}}$$

Parameters defining transistors



$$\left\{ \begin{array}{l} \frac{V_o}{V_i} = \text{Gain} \\ \left| \frac{V_o}{I_o} \right| = \text{Output resistance} \end{array} \right.$$
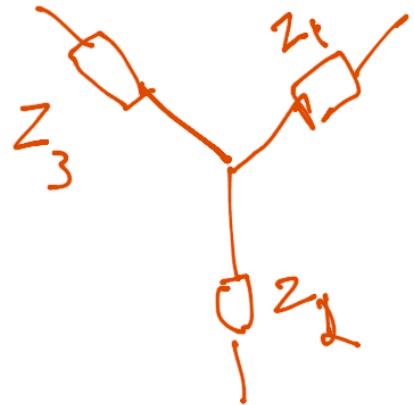
$$\frac{I_o}{V_i} = \text{Trans-conductance} \left(\frac{\partial i_d}{\partial V_{gs}} \right)$$



$Y \leftrightarrow Z$ conversion

\equiv

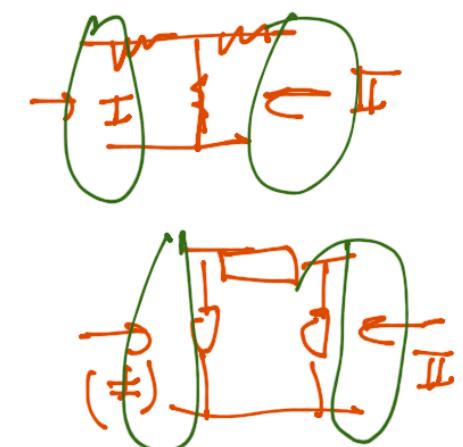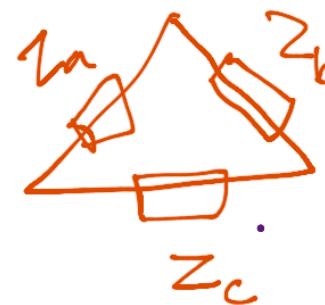

Same results as impedance