 


# Lecture 21 – Registers and Counters 2


Chapter 6

# Design of sequential circuits - The vending machine

- Let's say we are asked to design a circuit for a vending machine that dispenses candy for Rs. 3
- The input consists of a coin slot that can accept Rs. 1 and Rs. 2 coins
- The deposit of these coins by the user is detected by a circuit that gives out two outputs x and y
  - when Rs. 1 is inserted, y goes to one for one clock cycle
  - when Rs. 2 is inserted, x goes to one, for one clock cycle.
  - x and y are at zero by default
- Only one coin can be entered at once
- We need to design a circuit that takes x and y as inputs and outputs 1 if the sum is  $\geq 3$ , so that the machine can dispense the candy




# The vending machine

 

# The vending machine

A	B	x	y	A(t+1)	B(t+1)	Z (output)
0	0	0	0	0	0	0
0	0	0	1	0	1	0
0	0	1	0	1	0	0
0	0	1	1	x	x	0
0	1	0	0	0	1	0
0	1	0	1	1	0	0
0	1	1	0	1	1	0
0	1	1	1	X	X	0
1	0	0	0	1	0	0
1	0	0	1	1	1	0
1	0	1	0	1	1	0
1	0	1	1	X	x	0
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	x	x	1

 

# The vending machine

$A(t+1)$

xy		x			
		00	01	11	10
AB	00	$m_0$ 0	$m_1$ 0	$m_3$ X	$m_2$ 1
	01	$m_4$ 0	$m_5$ 1	$m_7$ X	$m_6$ 1
	11	$m_{12}$ 1	$m_{13}$ 1	$m_{15}$ X	$m_{14}$ 1
	10	$m_8$ 1	$m_9$ 1	$m_{11}$ X	$m_{10}$ 1

$A$  (rows 11, 10)  
 $B$  (columns 01, 11)  
 $y$  (columns 00, 01)  
 $x$  (columns 11, 10)

$$A(t + 1) = A + x + By$$

# The vending machine

$B(t+1)$

xy

AB

	00	01	11	10
00	$m_0$ 0	$m_1$ 1	$m_3$ X	$m_2$ 0
01	$m_4$ 1	$m_5$ 0	$m_7$ X	$m_6$ 1
11	$m_{12}$ 1	$m_{13}$ 1	$m_{15}$ X	$m_{14}$ 1
10	$m_8$ 0	$m_9$ 1	$m_{11}$ X	$m_{10}$ 1

A

B

x

y

$$B(t + 1) = (B + y + Ax)(B' + y' + A)$$

# The vending machine

---


$$A(t + 1) = A + x + By$$

$$B(t + 1) = (B + y + Ax)(B' + y' + A)$$

$$z = AB$$

 
# Sequential circuit - pattern detector

- A sequence/pattern detector to detect a sequence of **1010**. Output should go to high when the sequence is detected.
  - Eg: input x ... **1 0 1 0** 1 0 1 0 0 0 0 ...  
output y ... 0 0 0 **1** 0 **1** 0 1 0 1 0 0 0 ...





# Sequential circuit - design

 


A → 00  
B → 01  
C → 10  
D → 11

Present state		Input	Next state		Output
$Q_1$	$Q_0$		$Q_1(t+1)$	$Q_0(t+1)$	
0	0	0	0	0	0
0	1	0	1	0	0
1	0	0	0	0	0
1	1	0	1	0	1
0	0	1	0	1	0
0	1	1	0	1	0
1	0	1	1	1	0
1	1	1	0	1	0

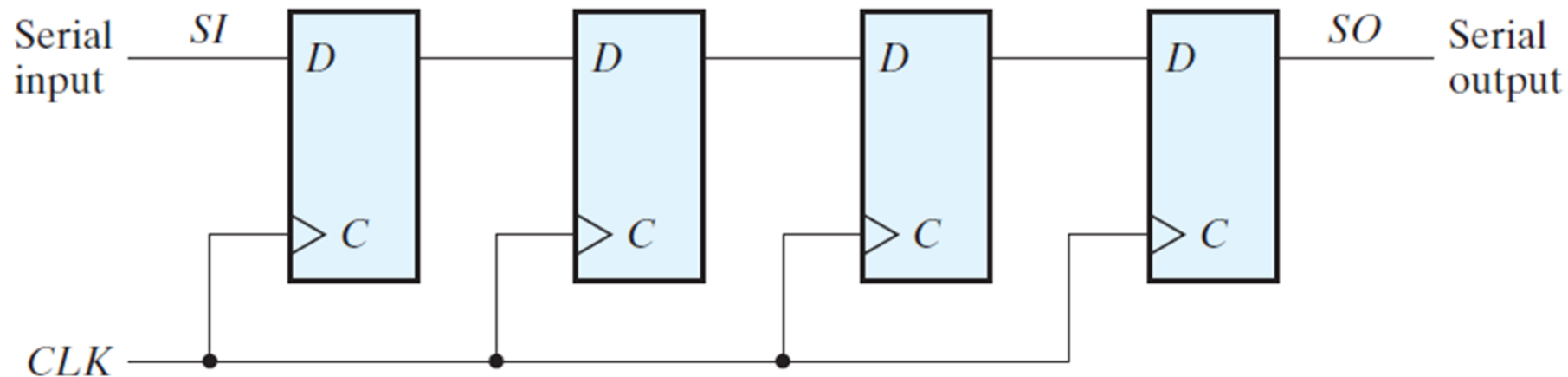
# Universal register

- If the flip-flop outputs of a shift register are accessible, then information entered serially by shifting can be taken out in parallel from the outputs of the flip-flops
- If a parallel load capability is added to a shift register, then data entered in parallel can be taken out in serial fashion by shifting the data stored in the register
- Some shift registers provide the necessary input and output terminals for parallel transfer
- They may also have both shift-right and shift-left capabilities


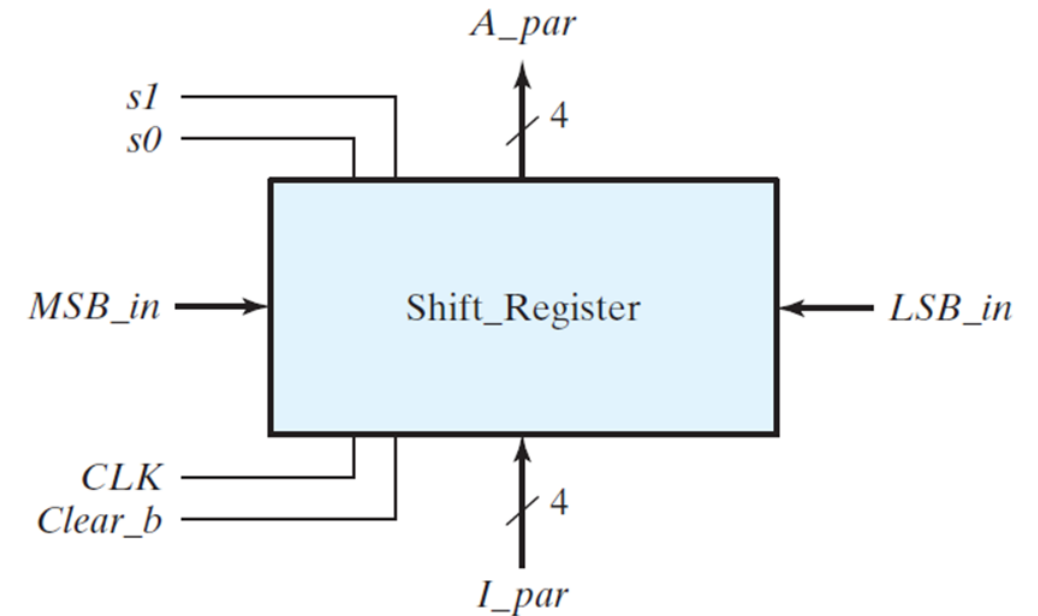
# Universal register


- The most general shift register has the following capabilities:
  1. A *clear* control to clear the register to 0
  2. A *clock* input to synchronize the operations
  3. A *shift-right* control to enable the shift-right operation and the *serial input* and *output* lines associated with the shift right
  4. A *shift-left* control to enable the shift-left operation and the *serial input* and *output* lines associated with the shift left
  5. A *parallel-load* control to enable a parallel transfer and the  $n$  input lines associated with the parallel transfer
  6.  $n$  parallel output lines
  7. A *control state* that leaves the information in the register unchanged in response to the clock



Mode Control		Register Operation
$s_1$	$s_0$	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

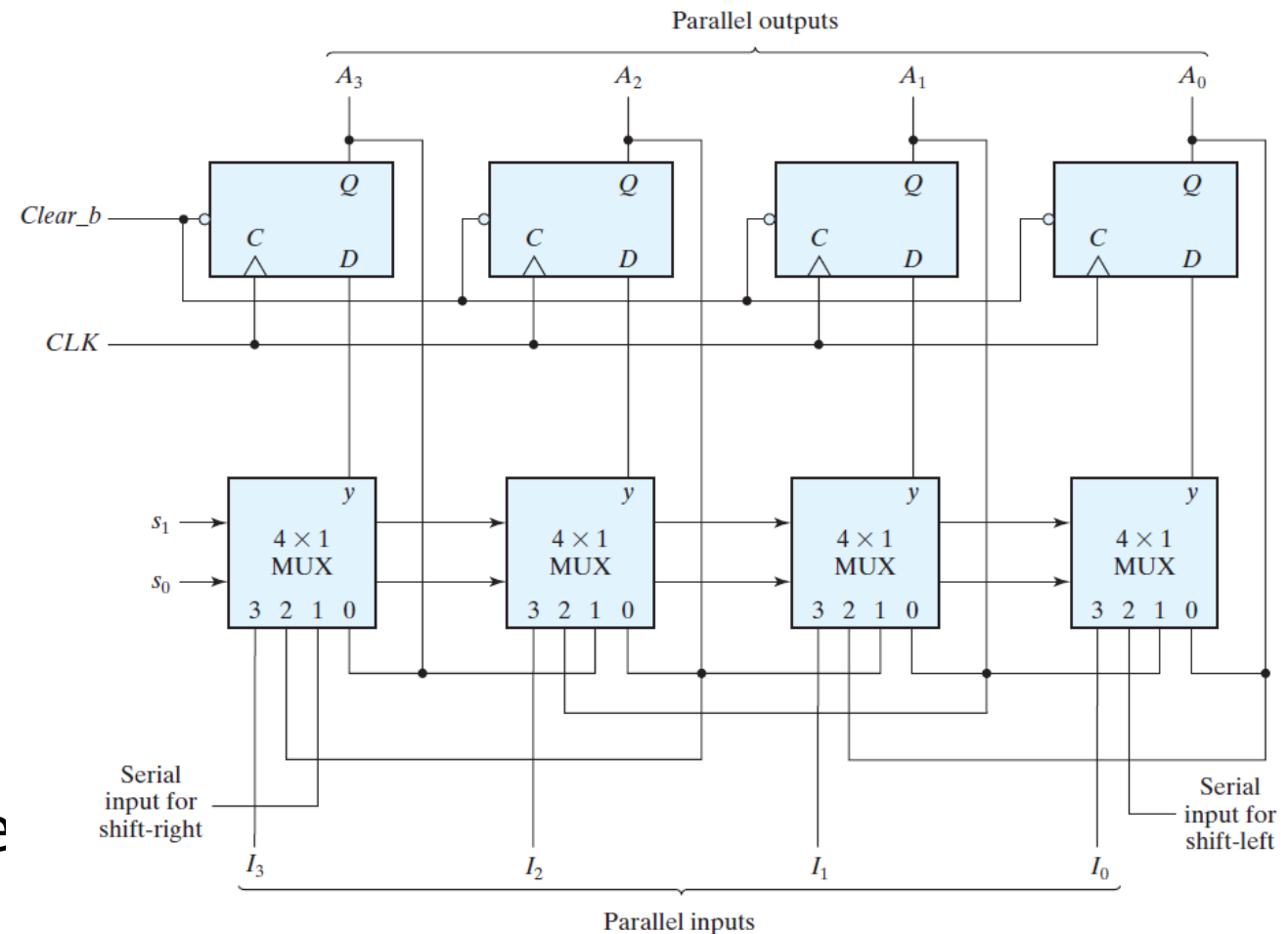
# Universal register

- The circuit consists of four  $D$  flip-flops and four multiplexers
- The four multiplexers have two common selection inputs  $s_1$  and  $s_0$
- The selection inputs control the mode of operation of the register according to the function required
- The output of the MUXes are applied to the inputs of the FFs which controls the next state of the FF



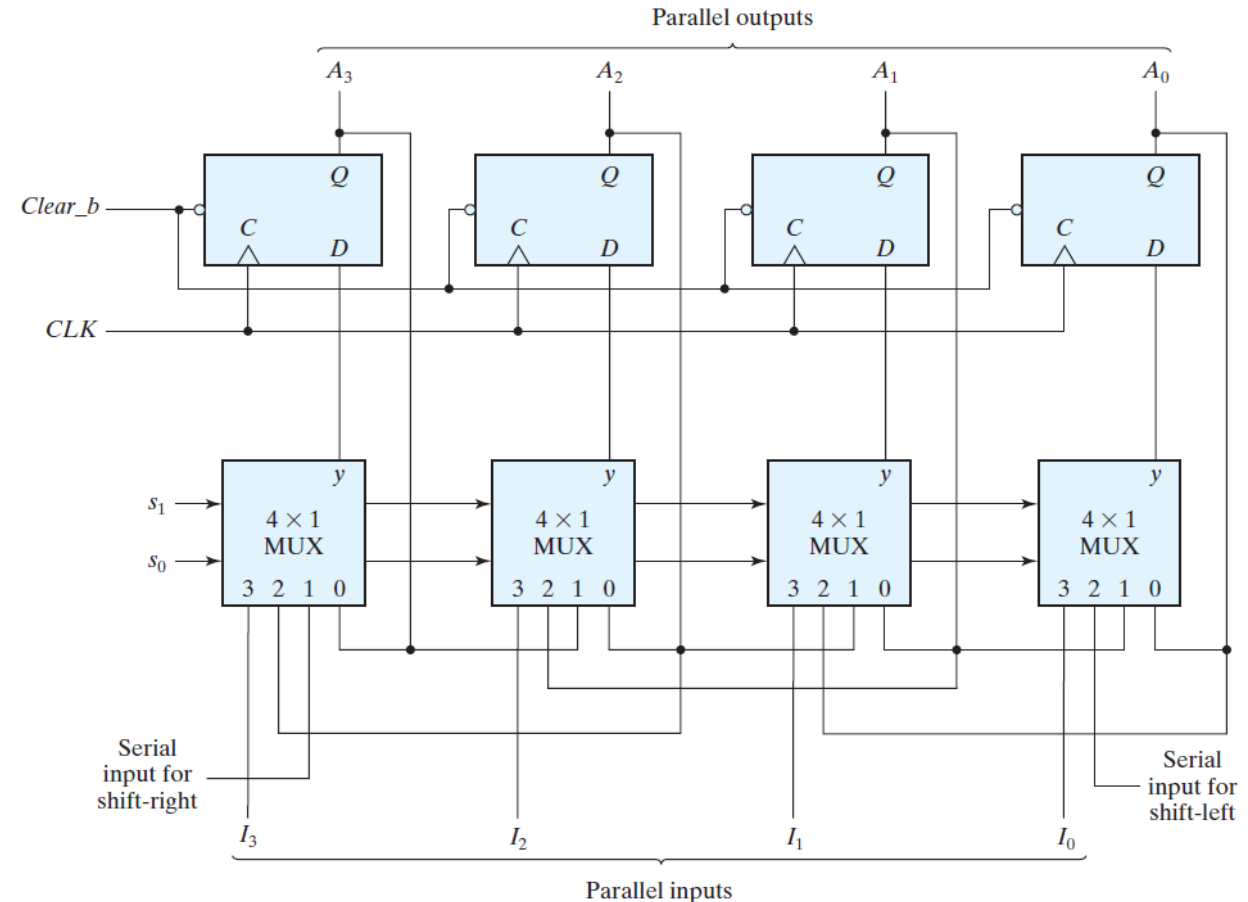
# Universal register

- When  $s_1s_0 = 00$ , the present value of the register is applied to the  $D$  inputs of the flip-flops
- This condition forms a path from the output of each flip-flop into the input of the same flip-flop, so that the output recirculates to the input in this mode of operation
- The next clock edge transfers into each flip-flop the binary value it held previously, and no change of state occurs


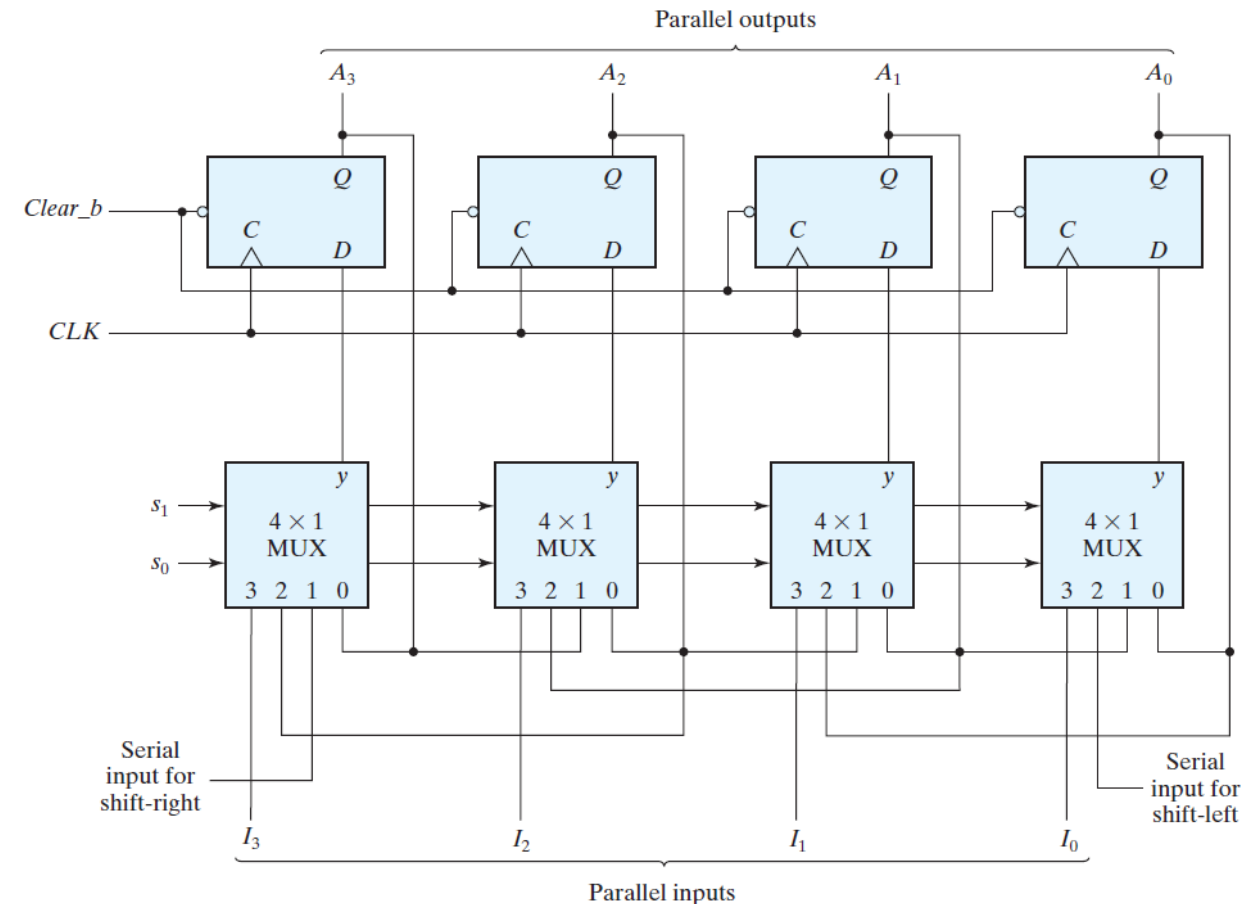
# Universal register

- When  $s_1s_0 = 01$ , terminal 1 of the multiplexer inputs has a path to the  $D$  inputs of the flip-flops
- This causes a shift-right operation, with the serial input transferred into flip-flop  $A_3$
- When  $s_1s_0 = 10$ , a shift-left operation results, with the other serial input going into flip-flop  $A_0$
- Finally, when  $s_1s_0 = 11$ , the binary information on the parallel input lines is transferred into the register simultaneously during the next clock edge




# Counters

- A register that goes through a prescribed sequence of states upon the application of input pulses is called a *counter*
- The input pulses may be clock pulses, or they may originate from some external source and may occur at a fixed interval of time or at random
- The sequence of states may follow the binary number sequence or any other sequence of states
- Counters are available in two categories: **ripple counters and synchronous counters**
- In a ripple counter, a flip-flop output transition serves as a source for triggering other flip-flops
- In a synchronous counter, the  $C$  inputs of all flip-flops receive the common clock
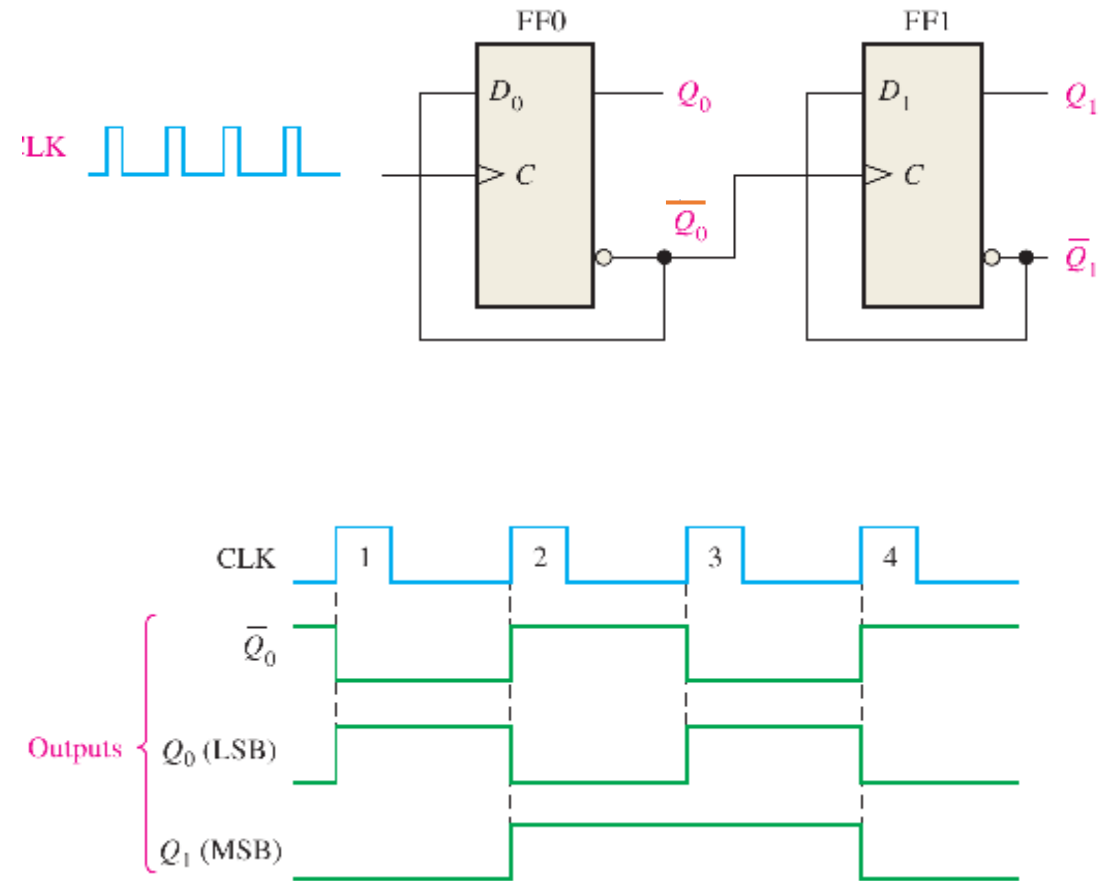
# Ripple counter - binary



- A binary ripple counter consists of a series connection of complementing flip-flops, with the output of each flip-flop connected to the  $C$  input of the next higher order flip-flop
- The flip-flop holding the least significant bit receives the incoming count pulses
- A complementing flip-flop can be obtained from a  $JK$  flip-flop with the  $J$  and  $K$  inputs tied together or from a  $T$  flip-flop
- Another possibility is to use a  $D$  flip-flop with the complement output connected to the  $D$  input
- In this way, the  $D$  input is always the complement of the present state, and the next clock pulse will cause the flip-flop to complement





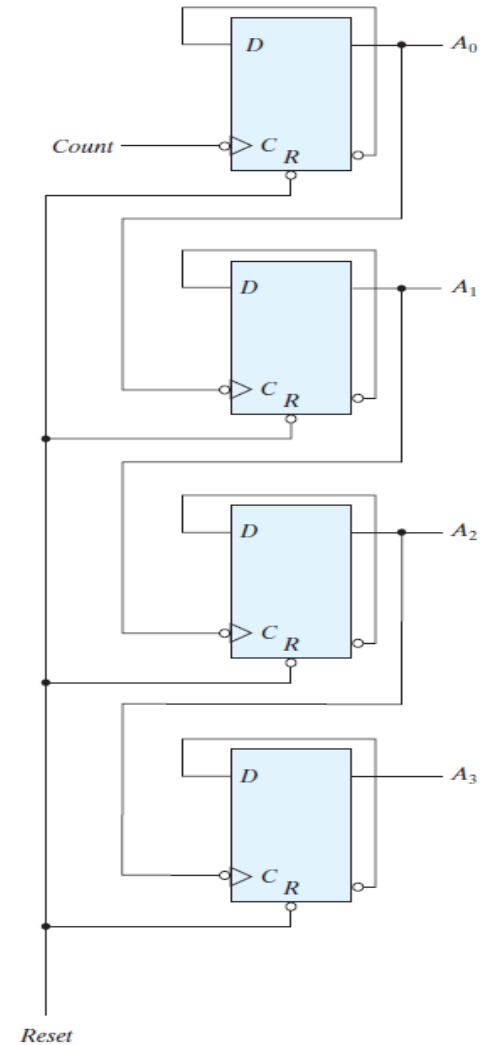
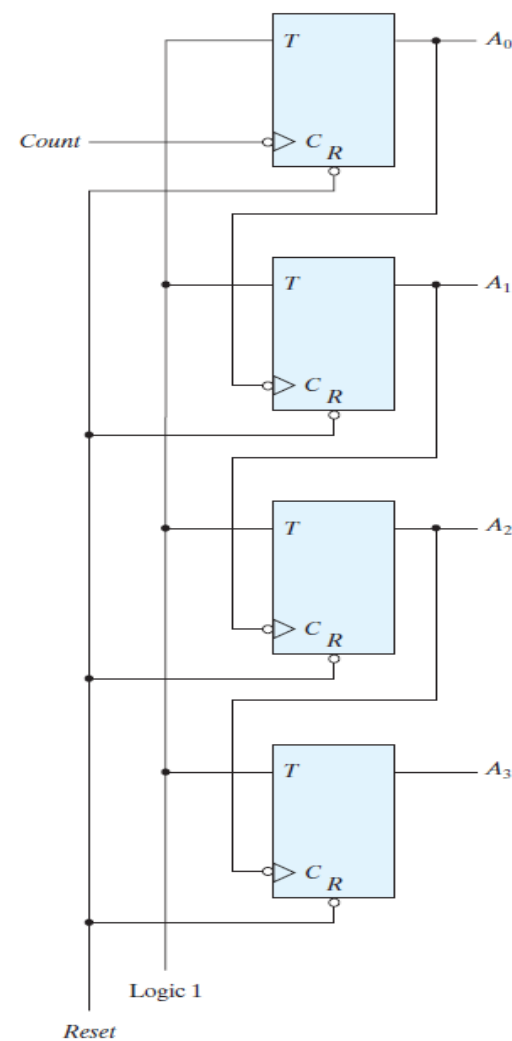
# Ripple counter - binary

- The count starts with binary 0 and increments by 1 with each count pulse input
- After the count of 15, the counter goes back to 0 to repeat the count
- The least significant bit,  $A_0$ , is complemented with each count pulse input
- Every time that  $A_0$  goes from 1 to 0, it complements  $A_1$  and so on...



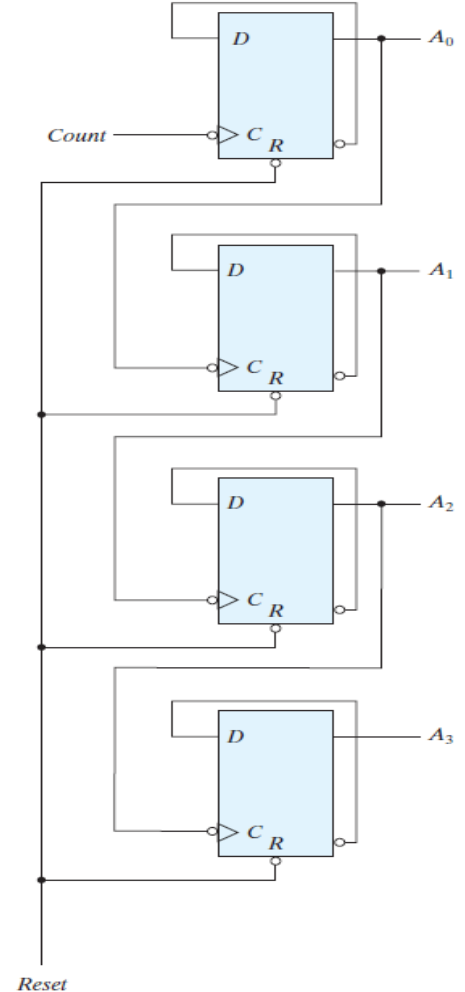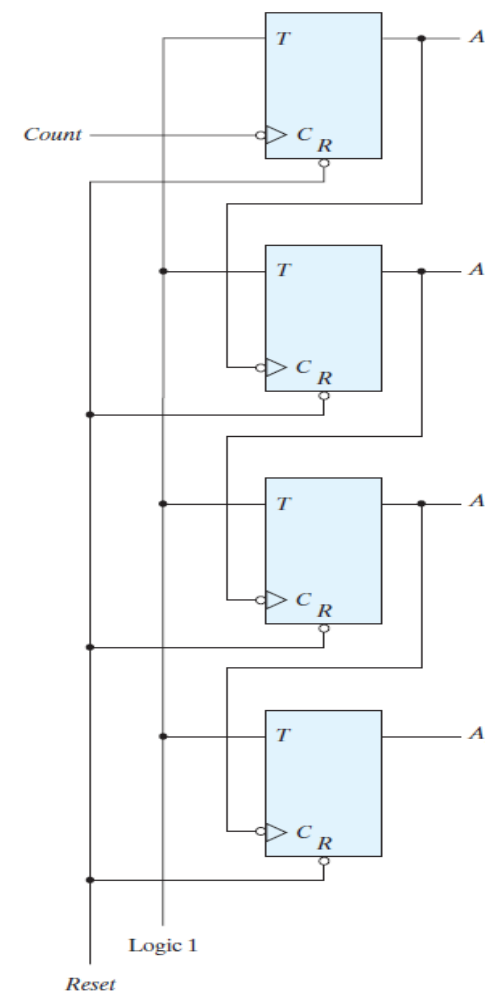
# Ripple counter - binary

- For example, consider the transition from count 0011 to 0100
- $A_0$  is complemented with the count pulse
- Since  $A_0$  goes from 1 to 0, it triggers  $A_1$  and complements it
- As a result,  $A_1$  goes from 1 to 0, which in turn complements  $A_2$ , changing it from 0 to 1
- $A_2$  does not trigger  $A_3$ , because  $A_2$  produces a positive transition, and the flip-flop responds only to negative transitions



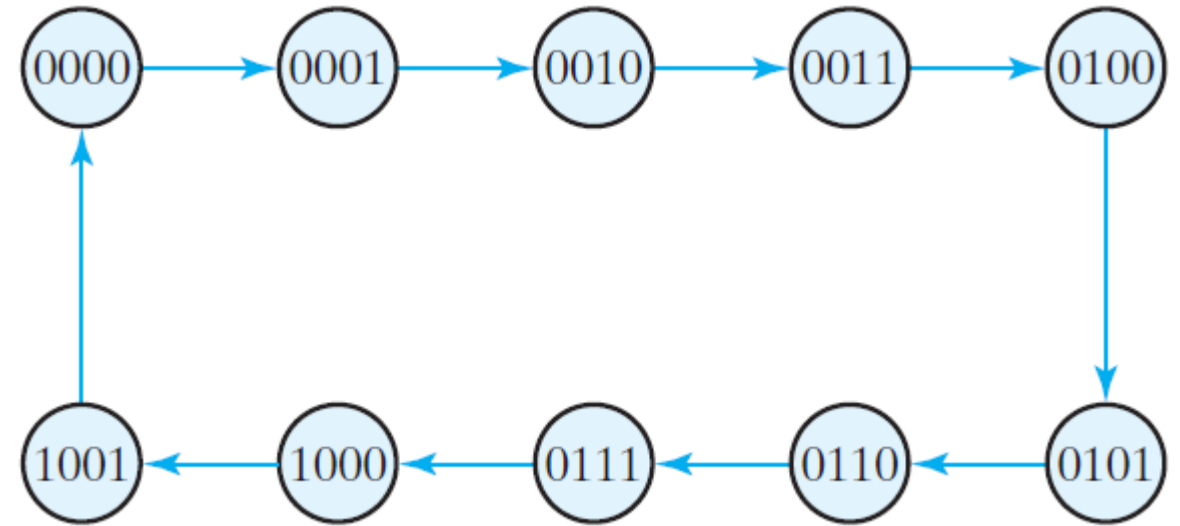
# Ripple counter - BCD

- A decimal counter follows a sequence of 10 states and returns to 0 after the count of 9
- Such a counter must have at least four flip-flops to represent each decimal digit, since a decimal digit is represented by a binary code with at least four bits
- The sequence of states in a decimal counter is dictated by the binary code used to represent a decimal digit
- A decimal counter is similar to a binary counter, except that the state after 1001 (the code for decimal digit 9) is 0000 (the code for decimal digit 0)


 
# Ripple counter - BCD

- We can obtain a decade counter by clearing all the flip-flops as soon as the state 1010 is obtained
- This can be done with the asynchronous input of CLR
- The condition for 1010 is checked by ANDing  $Q_3$  and  $Q_1$
- This is a very commonly used counter for making clocks/timer circuits



# Ripple counter - BCD

- A **decade counter** counts from 0 to 9
- To count in decimal from 0 to 99, we need a two-decade counter
- To count from 0 to 999, we need a three-decade counter
- Multiple decade counters can be constructed by connecting BCD counters in cascade, one for each decade
- The inputs to the second and third decades come from  $Q_8$  of the previous decade
- When  $Q_8$  in one decade goes from 1 to 0, it triggers the count for the next higher order decade while its own decade goes from 9 to 0

