

## Summary of Basic Superposition Procedure


1. **Select one of the independent sources. Set all other independent sources to zero.** This means voltage sources are replaced with short circuits and current sources are replaced with open circuits. Leave dependent sources in the circuit.
2. **Relabel voltages and currents using suitable notation** (e.g.,  $v'$ ,  $i_2''$ ). Be sure to relabel controlling variables of dependent sources to avoid confusion.
3. **Analyze the simplified circuit to find the desired currents and/or voltages.**
4. **Repeat steps 1 through 3 until each independent source has been considered.**
5. **Add the partial currents and/or voltages obtained from the separate analyses.** Pay careful attention to voltage signs and current directions when summing.
6. **Do not add power quantities.** If power quantities are required, calculate only after partial voltages and/or currents have been summed.

$$\begin{array}{ccc} \left. \begin{array}{l} V_1 \\ V_2 \end{array} \right\} & \begin{array}{l} P_1 \\ P_2 \end{array} & \begin{array}{c} \cancel{P_1 + P_2} \end{array} \end{array} \quad \begin{array}{c} i^2 R \\ \uparrow \uparrow \end{array} \quad \begin{array}{c} i = i_1 + i_2 \\ \downarrow \end{array}$$

## Norton & Thevenin Equivalent




Function generator

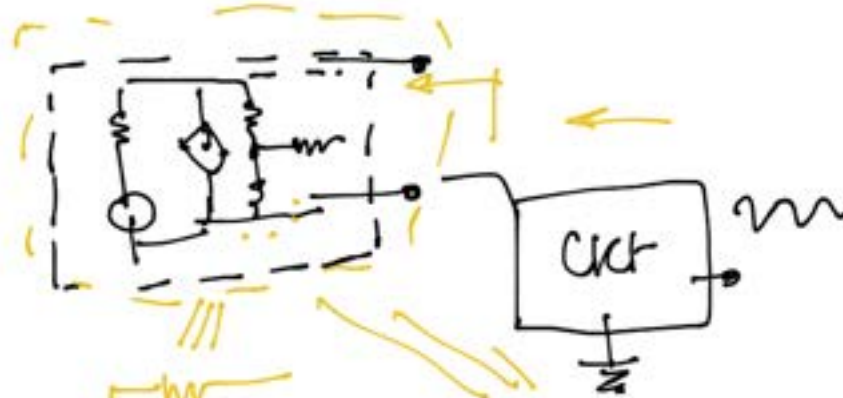


Thevenin  
Equivalent




Norton  
Equivalent

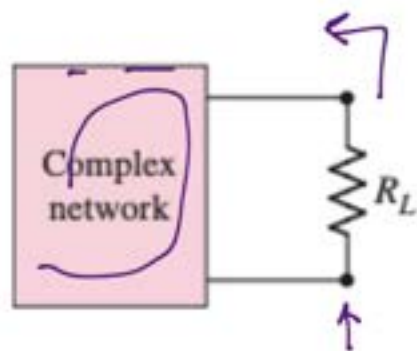

(a)


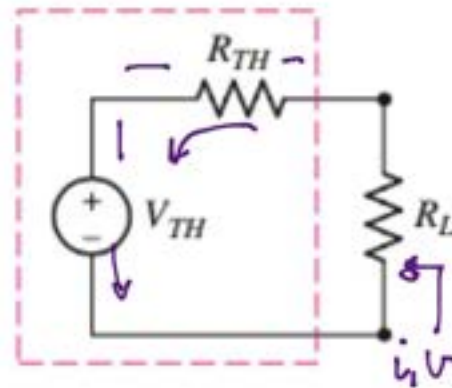


Thévenin Eq.

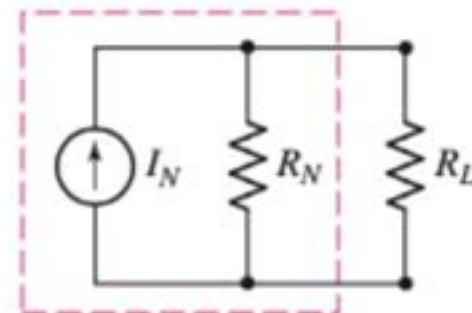



Norton Eq.

Example 5.6

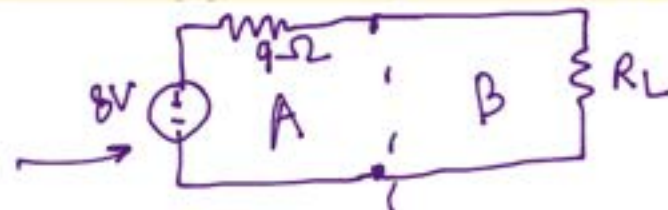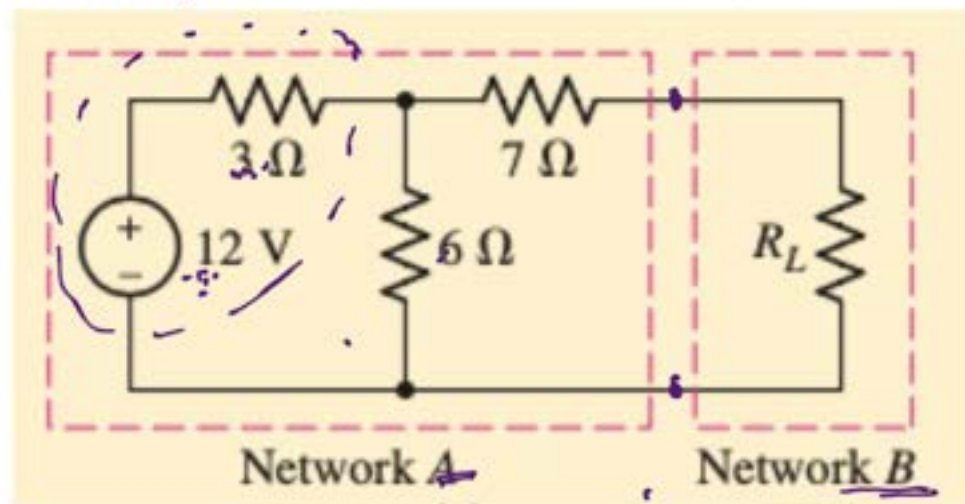

$\equiv$

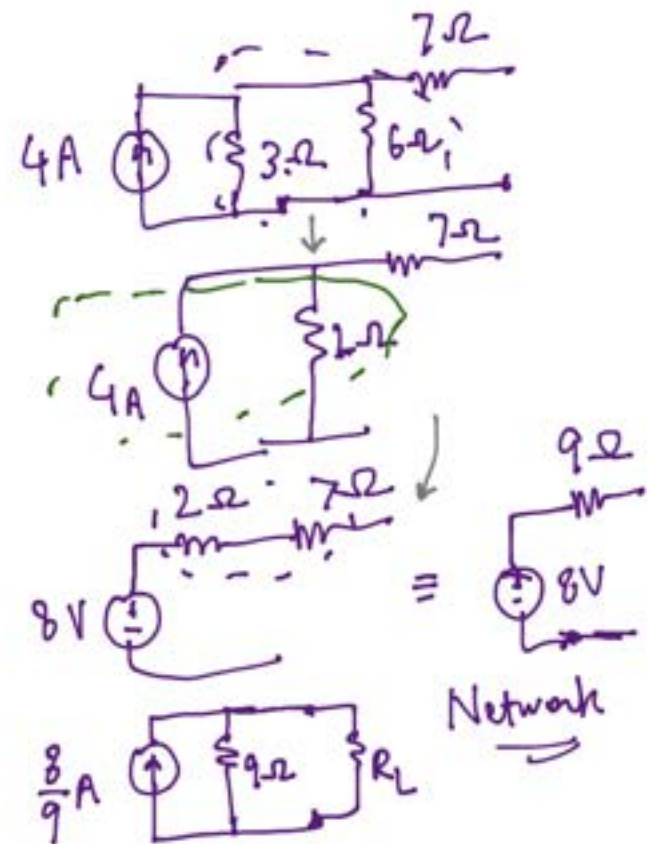

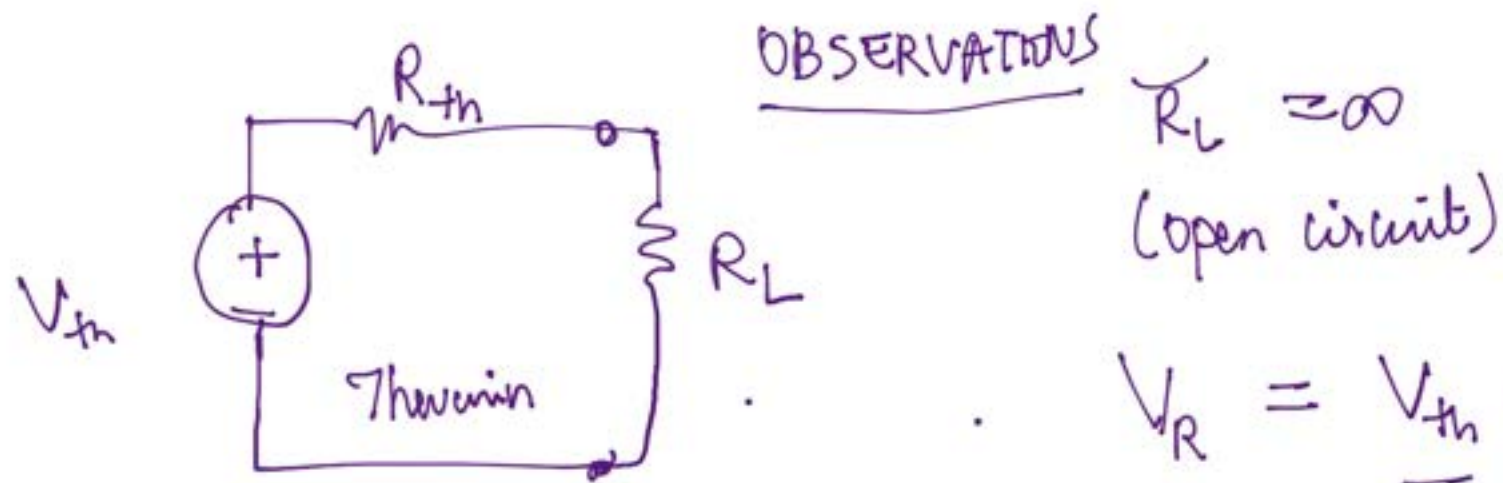

$R_L \approx \infty$   
(open circuit)

$$V_R = V_{th} = V_{max} \\ = V_{oc}$$

↕ source term.



$$I_{max} = I_N = I_{sc}$$

$R_L = 0$   
(Short circuit)

Practice 5.5



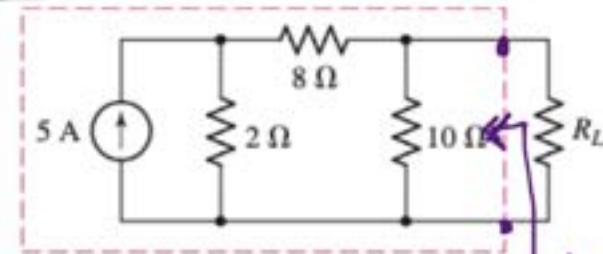
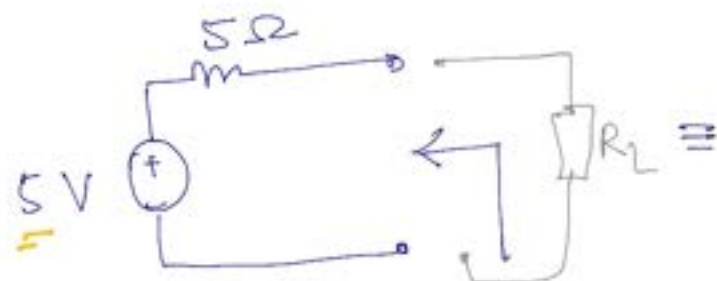


FIGURE 5.26


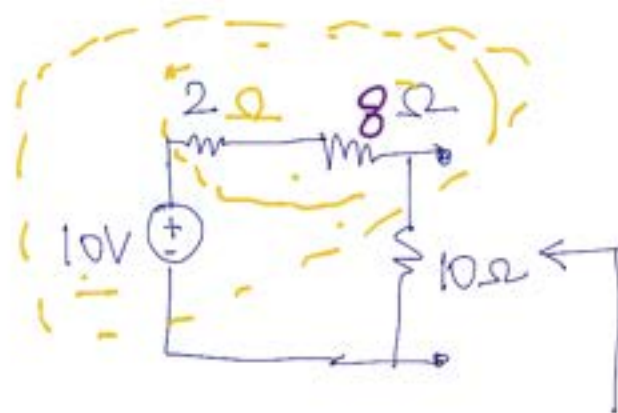


Ex 5.5

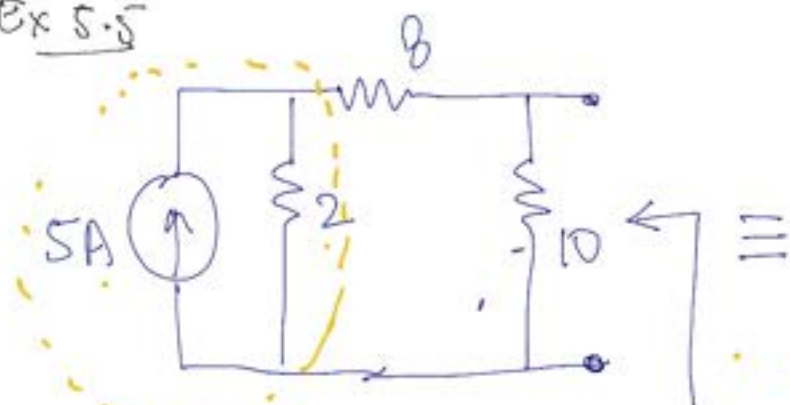


Thevenin  
Equivalent

Independent Sources

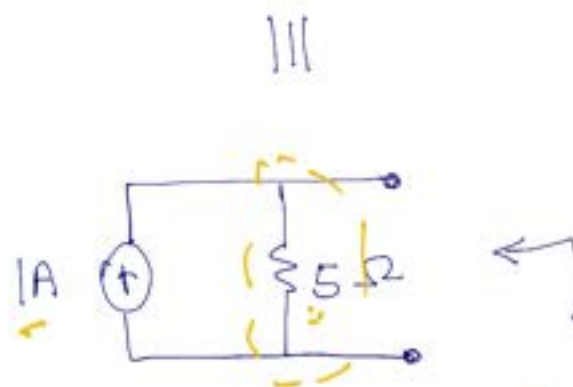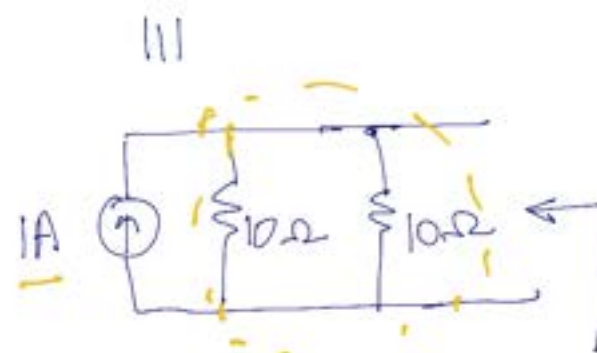

Norton Equivalent


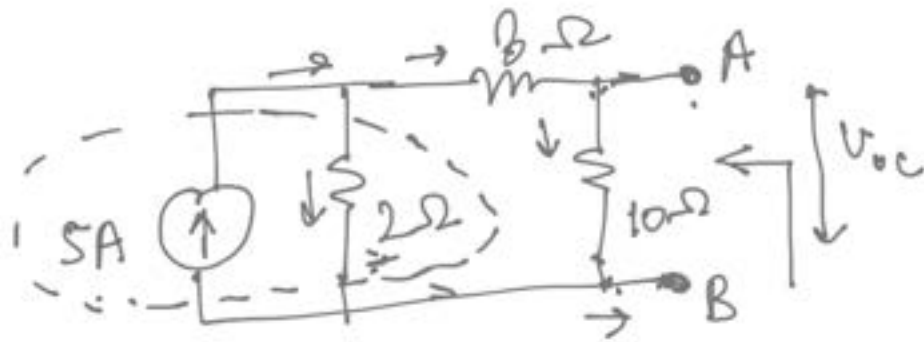


$AB : \left. \begin{array}{l} \text{Voltage} \\ \text{Resistor} \end{array} \right\} \text{Then}$

or  $\left. \begin{array}{l} \text{Current} \\ \text{Resistor} \end{array} \right\} \text{Nah}$



$$V_{eq} = 5A \times 2\Omega = 10V$$

$$R_{eq} = (R_s = R_p = R) = 2\Omega$$

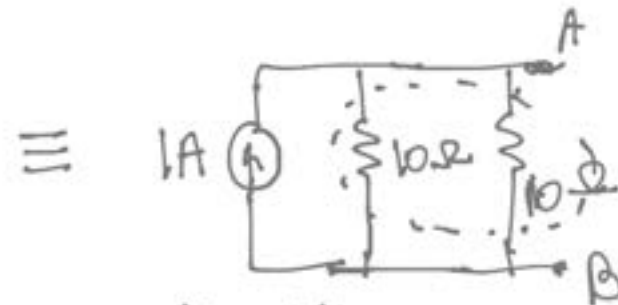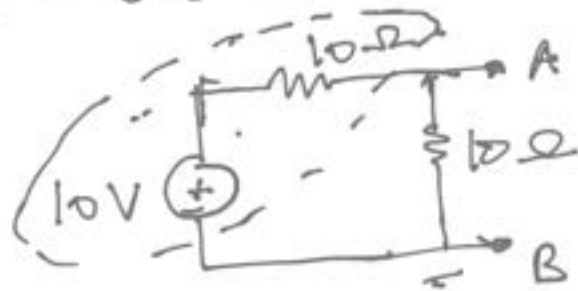

$$I_{eq} = \frac{V}{R} = \frac{10V}{10\Omega} = 1A$$

$$R_{eq} = R_s = R_p = 10\Omega$$

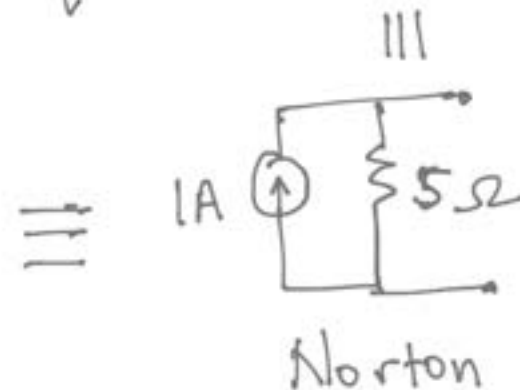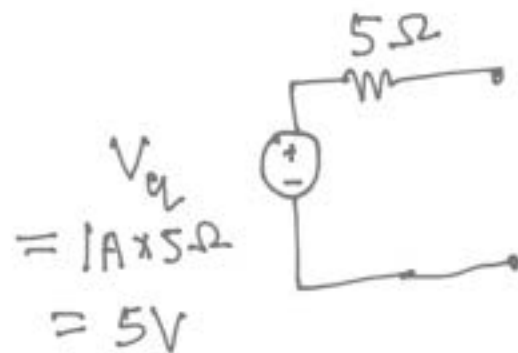

## A Statement of Thévenin's Theorem


1. **Given any linear circuit, rearrange it in the form of two networks,  $A$  and  $B$ , connected by two wires. Network  $A$  is the network to be simplified;  $B$  will be left untouched.**
2. **Disconnect network  $B$ .** Define a voltage  $v_{oc}$  as the voltage now appearing across the terminals of network  $A$ .
3. **Turn off or "zero out" every independent source in network  $A$  to form an inactive network.** Leave dependent sources unchanged.
4. **Connect an independent voltage source with value  $v_{oc}$  in series with the inactive network.** Do not complete the circuit; leave the two terminals disconnected.
5. **Connect network  $B$  to the terminals of the new network  $A$ .** All currents and voltages in  $B$  will remain unchanged.

$\equiv R_{eq}$   
 $R_{TH}$   
 $R_N$

$I_{sc}$  = short circuit current  
 ↓  
 short circuit

$V_{oc} = V_{AB}$   
 ||  
 Open Circuit Voltage.  
 (o c)

P 5.6

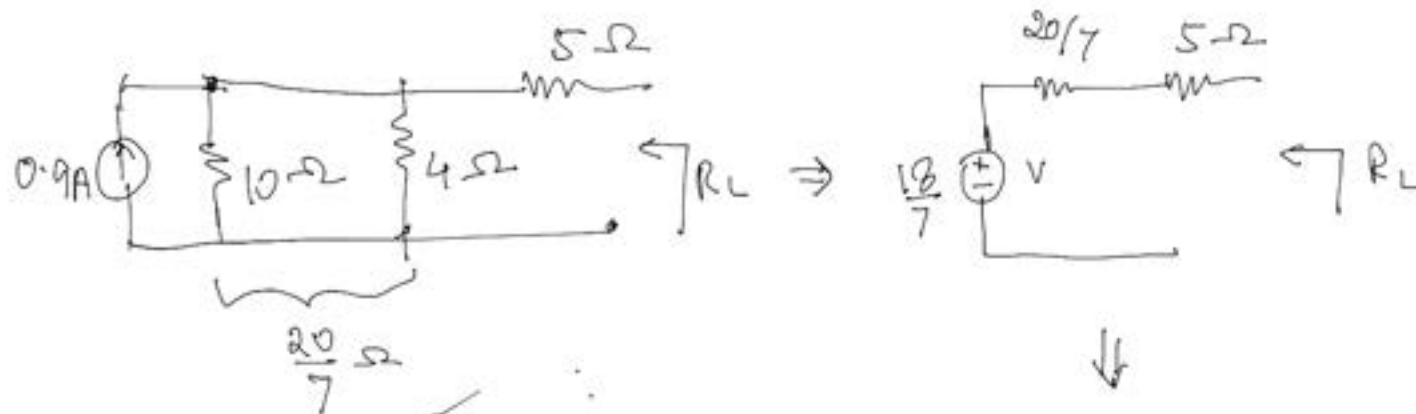

$$V_{th} = 18/7 \text{ V}$$

$$R_{th} = 7.857 \Omega$$

$$R_L = 2 \Omega$$

$$I_L = \frac{18/7}{9.857} = 0.26 \text{ A}$$

Practice Prob 5.6

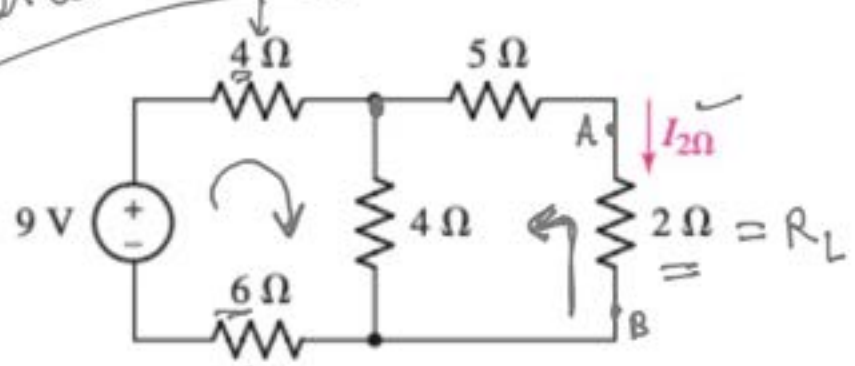



FIGURE 5.28

- a) KCL
  - b) KVL
  - c) Thevenin  $E_L$
- $I_{2\Omega} = ?$



# Example 5.9

## SPECIAL CASE

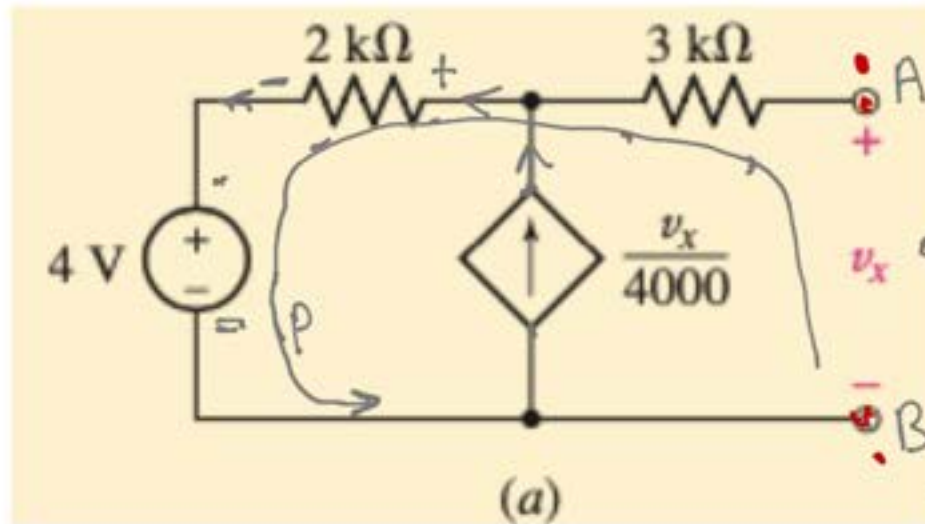

VCCS

$$\textcircled{1} \quad V_{oc} = V_{AB} = V_x$$

$$\textcircled{2} \quad R_{Th}$$

Case  $V_{oc}$ , No current flows through  $3k\Omega$

Apply KVL (p)  
(open circuit  $V_x = \text{open}$ )


$$V_x - 2 \times 10^3 \times \frac{V_x}{4000} - 4 = 0$$

$$\frac{V_x}{2} = 4 \Rightarrow$$

$$V_x = 8V$$

$$V_{oc} = V_x = 8V$$



Case  $I_{sc}$  (Short A-B)

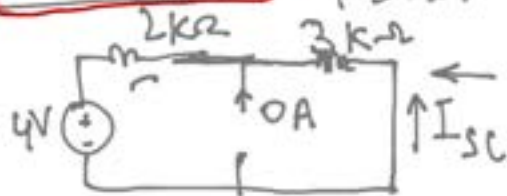

$$I_{sc} = \frac{4V}{5k\Omega} = 0.8mA$$


$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{8}{0.8mA} = 10k\Omega$$
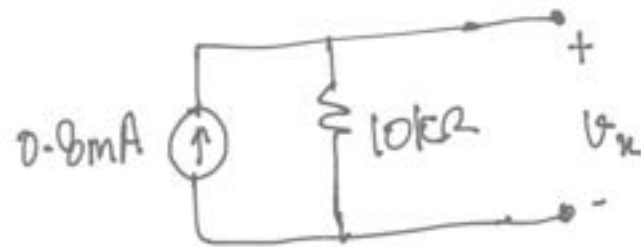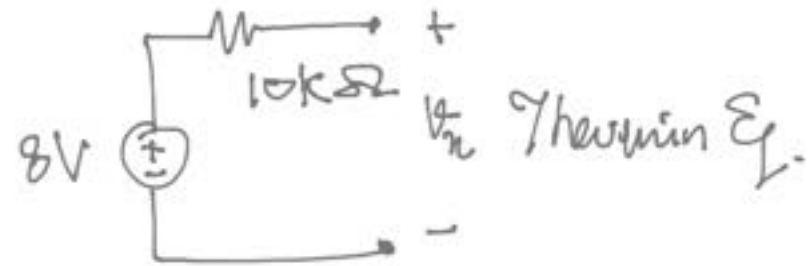
$$R_{TH} = \frac{V_{OC}}{I_{SC}} \rightarrow \begin{array}{l} \text{open circuit voltage } (R=\infty) \\ \text{short circuit current } (R=0) \end{array}$$




Norton Equivalent.

# Example 5.10

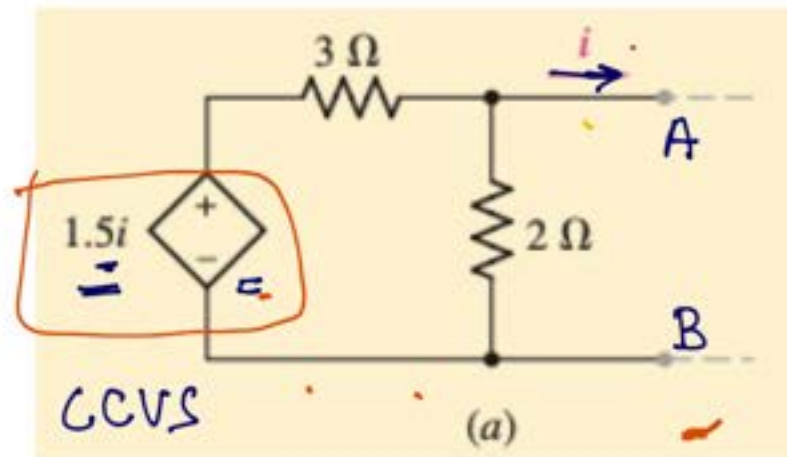


$V_{oc}$   
Dependent source is inactive  
 $i = 0$   
 $V_{oc} = ??$

$i_{sc}$  shorted terminal

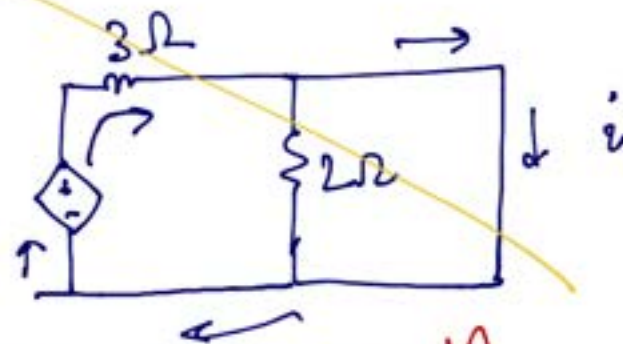

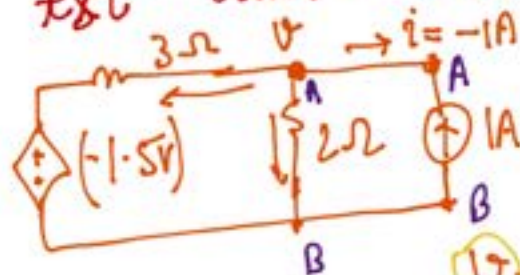I apply a test current source  $I_{test} = 1A$



$i_x$   
2A  
...

$V_x$

$$\frac{V}{3} - (-1.5) - \frac{V}{2} + 1 = 0$$

$$-\frac{V}{3} - 0.5 - \frac{V}{2} + 1 = 0 \Rightarrow \frac{5}{6}V = 0.5 \Rightarrow \boxed{V = 0.6 V} \Rightarrow$$


$$R = \frac{V}{i} = \frac{0.6V}{1A} = 0.6\Omega$$

$$\underline{1A}$$


$$V_{AB}, R_{AB} = 0.6\Omega$$

$$\parallel$$
  

$$0.6V$$

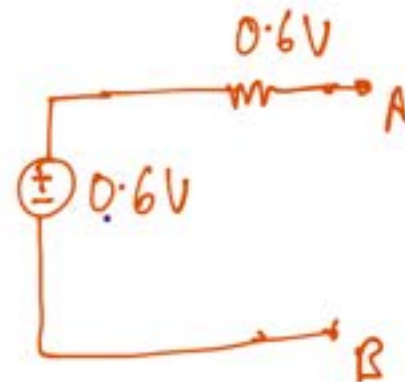


Thevenin  
Eq

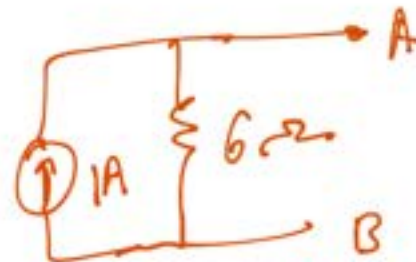

Norton.



# Source Transformation

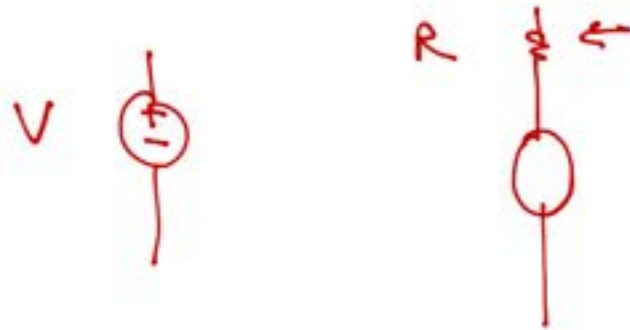

Source Resistance





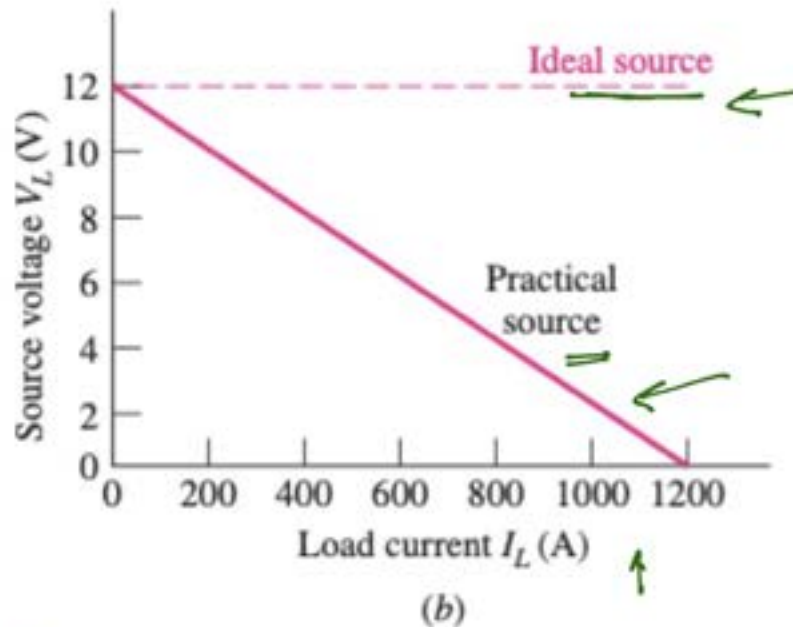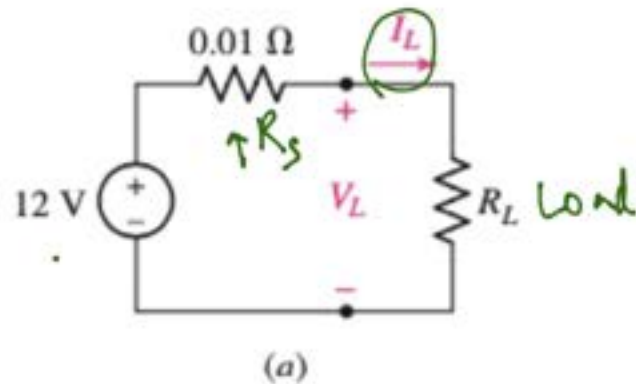

**FIGURE 5.12** (a) A practical source, which approximates the behavior of a certain 12 V automobile battery, is shown connected to a load resistor  $R_L$ . (b) The relationship between  $I_L$  and  $V_L$  is linear.

## Voltage Sources (Non ideal)

$R_s$  = Source Resistance

$I_L$  = Current = Load Current



$$V_s = I_L R_L + I_L R_s$$

Drop  
across  
Source  
Resistance


$$I_L R_L = V_s - I_L R_s$$

↓  
Voltage across the Load


↑  
Drop  $R_s$

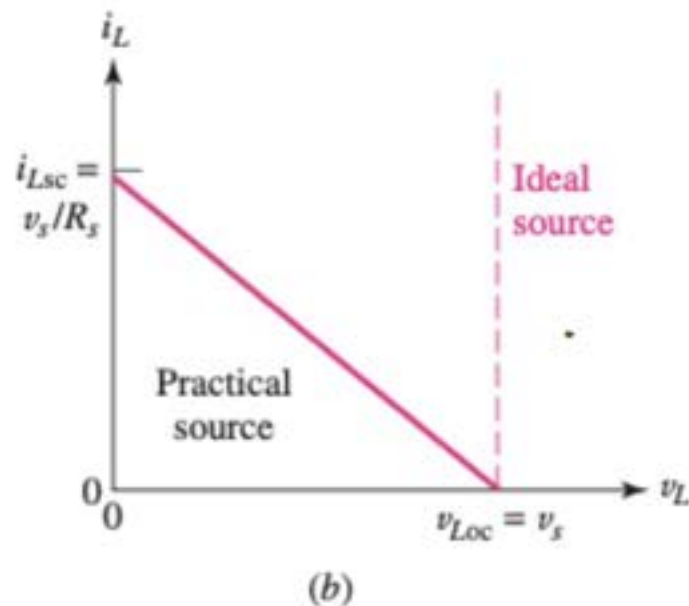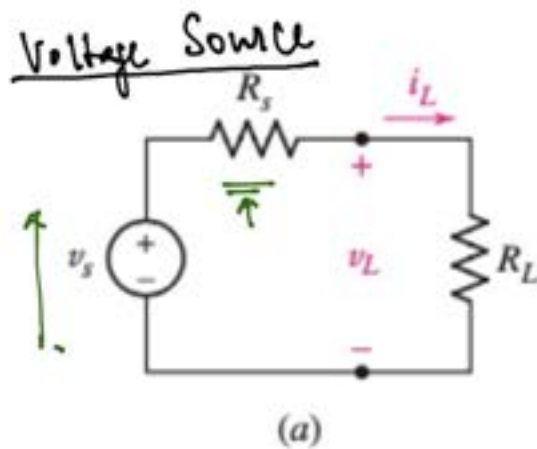

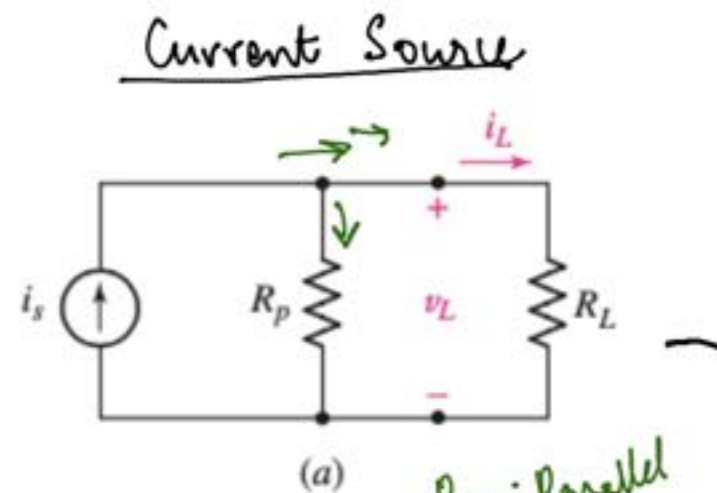■ **FIGURE 5.13** (a) A general practical voltage source connected to a load resistor  $R_L$ . (b) The terminal voltage of a practical voltage source decreases as  $i_L$  increases and  $R_L = v_L / i_L$  decreases. The terminal voltage of an ideal voltage source (also plotted) remains the same for any current delivered to a load.




$R_p$  : Parallel  
Source  
Resistance

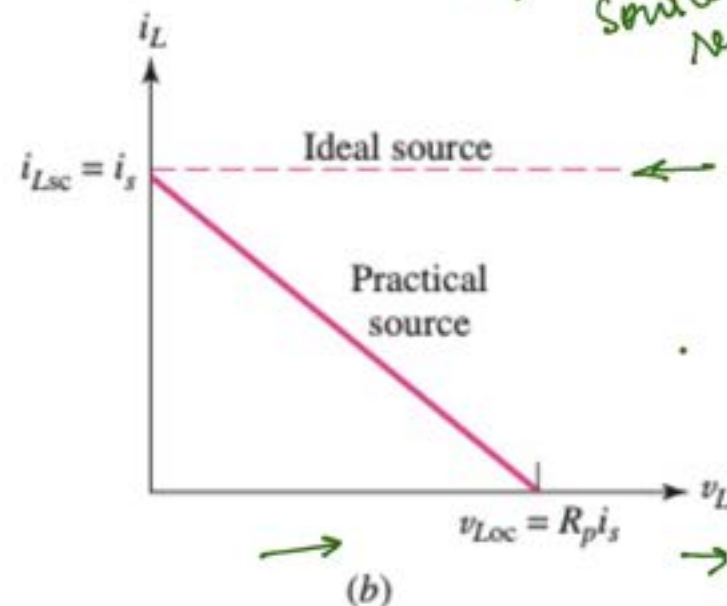


■ **FIGURE 5.14** (a) A general practical current source connected to a load resistor  $R_L$ . (b) The load current provided by the practical current source is shown as a function of the load voltage.
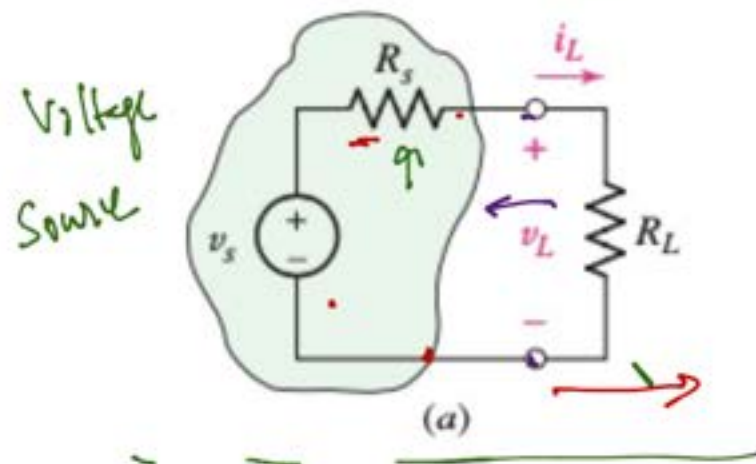
# Voltage Source $\leftrightarrow$ Current Source



$$i_L = \frac{V_s}{R_s + R_L}$$
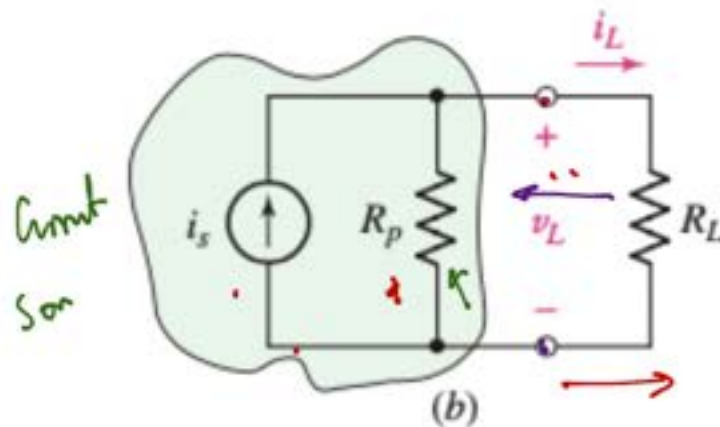
$$\Rightarrow V_L = R_L \frac{V_s}{R_s + R_L}$$



$$i_L = \frac{R_p}{R_p + R_L} i_s$$

$$\Rightarrow V_L' = R_L \cdot \frac{R_p}{R_p + R_L} i_s \equiv$$

**FIGURE 5.15** (a) A given practical voltage source connected to a load  $R_L$ .  
(b) The equivalent practical current source connected to the same load.


For  $R_L$ :  $V_L$  (volts) =  $V_L$  (current source)

$$R_L \frac{V_s}{R_s + R_L} = R_L \frac{R_p}{R_p + R_L} i_s$$


$$R_s \equiv R_p \equiv R$$

$$V_s = R i_s$$

### Example

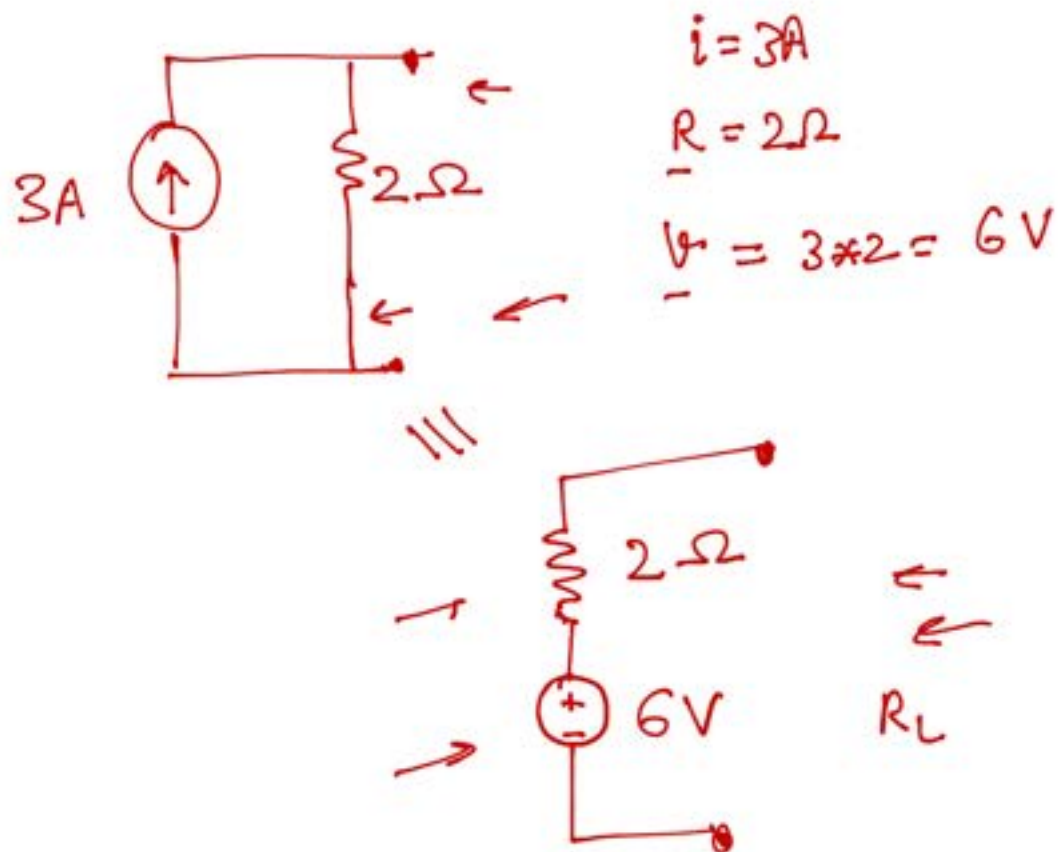


### Generalization:

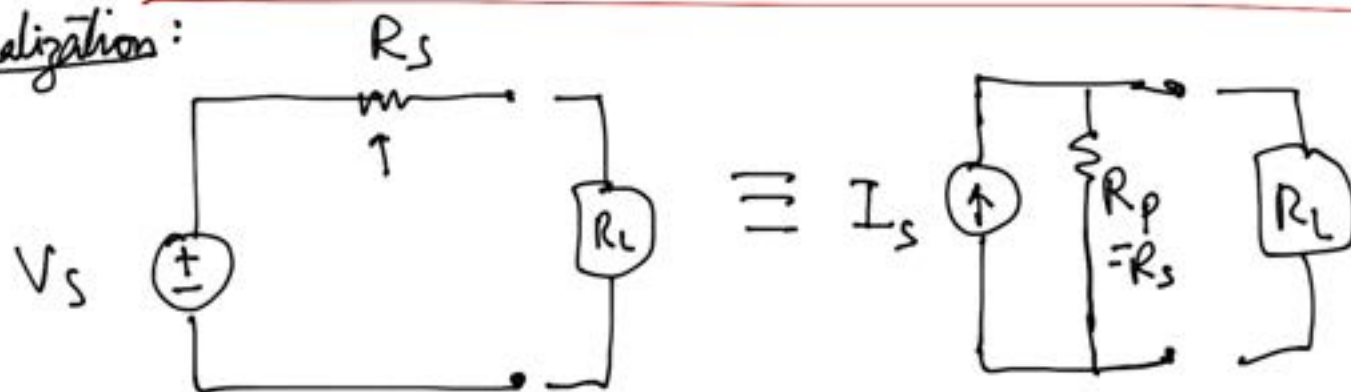




# Example 5.4

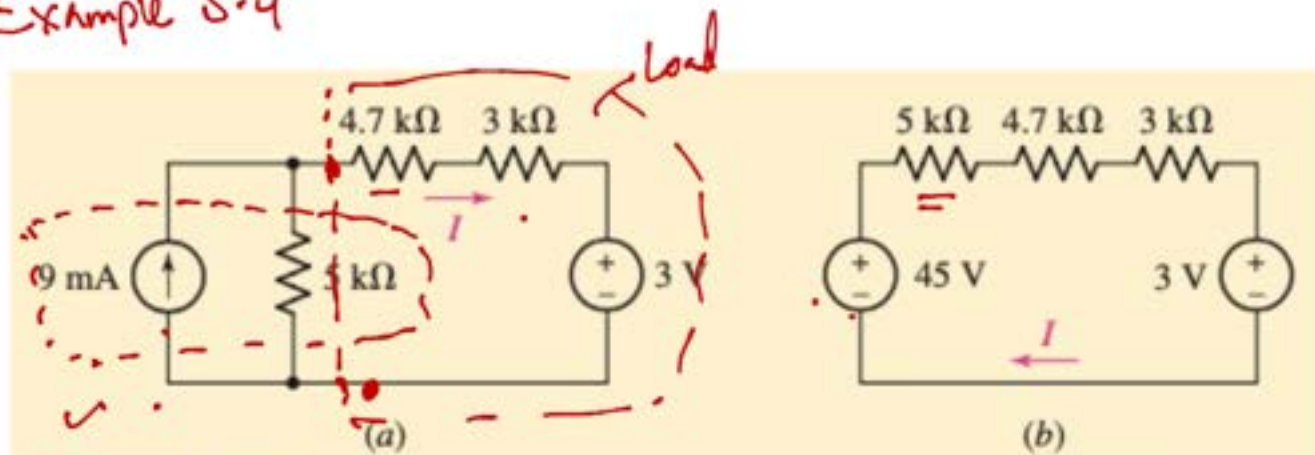

**FIGURE 5.17** (a) A circuit with both a voltage source and a current source. (b) The circuit after the 9 mA source is transformed into an equivalent voltage source.

$$V_s = 9 \text{ mA} \times 5 \text{ k} = 45 \text{ V}$$

$$R_s = 5 \text{ k}\Omega$$

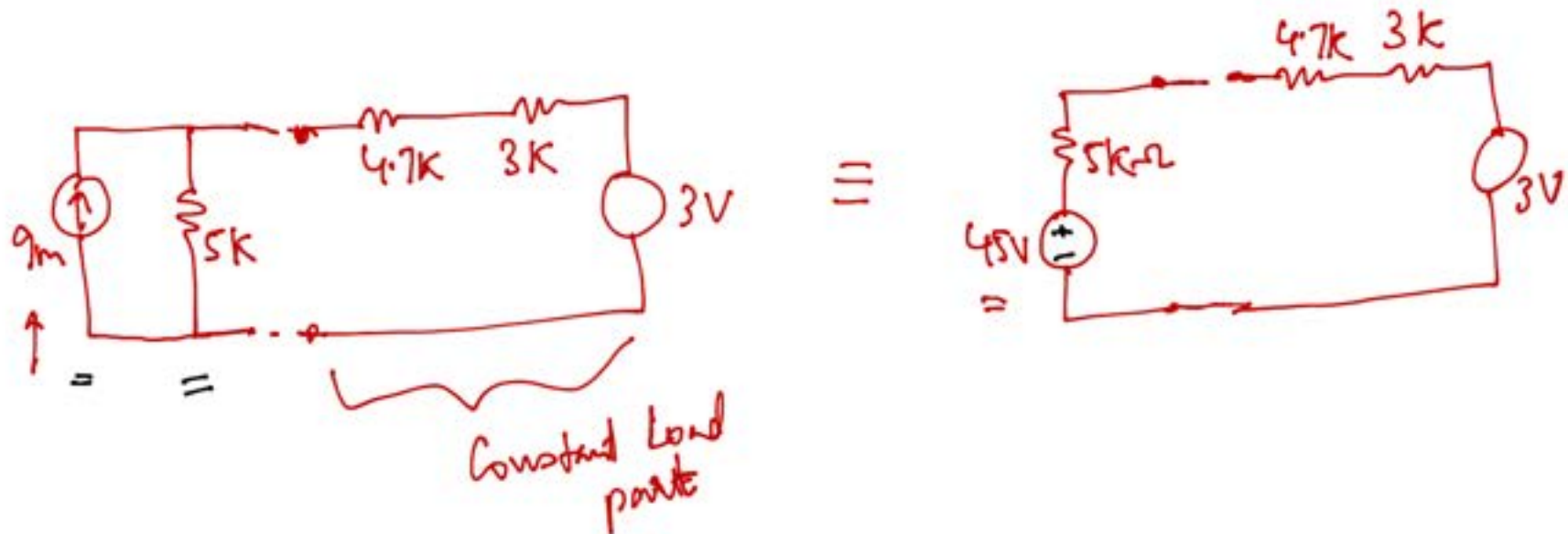



### Practice Prob 5.3

5.3 For the circuit of Fig. 5.18, compute the current  $I_X$  through the  $47\text{ k}\Omega$  resistor after performing a source transformation on the voltage source.

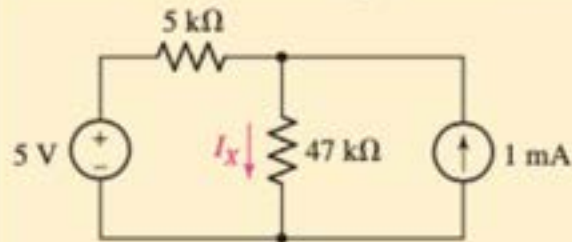



FIGURE 5.18

Ans:  $192\text{ }\mu\text{A}$ .

$$V_s \rightarrow 5\text{V} \quad R_s \rightarrow 5\text{k}\Omega$$


$$i_s = \frac{V_s}{R_s} = \frac{5}{5\text{k}} = 1\text{mA}$$

$$R_p = R_s = 5\text{k}\Omega$$

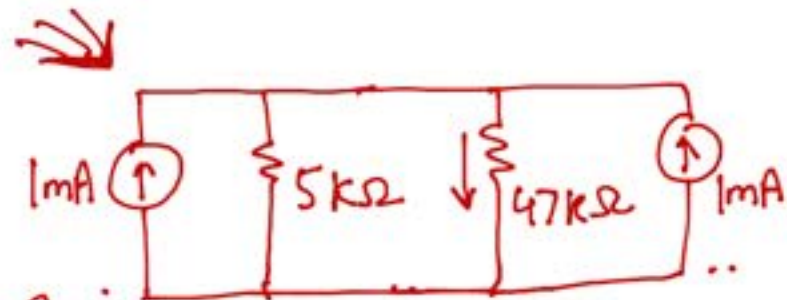


$$i_x = \frac{5}{52\text{k}} * 2\text{mA} = 192\text{ }\mu\text{A}$$

## Example 5.5

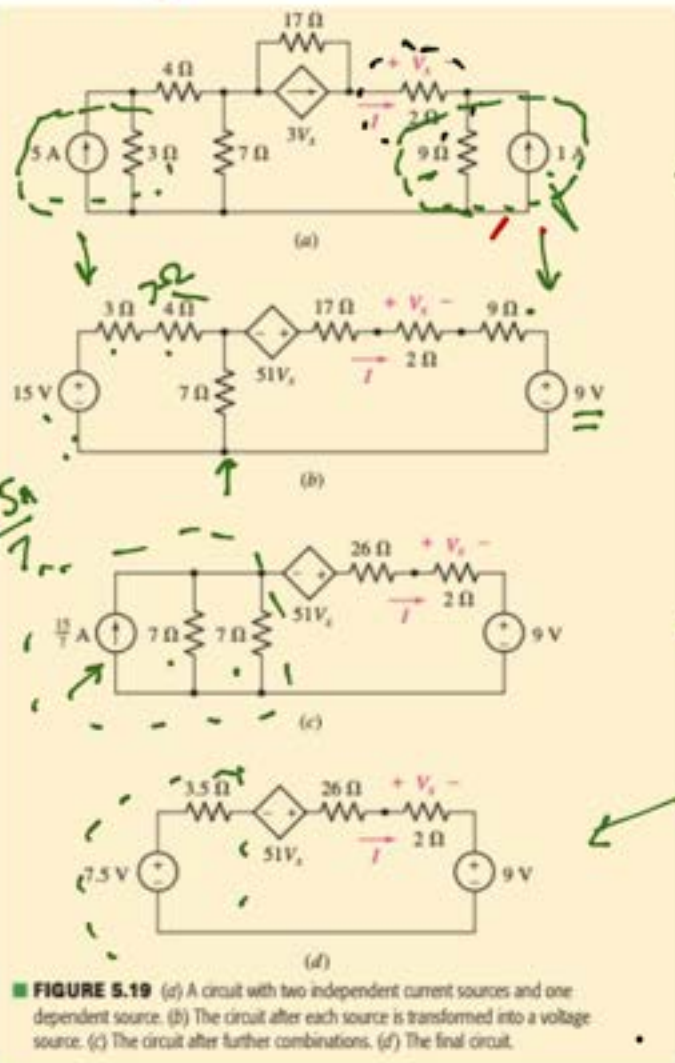




**FIGURE 5.19** (a) A circuit with two independent current sources and one dependent source. (b) The circuit after each source is transformed into a voltage source. (c) The circuit after further combinations. (d) The final circuit.

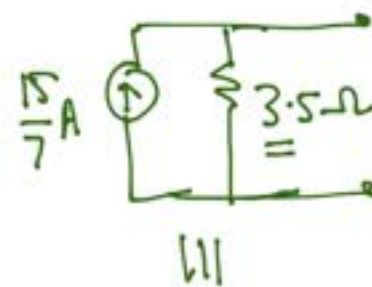


$$V = \frac{15}{7} \times \frac{7}{2} = 7.5V$$

### Summary of Source Transformation

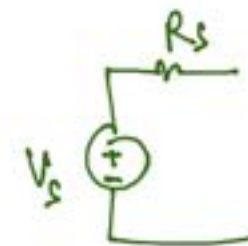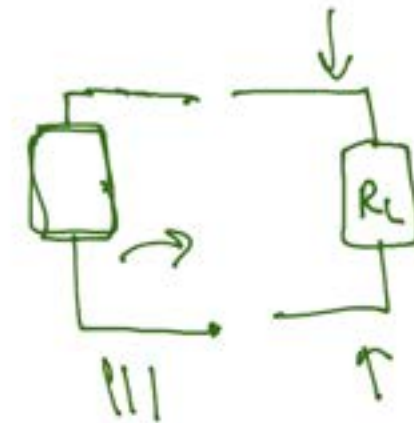
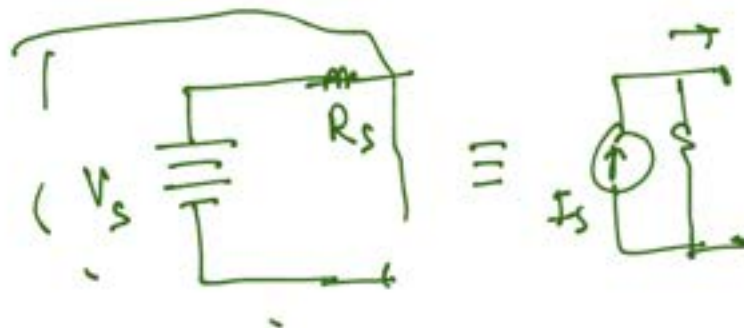
1. A common goal in source transformation is to end up with either all current sources or all voltage sources in the circuit. This is especially true if it makes nodal or mesh analysis easier.
2. Repeated source transformations can be used to simplify a circuit by allowing resistors and sources to eventually be combined.
3. The resistor value does not change during a source transformation, but it is not the same resistor. This means that currents or voltages associated with the original resistor are irretrievably lost when we perform a source transformation.
4. If the voltage or current associated with a particular resistor is used as a controlling variable for a dependent source, it should not be included in any source transformation. The original resistor must be retained in the final circuit, untouched.
5. If the voltage or current associated with a particular element is of interest, that element should not be included in any source transformation. The original element must be retained in the final circuit, untouched.
6. In a source transformation, the head of the current source arrow corresponds to the "+" terminal of the voltage source.
7. A source transformation on a current source and resistor requires that the two elements be in parallel.
8. A source transformation on a voltage source and resistor requires that the two elements be in series.



Thevenin  
 $\epsilon_L$

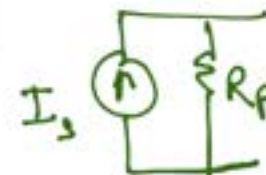


Norton  
 $\epsilon_s$

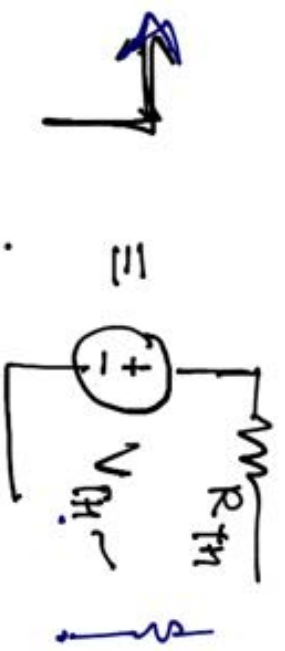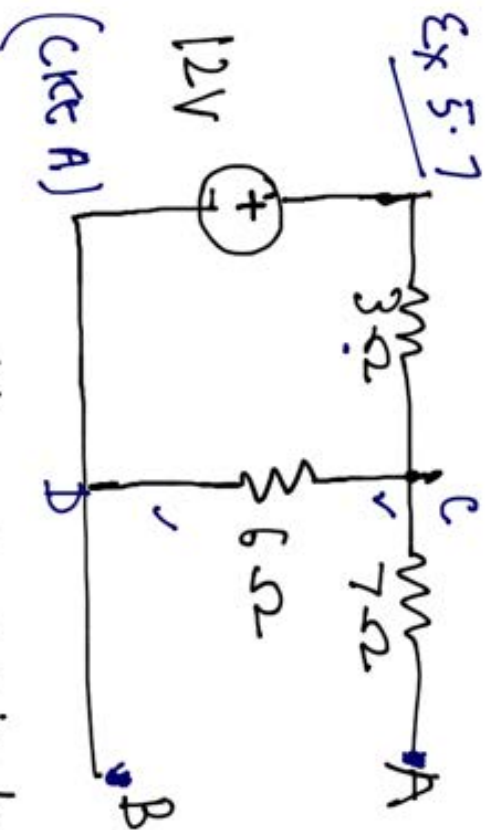

Find Thévenin equivalent between A & B

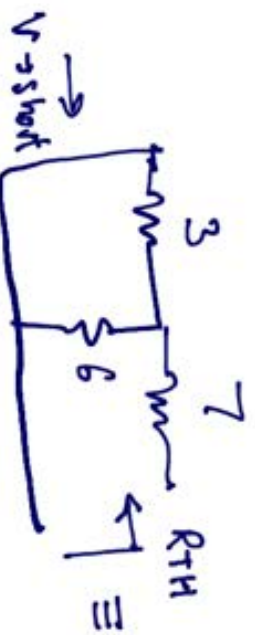Step 1  $R_{th}$  . Make current/voltage source = 0  
 $V \rightarrow$  Short Circuit



$I_{source} \rightarrow$  open circuit


$$2 \Omega \{ \begin{matrix} R_{TH} \\ R_{TH} \end{matrix} \Rightarrow R_{TH} = 9 \Omega$$

Step 2  $V_{TH}$  . Find  $V_{AB}$

In Ckt A  $V_{CD} = V_{AB}$

$$V_{AB} = V_{in} = V_{CD} = \frac{2}{3} \times 12 = 8 \text{ V}$$
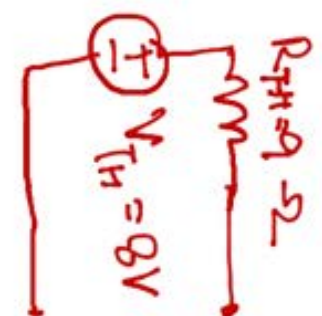
$$; V_{CD} = \frac{6 \Omega \times 12}{6 + 3 \Omega}$$



Thévenin Eq.



## Steps: Thevenin E.

1(a) Know the terminals <sup>(AB)</sup> across which Equivalent has to be calculated.

1(b) Remove the load put

2  ~~$R_{TH}$~~  All independent sources  $\rightarrow 0$

i.e. Voltage Sources  $\rightarrow$  Short Ckt. (S.C)  
Current Sources  $\rightarrow$  Open Ckt (O.C)


Leave dependent sources as they are.

2(b) Find the Equivalent Resistance between A & B.

3. Find voltage  $V_{AB}$  across the two terminals.





# S.G Practice

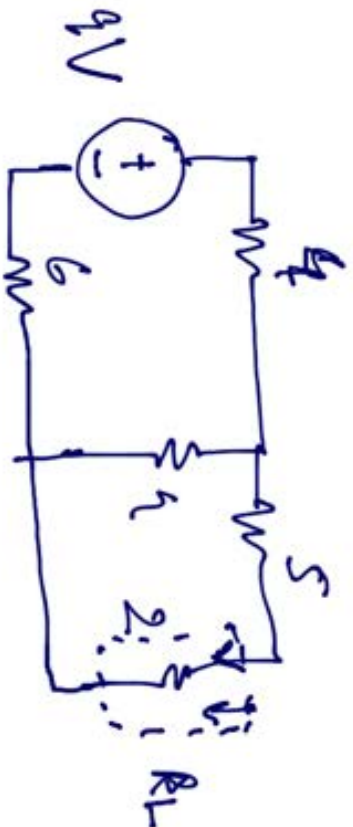


\* In Superposition Theorem, we consider only independent voltage/current

source.

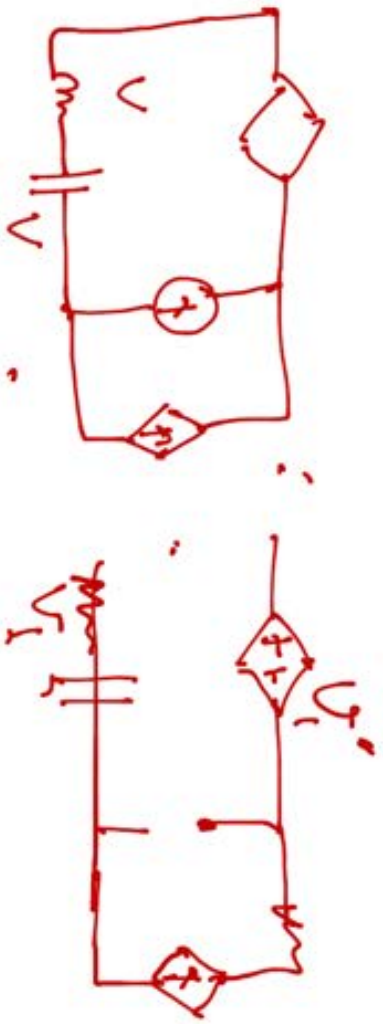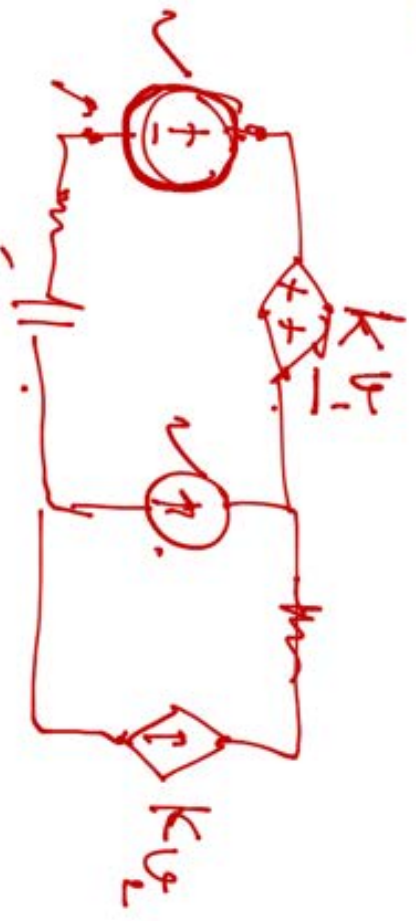


# Norton Equivalent

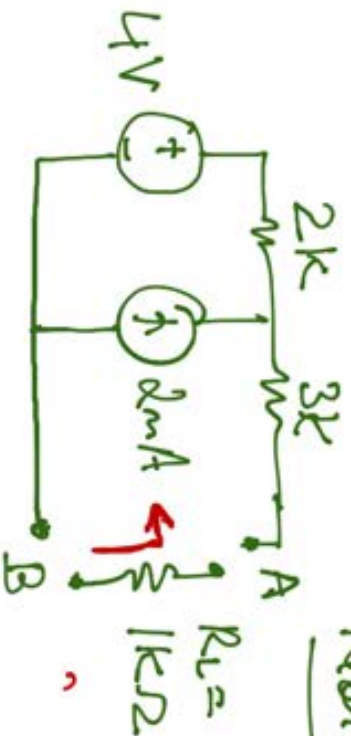

Step 1 Find  $R_N$  :  $V \rightarrow$  S.C

$I_{source} \rightarrow$  O.P

& Solve.

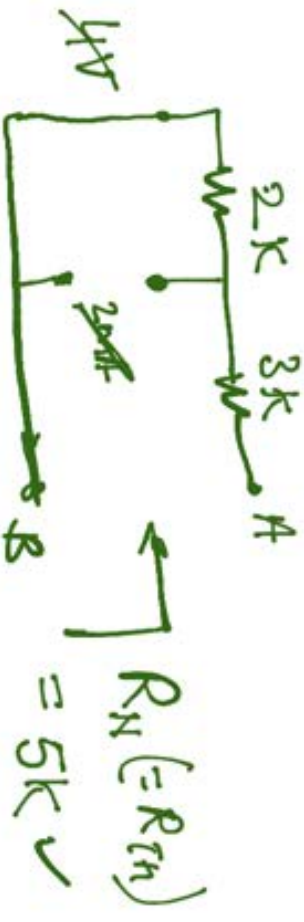

Step 2  $I_N$


S.C terminals



Source Trans. :  $2mA$

$\Rightarrow I_{SC} = -\frac{2}{5} * 4mA = -\frac{8}{5} mA = -1.6mA$

# Maximum Power Transfer Theorem

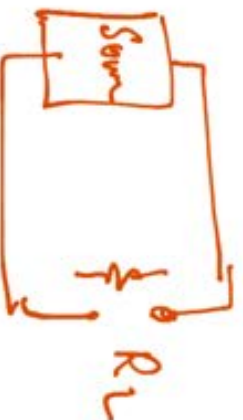


Power transferred to the load =  $\underline{P_L}$

Plot the power vs  $R_L$

$$\frac{\partial P_L}{\partial R_L} = 0$$

$R_L$  is known value.

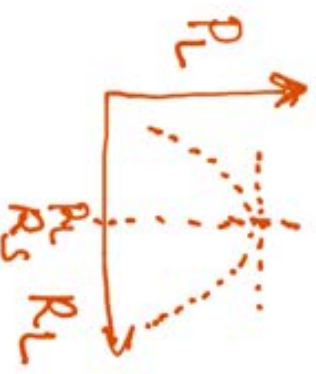

$$R_s = R_L :$$

$$\underline{P_{L_{max}}} = ?$$

## CHAPTER 7

$$\text{Power} = V i = V_c C \frac{dV_c}{dt}$$

Current-Voltage Relationship  $i = C \frac{dv}{dt}$

$$\int_{t_0}^t \underline{dV} = \frac{1}{C} \int_{t_0}^t i \, dt.$$

$$V(t) - \underline{V(t_0)} = \frac{1}{C} \int_{t_0}^t i \, dt$$

$t_0 \rightarrow$  starting / initial time  $\leftarrow$

$Q$ - $V$  Relationship  $Q = CV$

$\downarrow$   
Capacitance

Ex 7.1, 7.2.  
Practice  $\rightarrow$  7.2

Energy & Power of a Cap

$$\text{Power} = C v_c \frac{dv_c}{dt}$$

$$\text{Energy} = \int_{t_0}^t P \cdot dt$$

$$= C \int_{t_0}^t v_c \frac{dv_c}{dt} \cdot dt$$

$$= C \int_{t_0}^t v_c dv_c = C \left[ \frac{v_c^2}{2} \right]_{v_c(t_0)}^{v_c(t)}$$


$$\text{Energy} = \frac{C}{2} \left[ v_c^2(t) - v_c^2(t_0) \right]$$

If initial  $v_c$  at  $t_0 (v_c = 0)$

$$\text{Energy} = \frac{1}{2} C v_c^2(t)$$



## Inductor

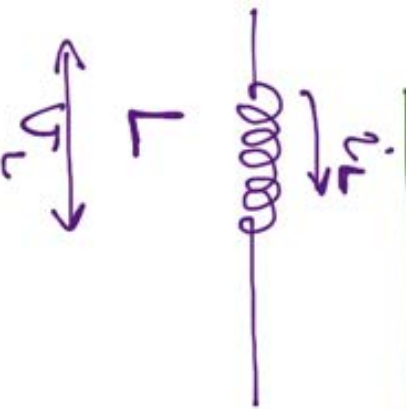

$$V_L = L \frac{di_L}{dt}$$

$L \rightarrow$  inductor

'Inductance' . Units : Henry (H)

Current ~ Voltage Relation.

$$\int_{t_0}^t di_L = \frac{1}{L} \int_{t_0}^t V_L dt$$

$$i_L(t) - i_L(t_0) = \frac{1}{L} \int_{t_0}^t V_L dt$$

## Energy Storage

$$\text{Power} = P = v \cdot i$$

$$P_L = v_L i_L$$

$$= L \frac{di_L}{dt} \cdot i_L$$

$$\text{Energy} = \int_{t_0}^t P_L \cdot dt = L \int_{t_0}^t i_L \cdot \frac{di_L}{dt} dt$$

$$= L \left[ \frac{i_L^2}{2} \right]_{i_L(t_0)}^{i_L(t)}$$


$$\text{Energy} = \frac{L}{2} (i_L^2(t) - i_L^2(t_0))$$

Stored in  
an inductor


$$W_L = \frac{1}{2} L i \quad (\text{if initial condition is zero})$$

7.5, 7.6

# C & L

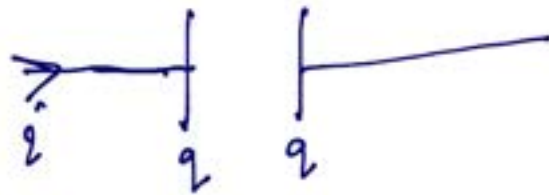

$$i = C \frac{dv}{dt}$$

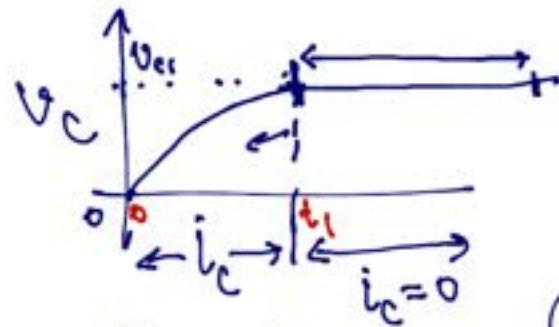


Energy  
building

$v = \text{constant} : \text{D.C}$   
 $i = 0 \Rightarrow \text{Open circuit}$

$C \rightarrow \text{O.C in D.C}$

$v_{c1}$   $v_{c1} \text{ } t > t_1$   
 $\uparrow$   $\uparrow$

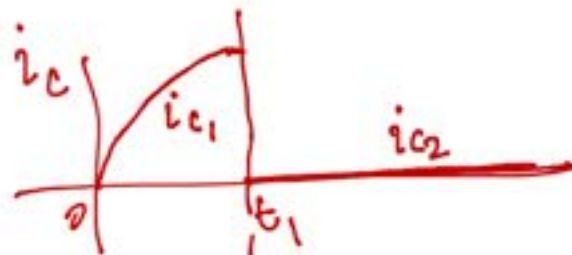
$$\text{Energy} = \frac{1}{2} C (v^2 - v(0)^2) = 0$$



$i_{c2} = 0$   $\frac{dv_c}{dt} = 0$   $(t > t_1)$   
 $t < t_1$   $i = \frac{dv_{c1}}{dt}$   $E = \frac{1}{2} C (v_{c1}^2 - 0)$

## Important Characteristics of an Ideal Capacitor

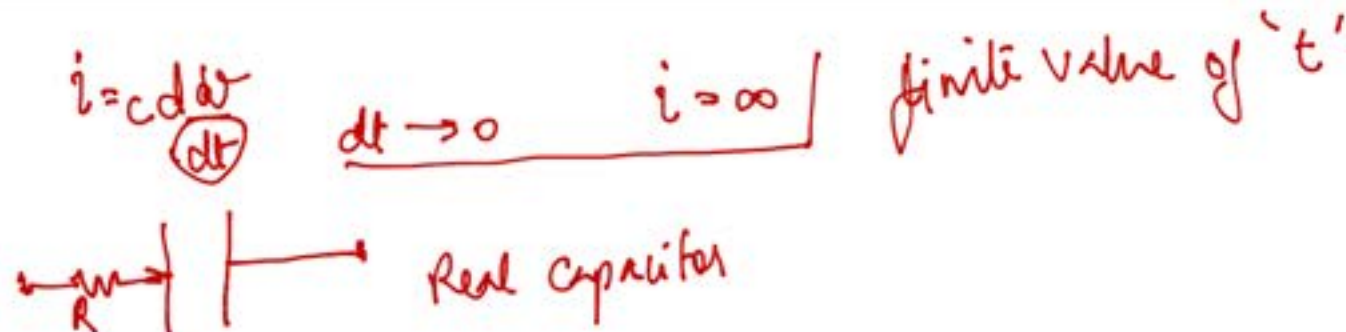
1. There is no current through a capacitor if the voltage across it is not changing with time. A capacitor is therefore an *open circuit to dc*.
2. A finite amount of energy can be stored in a capacitor even if the current through the capacitor is zero, such as when the voltage across it is constant.
3. It is impossible to change the voltage across a capacitor by a finite amount in zero time, as this requires an infinite current through the capacitor. (A capacitor resists an abrupt change in the voltage across it in a manner analogous to the way a spring resists an abrupt change in its displacement.)
4. A capacitor never dissipates energy, but only stores it. Although this is true for the *mathematical model*, it is not true for a *physical* capacitor due to finite resistances associated with the dielectric as well as the packaging.





## Important Characteristics of an Ideal Inductor

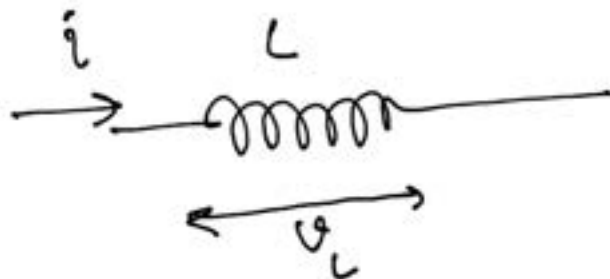
1. There is no voltage across an inductor if the current through it is not changing with time. An inductor is therefore a *short circuit to dc*.
2. A finite amount of energy can be stored in an inductor even if the voltage across the inductor is zero, such as when the current through it is constant.
3. It is impossible to change the current through an inductor by a finite amount in zero time, for this requires an infinite voltage across the inductor. (An inductor resists an abrupt change in the current through it in a manner analogous to the way a mass resists an abrupt change in its velocity.)
4. The inductor never dissipates energy, but only stores it. Although this is true for the *mathematical* model, it is not true for a *physical* inductor due to series resistances.



$$v_L = L \frac{di}{dt}$$


$$i = \text{constant}$$

$$v_L = 0$$

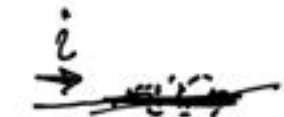  
Short Circuit

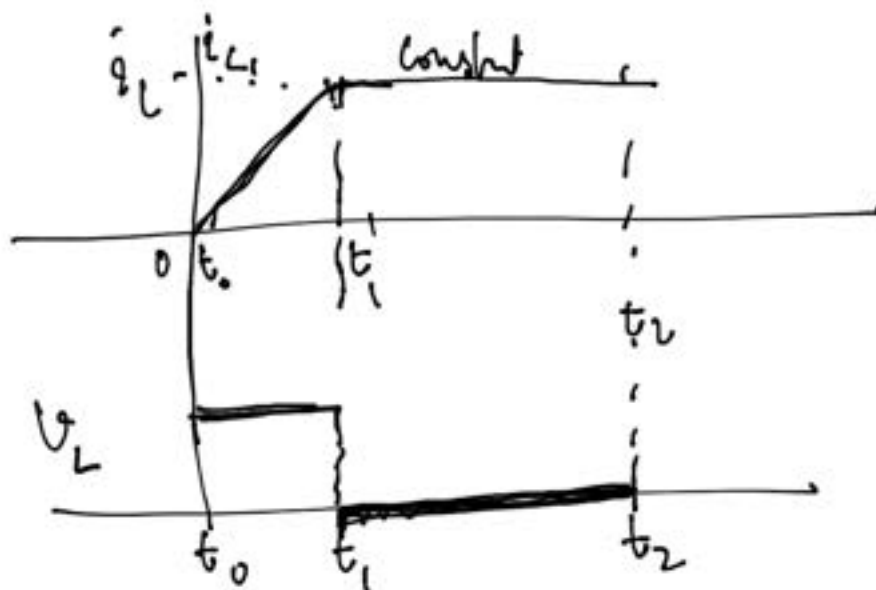
$$E = \frac{1}{2} L \left[ i^2(t_f) - i^2(t_0) \right]$$






$$V_L = \frac{di}{dt} = \text{const}$$

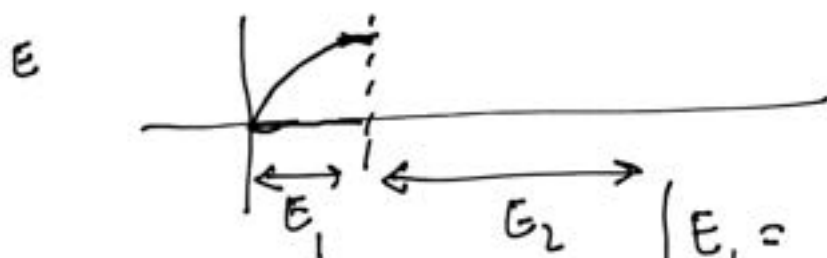$\times \left\{ \begin{array}{l} dt \rightarrow 0 \Rightarrow V_L = \infty \\ \text{Always } dt \rightarrow \text{finite.} \end{array} \right.$




$$\left\{ \begin{array}{l} E_1 = \frac{1}{2} L [i(t_1)^2 - i(t_0)^2] \rightarrow E_1 \\ E_2 = \frac{1}{2} L [i(t_2)^2 - i(t_1)^2] = 0 \\ i(t_2) = i(t_1) \end{array} \right. \quad \begin{array}{l} \text{stored} \\ \uparrow \\ E_1 \end{array}$$

Ideal ( $R=0$ )

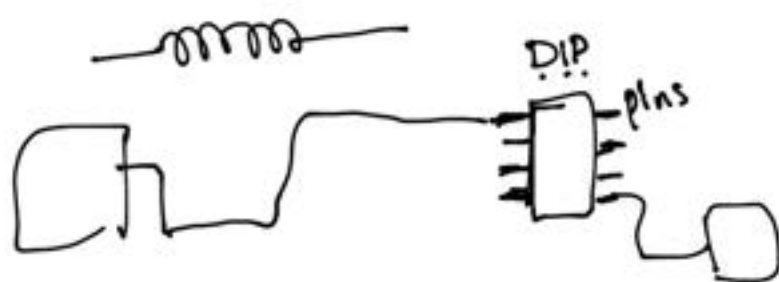


inductor : Induction cooking.  
Hertz

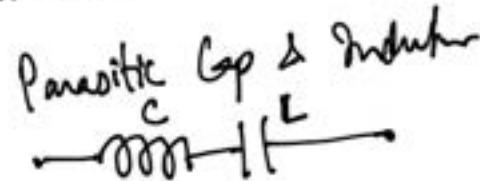

## Combination

### Capacitive

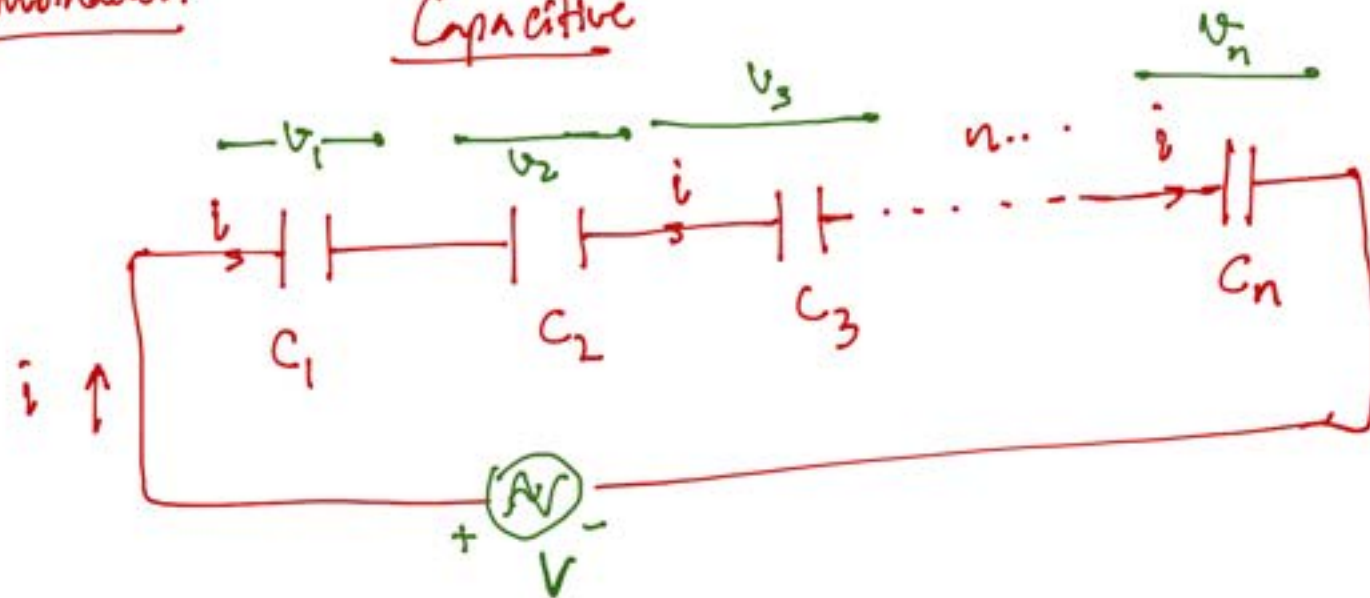



$$V = V_1 + V_2 + \dots + V_n$$
$$V = \frac{1}{C} \int_0^t i \cdot dt$$
$$\int dV_c = \int \frac{1}{C} i_c dt \quad \left( i_c = C \frac{dV_c}{dt} \right)$$

$$V = \frac{1}{C_1} \int_0^t i dt + \frac{1}{C_2} \int_0^t i dt + \dots + \frac{1}{C_n} \int_0^t i dt$$

$$\underline{V} = \left[ \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right] \int_0^t i dt = \frac{1}{C_{eq}} \int_0^t i dt$$

$$\left( \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right)$$

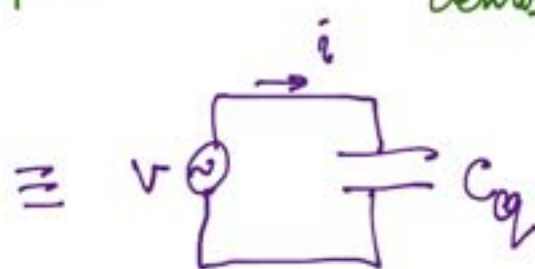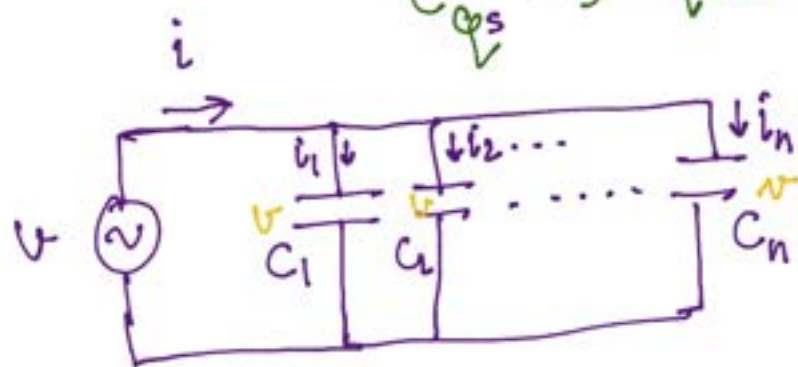$C_{eqs} \rightarrow$  Equivalent Capacitance.  $\rightarrow$  Series Combination.




$$\begin{aligned} i &= i_1 + i_2 + \dots + i_n \\ &= C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \dots + C_n \frac{dv}{dt} \\ &= (C_1 + C_2 + \dots + C_n) \frac{dv}{dt} \\ &= C_{eq} \frac{dv}{dt} \end{aligned}$$

Parallel  $C_{eq} = C_1 + C_2 + C_3 + \dots + C_n$

# Inductor

Series

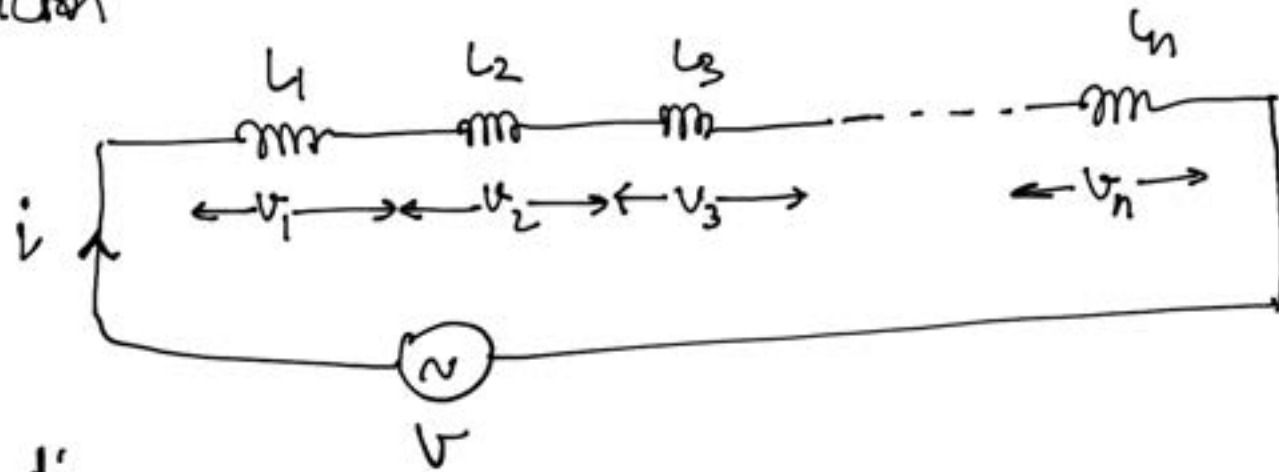

$$V_1 = L_1 \frac{di}{dt} \quad \text{or}$$

$$V = V_1 + \dots + V_n$$


$$= L_1 \frac{di}{dt} + \dots + L_n \frac{di}{dt}$$

$$= (L_1 + \dots + L_n) \frac{di}{dt}$$

$$V = L_{eq} \frac{di}{dt}$$


$$L_{eq} = L_1 + L_2 + \dots + L_n$$

: Series Equivalent Inductance

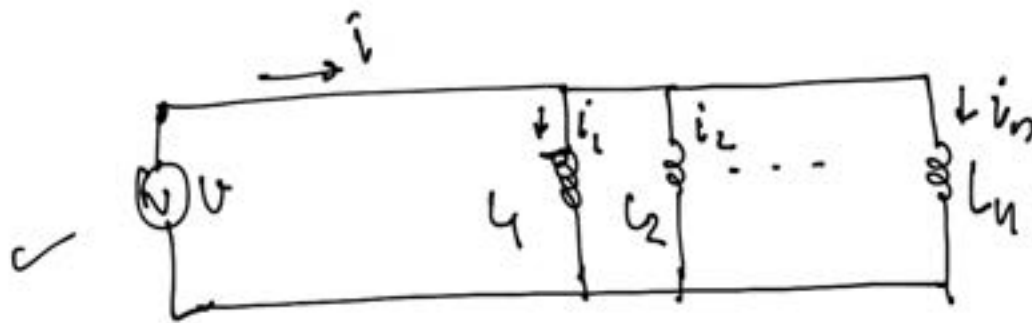

$$V = L \frac{di}{dt}$$
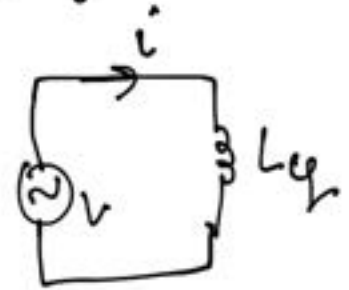
$$\Rightarrow i = \frac{1}{L} \int_0^t V dt$$




$$\begin{aligned}
 i &= i_1 + \dots + i_n \\
 &= \frac{1}{L_1} \int_0^t V dt + \dots + \frac{1}{L_n} \int_0^t V dt \\
 &= \left( \frac{1}{L_1} + \dots + \frac{1}{L_n} \right) \int_0^t V dt \\
 &= \frac{1}{L_{eq}} \int_0^t V dt
 \end{aligned}$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$

Equivalent  
Parallel Inductance




# Example 7.8

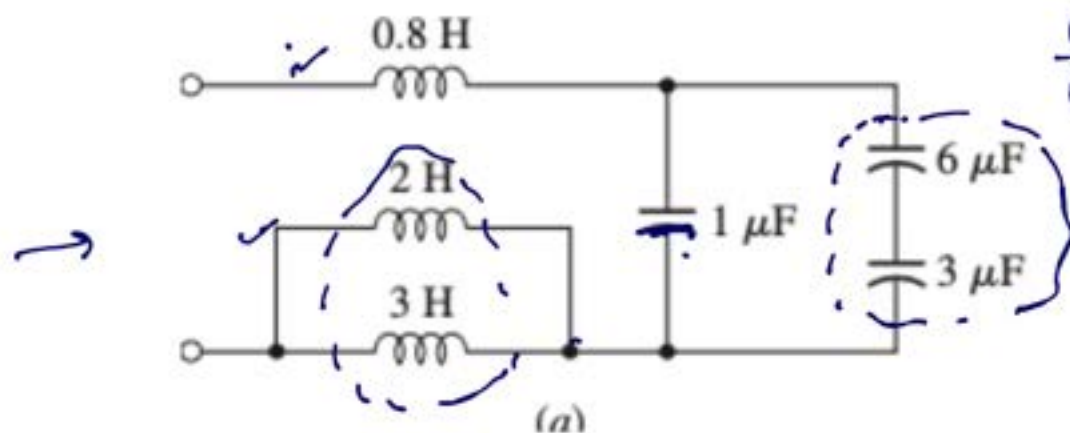


$$\frac{6 \times 3}{6+3} = 2 \mu F$$

Initial value of capacitor

observation

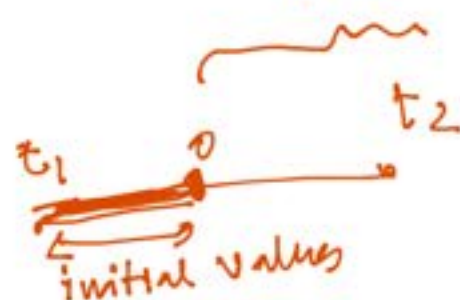
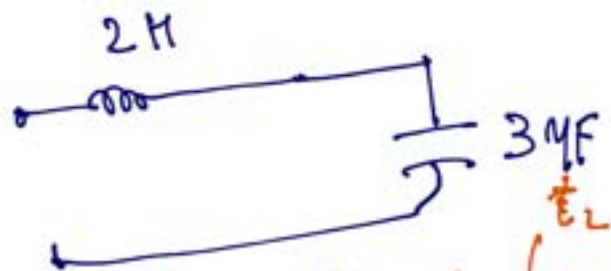
$$\frac{1}{L} = \frac{1}{2} + \frac{1}{3} \Rightarrow L = \frac{6}{5} H = 1.2 H$$



1

$$v = L \frac{di}{dt} \Rightarrow i = \frac{1}{L} \int_{t_1}^{t_2} v \cdot dt$$

$$i = \underbrace{\frac{1}{L} \int_{t_1}^{t_2} v \cdot dt}_{\text{Initial value of inductor}} + \frac{1}{L} \int_{t_2}^{t_2} v \cdot dt = i_{L0} + \frac{1}{L} \int_0^{t_2} v \cdot dt$$


$$i = C \frac{dv}{dt}$$

$$v = \frac{1}{C} \int_{t_1}^{t_2} i \cdot dt$$

$$= \underbrace{\frac{1}{C} \int_{t_1}^0 i \cdot dt}_{V_{C0}} + \frac{1}{C} \int_0^{t_2} i \cdot dt$$

$$v = V_{C0} + \frac{1}{C} \int_0^{t_2} i \cdot dt$$

(c)

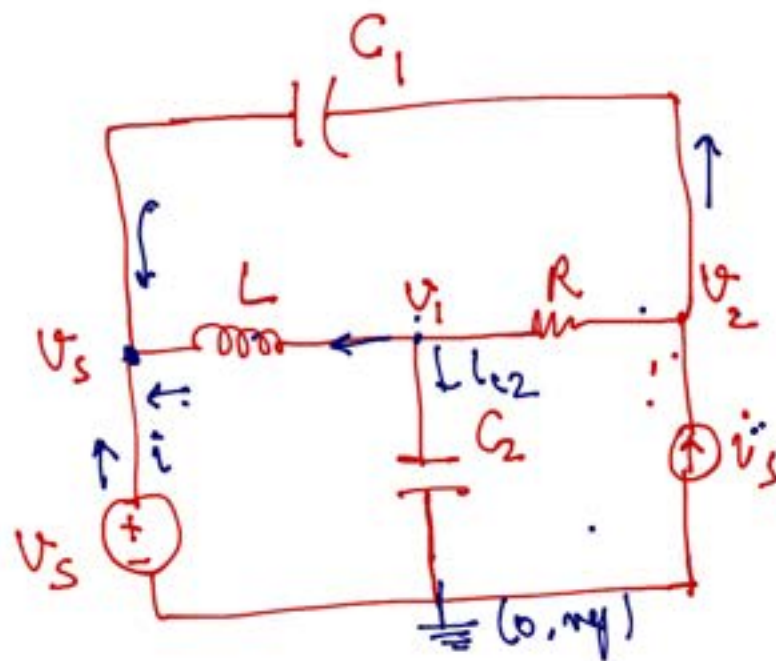

Nodal KCL

$$i_{C_1} = C_1 \frac{d(v_2 - v_s)}{dt}$$

$$i_L = \frac{1}{L} \int_0^t (v_1 - v_s) dt + i_{L0}$$

$$C_1 \frac{d(v_2 - v_s)}{dt} + \frac{1}{L} \int_0^t (v_1 - v_s) dt + i_{L0} + i = 0 \quad \text{--- (1)}$$

$$i_{C_2} = C_2 \frac{dv_1}{dt}$$

[v\_1]

$$\frac{1}{L} \int_0^t (v_1 - v_s) dt + i_{L0} + C_2 \frac{dv_1}{dt} + \frac{v_1 - v_2}{R} = 0 \quad \text{--- (2)}$$

$$(v_2) - C_1 \frac{d(v_2 - v_s)}{dt} + \frac{v_2 - v_1}{R} + i_s = 0 \quad \text{--- (3)}$$

Integro differential Equation

KCL, KVL are satisfied,

## Linearity of L & C circuits

Equation 1

$$\text{LHS1} = R \underline{i} + L \frac{d\underline{i}}{dt} + \frac{1}{C} \int_0^t i dt + \underline{V_{C0}} = \underline{V_S} \quad \text{RHS1}$$

Increase current 'k' time

$$\text{LHS2: } R \hat{i} k + L k \frac{d\hat{i}}{dt} + \frac{k}{C} \int_0^t i dt + \underline{k V_{C0}} \Rightarrow$$

$$i \text{ (circled)} = k \times \text{LHS1} = k \times \underline{\text{RHS1}}$$

given that k is multiplied to constant  $V_{C0}$  also  
i.e.  $V_{C0}$  as a input independ voltage source.

if all inputs are changed k  $\Rightarrow$  output also change 'k'  
 $\Rightarrow$  Linearity 'Equation 1 is linear!'