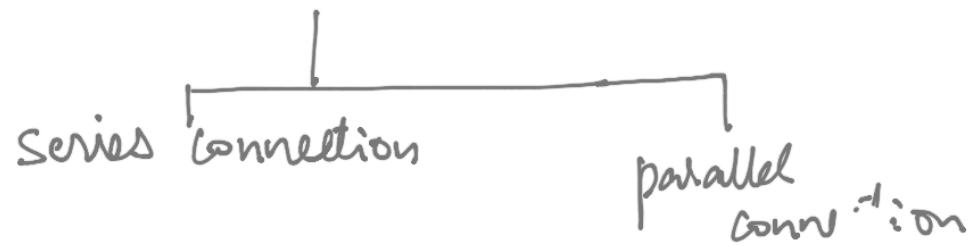





Chapter 9

R - L - C circuits




Applications

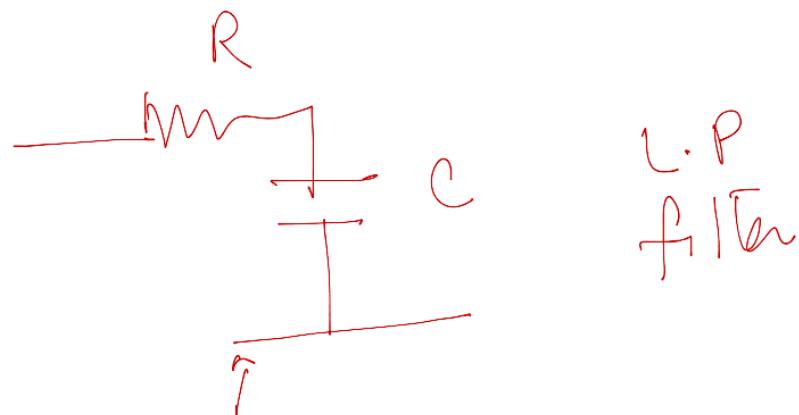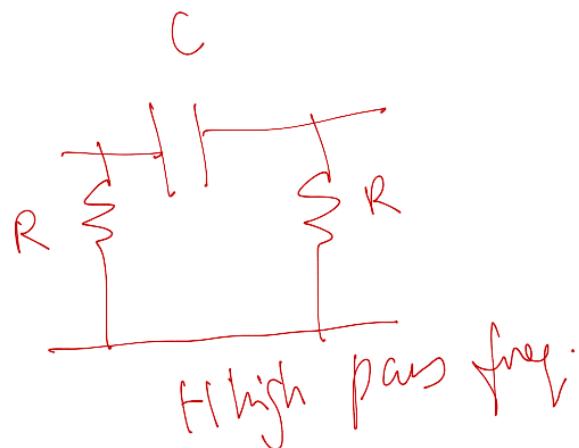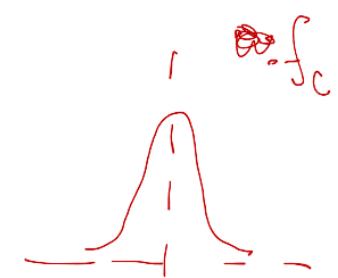- 1) Radio tuners (series ckt.)
- 2) Freq. multiplexers
- 3) Harmonic suppression filters.



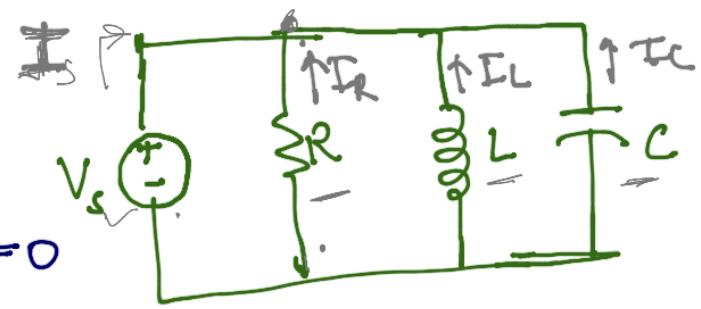With Source $R \parallel L \parallel C$ circuit



KCL
(flowing into the node)

$$I_s + \frac{V_s}{R} + i_L + C \frac{dV_s}{dt} = 0$$

$$i_L = \frac{1}{L} \int V_s dt$$

\Rightarrow Taking derivative of natural part (leave out I_s, V_s for simplicity)

$$\frac{1}{R} \frac{dV_s}{dt} + \frac{V_s}{L} + C \frac{d^2 V_s}{dt^2} = 0 \quad \text{2nd ODE}$$

if $V_s = A e^{st}$ (General Solution)

$$\frac{1}{R} A s e^{st} + \frac{A e^{st}}{L} + C s^2 A e^{st} = 0$$

Quadratic Equation.

$$s^2 + \frac{s}{RC} + \frac{1}{LC} = 0$$

Characteristic Equation
2 solutions

Solutions for 's': $s_1, s_2 = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$

$\left\{ \begin{array}{l} s_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} \\ \text{+ve, Negative imaginary.} \end{array} \right.$

2nd ODE

\Rightarrow Solution (natural response)

$$V_n = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$V_f = V_f \quad (\text{found by } L \rightarrow s.c \text{ & } C \rightarrow 0.c \text{ & solving})$$

$$\therefore V_s = V_f + V_n = \boxed{V_f + A_1 e^{s_1 t} + A_2 e^{s_2 t}} \quad \begin{matrix} \checkmark \\ \checkmark \end{matrix}$$

Solution

forcing

Finding A_1 & A_2 (A_1 & $A_2 \rightarrow \text{constants}$)

$$\boxed{V_s(t=0)} = \text{Initial Condition 1} = \boxed{V_f + A_1 + A_2 = V_0} \quad \rightarrow ①$$

$(V_s = V_0 \text{ at } t=0)$

$$\frac{dV}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

$$\boxed{\frac{dV}{dt} \Big|_{t=0}} = \text{Initial Condition 2} =$$

$$\boxed{A_1 s_1 + A_2 s_2 = \frac{dV}{dt} \Big|_{t=0}} \quad \rightarrow ②$$

Simultaneously solve. ① & ② to find A_1 & A_2

$$V_s = V_f + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Analysis of solutions s_1 & s_2

$$s_1, s_2 = -\frac{1}{2RC} \pm \sqrt{\frac{1}{(2RC)^2} - \frac{1}{LC}} \rightarrow \text{units should be } \frac{1}{\text{seconds}}$$

Let,

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

: Resonant frequency

$$\alpha = \frac{1}{2RC}$$

: Damping coefficient

$s_1, s_2 \rightarrow$ complex frequencies

$$\rightarrow s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad \& \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

Case I $\alpha > \omega_0$

s_1 & s_2 are Real no.s
& Negative

Over damped response

Case II $\alpha = \omega_0$

$$s_1 = s_2 = -\alpha$$

Critically damped response

Case III $\alpha < \omega_0$

s_1, s_2 are complex no.s

Under damped response

$\alpha > \omega_0$: Over damped response

$$\Rightarrow \frac{1}{(2RC)^2} > \frac{1}{LC} \Rightarrow LC > 4R^2C^2 \Rightarrow L > 4R^2C \quad s_1, s_2 \quad \left\{ \begin{array}{l} \text{Negative} \\ \text{Real} \end{array} \right.$$

Time constants: $s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$ > $s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$

$$\tau_1 = \frac{1}{s_1} ; \tau_2 = \frac{1}{s_2}$$

negative


$$|s_1| < |s_2| \Rightarrow \left| \frac{1}{\tau_1} \right| < \left| \frac{1}{\tau_2} \right| \Rightarrow |\tau_2| < |\tau_1|$$

$|s| \rightarrow \text{magnid}$

$$\downarrow \quad \swarrow$$

slow decay

faster decay

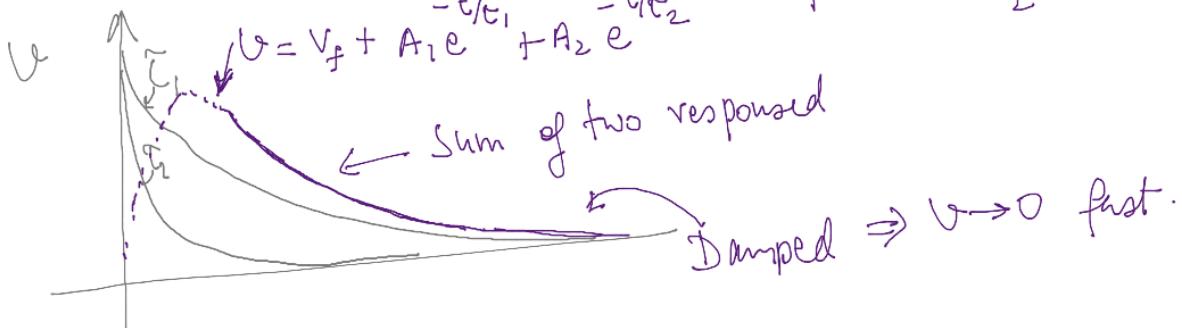

$\alpha = \omega_0$: Critically damped

$$LC = 4R^2C^2 \Rightarrow$$


$$L = 4R^2C$$

↑↑

$$s_1 = s_2 = -\alpha$$

\therefore characteristic equation

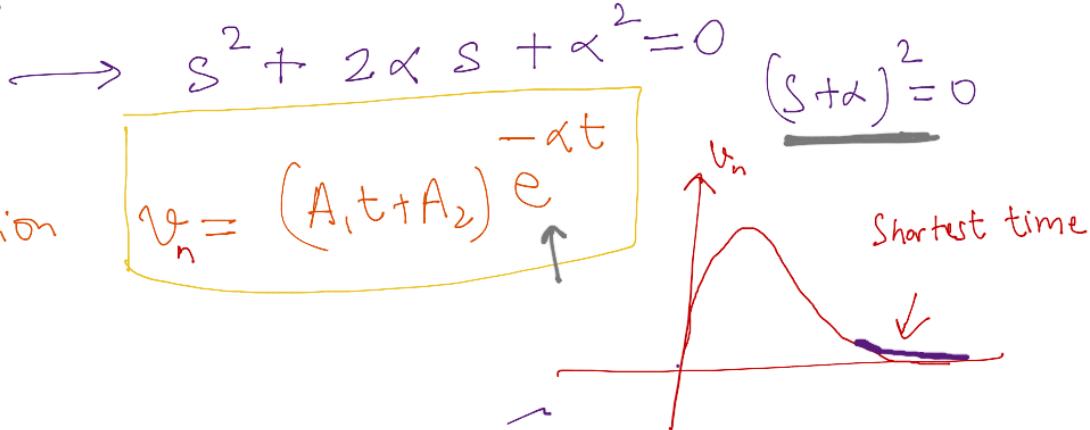Differential Equation solution
(General Solution)



$$\alpha < \omega_0$$

Underdamped Response

$$\frac{1}{2^2 R C^2} < \frac{1}{L C} \Rightarrow L C < 4 R^2 C^2 \text{ or } L < 4 R^2 C$$

$$S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

Complex

$$\begin{aligned} &= -\alpha + j \sqrt{\omega_0^2 - \alpha^2} \\ &= -\alpha + j \omega_d \end{aligned}$$

$$S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

Complex

Imaginary

$$\begin{aligned} S_2 &= -\alpha - j \sqrt{\omega_0^2 - \alpha^2} \\ &= -\alpha - j \omega_d \end{aligned}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$


Natural Response :-

$$V_n = A_1 e^{-\alpha t} e^{j\omega_d t} + A_2 e^{-\alpha t} e^{-j\omega_d t}$$

Sinusoid

Sinusoid

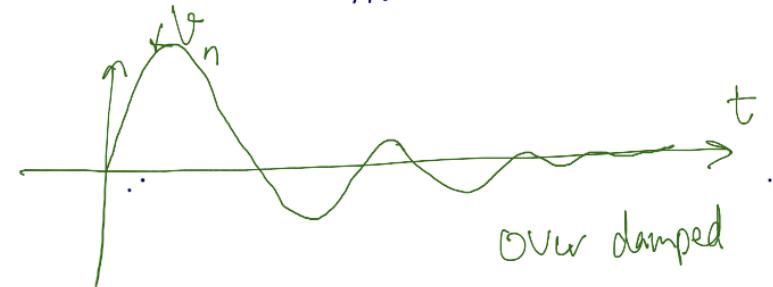
$$\left. \begin{aligned} e^{j\omega_d t} &= \cos \omega_d t + j \sin \omega_d t \\ \bar{e}^{j\omega_d t} &= \cos \omega_d t - j \sin \omega_d t \end{aligned} \right\}$$



$$V_n = e^{-\alpha t} (\underbrace{B_1 \cos \omega_d t}_{\text{---}} + \underbrace{B_2 \sin \omega_d t}_{\text{---}})$$

over damped


Over damped Case

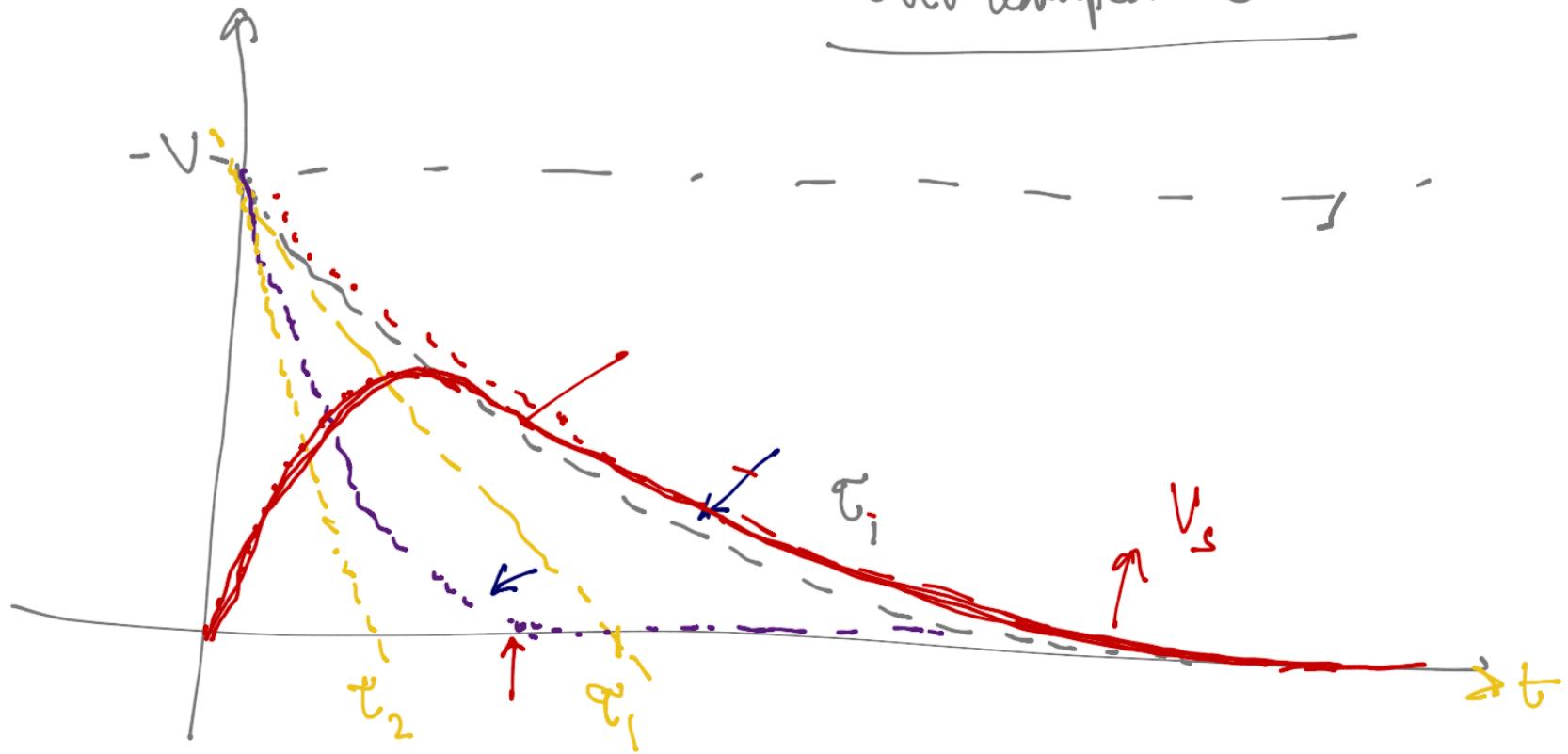

$$V_s = V_f + A_1 e^{-\frac{t}{\tau_1}} + A_2 e^{-\frac{t}{\tau_2}}$$

Critically Damped Case
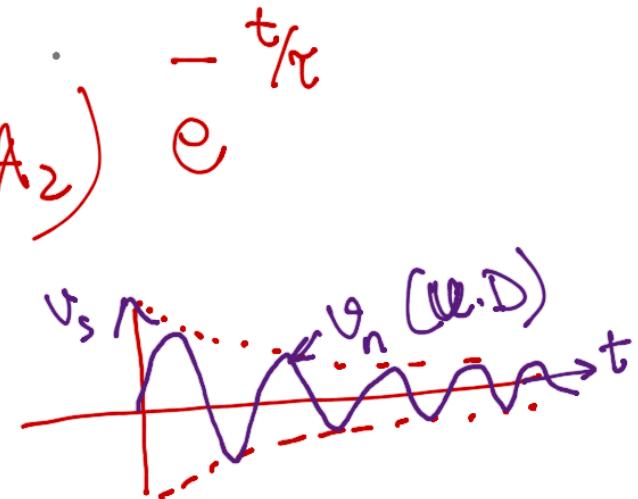
$$v_s = v_f + (A_1 t + A_2) e^{-t/\tau}$$




Under damped case

Natural solution

$$v_s = A_1 e^{-(\alpha+j\omega_n)t} + A_2 e^{-(\alpha-j\omega_n)t}$$

$$\begin{aligned}
 v_s &= A_1 e^{-\alpha t} \underbrace{e^{-j\omega_n t}}_{e^{+j\omega_n t}} + A_2 e^{-\alpha t} \underbrace{e^{+j\omega_n t}}_{e^{-j\omega_n t}} \\
 &= A_1 e^{-\alpha t} (\cos \omega_n t - j \sin \omega_n t) + A_2 e^{-\alpha t} (\cos \omega_n t + j \sin \omega_n t) \\
 &= e^{-\alpha t} \left[(A_1 + A_2) \cos \omega_n t + (-A_1 j + A_2 j) \sin \omega_n t \right] \\
 \boxed{v_s = e^{-\alpha t} (B_1 \cos \omega_n t + B_2 \sin \omega_n t)}
 \end{aligned}$$

Driven (with Source) R-C-L series

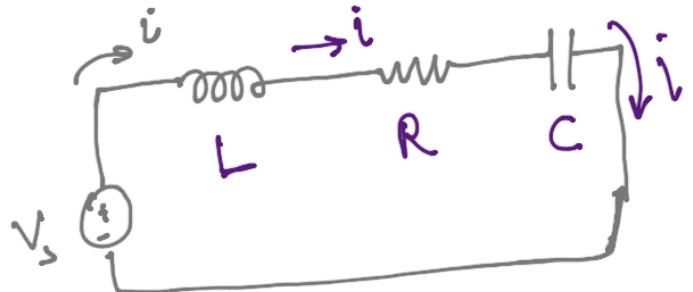

KVL

$$\Rightarrow V_s + V_R + V_C + V_L = 0$$

$$V_s + iR + \frac{1}{C} \int i dt + L \frac{di}{dt} = 0$$

Fring Natural ckt.

Fring Natural ckt.

$$\text{Taking derivative } R \frac{di}{dt} + \frac{1}{C} i + L \frac{d^2i}{dt^2} = 0 \rightarrow \text{2nd order D.E}$$

$$\text{General solution: } i = A e^{st}$$

$$\therefore \Rightarrow R s + \frac{1}{C} + L s^2 = 0 \Rightarrow \boxed{s^2 + \frac{R}{L} s + \frac{1}{LC} = 0}$$

$$\Rightarrow s_1, s_2 = \frac{-R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} : \text{solutions.}$$

$$\begin{cases} ax^2 + bx + c = 0 \\ x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} \end{cases}$$

$$\text{Natural Response: } \Rightarrow i_n = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$i_f \rightarrow$ forced response

$$i = i_f + i_n = \boxed{i_f + A_1 e^{s_1 t} + A_2 e^{s_2 t} = i}$$

Solve A_1 & A_2 using $\underline{i(t=0)}$ and $\underline{\frac{di(t=0)}{dt}}$.

Char. eqⁿ $s^2 + 2\alpha s + \omega_0^2 = 0$

where $\alpha = \frac{R}{2L}$, $\omega_0^2 = \frac{1}{LC}$

Damping coefficient


Resonant frequency.

Over damping

$$\alpha > \omega_0$$

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$i_n = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

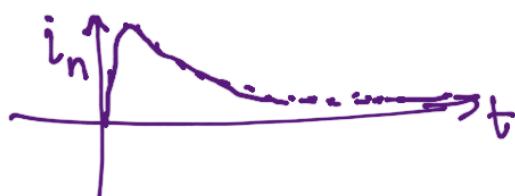


Critically Damped

$$\alpha = \omega_0$$

$$s_1 = s_2 = -\alpha$$

$$i_n = e^{-\alpha t} (A_1 t + A_2)$$

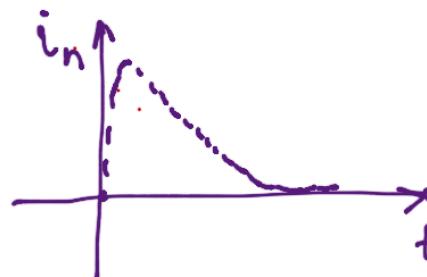


Under damped

$$\alpha < \omega_0$$

$$s_1 = s_2 = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2}$$


$$i_n = e^{-\alpha t} (B_1 \cos \omega_2 t + B_2 \sin \omega_2 t)$$

$$\omega_2 = \sqrt{\omega_0^2 - \alpha^2}$$

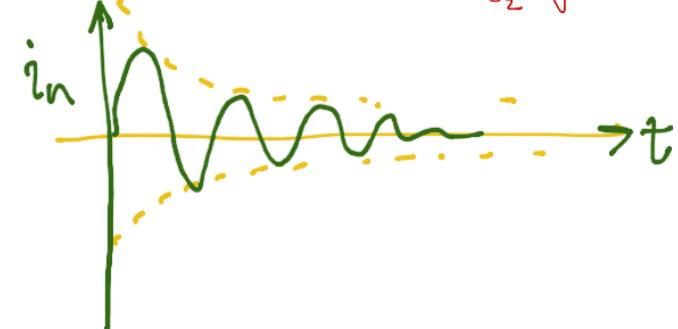

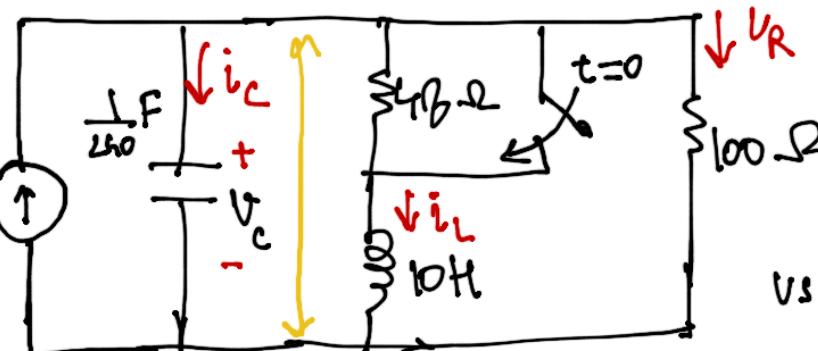
Example 9.G

$$\begin{cases} 3A & t < 0 \\ 0 & t > 0 \end{cases}$$



$$i_L(t) = ?$$

finding i_L
using

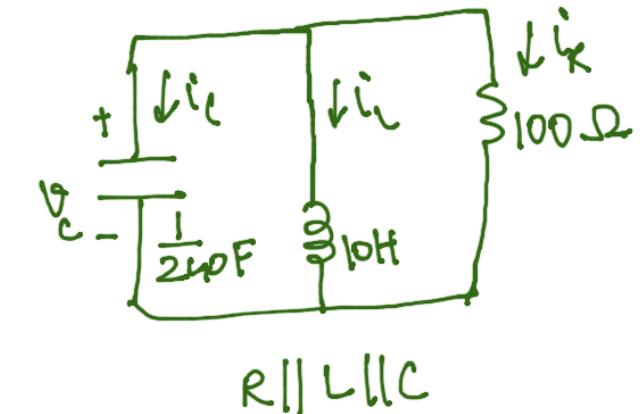

Step Response, i) Nat. Resp.

$$L = 10 \quad C = \frac{1}{240} \quad R = 100$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 100 \times \frac{1}{240}} = \frac{1.2}{}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10 \times \frac{1}{240}}} = \sqrt{24} \approx 4.9$$

$\omega_0 > \alpha$
Under damped

$$i_L = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \approx \sqrt{24 - 1.2^2} \approx 4.8$$

$\rightarrow B_1, B_2 = ?$

$$i_L(t=0) \quad ; \quad \frac{di_L}{dt}(t=0)$$


Step 2 Finding initial conditions

$$i_L(t=0) = \frac{100}{14B} + 3A = 2.027A$$

$$V_C(t=0^-) = 3 * \frac{4800}{14B} = 97.3V$$

\downarrow
 $V(0^+)$
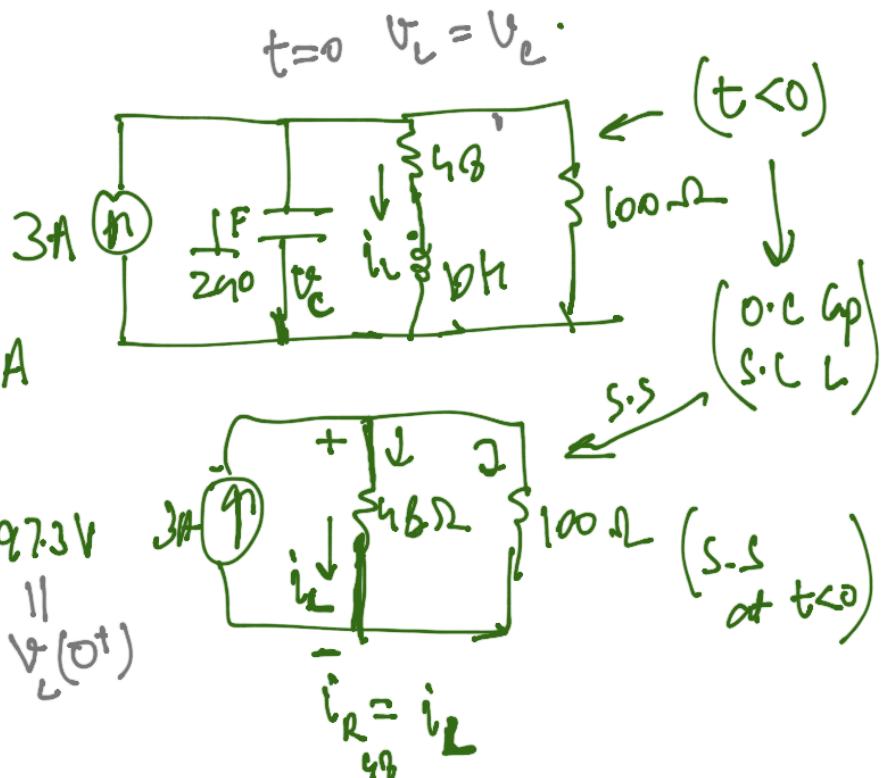
$$\left\{ \begin{array}{l} i_L(0^-) = i_L(0^+) \\ v_C(0^-) = v_C(0^+) \end{array} \right.$$



$$i_L(t=0) \xrightarrow{\frac{d i_L}{dt}} V_L(t=0)$$

$$i_C = e^{-\omega t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$\frac{d\psi}{dt} = (-\omega) e^{-\alpha t} \left(A \cos(\omega t) + B \sin(\omega t) \right)$$

$$L \frac{dt}{di} = V_L = V_C(t=0^+) = 97.3 = -L(B_1 + 0) + L(-0 + B_2 w t) \quad \text{---} \text{D}$$

$$i_L = e^{-\alpha t} \left(B_1 \cos \omega_d t + B_2 \sin \omega_d t \right)$$

$$i_L(0^-) = i_L(0^+) = B_1 \quad \text{--- (2)}$$

Solve ① & ②

$$i_L = e^{-1.2t} \left(2.027 \cos 4.7t + 2.56 \sin 4.75t \right)$$

