
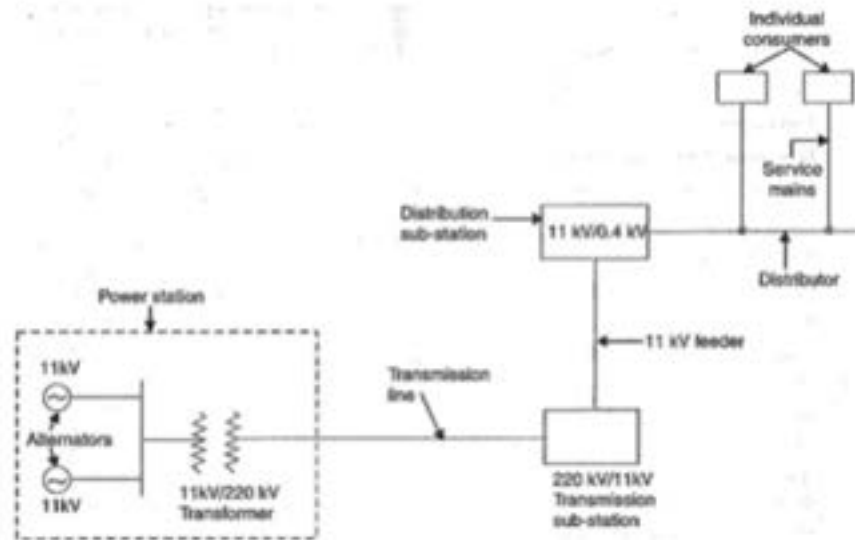



# Electrical Substation

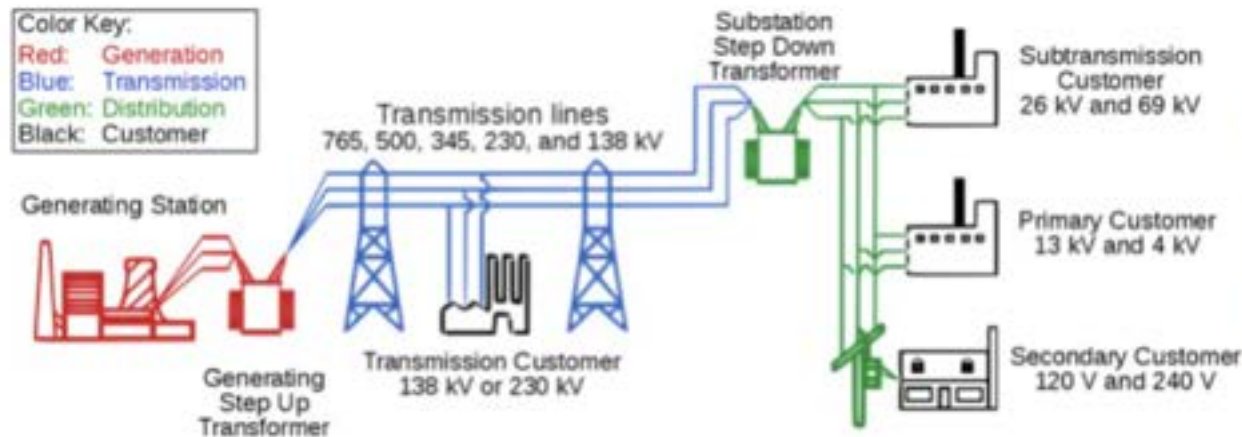

<https://www.youtube.com/watch?v=l53NrBvlorQ>




# Lect 1: Chapter 2

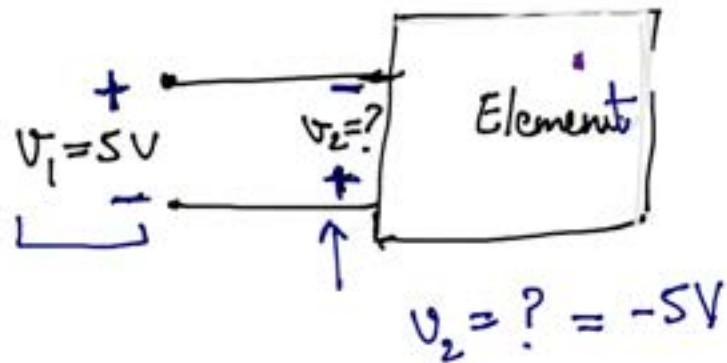

$$1V = 1J/C$$

$$1J = 1V * 1C$$

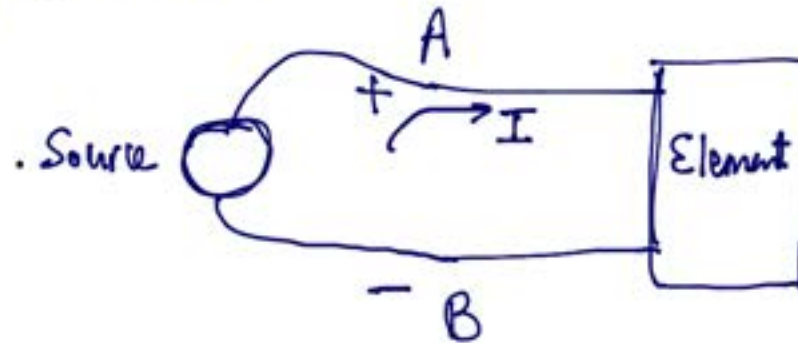

Power

Rate of work done




$$1J \quad 1C \quad \xrightarrow{1sec} : 1Watts$$

$$Power = \frac{1V * 1C}{1sec} = 1V * \left( \frac{1C}{1sec} \right) = 1V * 1A$$

$$P = V * I$$

$$p(t) = v(t) i(t)$$

$$p = vi$$

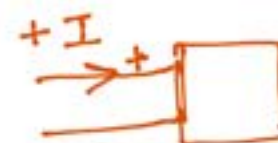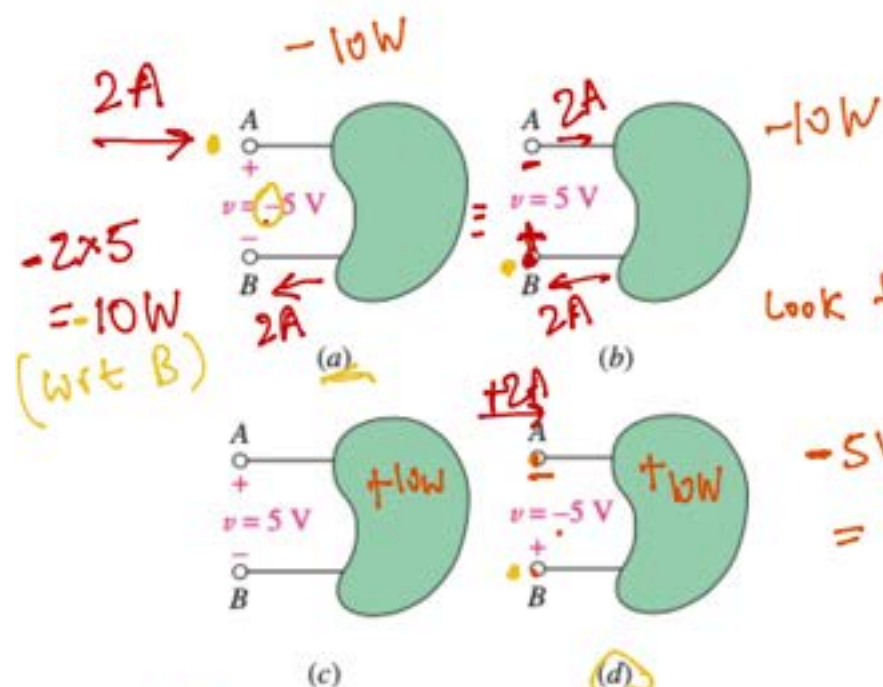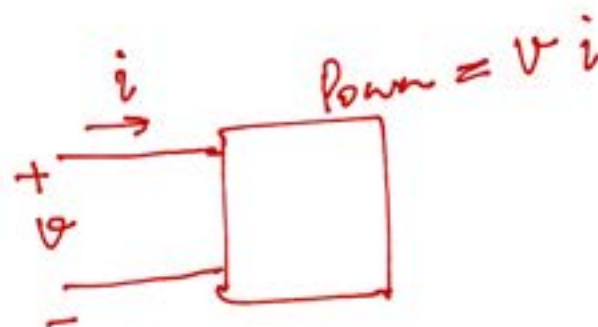

...

**FIGURE 2.9** (a, b) Terminal B is 5 V positive with respect to terminal A; (c, d) terminal A is 5 V positive with respect to terminal B.



Compute the power absorbed by each part in Fig. 2.13.


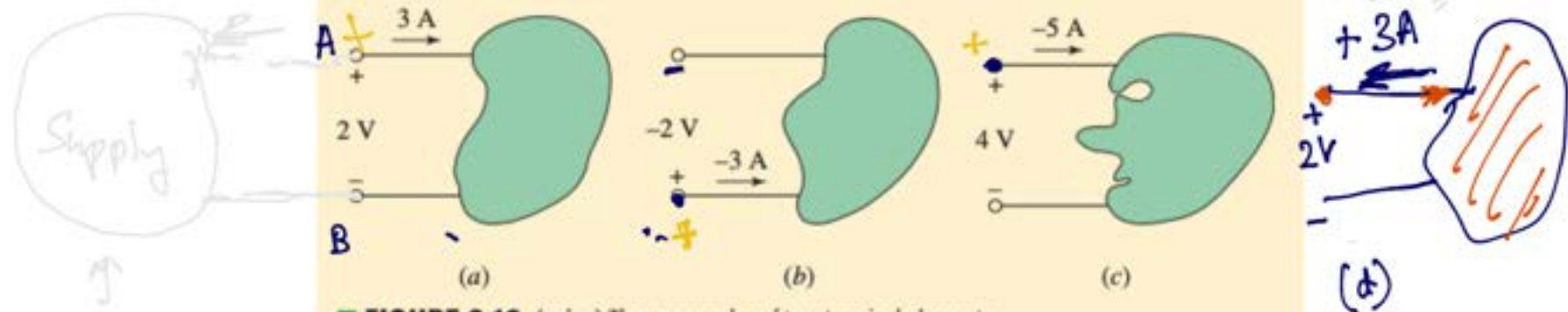


FIGURE 2.13 (a, b, c) Three examples of two-terminal elements.

(a) Power =  $V \times I = 2V \times 3A = +6W \Rightarrow$  Absorbed  
(wrk '+')

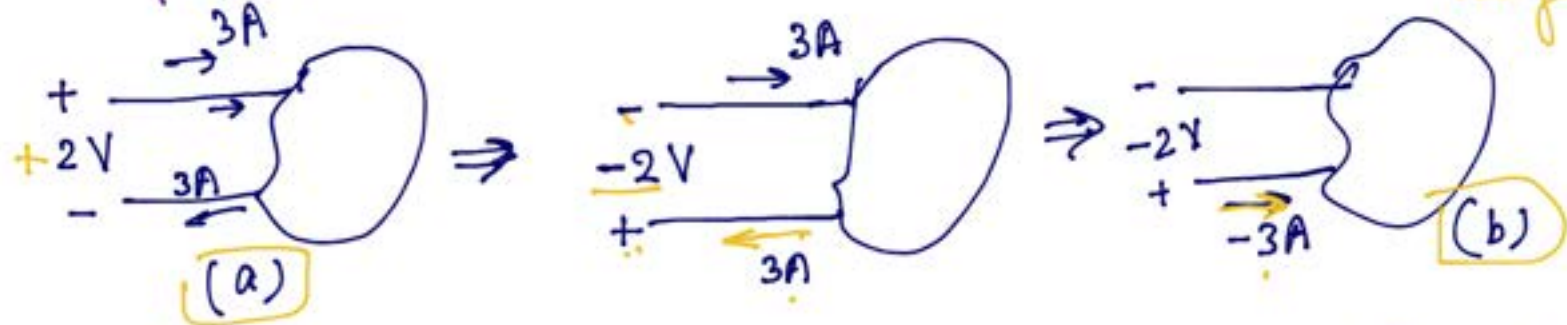
(b) Power =  $V \times I = -2V \times -3A = +6W$  Absorbed  
(wrk '+')



(c) Power =  $V \times I = 4V \times (-5A) = -20W$   
 $\hookrightarrow$  Supply



(d) Power =  $V \times I = 2V \times (-3A) = -6W$   
Source  
Generated

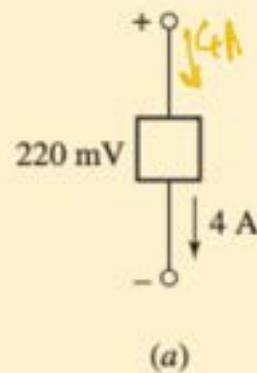2.6 Determine the power being absorbed by the circuit element in Fig. 2.14a.



$$P = (1.75 \text{ A}) * (-3.8 \text{ V}) = -6.65 \text{ W} \rightarrow \text{absorbed}$$

$$\text{Generated} = +6.65 \text{ W}$$

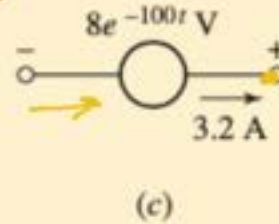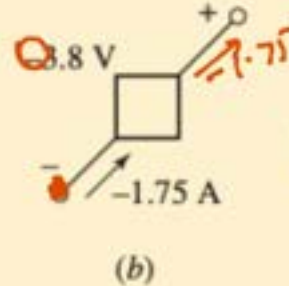

$$-3.2 * 8e^{-100t} = -3.2 * 8e^{-100t}$$


FIGURE 2.14

2.7 Determine the power being generated by the circuit element in Fig. 2.14b.

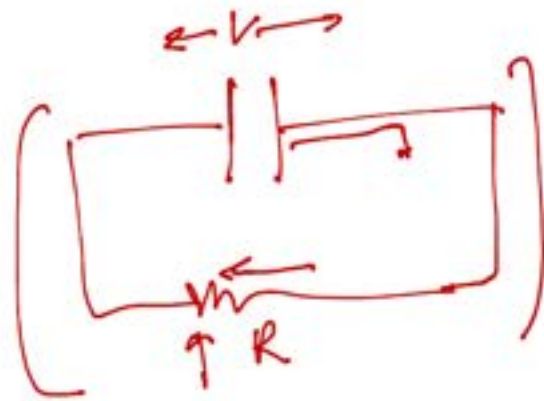
2.8 Determine the power being delivered to the circuit element in Fig. 2.14c at  $t = 5 \text{ ms}$ .

Sources  $\rightarrow$   $\left\{ \begin{array}{l} \text{Independent} \rightarrow \left\{ \begin{array}{l} \text{Voltage} \\ \text{Current} \end{array} \right. \\ \text{Dependent} \rightarrow \left\{ \begin{array}{l} \text{Voltage} \\ \text{Current} \end{array} \right. \end{array} \right.$

Circuit Element  $\rightarrow ?$   $\left\{ \begin{array}{l} 2 \text{ terminals} \\ \text{Mathematical model} \\ V-I \text{ relationship} \end{array} \right.$



Symbols for Independent Source

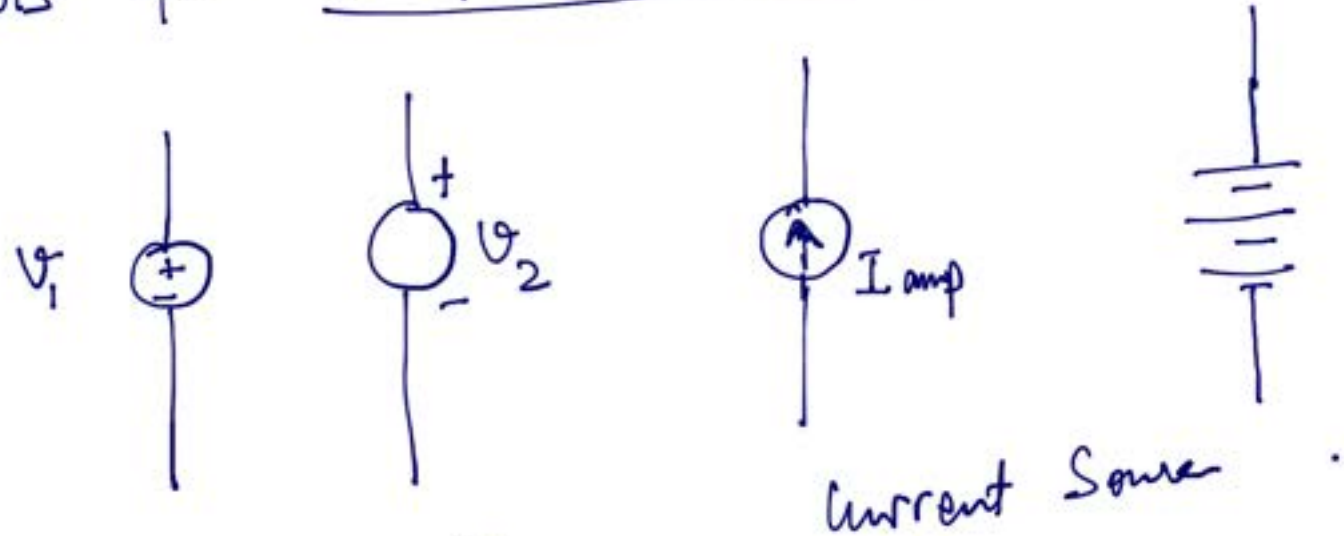


Voltage sources

Voltage Source : D.C source (constant); A.C (sinusoidal)



Dependent →

VCVS

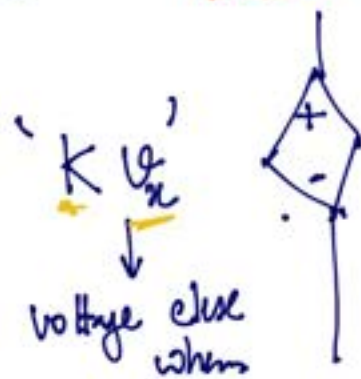

Volt. dependent  
voltage source

CCVS



Current Dep. Volt. source

VCCS




Volt. dependent current  
source

CCCS



Current Dep. current. source



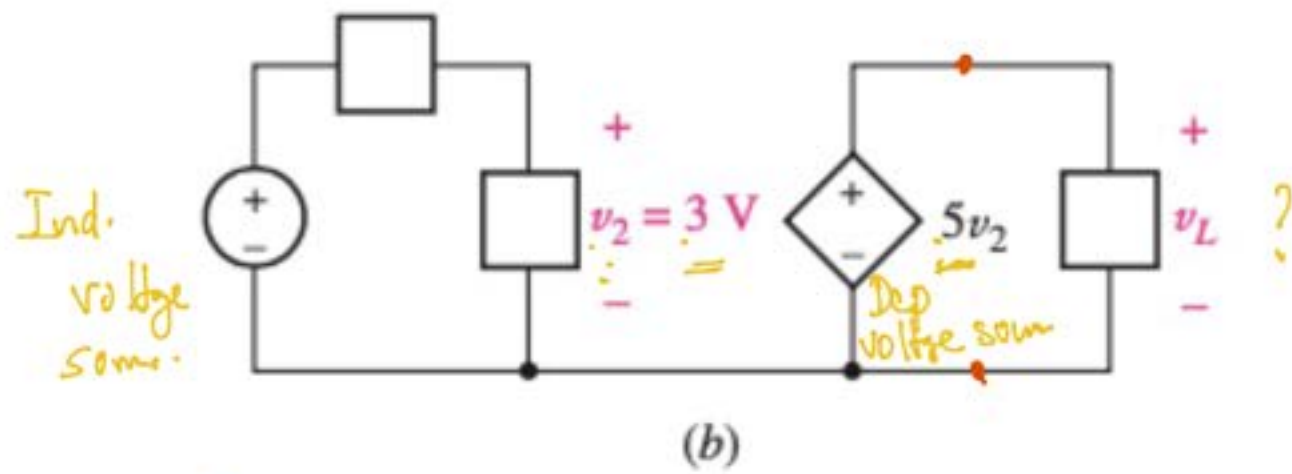

**FIGURE 2.19** (a) An example circuit containing a voltage-controlled voltage source. (b) The additional information provided is included on the diagram.

$$\begin{aligned}
 \text{Volt. dep. volt. source (VCVS)} &= 5v_2 \\
 \downarrow \text{controlled} &= 5 * 3\text{ V} \\
 &= \underline{15\text{ V}}
 \end{aligned}$$

$$v_L = \text{voltage supplied by VCVS}$$

$$v_L = 15\text{ V}$$



## PRACTICE

2.9 Find the power absorbed by each element in the circuit in Fig. 2.20.

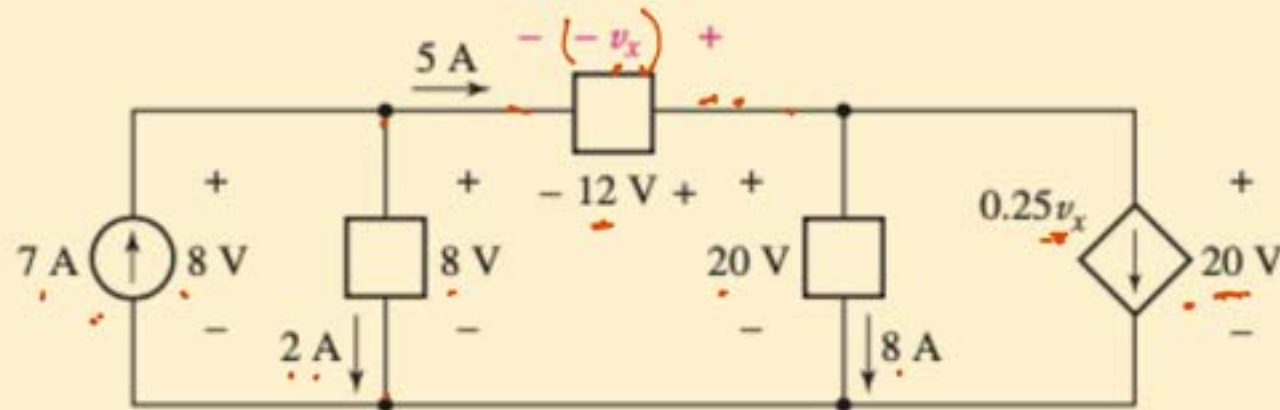



FIGURE 2.20

Ohm Law

$$V \propto I$$

$$V = R \cdot I$$

Resistance. ( $\Omega$  ohms)

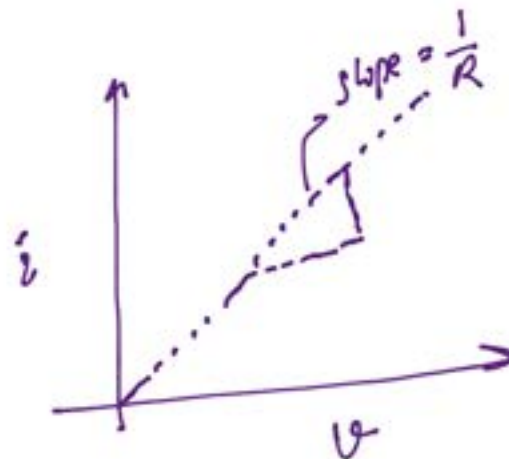

## Ohm's Law

$$V = I R \quad \text{Resistor}$$

## Power Absorption

$$\begin{aligned} P &= V i \\ &= \frac{V^2}{R} = V^2 G \quad \text{conductance} \\ &= \underline{i^2 R} \end{aligned}$$

$R \rightarrow \text{Resistor (ohm } \Omega = \frac{V}{A})$

## Conductance

$$G = \frac{1}{R} = \frac{i}{V}$$

Unit: Siemens,  $\frac{A}{V}$ ,  $\frac{\Omega}{\Omega}$  (mho)  
(S)  $\downarrow$   $\sigma$

# CHAPTER 3

## (lecture 2)

### CHAPTER 3

---

#### VOLTAGE AND CURRENT LAWS 39

- 3.1** Nodes, Paths, Loops, and Branches 39
  - 3.2** Kirchhoff's Current Law 40
  - 3.3** Kirchhoff's Voltage Law 42
  - 3.4** The Single-Loop Circuit 46
  - 3.5** The Single-Node-Pair Circuit 49
  - 3.6** Series and Parallel Connected Sources 51
  - 3.7** Resistors in Series and Parallel 55
  - 3.8** Voltage and Current Division 61
- SUMMARY AND REVIEW 66
- READING FURTHER 67
- EXERCISES 67

$\rightarrow R=0 \Rightarrow G=\infty = \text{Short Circuit}$  

$R=\infty \Rightarrow G=0 \equiv \text{Open Circuit (no connection)}$

## Voltage & Current Laws

Lumped parameter


Distributed parameter

Example: Resistor unit

Example: Transmission line capacitance.





Lumped

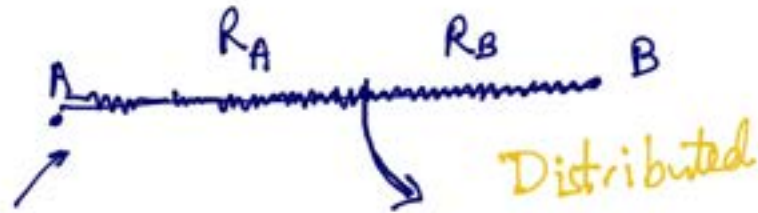




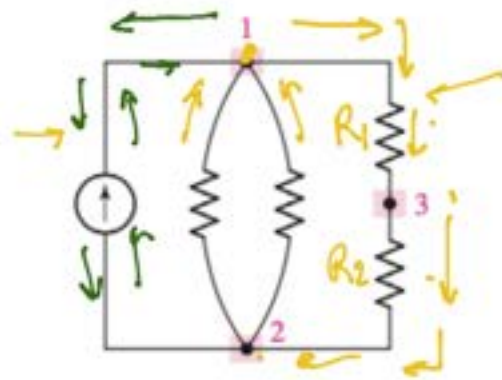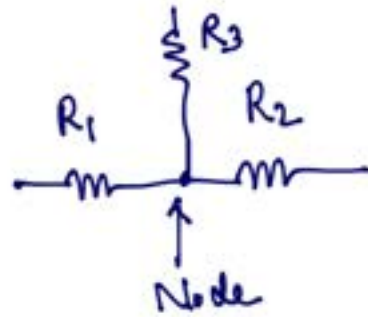NODE : A point at which two or more elements have a common connection.



(a)

Same circuit

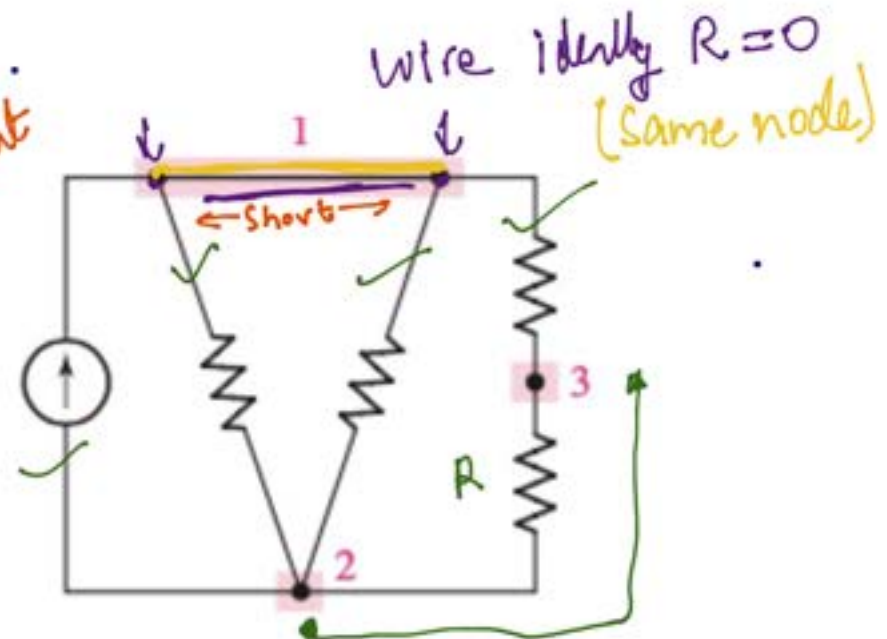

(b)


Path :  $1 \rightarrow R_1 \rightarrow 3 \rightarrow R_2 \rightarrow 2$

Path When moving along in a circuit, set of nodes and elements encountered once form a path.

Loop A path will become a loop if end at same node at which we started.



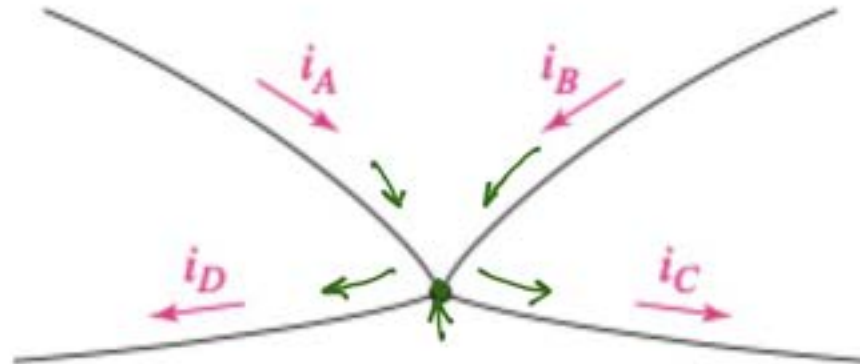Branch : A single path composed of a single element with a node at each end.



■ **FIGURE 3.2** Example node to illustrate the application of Kirchhoff's current law.

$$+ i_A + i_B - i_C - i_D = 0 \quad : KCL$$

## KCL Kirchhoff's Current Law

Algebraic sum of currents entering any node  
is zero.

$$\sum_{n=1}^N i_n = 0$$

for a node  
with N connections

$\Downarrow$

$$i_1 + i_2 + i_3 + \dots + i_N = 0$$




# KVL Kirchoff's Voltage Law

Sum of voltages around any closed path is zero.

$$\sum_{n=1}^N V_n = 0$$


In a closed loop with  $N$  elements (or branches).

$$V_1 + V_2 + V_3 + \dots + V_N = 0$$

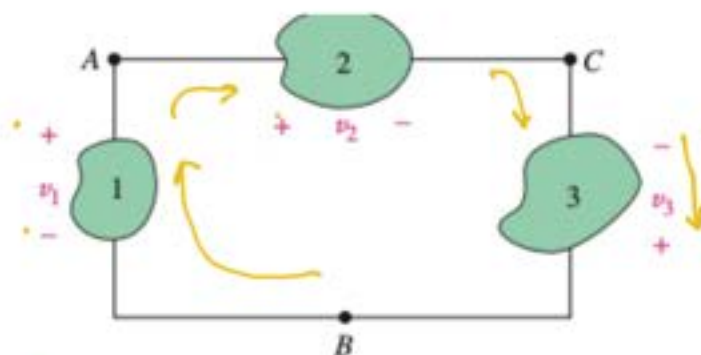

**FIGURE 3.5** The potential difference between points  $A$  and  $B$  is independent of the path selected.

$$+V_1 - V_2 + V_3 = 0$$

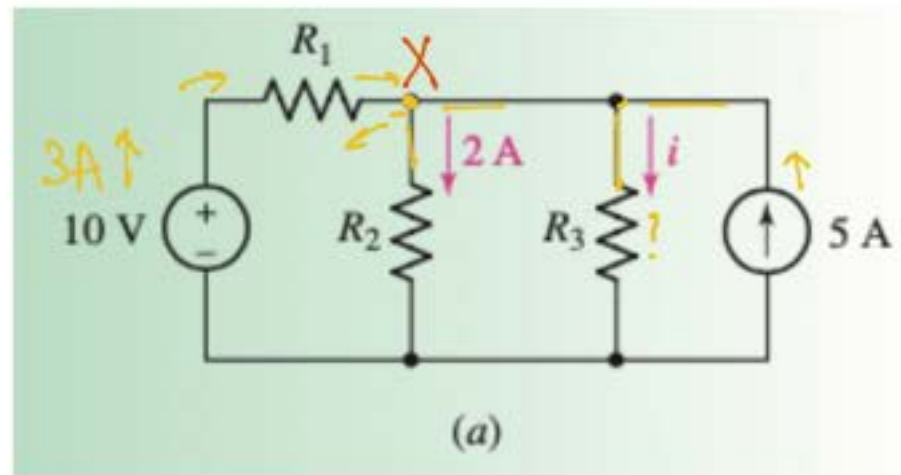


Ex 3.1

Apply KCL at node X:  $3A - 2A - i + 5A = 0$

$$\Rightarrow i = 6A$$

→ only one unknown

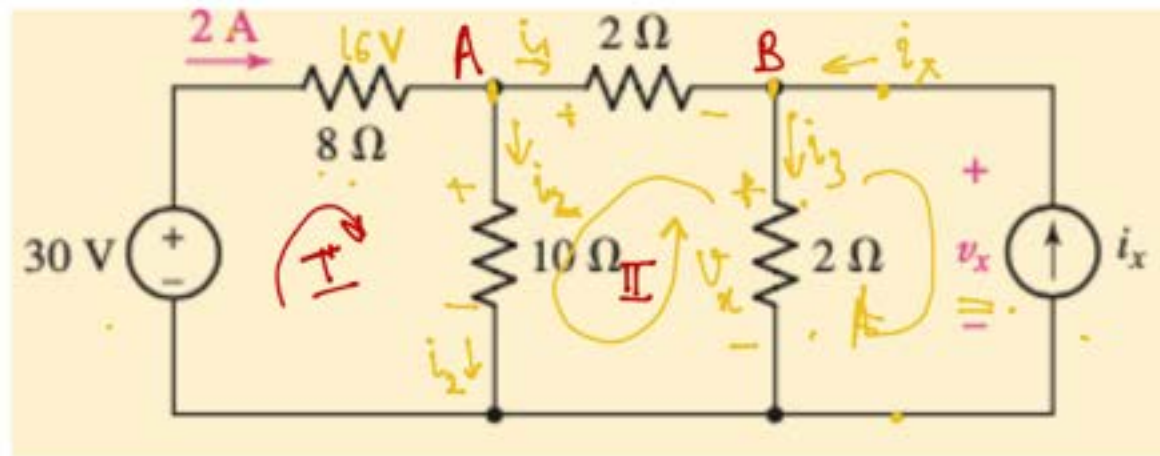

Ex. 3.4

4 unknown  
& 4 equation.

KCL & KVL  
↓  
↓

find the unknown.

$$+30 - 8 \times 2 - 10 \times i_2 = 0 \quad \text{KVL @ I} \quad \text{--- (4)}$$

(KCL @ A)

$$i_1 + i_2 = 2A \quad \text{--- (1)}$$

(KCL @ B)


$$i_x + i_1 + \frac{v_x}{2A} = 0 \quad \text{--- (2)}$$

Unknowns  $i_1, i_2, i_x, i_3$

$$\text{(KVL @ loop II): } -10 i_2 + v_x - 2 i_1 = 0 \quad \text{--- (3)}$$

$$\text{Ohm's Law (on } 2\Omega \text{): } v_x = 2\Omega (i_3) \Rightarrow i_x + i_1 = i_3 \quad \text{--- (4) (rewritten)}$$

## Single loop circuit

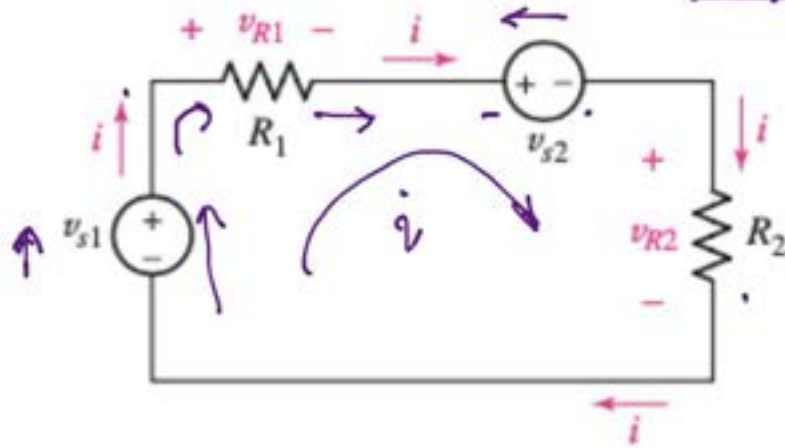

$$v_{R1} = -iR_1$$


$$v_{R2} = iR_2$$

$$+v_{s1} - R_1 i_1 - v_{s2} - i_1 R_2 = 0 \quad \text{KVL}$$

$$i_1 = \frac{(v_{s1} - v_{s2})}{(R_1 + R_2)}$$



3.8 For the single-node-pair circuit of Fig. 3.18, find  $i_A$ ,  $i_B$ , and  $i_C$ .

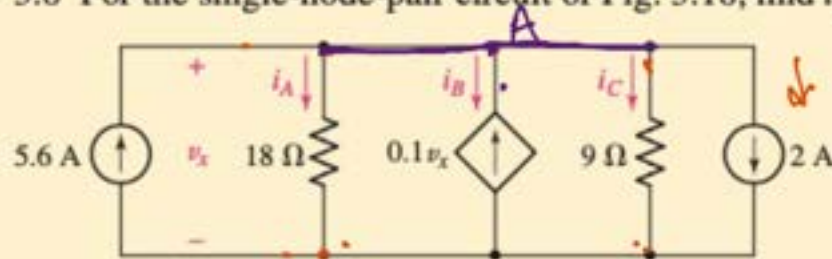

Ex 3.8

$$i_A, i_B, i_C = ?$$

KCL (A)

$$+5.6 \text{ A} - i_A - i_B - i_C - 2 \text{ A} = 0 \quad \text{--- (1) Total current A}$$

Ohm's Law

$$\begin{cases} \therefore i_B = -0.1 v_x & \text{--- (2)} \\ \therefore i_A = \frac{v_x}{18 \Omega} & \text{--- (3)} ; \quad i_C = \frac{v_x}{9 \Omega} & \text{--- (4)} \end{cases}$$

$$5.6 - \frac{v_x}{18} - (0.1)v_x - \frac{v_x}{9} - 2 = 0 \quad \leftarrow$$



## Voltage Source



Series  
voltage sources

$$v_{eq} = v_1 + v_2 - v_3$$

Parallel current Source

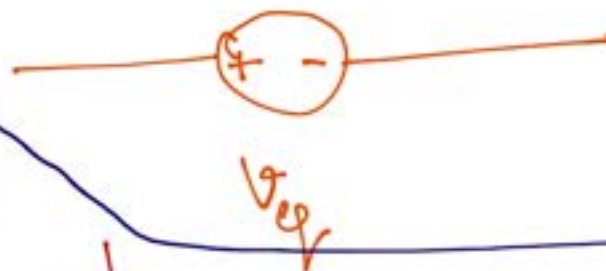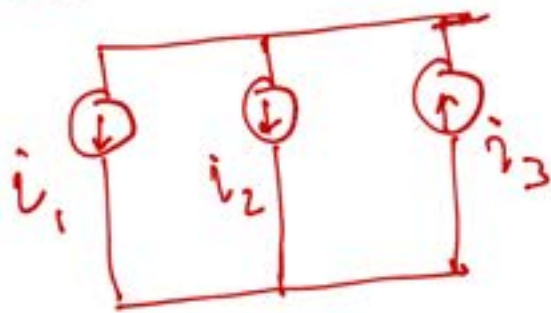


Equivalent Voltage  
Source


$$i_{eq} = i_1 + i_2 - i_3$$



3.9

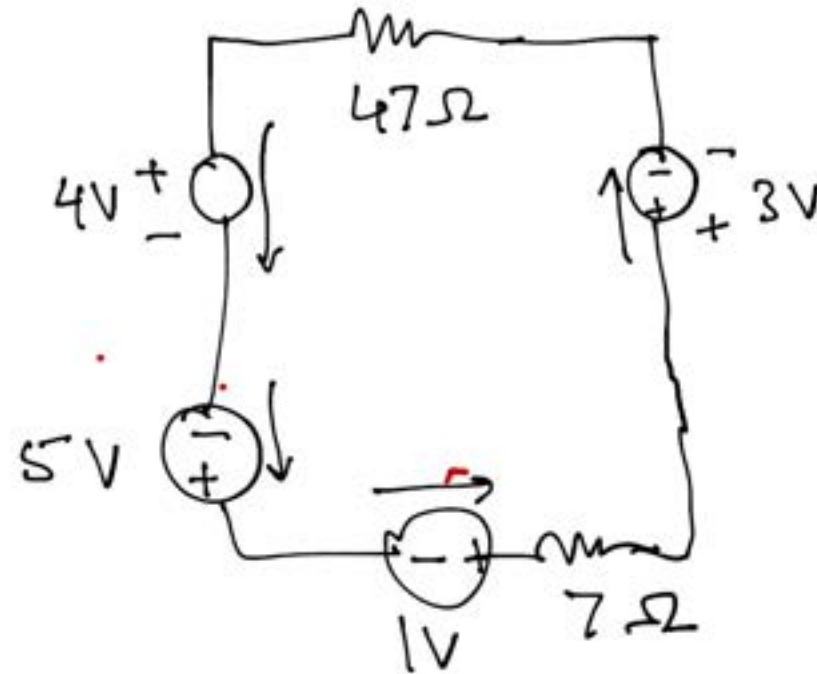

$$V_{eq} = +4 - 5 - 1 + 3 = 1V$$

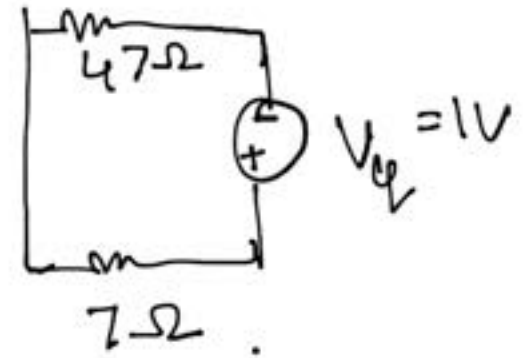


3.10

3.10 Determine the voltage  $v$  in the circuit of Fig. 3.23 after first replacing the three sources with a single equivalent source.



FIGURE 3.23

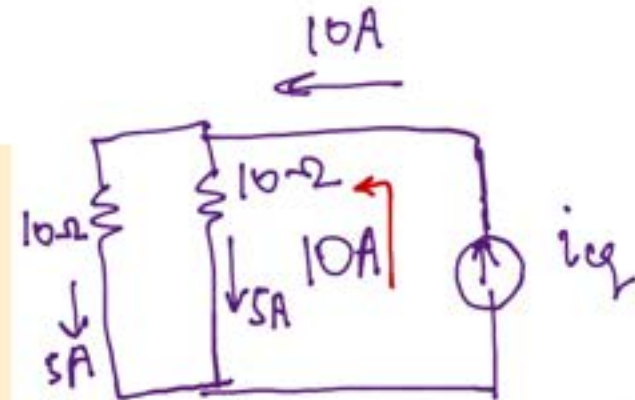

$$v = 5A \times 10\Omega = 50V$$

10A will split equally between two equal resistors ( $10\Omega$  &  $10\Omega$ ) = 5A through each resistor.

i

## Voltage Division in Series Resistance

$$V_1 = i R_1$$

$$V_2 = i R_2$$

$$i = \left\{ \frac{V_1}{R_1} \right\} = \frac{V_2}{R_2} \dots = \left\{ \frac{V_N}{R_N} \right\}$$

⇒ Higher resistance  
will have higher  
voltage drop


$$V_2 = \frac{R_2}{R_1 + R_2 + \dots + R_N} \cdot V$$

Voltage Division  
Based on Resistance

⇓  
Resistor Voltage Divider



## Parallel Resistors

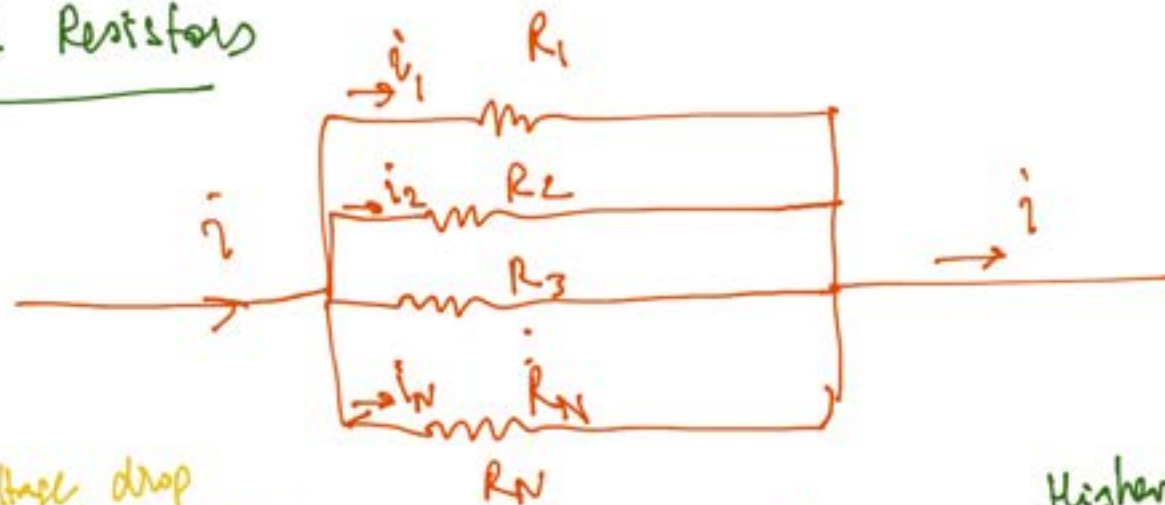


Same voltage drop across all resistances.

Current division in parallel resistances.

Higher resistance will have lower current.
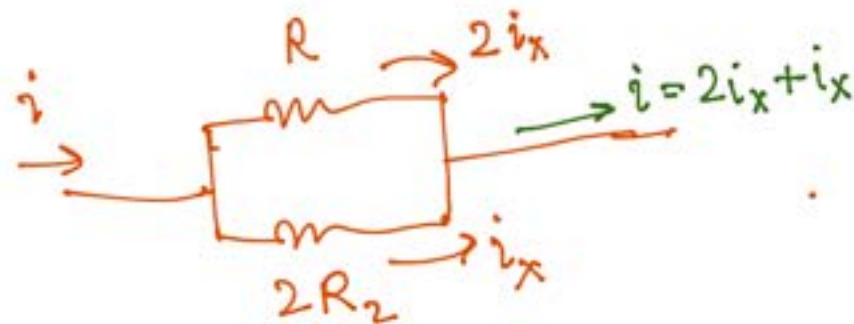
$$V = i_1 \cdot R_1 = i_2 R_2 = \dots = i_N R_N$$



# CHAPTER 4

## CHAPTER 4

---

### BASIC NODAL AND MESH ANALYSIS 79

- 4.1** Nodal Analysis 80
- 4.2** The Supernode 89
- 4.3** Mesh Analysis 92
- 4.4** The Supermesh 98
- 4.5** Nodal vs. Mesh Analysis: A Comparison 101
- 4.6** Computer-Aided Circuit Analysis 103
- SUMMARY AND REVIEW 107
- READING FURTHER 109
- EXERCISES 109

P

4.1 For the circuit of Fig. 4.3, determine the nodal voltages  $v_1$  and  $v_2$ .

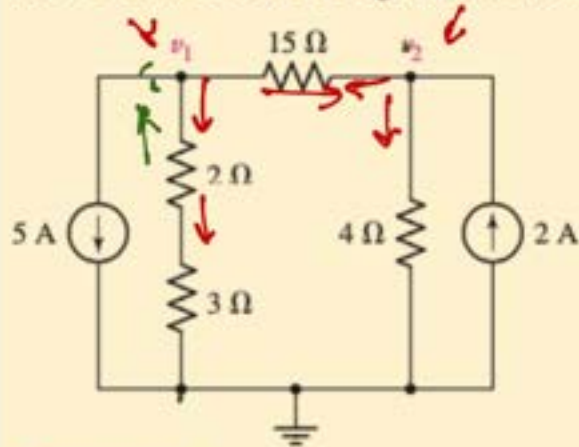


FIGURE 4.3

$$4v_1 - 19v_2 + 120 = 0$$

$v_1 - v_2 =$  current  
flowing  
from higher  
to lower  
node

$$\text{KCL @ } v_1 \quad -5 - \frac{v_1 - 0}{2+3} + \frac{v_1 - v_2}{15} = 0$$


$$\begin{aligned} -5 - \frac{v_1}{5} - \frac{v_1}{15} + \frac{v_2}{15} &= -75 - 3v_1 - v_1 + v_2 = 0 \\ &= -4v_1 + v_2 - 75 = 0 \end{aligned} \quad (1)$$

$$\text{KCL @ } v_2 \quad + \frac{v_1 - v_2}{15} - \frac{v_2}{4} + 2 = 0$$

$$4v_1 - 19v_2 + 120 = 0$$

$$4v_1 - 19v_2 + 120 = 0 \quad (2)$$

Ex 4.1  
(Solved for reference)

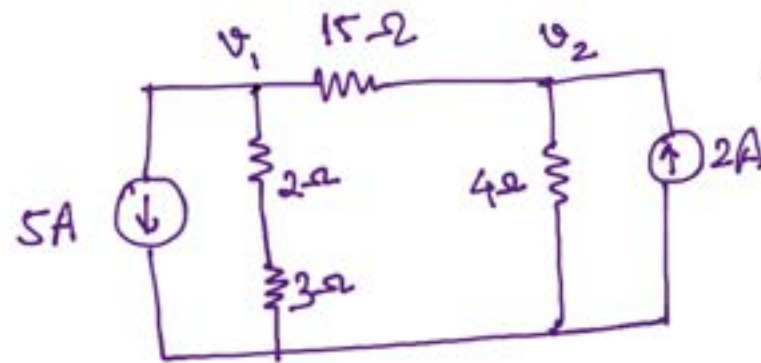

$v_1, v_2 = ?$

Node  $v_1$  KCL:  $-5 - \frac{v_1}{5} - \frac{v_1 - v_2}{15} = 0$

$$\Rightarrow +75 + 3v_1 + v_1 - v_2 = 0$$

$$\Rightarrow 4v_1 - v_2 + 75 = 0 \quad \text{--- (1)}$$

Node  $v_2$  KCL:  $-\frac{v_2 - v_1}{15} + 2 - \frac{v_2}{4} = 0$

$$\Rightarrow -4v_2 + 4v_1 + 120 - 15v_2 = 0$$

$$\Rightarrow 4v_1 - 19v_2 + 120 = 0 \quad \text{--- (2)}$$

$$\textcircled{1} - \textcircled{2} \Rightarrow 18v_2 = 45 \Rightarrow v_2 = \frac{5}{2} \text{ V}$$

$$\textcircled{1} \Rightarrow v_1 = \frac{1}{4} \left( -75 + \frac{5}{2} \right) = \frac{1}{4} \left( \frac{-145}{2} \right) = -\frac{145}{8} \text{ V}$$



P 4.2

# PRACTICE

4.2 For the circuit of Fig. 4.5, compute the voltage across each current source.

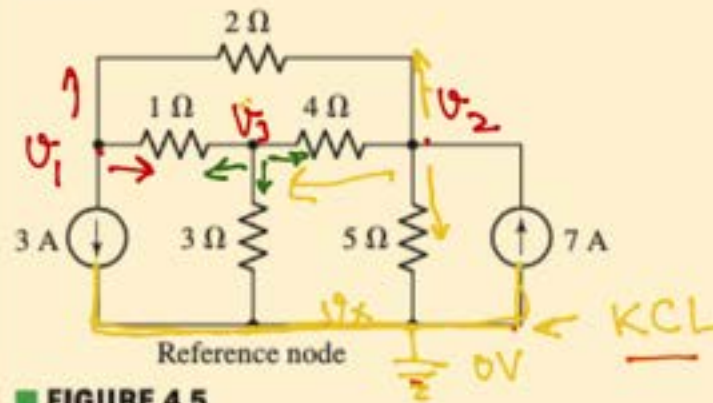


FIGURE 4.5

KCL @  $v_1$  :  $\frac{v_1 - v_2}{2} + \frac{v_1 - v_3}{1} + 3 = 0 \Rightarrow v_1 - v_2 + 2v_1 - 2v_3 + 6 = 0$   
 $\Rightarrow 3v_1 - v_2 - 2v_3 + 6 = 0$  — (1)  
*Handwritten notes:*  $v_1 = A$  with  $v_1 - v_3 = A$

KCL @  $v_2$  :  $\frac{v_2 - v_1}{2} + \frac{v_2 - v_3}{4} + \frac{v_2}{5} - 7 = 0$   
 $\Rightarrow -10v_2 + 10v_1 - 5v_2 + 5v_3 - 4v_2 + 140 = 0$   
 $\Rightarrow 10v_1 - 19v_2 + 5v_3 + 7 = 0$  — (2)

KCL @  $v_3$  :  $\frac{v_3 - v_1}{1} + \frac{v_3}{3} + \left( \frac{v_3 - v_2}{4} \right) = 0$  — (3)



Determine the node-to-reference voltages in the circuit of Fig. 4.11.

After establishing a supernode about each voltage source, we see that we need to write KCL equations only at node 2 and at the supernode containing the dependent voltage source. By inspection, it is clear that  $v_1 = -12$  V.

At node 2,

$$\frac{v_2 - v_1}{0.5} + \frac{v_2 - v_3}{2} = 14 \quad [20]$$

while at the 3-4 supernode,

$$0.5v_x = \left( \frac{v_3 - v_2}{2} + \frac{v_4}{1} + \frac{v_4 - v_1}{2.5} \right) \quad [21]$$

We next relate the source voltages to the node voltages:

$$v_3 - v_4 = 0.2v_y \quad [22]$$

and

$$0.2v_y = 0.2(v_4 - v_1) \quad [23]$$

Finally, we express the dependent current source in terms of the assigned variables:

$$0.5v_x = 0.5(v_2 - v_1) \quad [24]$$

Five nodes requires four KCL equations in general nodal analysis, but we have reduced this requirement to *only two*, as we formed two separate supernodes. Each supernode required a KVL equation (Eq. [22] and  $v_1 = -12$ , the latter written by inspection). Neither dependent source was controlled by a nodal voltage, so two additional equations were needed as a result.

With this done, we can now eliminate  $v_x$  and  $v_y$  to obtain a set of four equations in the four node voltages:

$$\left. \begin{aligned} -2v_1 + 2.5v_2 - 0.5v_3 &= 14 \\ 0.1v_1 - v_2 + 0.5v_3 + 1.4v_4 &= 0 \\ v_1 &= -12 \\ 0.2v_1 + v_3 - 1.2v_4 &= 0 \end{aligned} \right\}$$

Solving,  $v_1 = -12$  V,  $v_2 = -4$  V,  $v_3 = 0$  V, and  $v_4 = -2$  V.

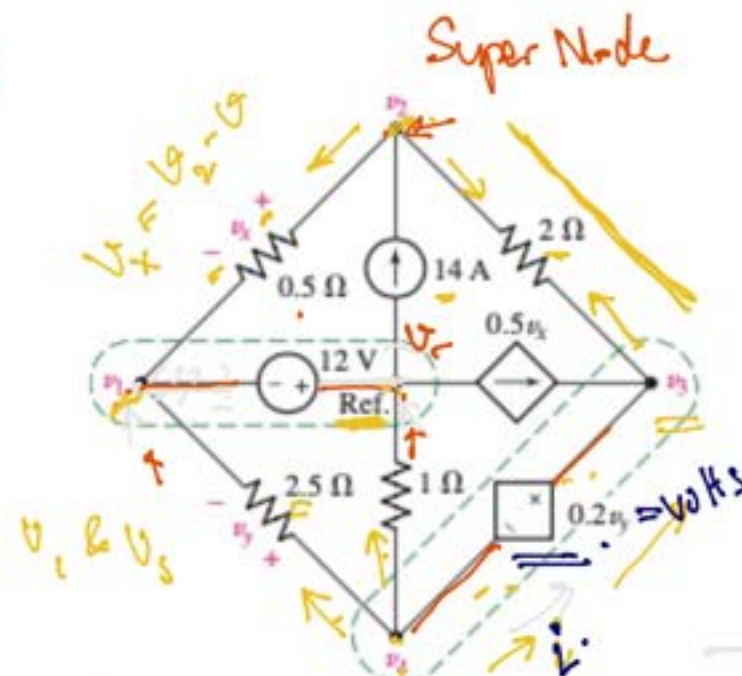


FIGURE 4.11 A five-node circuit with four different types of sources.

$$\left. \begin{aligned} v_4 \\ v_3 \end{aligned} \right\} \begin{aligned} \frac{v_4 - v_1}{2.5} + \frac{v_4}{1} + i &= 0 \\ -\frac{v_3 - v_2}{2} + 0.5v_x + i &= 0 \end{aligned}$$

$$\begin{aligned} v_4 - v_3 &\Rightarrow \text{Super node} \\ \rightarrow \frac{v_4 - v_1}{2.5} + \frac{v_4}{1} + \frac{v_3 - v_2}{2} - 0.5v_x &= 0 \end{aligned}$$

## Summary of Supernode Analysis Procedure

1. **Count the number of nodes ( $N$ ).**
2. **Designate a reference node.** The number of terms in your nodal equations can be minimized by selecting the node with the greatest number of branches connected to it.
3. **Label the nodal voltages** (there are  $N - 1$  of them).
4. **If the circuit contains voltage sources, form a supernode about each one.** This is done by enclosing the source, its two terminals, and any other elements connected between the two terminals within a broken-line enclosure.
5. **Write a KCL equation for each nonreference node and for each supernode *that does not contain the reference node*.** Sum the currents flowing *into* a node/supernode from current sources on one side of the equation. On the other side, sum the currents flowing *out* of the node/supernode through resistors. Pay close attention to “-” signs.
6. **Relate the voltage across each voltage source to nodal voltages.** This is accomplished by simple application of KVL; one such equation is needed for each supernode defined.
7. **Express any additional unknowns (i.e., currents or voltages other than nodal voltages) in terms of appropriate nodal voltages.** This situation can occur if dependent sources appear in our circuit.
8. **Organize the equations.** Group terms according to nodal voltages.
9. **Solve the system of equations for the nodal voltages** (there will be  $N - 1$  of them).

$N$  KCL

$(N-1)$  No  $v_n$   
= ref. node


KCL  $(N-1)$   
Super  $\underbrace{A \& B}$   
↓  
Voltage Source  
 $V_A - V_B = V_{\text{source}}$



KVL

Planar circuit →


Mesh → no loop inside it.

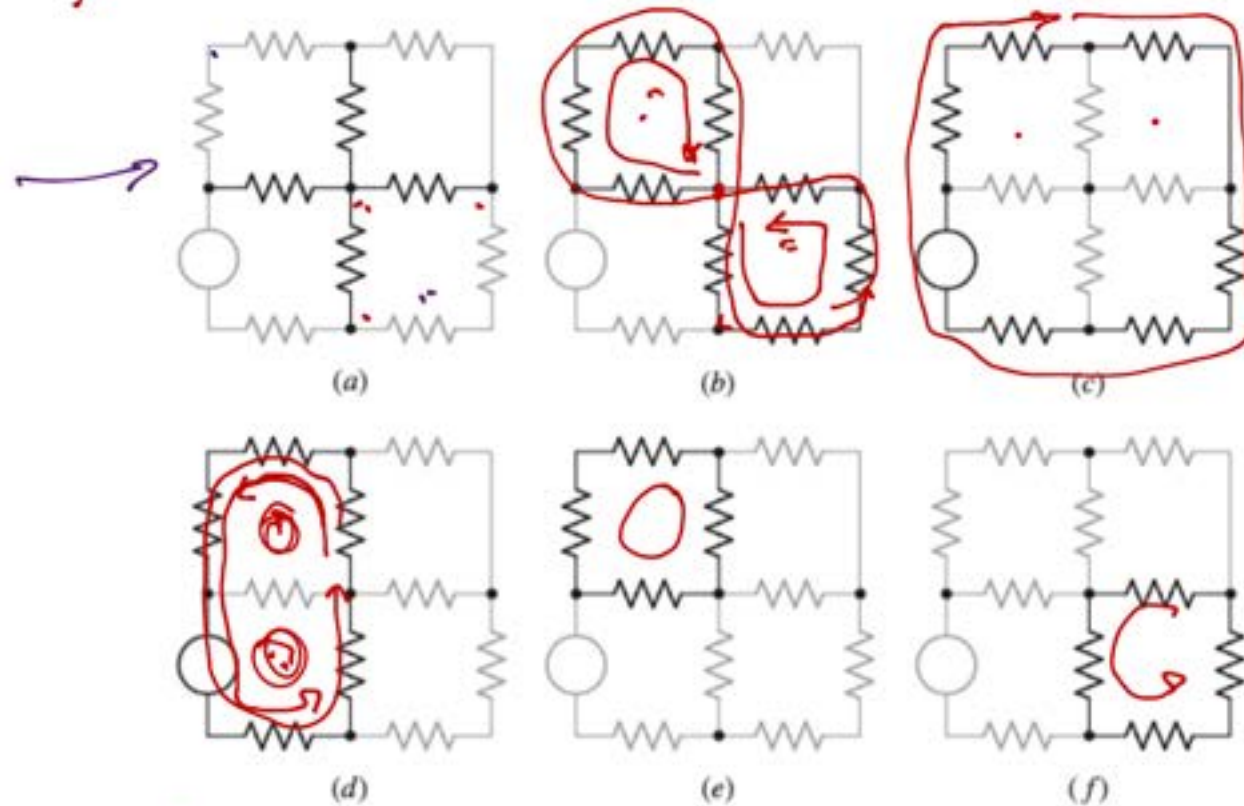


**FIGURE 4.14** (a) The set of branches identified by the heavy lines is neither a path nor a loop. (b) The set of branches here is not a path, since it can be traversed only by passing through the central node twice. (c) This path is a loop but not a mesh, since it encloses other loops. (d) This path is also a loop but not a mesh. (e, f) Each of these paths is both a loop and a mesh.

# **PRACTICE**

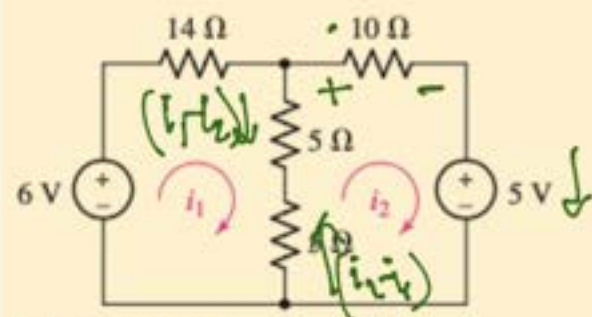4.6 Determine  $i_1$  and  $i_2$  in the circuit in Fig. 4.18.



■ FIGURE 4.18

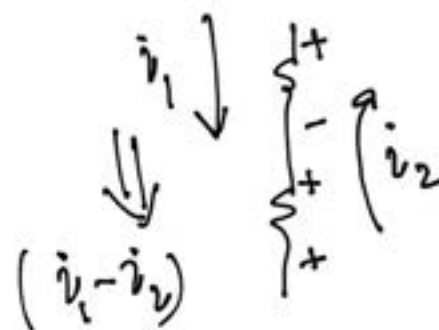

$i_1$  &  $i_2$

$$\text{KVL @ I} \quad +6V - 14i_1 - 10(i_1 - i_2) = 0$$

$$\text{@ II} \quad -10(i_2 - i_1) - 10i_2 - 5V = 0$$

P 4.6)

$$\textcircled{\text{I}} \text{ KVL : } 6 - 14i_1 - 10(i_1 - i_2) = 0$$

$$\Rightarrow 6 - 24i_1 + 10i_2 = 0 = 3 - 12i_1 + 5i_2 = 0 \quad \textcircled{1}$$

$$\textcircled{\text{II}} \text{ KVL } -10(i_2 - i_1) - 10i_2 - 5 = 0$$

$$\Rightarrow 10i_1 - 20i_2 - 5 = 2i_1 - 4i_2 - 1 = 0 \quad \textcircled{2}$$

$\textcircled{1} + 6 \times \textcircled{2}$

$$\left. \begin{array}{l} 3 - 12i_1 + 5i_2 = 0 \\ -6 + 12i_1 - 24i_2 = 0 \end{array} \right\}$$

$$19i_2 = -3$$

$$i_2 = -157.89 \text{ mA}$$

$$i_1 = \frac{4(-157.89) + 1}{2} = 184.2 \text{ mA}$$

(Solved)



# PRACTICE

4.8 Determine  $i_1$  in the circuit of Fig. 4.23 if the controlling quantity A is equal to (a)  $2i_2$ ; (b)  $2v_x$ .

Ans: (a) 1.35 A; (b) 546 mA.

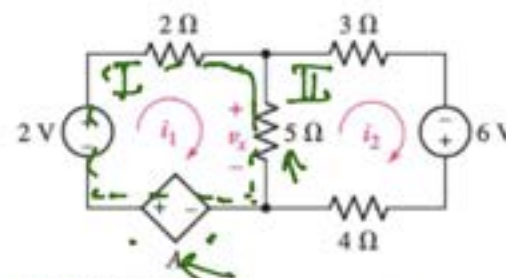


FIGURE 4.23

(a)  $A = 2i_2$  (CCVS)

(b)  $A = 2v_x$  (VCVS)

Dependent Voltage Source

KVL @ I

$$A + 2 - 2(i_1) - 5(i_1 - i_2) = 0$$

$$2i_2 + 2 - 2i_1 - 5i_1 + 5i_2 = 0 \quad \text{--- (1)}$$


$$2\underline{v_x} + 2 - 2i_1 - 5i_1 + 5i_2 = 0 \quad \text{--- (3)(b)}$$

KVL @ II

$$\rightarrow -5(i_2 - i_1) - 3i_2 + 6 - 4i_2 = 0 \quad \text{--- (2)}$$

$$v_x = 5(i_1 - i_2) \quad (\text{case b})$$

Ex 4.8

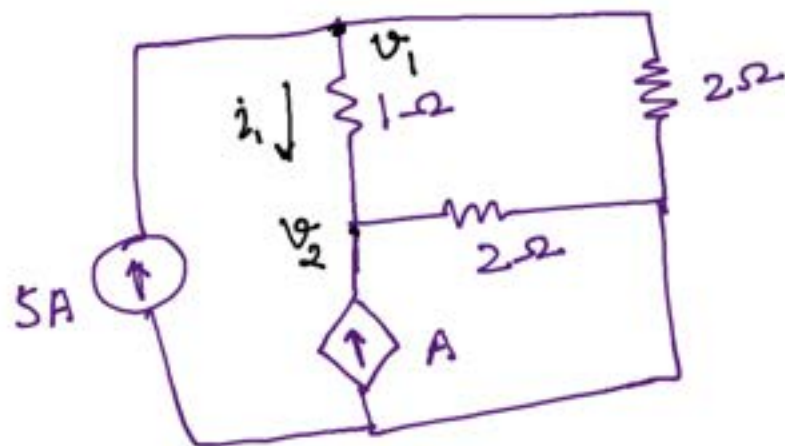

$$A = 2i_1$$

$$i_1 = \frac{v_1 - v_2}{1}$$

KCL @  $v_1$

$$5A - \frac{v_1 - v_2}{1} - \frac{v_1}{2} = 0 \Rightarrow -3v_1 + 2v_2 + 10 = 0 \quad (1)$$

KCL @  $v_2$

$$A - \frac{v_2}{2} + \frac{v_1 - v_2}{1} = 0 \Rightarrow 6v_1 - 7v_2 = 0 \quad (2)$$

$$3v_2 = 20$$

$$v_1 = \frac{7}{6} \times \frac{20}{3} = \frac{70}{9} V$$

$$A = 2v_1$$

(2)  $\Rightarrow$

$$2v_1 - v_2 + 2v_1 - 2v_2 = 0 \Rightarrow 4v_1 - 3v_2 = 0 \quad (2)$$

$$-3v_1 + 2v_2 + 10 = 0$$

P 4.8  
Fig 4.23

$$A = 2i_2$$

$$\text{KVL } \textcircled{1} \quad 2 - 2i_1 - 5(i_1 - i_2) + 2i_2 = 0$$

$$2 - 7i_1 + 7i_2 = 0 \quad \text{--- } \textcircled{1}$$

$$\text{KVL } \textcircled{2} \quad -5(i_2 - i_1) - 3i_2 + 6 - 4i_2 = 0$$

$$5i_1 - 12i_2 + 6 = 0 \quad \text{--- } \textcircled{2}$$

### PRACTICE

4.8 Determine  $i_1$  in the circuit of Fig. 4.23 if the controlling quantity  $A$  is equal to (a)  $2i_2$ ; (b)  $2v_x$ .

Ans: (a) 1.35 A; (b) 546 mA.

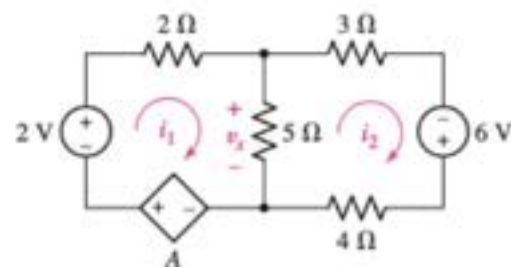


FIGURE 4.23

# CHAPTER 5


## Linear Elements :

Linear current-voltage relationship


$$v \propto i$$

$$v = 'R' i$$

↓  
constants

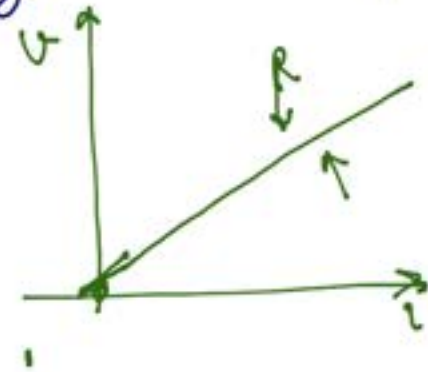
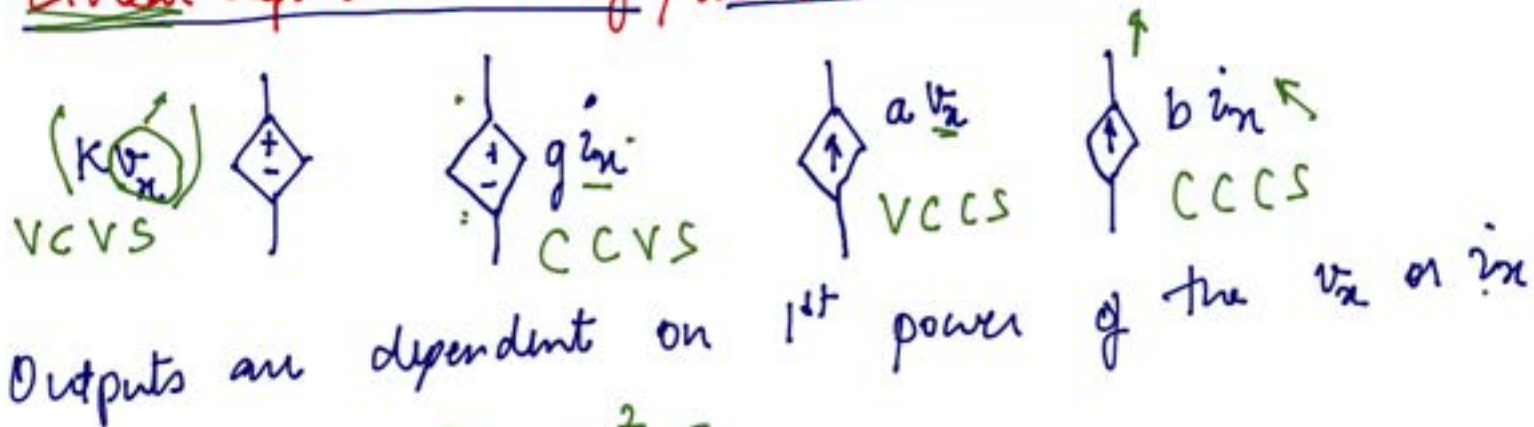
## Linear dependent voltage/current sources




~~$$Kx \frac{v_x^2}{2}$$~~


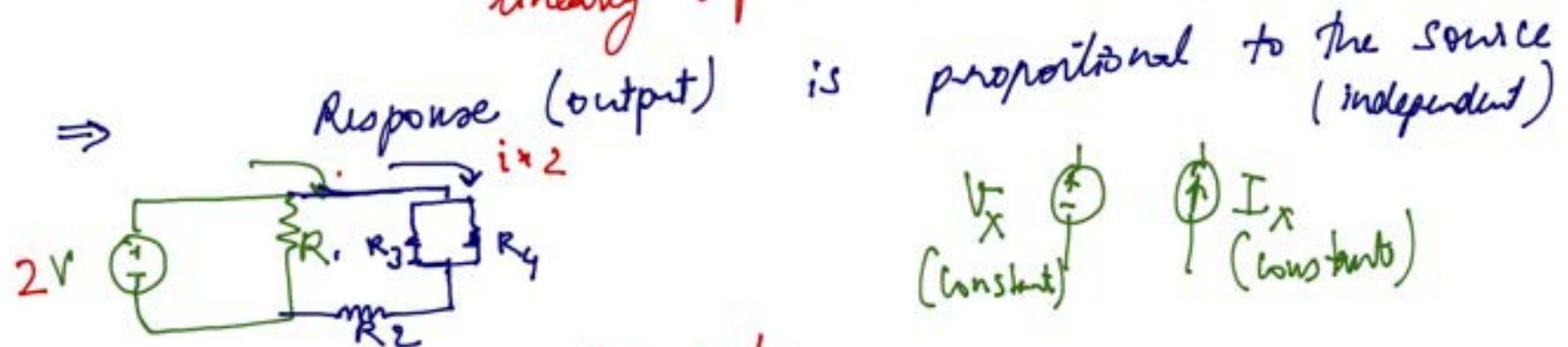
## Linear Circuits

Contains only linear element, independent sources or linearly dependent sources.




## Superposition Principle


Response of a **linear circuit** with more than one independent source can be obtained by adding the response from individual source.



# $V_s$ & $I_s$ for Superposition

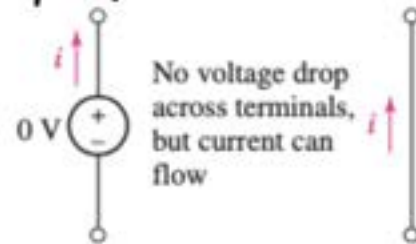

(a)

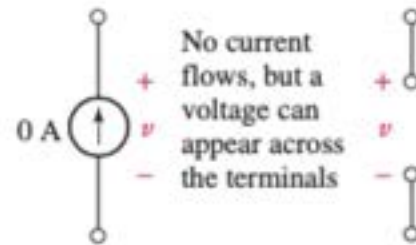

(b)


**FIGURE 5.2** (a) A voltage source set to zero acts like a short circuit. (b) A current source set to zero acts like an open circuit.

Applying Superposition  
Volts  $\rightarrow$  Short


Current sources  $\rightarrow$  open

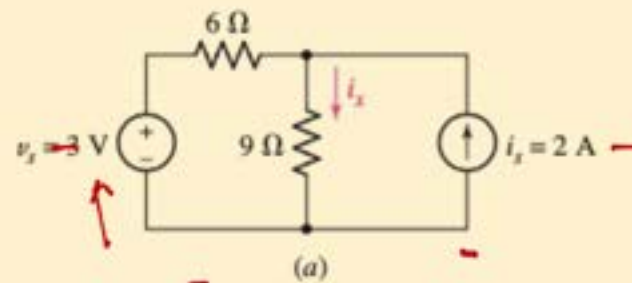Example 5.1


For the circuit of Fig. 5.3a, use superposition to determine the unknown branch current  $i_x$ .




(a)

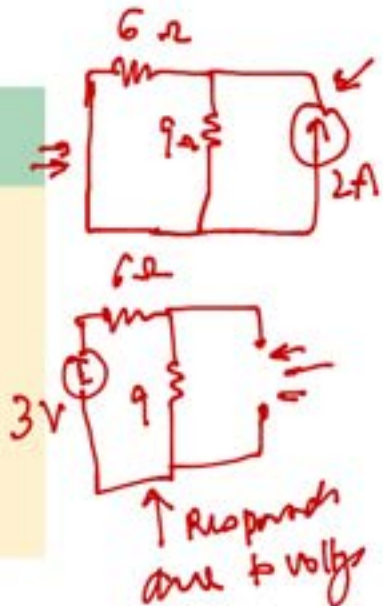

Ex 5.1

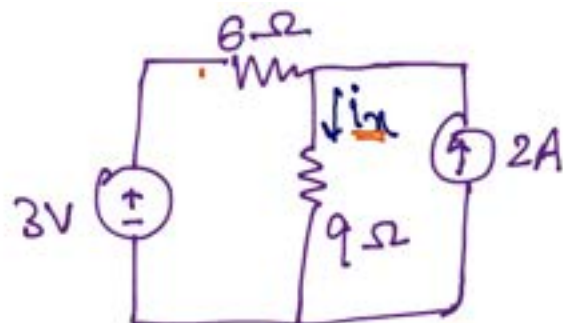


$$i_x = i_2 + i_3$$

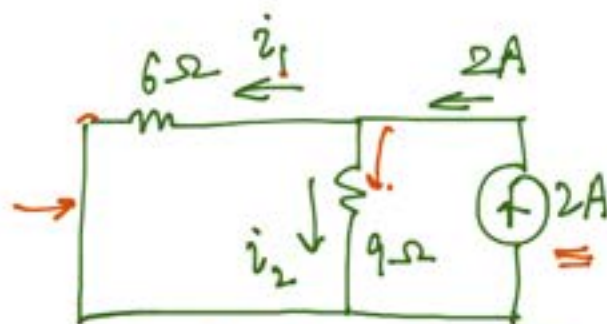

$$i_1 = \frac{9}{15} \times 2 = \frac{6}{5} = 1.2A$$

$$i_2 = \frac{6}{15} \times 2 = \frac{4}{5} = 0.8A$$

Response  
from  
I source

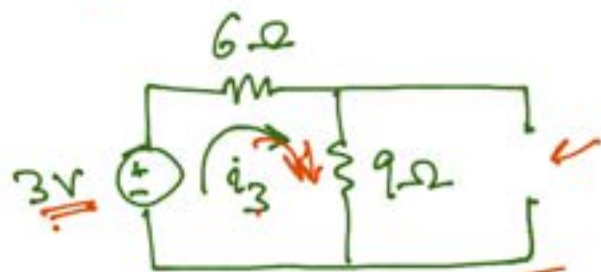


$$i_3 = \frac{3}{15} = \frac{1}{5} = 0.2A$$

Response  
from  
V source

$$\begin{aligned} i_x &= i_2 + i_3 = 0.8A + 0.2A \\ &= \underline{1A} \end{aligned}$$

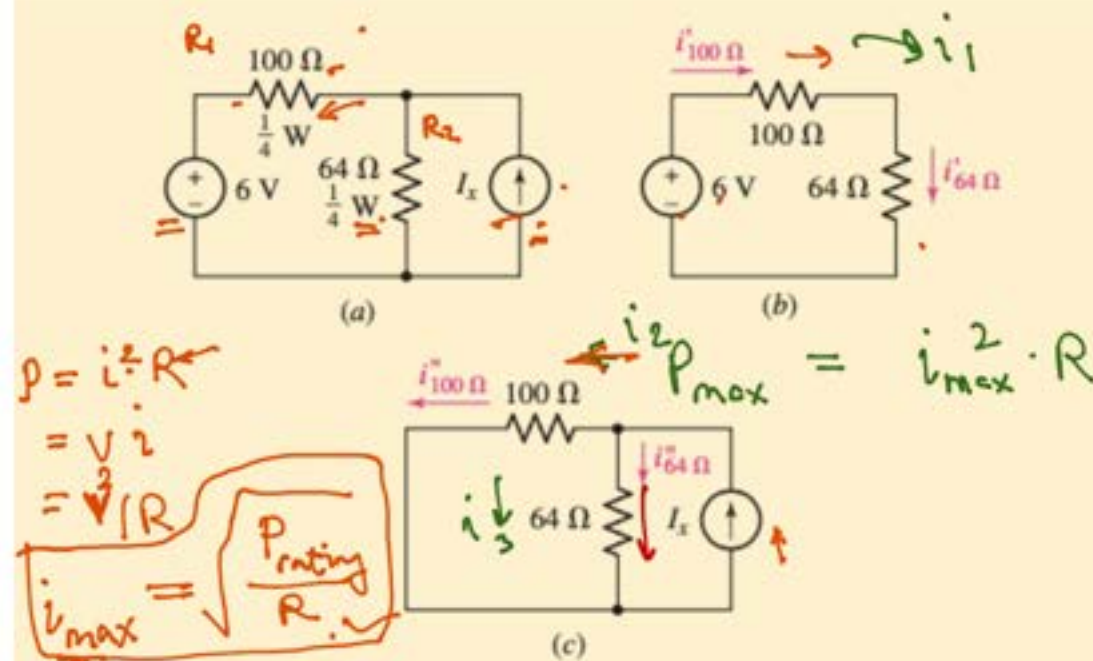Referring to the circuit of Fig. 5.5a, determine the maximum positive current to which the source  $I_x$  can be set before any resistor exceeds its power rating and overheats.



■ **FIGURE 5.5** (a) A circuit with two resistors each rated at  $\frac{1}{4}$  W. (b) Circuit with only the 6 V source active. (c) Circuit with the source  $I_x$  active.

Example 5.2

$$i_1 = \frac{6}{164} \text{ A} = 36.59 \text{ mA}$$

$$i_2 = \frac{64}{164} I_x$$

$$i_3 = \frac{100}{164} I_x$$

$$i_{max}(100\Omega) = \pm \sqrt{\frac{P_{max}}{R}} = \sqrt{\frac{1/4}{100}}$$

$$= \frac{1}{20} = 0.05 \text{ A}$$

$$i_{max}(64\Omega) = \sqrt{\frac{1/4}{64}} = \frac{1}{16} = 62.5 \text{ mA}$$

$$i_{max} = 0.05 = i_1 - i_2 = 36.59 \text{ mA} - \frac{64}{164} I_x \rightarrow$$



$$62.5 \text{ mA} = \frac{100}{164} I_x + 36.59 \text{ mA} \rightarrow I_x =$$



## Summary of Basic Superposition Procedure

1. **Select one of the independent sources. Set all other independent sources to zero.** This means voltage sources are replaced with short circuits and current sources are replaced with open circuits. Leave dependent sources in the circuit.
2. **Relabel voltages and currents using suitable notation** (e.g.,  $v'$ ,  $i_2''$ ). Be sure to relabel controlling variables of dependent sources to avoid confusion.
3. **Analyze the simplified circuit to find the desired currents and/or voltages.**
4. **Repeat steps 1 through 3 until each independent source has been considered.**
5. **Add the partial currents and/or voltages obtained from the separate analyses.** Pay careful attention to voltage signs and current directions when summing.
6. **Do not add power quantities.** If power quantities are required, calculate only after partial voltages and/or currents have been summed.

$$\begin{array}{ccc} \left. \begin{array}{l} V_1 \\ V_2 \end{array} \right\} & \begin{array}{l} P_1 \\ P_2 \end{array} & \begin{array}{c} \cancel{P_1 + P_2} \end{array} \end{array} \quad \begin{array}{c} i^2 R \\ \uparrow \uparrow \end{array} \quad \begin{array}{c} i = i_1 + i_2 \\ \downarrow \end{array}$$

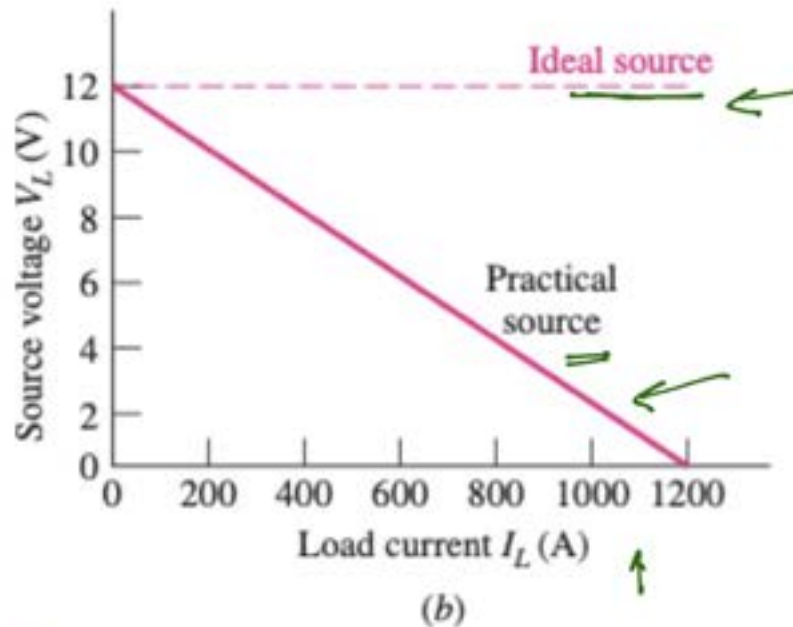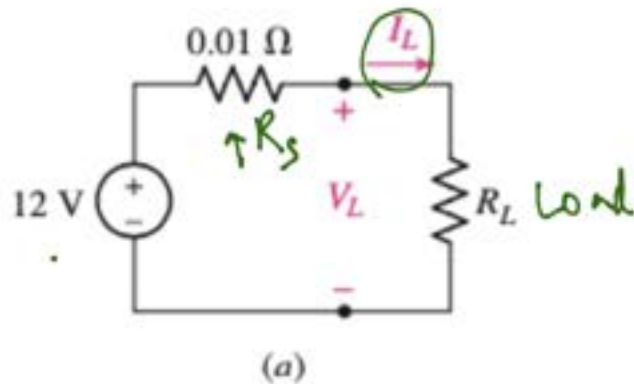

**FIGURE 5.12** (a) A practical source, which approximates the behavior of a certain 12 V automobile battery, is shown connected to a load resistor  $R_L$ . (b) The relationship between  $I_L$  and  $V_L$  is linear.

## Voltage Sources (Non ideal)

$R_s$  = Source Resistance

$I_L$  = Current = Load Current

$$V_s = I_L R_L + I_L R_s$$



Drop  
across  
Source  
Resistance

$$I_L R_L = V_s - I_L R_s$$


↓  
Voltage across the Load

↑  
Drop  $R_s$




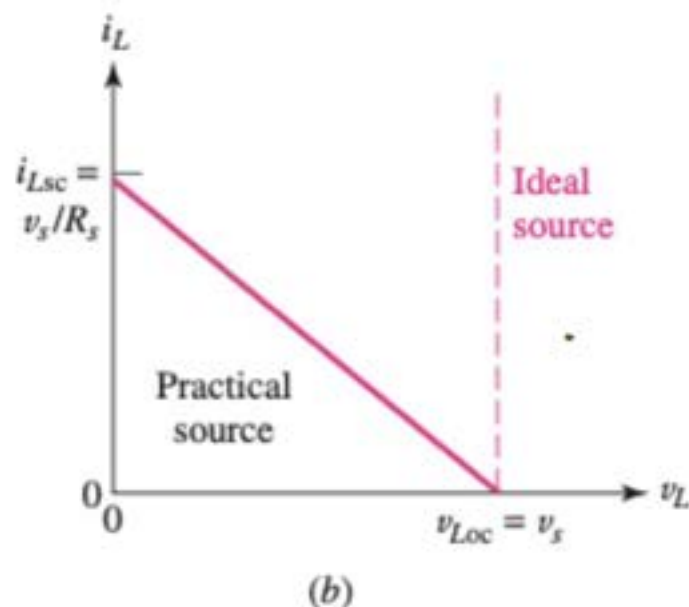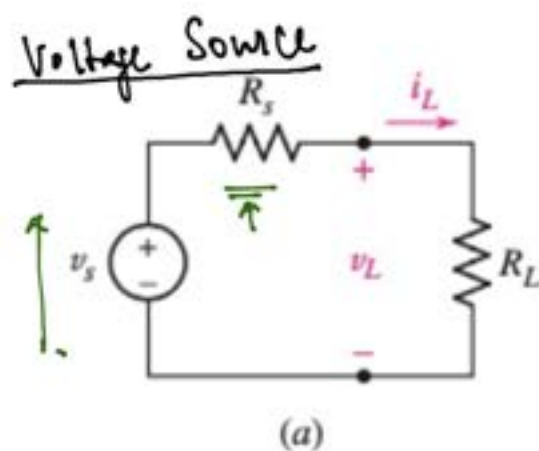

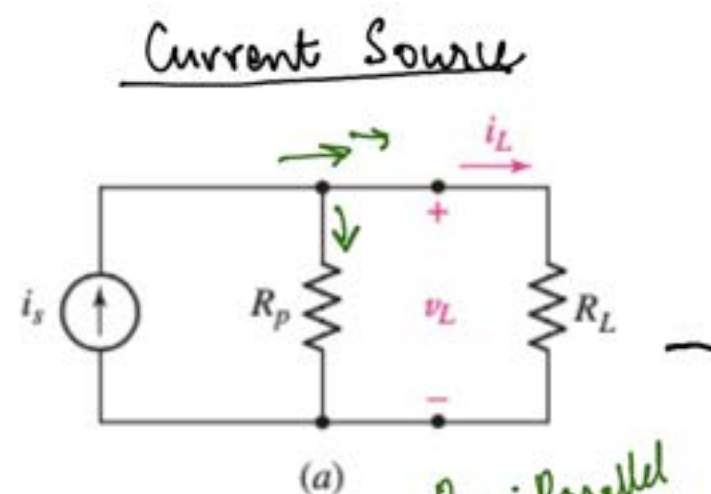■ **FIGURE 5.13** (a) A general practical voltage source connected to a load resistor  $R_L$ . (b) The terminal voltage of a practical voltage source decreases as  $i_L$  increases and  $R_L = v_L/i_L$  decreases. The terminal voltage of an ideal voltage source (also plotted) remains the same for any current delivered to a load.



$R_p$  : Parallel  
Source  
Resistance

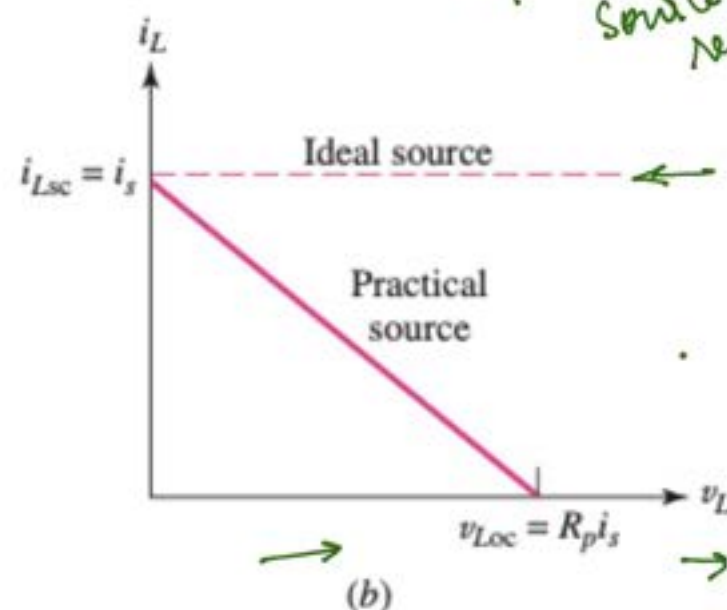

■ **FIGURE 5.14** (a) A general practical current source connected to a load resistor  $R_L$ . (b) The load current provided by the practical current source is shown as a function of the load voltage.