

---

# Analog Electronic Circuits (EC2.103) : Assignment-2

Spring 2024, IIIT Hyderabad, Due date : Wed 17<sup>th</sup> Jan, 2024 (18:00 hrs)

(Instructor: Prof. Abhishek Srivastava, CVEST, IIIT Hyderabad)

---

## Instructions:

1. Submit your assignment as a single pdf (Name\_RollNo.pdf) at moodle on or before the due date
  2. Hand-written/typed (latex/word) submissions are allowed
  3. Report should be self explanatory and must carry complete solution - Answers with schematics, SPICE directives, annotated waveforms, inference/discussion on results
  4. Post your queries on moodle, discussions are highly encouraged on moodle
- 

### 1. Two capacitor problem

For the circuit shown in Fig. 1, switch Sw1 is closed at  $t=0$ . Initial condition of capacitors are given as  $V_{C_1}(0^-) = V_0$  V and  $V_{C_2}(0^-) = 0$  V.

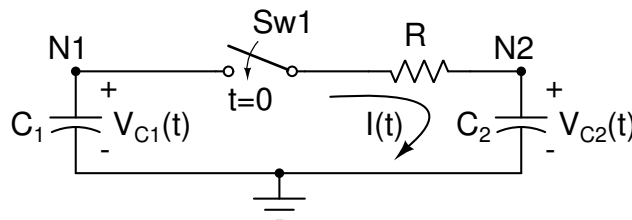


Figure 1

- (a) Derive and plot the expression of  $V_{C_1}(t)$ ,  $V_{C_2}(t)$  and current  $I(t)$  in the network as a function of time. Give plots and intuitive explanation for the cases- i)  $C_1 = C_2$ , ii)  $C_1 = 10 \times C_2$  and iii)  $C_1 = \frac{1}{10} C_2$ .
- (b) Consider  $C_1 = 10$  nF and  $V_{C_1}(0^-) = V_0 = 1$  V and  $V_{C_2}(0^-) = 0$  V,  $R = 1$  k $\Omega$ . Using LTSPICE, run transient analysis and plot  $V_{C_1}(t)$ ,  $V_{C_2}(t)$  for the cases - 1)  $C_1 = C_2$ , ii)  $C_1 = 10 \times C_2$  and iii)  $C_1 = \frac{1}{10} C_2$ .  
(Hint: To give Initial condition to capacitors  $C_1$  &  $C_2$ , Go to **Edit**  $\rightarrow$  **Spice Directive** and write **.ic V(N1)=1 V(N2)=0** in the command box and click OK. For implementing switch use SW component (voltage controlled switch) and add spice directive **.model SW SW(Ron=1m Roff=1Meg Vt=.5 Vh=0)** (Why?) Give Control voltage to switch as **PULSE(0 1 10u 10n 10n 1000u 2000u)** (why?), run transient for 200  $\mu$ s.)
- (c) At time  $t = 0$ , calculate the energy stored ( $E_0$ ) in the circuit. (hint :- Energy stored in Capacitor  $\frac{1}{2} \times CV^2$ ). From your simulation plots in the previous part (b), find total energy at steady state ( $t = \infty$ ) and compare with  $E_0$  for all three cases (give a table). Do you have any answer/thoughts for this paradox?
- (d) Consider  $C_1 = C_2 = 10$  nF and  $V_{C_1}(0^-) = V_0 = 1$  V and  $V_{C_2}(0^-) = 0$  V, plot  $V_{C_1}(t)$ ,  $V_{C_2}(t)$  for the cases - a)  $R = 10$  k $\Omega$ , b)  $R = 10$   $\Omega$  and c)  $R = 1$  m $\Omega$ . Qualitatively discuss effect of reducing  $R$  value on the settling time of  $V_{C_1}(t)$  and  $V_{C_2}(t)$


**Suggested reading: Interested students may have a look, no grades for reading**

1) R. C. Levine, "Apparent Nonconservation of Energy in the Discharge of an Ideal Capacitor," in IEEE Transactions on Education, vol. 10, no. 4, pp. 197-202, Dec. 1967, doi: 10.1109/TE.1967.4320288.

2) J. Hoekstra, "A Solution of the Two-Capacitor Problem Through its Similarity to Single-Electron Electronics," in IEEE Open Journal of Circuits and Systems, vol. 1, pp. 13-21, 2020, doi: 10.1109/OJCAS.2020.2977216.


## 2. RC circuits as filters

- (a) For the circuit shown in Fig. 2, it is given that  $R = 20 \text{ M}\Omega$  and  $C = 10 \text{ pF}$  and  $V_C(0^-) = 0 \text{ V}$  (zero initial voltage across capacitor).

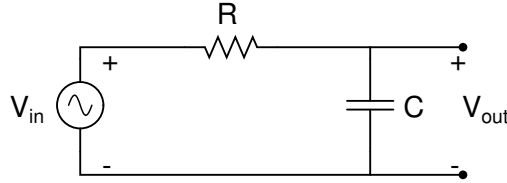

**Figure 2**


- i) As discussed in the lecture, present intuitive explanation for  $V_{out}(t)$  as a function of time for a step input  $V_{in} = V_0 u(t)$ . ( $V_{out}$  initial, final type of rise/fall - linear/exponential). Also discuss, how it acts as a **low pass filter**.
  - ii) Derive the expression for  $V_{out}(t)$  and current across the capacitor for the input  $V_{in} = V_0 u(t)$ . Using LTSPICE simulations, plot the voltage and current with  $V_{in} = 5u(t) \text{ V}$  and verify your theoretical expressions.  
(Hint: Run Transient analysis for the Step input signal  $PWL(0 \ 0 \ 1m \ 5)$ , Run the transient for 20 ms.)
  - iii) Write the expression for Transfer Function  $\frac{V_{out}(s)}{V_{in}(s)}$ . Find the expressions for gain ( $|\frac{V_{out}(j\omega)}{V_{in}(j\omega)}|$ ) and phase ( $\phi$ ) as a function of frequency ( $\omega$ ) and find the 3 dB cut-off frequency.
  - iv) Verify your derivation and hand calculations with AC analysis of the circuit by plotting gain and phase w.r.t frequency.  
(Hint: Set AC amplitude for  $V_{in}$  voltage source as 1. For AC analysis set Type of Sweep = Decade, Number of points = 1000, Start Frequency = 5 Hz, Stop Frequency = 50 MHz).
- (b) For the circuit given in figure 3, repeat all the analysis from part (a) for  $R = 20 \text{ k}\Omega$  and  $C = 10 \text{ pF}$ . Please note that this circuit acts as a **high pass filter**. Give intuitive explanation and derive/calculate/simulate accordingly.  
(Hint: For AC analysis Set Type of Sweep = Decade, Number of points = 1000, Start Frequency = 5 Hz, Stop Frequency = 50 MHz).

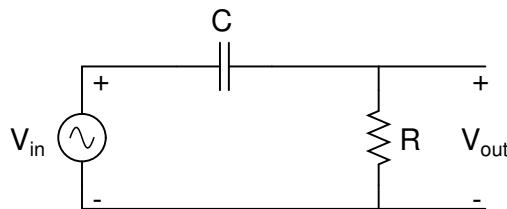

**Figure 3**

- (c) Fig. 4 depicts a scenario, where  $Z_1$  represents the impedance of a probe and  $Z_2$  represents the impedance of an oscilloscope. Consider that the input voltage ( $V_{in}(t)$ ) is a pulse of width  $T_b (>> R_i C_i)$  ( $i=1,2$ ) as described below:

$$V_{in}(t) = \begin{cases} V_1 & t \leq 0 \\ V_2 & 0 \leq t \leq T_b \text{ } (V_2 \geq V_1) \\ V_1 & t \geq T_b \end{cases}$$

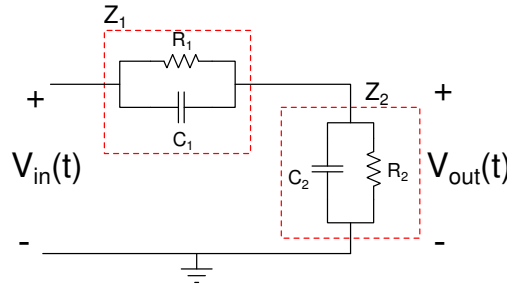

**Figure 4**

- i) Intuitively find and explain the values of  $V(C_1)$ ,  $V(C_2)$ ,  $I(R_1)$ ,  $I(C_1)$ ,  $I(R_2)$ ,  $I(C_2)$  at  $t = 0^-$  and  $t = 0^+$ , for the two cases given below:
    - A. ( $R_1 C_1$  not equal to  $R_2 C_2$ )  $R_1 = 10 \text{ M}\Omega$ ,  $C_1 = 2 \text{ pF}$ ,  $R_2 = 5 \text{ M}\Omega$ ,  $C_1 = 50 \text{ pF}$ .
    - B. ( $R_1 C_1$  is equal to  $R_2 C_2$ )  $R_1 = 10 \text{ M}\Omega$ ,  $C_1 = 2 \text{ pF}$ ,  $R_2 = 1 \text{ M}\Omega$ ,  $C_1 = 20 \text{ pF}$ .
  - ii) Does this circuit allows to pass quick transitions in the input to output (high pass)? What about slow transitions (low pass)? Briefly comment.
  - iii) Verify your theoretical/intuitive values by simulating the above circuit using LT-SPIICE for both cases (A and B). (Plot  $V(C_1)$ ,  $V(C_2)$ ,  $I(R_1)$ ,  $I(C_1)$ ,  $I(R_2)$ ,  $I(C_2)$  as a function of time).  
(Hint: Run Transient analysis for the input pulse signal `PULSE(2 5 0 1p 1p 200u)`, Run the transient for  $400 \mu\text{s}$ ).
  - iv) Derive the transfer function  $\frac{V_{out}(s)}{V_{in}(s)}$  for the given circuit. From the transfer function comment on the nature of the circuit - low-pass, high-pass or **all-pass filter**?
  - v) Give a sinusoidal input(`SINE(0 5 5k)`) to the above circuit with the values of R,C same as in case-B ( $R_1 = 10 \text{ M}\Omega$ ,  $C_1 = 2 \text{ pF}$ ,  $R_2 = 1 \text{ M}\Omega$ ,  $C_1 = 20 \text{ pF}$ ), perform AC analysis and find the -3 dB bandwidth (BW) of the circuit.
  - vi) Run transient analysis by varying the frequency of the sinusoidal input and plot the output waveforms.  
(Hint: For AC analysis Set Type of Sweep = Decade, Number of points = 1000, Start Frequency = 5k Hz, Stop Frequency = 5GHz).
3. Plot Bode magnitude and phase plots for following functions.  $T$  is a constant. (References: Lecture notes. For further readings text books on control system - 1) Linear control system by B.S. Manke, 2) Control System by Nagrath Gopal, 3) Control Systems by Ogata)
- |  |   |
|--|---|
| (a) $H(j\omega) = 1 + j\omega T$                       | (e) $H(s) = \frac{10}{(s+1)(s+2)}$          |
| (b) $H(j\omega) = \frac{1}{1+j\omega T}$               | (f) $H(s) = \frac{(s-1)}{(s+1)(s+2)}$       |
| (c) $H(j\omega) = \frac{1+j\omega T_1}{1+j\omega T_2}$ | (g) $H(s) = \frac{2(s+1)}{s^2(s+2)(s+0.5)}$ |
| (d) $H(j\omega) = \frac{1-j\omega T_1}{1+j\omega T_2}$ |   |