
Analog Electronic Circuits (EC2.103) : Assignment-4

Spring 2024, IIIT Hyderabad, Due date : Tue 5-Mar-2024 (18:00 Hrs)

Instructor: Prof. Abhishek Srivastava, CVEST, IIIT Hyderabad

Instructions:

1. Submit your assignment as a single pdf (Name_RollNo.pdf) at moodle on or before the due date
 2. Hand-written/typed (latex/word/notion/others) submissions are allowed
 3. Report should be self explanatory and must carry complete solution - Answers with schematics, SPICE directives, annotated waveforms, inference/discussion on results
 4. Post your queries on moodle. Discussions are highly encouraged on moodle
-

1. BJT characterization

- (a) Take BC547B npn transistor from the LTSPICE library and make a circuit as shown in Fig. 1(a). Use $V_{CC} = 12\text{ V}$, sweep I_B from 0 to 100 μA in step size of 10 μA and plot V_{BE} with respect to I_B . What is the forward bias emitter-base junction (EBJ) voltage obtained from the plot? Repeat experiment for $V_{CC} = 0\text{ to }12\text{ V}$ in step size of 2 V and give superimposed plots for different V_{CC} on same graph.

(Hint: `.dc IB 0 100u 10u VCC 0 12 2`)

 


Figure 1

- (b) Use the schematic shown in Fig. 1(b) in LTSPICE and plot I_C vs V_{BE} for $V_{CC} = 12\text{ V}$ at 20°C , 30°C , 40°C , 50°C by sweeping V_{BE} from 0 to 0.7 V in step size of 0.01 V. All plots should overlay on same graphical axis.

(Hint: `.dc VBE 0 0.7 0.01, .step TEMP 20 50 10` or `.step TEMP LIST 20 30 40 50`)

- (c) For Fig. 1(a), plot I_C vs V_{CE} by sweeping V_{CC} from 0 to 12 V in step size of 0.01 V and sweeping $I_B = 0\text{ } \mu\text{A}$ to 100 μA in step size of 10 μA . Clearly mark cut-off, saturation and active modes in your characteristic plot. Find and tabulate incremental current gain $\beta = \frac{\Delta I_C}{\Delta I_B}$ in saturation (at $V_{CE} = 100\text{ mV}$) and active (at $V_{CE} = 600\text{ mV}$) modes for $I_{B1} = 50\text{ } \mu\text{A}$ to $I_{B1} = 60\text{ } \mu\text{A}$. Comment on the reason for the difference observed. Tabulate the current gain $\beta = \frac{I_C}{I_B}$ at $V_{CE} = 1\text{ V}$ for different values of I_B . Do you observe Early effect. Estimate the value of early voltage (V_A) from your simulations.

(Hint: `slope at a point = $y/x = I_C/(V_A + V_{CE})$`)

- (d) In your exams, I will ask similar plots for a pnp transistor. Therefore practise and repeat above experiments for pnp transistor also. **(No need to submit this part)**

- (e) **Practise problems:** All solved examples and exercise problems of Chapter-4/5 of the reference textbook Microelectronics by Razavi. **(No need to submit this part)**

2. BJT amplifier analysis and design

Fig. 2 shows a common emitter (CE) voltage amplifier. Given that $V_{CC} = 12\text{ V}$, $C_B = 10\text{ }\mu\text{F}$,

 


Figure 2

$C_C = 10\text{ }\mu\text{F}$, $C_E = 100\text{ }\mu\text{F}$, $R_1 = 18.46\text{ k}\Omega$, $R_2 = 2.24\text{ k}\Omega$, $R_E = 2\text{ k}\Omega$, $R_C = 30.3\text{ k}\Omega$, $R_L = 1\text{ k}\Omega$ and $v_{in} = V_m \sin(2\pi f_0 t)\text{ V}$, where $f_0 = 1\text{ kHz}$. Implement the given circuit using BC547B (NXP) in LTSPICE and simulate following:

- Draw the DC picture of the given circuit and calculate theoretically V_C , V_B , V_E , I_C and I_B . Find the mode of operation of BJT in the given circuit.
(Hint: For DC picture: AC sources are replaced with its internal resistance and capacitors act as open (why?). In forward active mode, V_{BE} is fixed ($\approx 0.7\text{ V}$), $I_C = \beta I_B$, β for 547B you know from previous problem.)
- Run operating point simulation (.op) and verify your theoretical values with the simulated values. Give a table showing theoretical and simulated values of different parameters.
- Calculate small signal parameters g_m , r_π and r_o for the transistor.
- Draw the signal picture and small signal equivalent of the circuit.
(Hint: Capacitors should be replaced by its impedance values at the given frequency.)
- Derive the expression for the small signal voltage gain ($A_v = \frac{v_{out}}{v_{in}}$).
- Run transient analysis (.tran 50m) and plot v_{in} and v_{out} for $V_m = 10\text{ mV}$. Verify the gain from transient simulations with the calculated gain in the previous part.
- Plot FFT of v_{out} and report differences of 2nd, 3rd and 4th harmonics from the fundamental (1 kHz) component.
(Hint: To plot FFT: on waveform viewer, right click - view - FFT)
- By using the parametric sweep, vary the amplitude (V_m) of the input signal and report total harmonic distortion from the spice error log file. Report corresponding FFT plots also. You might observe that with increasing value of V_m , THD increases and FFT also shows prominent harmonics. Why does it happen? Briefly comment with supporting calculations.
(Hint: For parametric sweep: define $v_{in} = \text{SINE}(0 \{V_m\} 1k)$ (NOTE THAT '{ }' is must) and use spice directive .step param Vm 10m 200m 50m. For THD: right click on schematic editor - view - SPICE Error Log. For more details and help refer LTSPICE manual shared earlier.)

- (i) Run AC analysis (.ac dec 10 1m 1G), plot magnitude and phase of $A_v = \frac{v_{out}}{v_{in}}$ and report DC gain (dB) and -3 dB bandwidth of the amplifier.
(Hint: Comment .tran and other analysis, For v_{in} source in your simulation setup, give V_m a constant value, give AC amplitude = 1)
- (j) Now parametrize the resistance R_C and sweep its value from $28\text{ k}\Omega$ to $40\text{ k}\Omega$ in step size of $2\text{ k}\Omega$ and run ac simulation to plot $|A_v| = \frac{v_{out}}{v_{in}}$. Give a table showing DC gain for different values of R_C ? Why the gain is changing? Compare two cases ($30\text{ k}\Omega$ and $40\text{ k}\Omega$) quantitatively and justify your answers.
3. Redesign (give values of $C_B, C_C, C_E, R_1, R_2, R_E, R_C, I_C, I_B$) the CE amplifier shown in Fig. 2 to achieve same voltage gain with same $R_L = 1\text{ k}\Omega$ and same bandwidth but with reduced supply of 5 V , that is $V_{CC} = 5\text{ V}$. Show design procedure with detailed calculations and report DC, transient and AC simulation results to verify your design. Compare the total DC power ($P_{DC} = V_{CC} \times I_{Drawn}$) consumed for $V_{CC} = 12\text{ V}$ and 5 V .
-