


Analog Electronic Circuits

Assignment - 4

Question 1 : BJT Characterization

(a) Given , BC547B npn transistor


Circuit :

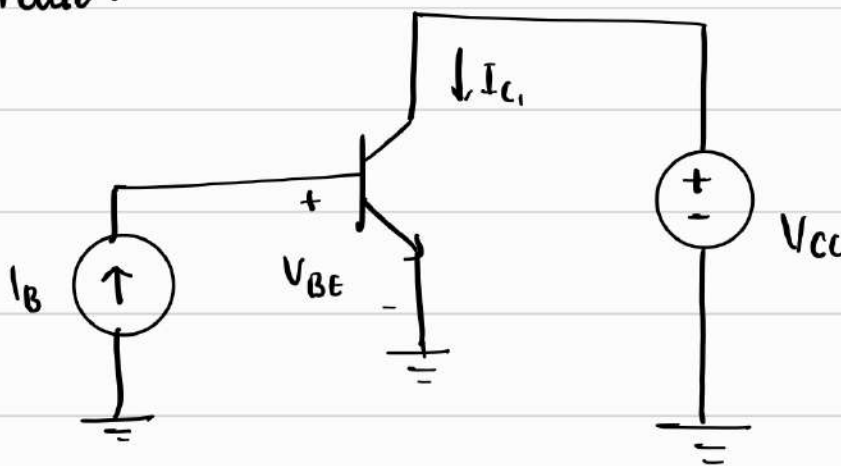


$$V_{CC} = 12V$$

The required DC sweep from 0 to 100 μA with step 10 μA

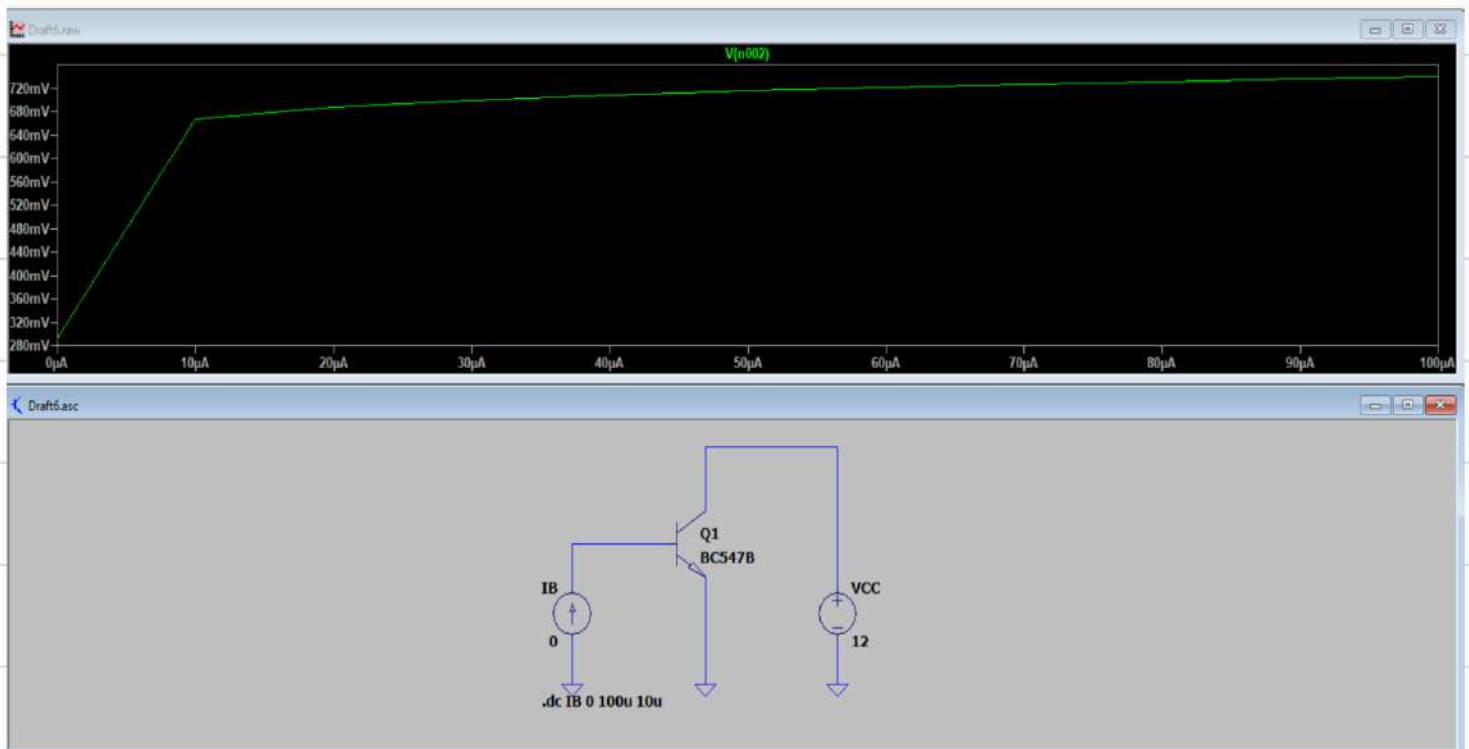
Below is the plot between V_{BE} and I_B .



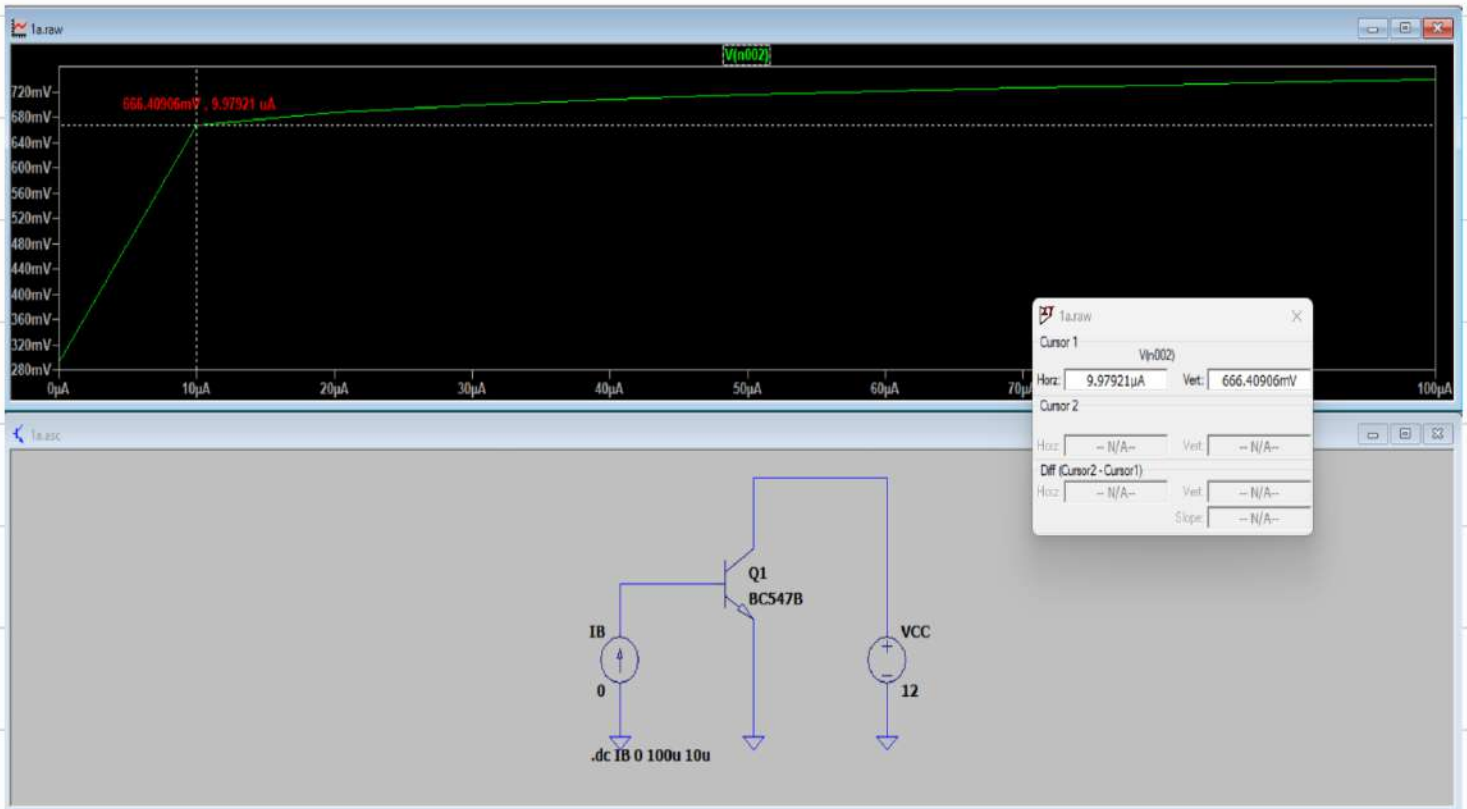The forward-bias emitter-base junction (EBJ)
voltage from the plot = 666.40906 mV




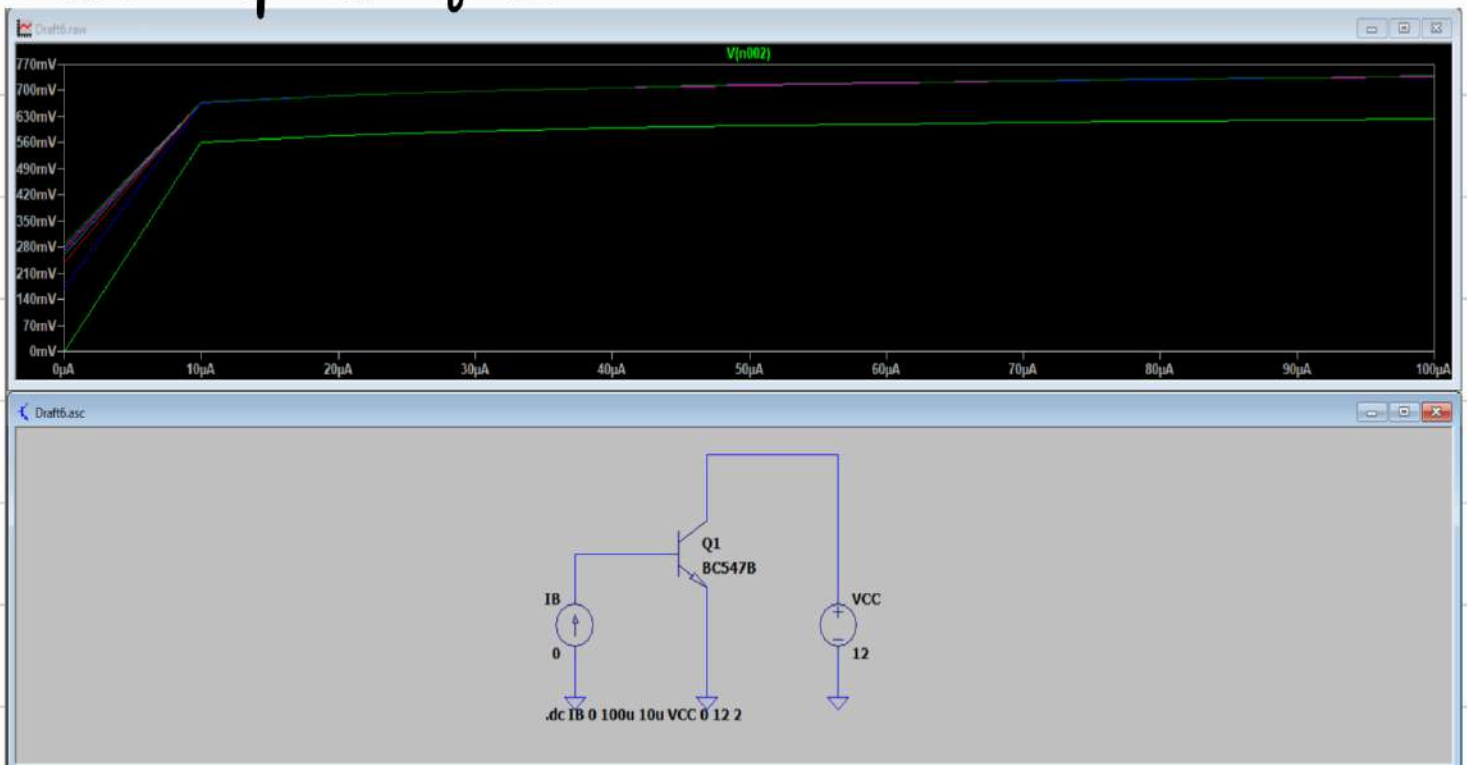Now, dc sweep of I_B with V_{CC} varying from 0 to 12V
and step size of 2V.




(b) BC547B npn transistor

Circuit :

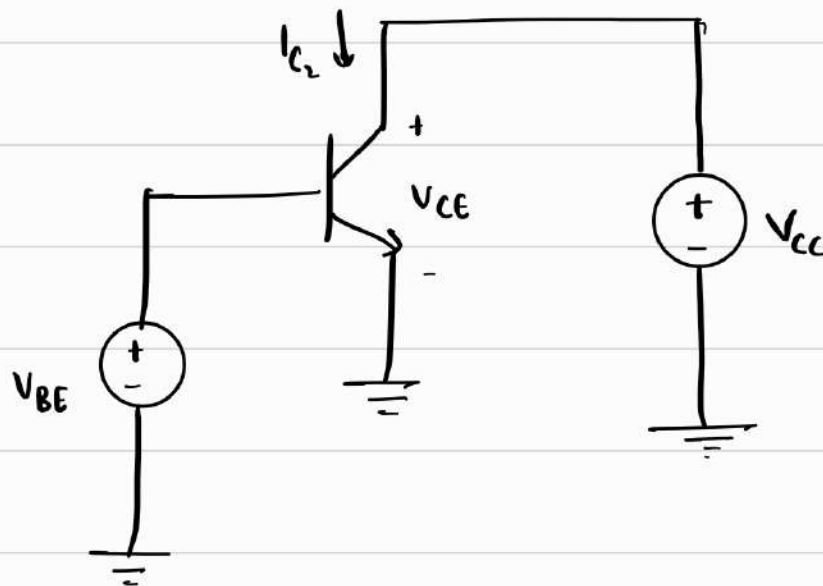

Plot of I_C vs V_{BE} for $V_{CC} = 12V$

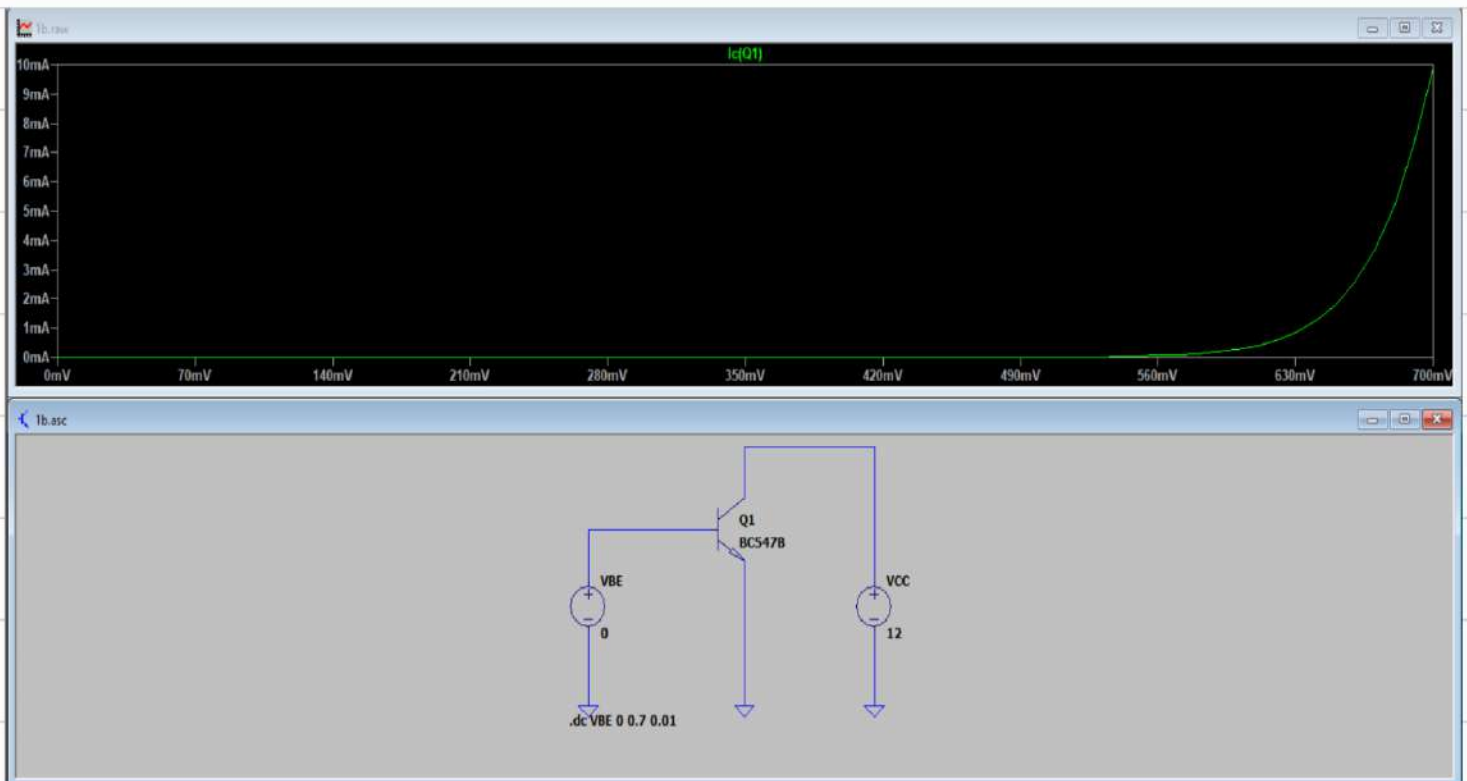

$$V_{BE}/V_T$$

We know that, $I_{C2} = I_S e$

$$\text{and } V_T = \frac{kT}{Q}$$



$$V_T$$

$$\Rightarrow I_{C2} \propto e^{\frac{V_{BE}}{V_T}}$$

As temperature, $T \uparrow \Rightarrow \frac{1}{T} \downarrow$

\therefore Collector current decreases

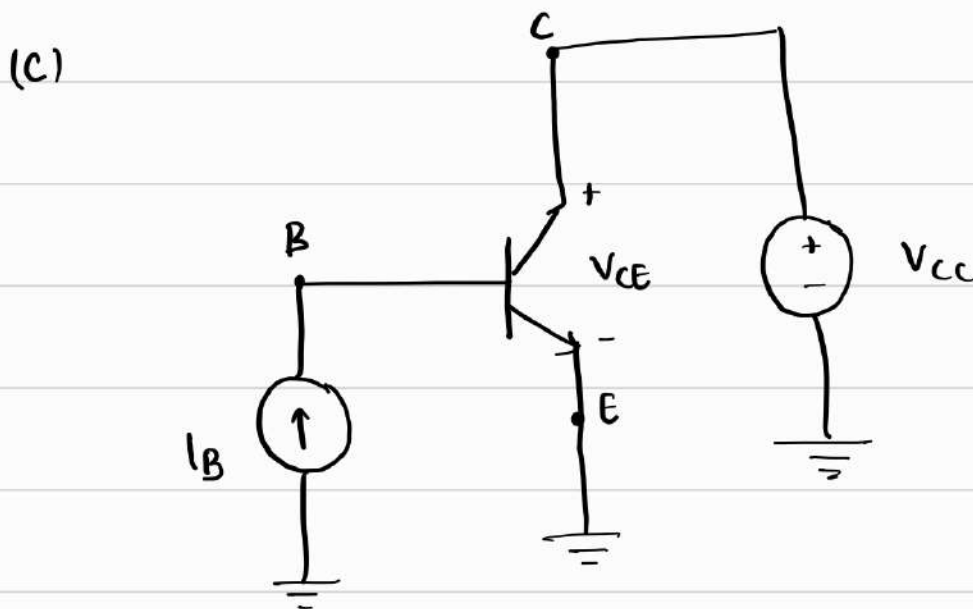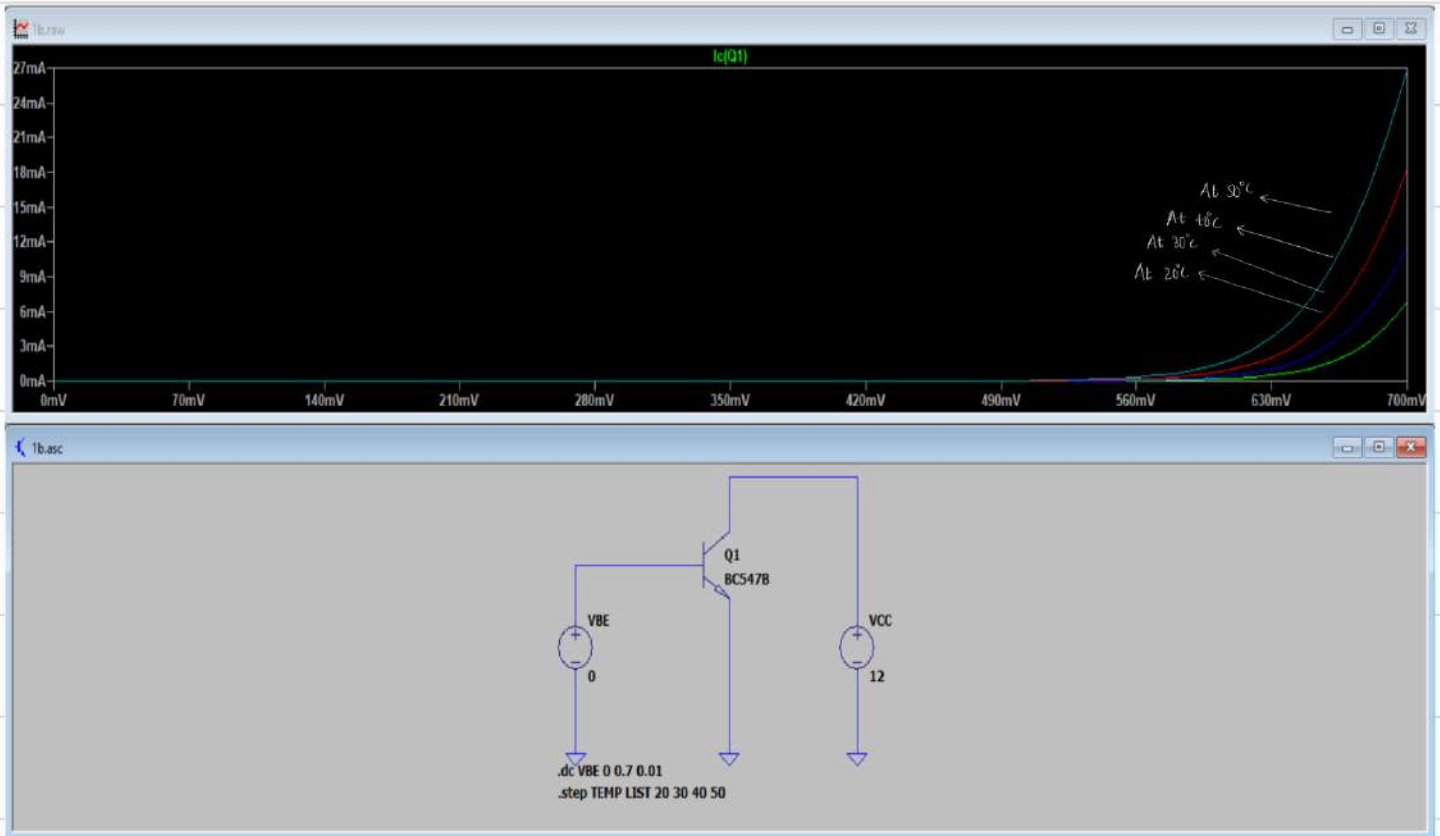The below is the required LtSpice simulation.



→

* At $V_{CE} = 100\text{mV} \rightarrow$ Saturation Mode

I_B	I_C	$\beta = I_C/I_B$	\rightarrow Incremental Current Gain
$50\text{ }\mu\text{A}$	5.22 mA	104.4	
$60\text{ }\mu\text{A}$	6.07 mA	101.16	

* At $V_{CE} = 600\text{mV} \rightarrow$ Active Mode

I_B	I_C	$\beta = I_C/I_B$	\rightarrow Incremental Current Gain
$50\text{ }\mu\text{A}$	12.95 mA	259	
$60\text{ }\mu\text{A}$	15.2 mA	253.33	

Reasons for the difference observed:

- * At $V_{CE} = 100\text{mV} \rightarrow$ The transistor is in saturation mode
 - \rightarrow The CB Junction is in forward bias
 - \rightarrow Collector current is very low
$$I_C = I_s$$

* At $V_{CE} = 600\text{mV} \rightarrow$ The transistor is in

active mode

→ The CB Junction is in reverse bias

→ Collector current is high

$$I_C = I_S e^{V_{BE}/V_T}$$

→ At $V_{CE} = 1V$

I_B	I_C	$\beta = I_C / I_B$
0 A	-180.28 μA	-
10 μA	2.8 mA	280
20 μA	5.502 mA	275.1
30 μA	8.11 mA	270.33
40 μA	10.61 mA	265.25
50 μA	13.01 mA	260.8
60 μA	15.39 mA	256.5
70 μA	17.68 mA	252.25
80 μA	19.91 mA	248.87
90 μA	22.01 mA	244.55
100 μA	24.20 mA	242

The average β value from above is

$$\beta = 259.56$$

Early Voltage:

The reverse-bias current in CB Junction increases

i.e., as we increase V_{CE} , the width of the depletion region in CB junction increases.

\Rightarrow Width of depletion increases

Because of this the no of e^- coming into collector wrt to time also increases. Hence collector current I_C increases.

Also, this trend is clearly seen in the simulation below.

Estimating V_A value :

Let's fix $I_B = 50 \mu$

$$\text{At } V_{CE} = 1V \quad \Rightarrow \quad I_C = 12.94 \text{ mA}$$

$$V_{CE} = 2V \quad \Rightarrow \quad I_C = 13.16 \text{ mA}$$

$$\text{Given, slope} = \frac{I_C}{V_A + V_{CE}}$$

As slopes must be equal,


$$\frac{0 - 13.16}{V_A - 2} = \frac{12.92 - 13.16}{1 - 2}$$

$$\frac{-13.16}{V_A - 2} = 0.24$$


$$\boxed{V_A = -54.67 \text{ V}}$$


∴ The estimated early voltage is -54.67 V

Below is the Lt Spice simulation with all the regions marked :

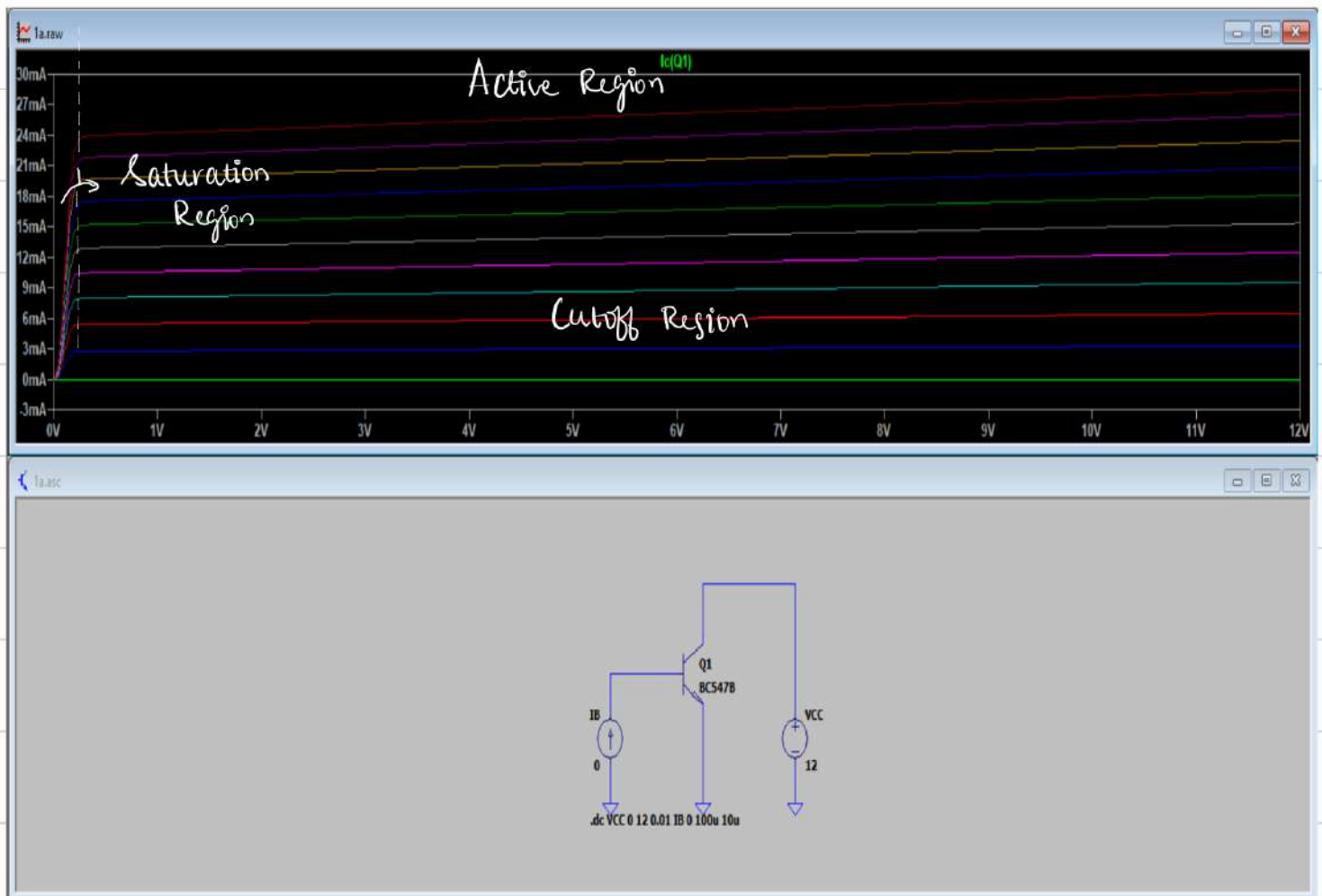

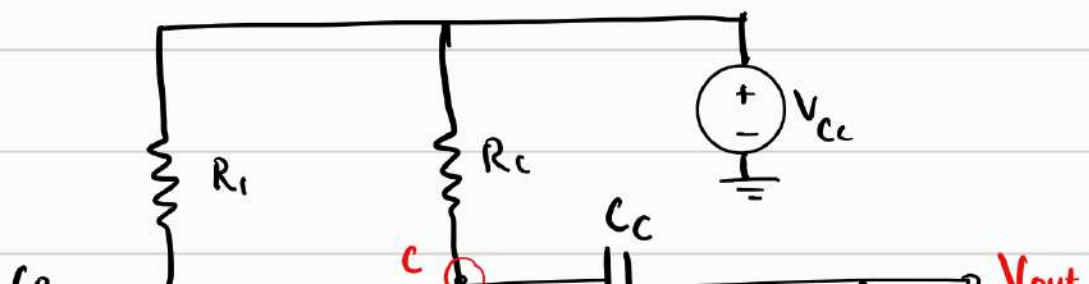Question 2: BJT Amplifier Analysis and Design



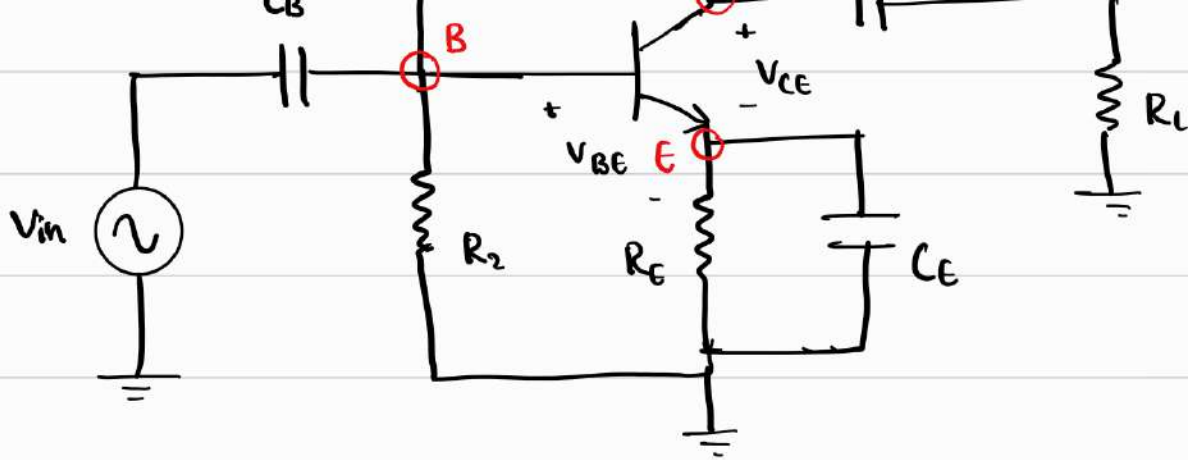

Given parameters,

$$V_{CC} = 12V$$

$$R_1 = 18.46 \text{ k}\Omega$$

$$C_B = 10 \mu F$$

$$R_2 = 2.29 \text{ k}\Omega$$

$$C_C = 10 \mu F$$

$$R_E = 2 \text{ k}\Omega$$


$$C_E = 10 \mu F$$


$$R_C = 30.3 \text{ k}\Omega$$

$$f_0 = 1 \text{ kHz}$$

$$R_L = 1 \text{ k}\Omega$$

$$V_{in} = V_m \sin(2\pi f_0 t)$$

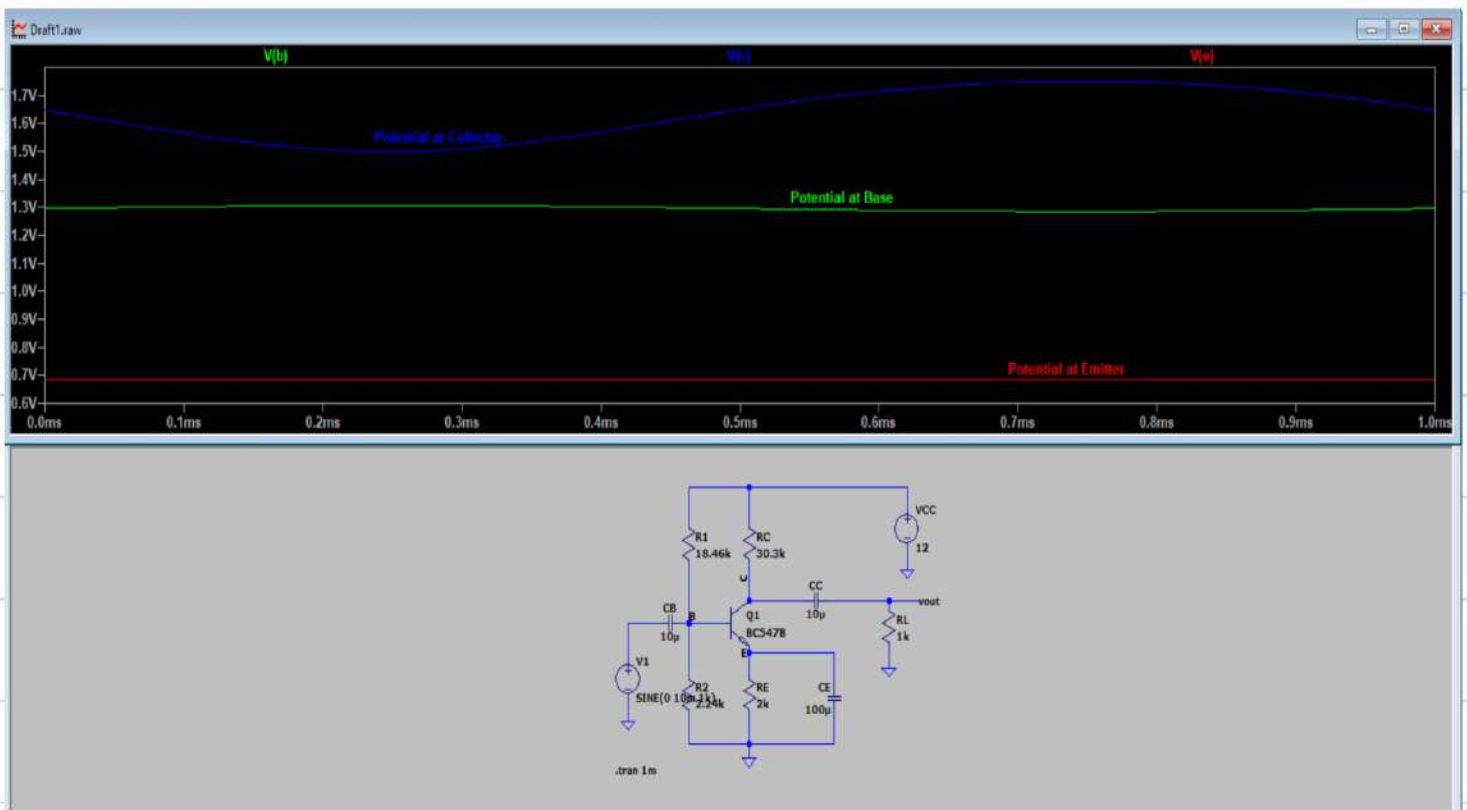

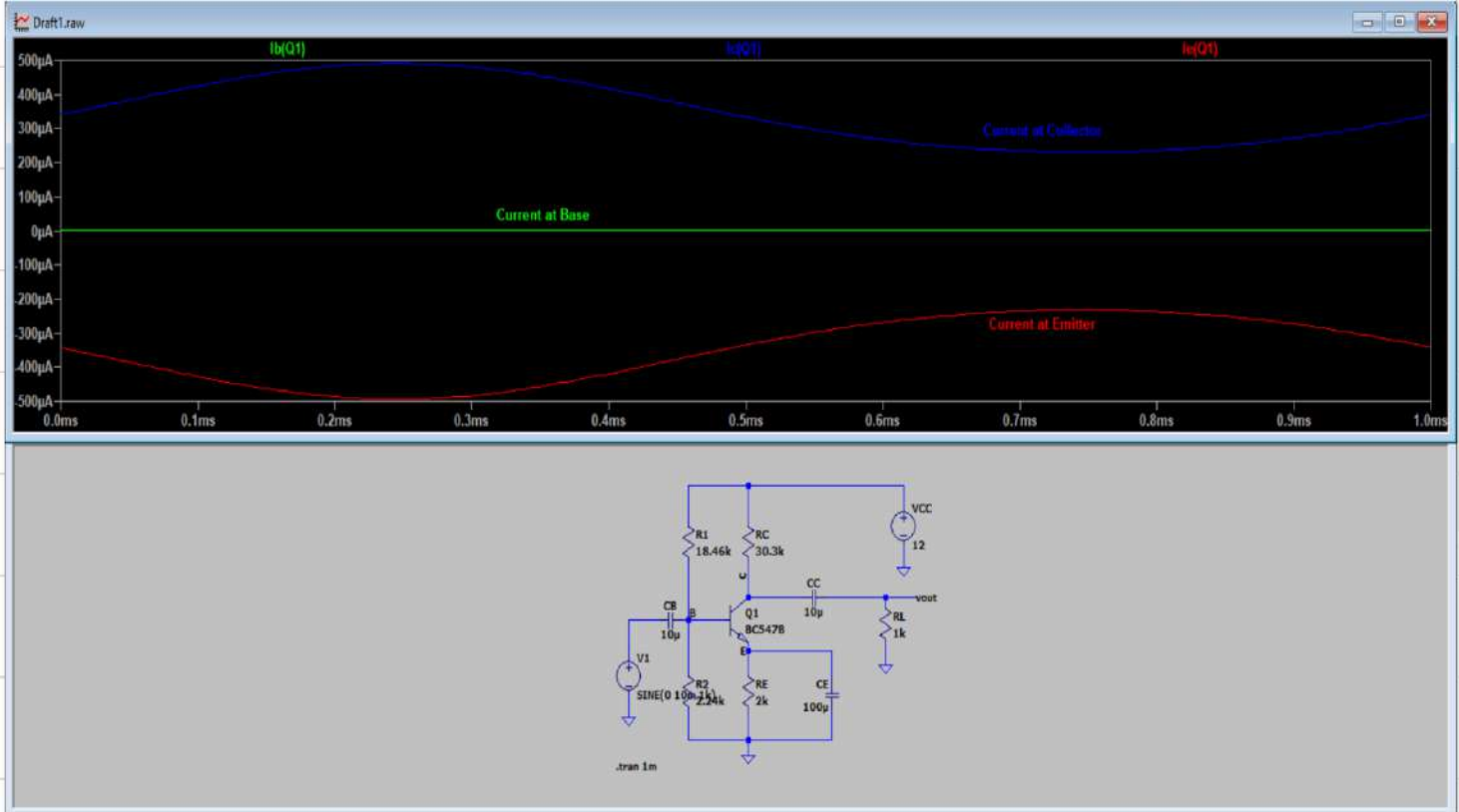

(a) DC Picture

When doing the DC analysis,

- All the AC voltage sources are shorted and all the AC current sources are opened.
- All the capacitors are open

Because : When a DC signal is sent in


$$\omega \rightarrow 0 \Rightarrow \frac{1}{\omega} \rightarrow \infty$$

$$X_c = \frac{1}{j\omega C} = \infty$$

Impedance of capacitor = ∞

\Rightarrow Open circuit

Large Signal Model

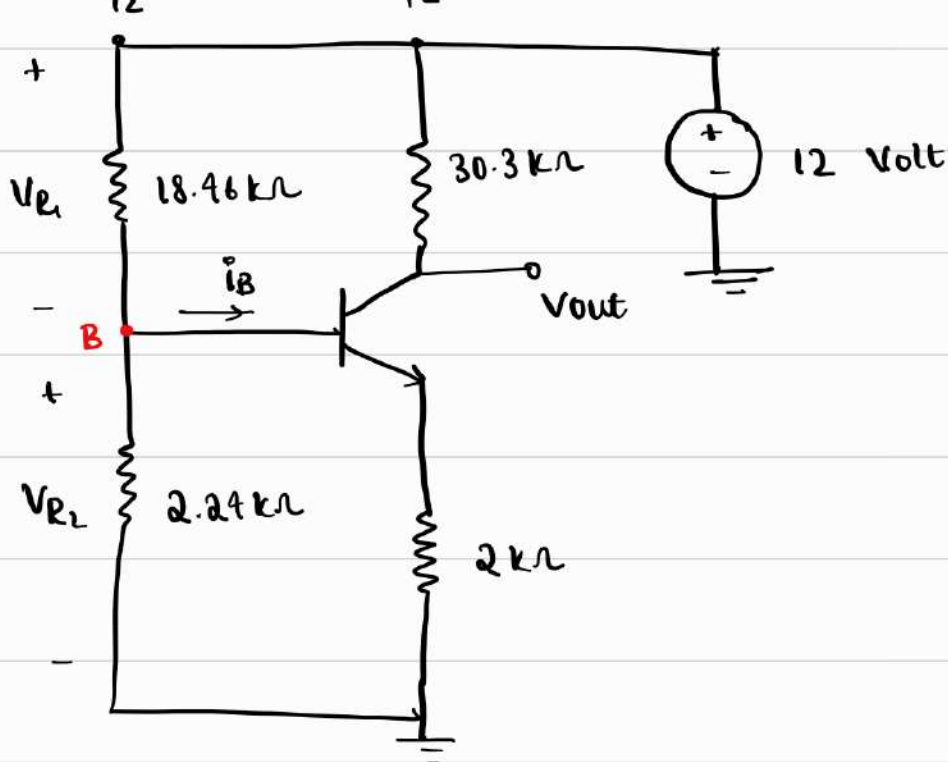

The value of i_B is very small.

Apply Voltage divider,

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$= \frac{2.24 \text{ k}}{2.24 \text{ k} + 18.46 \text{ k}} \times 12$$

$$= \frac{12 \times 2.24}{20.7}$$

$$\boxed{V_B = 1.2986 \text{ V}}$$

$$\frac{103.177}{9.288}$$

Given that , $V_{BE} = 0.7 \text{ V (fixed)}$

$$V_{BE} = V_B - V_E$$

$$V_E = 1.2986 - 0.7$$

$$\boxed{}$$

$$V_E = 0.5986 \text{ V}$$

$$I_E = \frac{V_E}{R_E} = \frac{0.5986 \text{ V}}{2 \text{ k}\Omega}$$

$$I_E = 0.2993 \text{ mA}$$

$$I_C = \frac{\beta}{1+\beta} I_E$$

From Q1 part c) the value of $\beta = 259.56$

$$I_C = \frac{259.56}{260.56} \times 0.2993 \text{ mA}$$

$$I_C = 0.298 \text{ mA}$$

We know that, $I_E = I_B + I_C$

$$\Rightarrow I_B = (0.2993 - 0.298) \text{ mA}$$


$$I_B = 0.0013 \text{ mA}$$

$$I_B = 1.3 \text{ }\mu\text{A}$$

$$V_C = V_{CC} - I_C R_C$$

$$= 12 - (0.298 \text{ mA})(30 \text{ k}\Omega)$$

$$V_c = 2.9706 \text{ V}$$

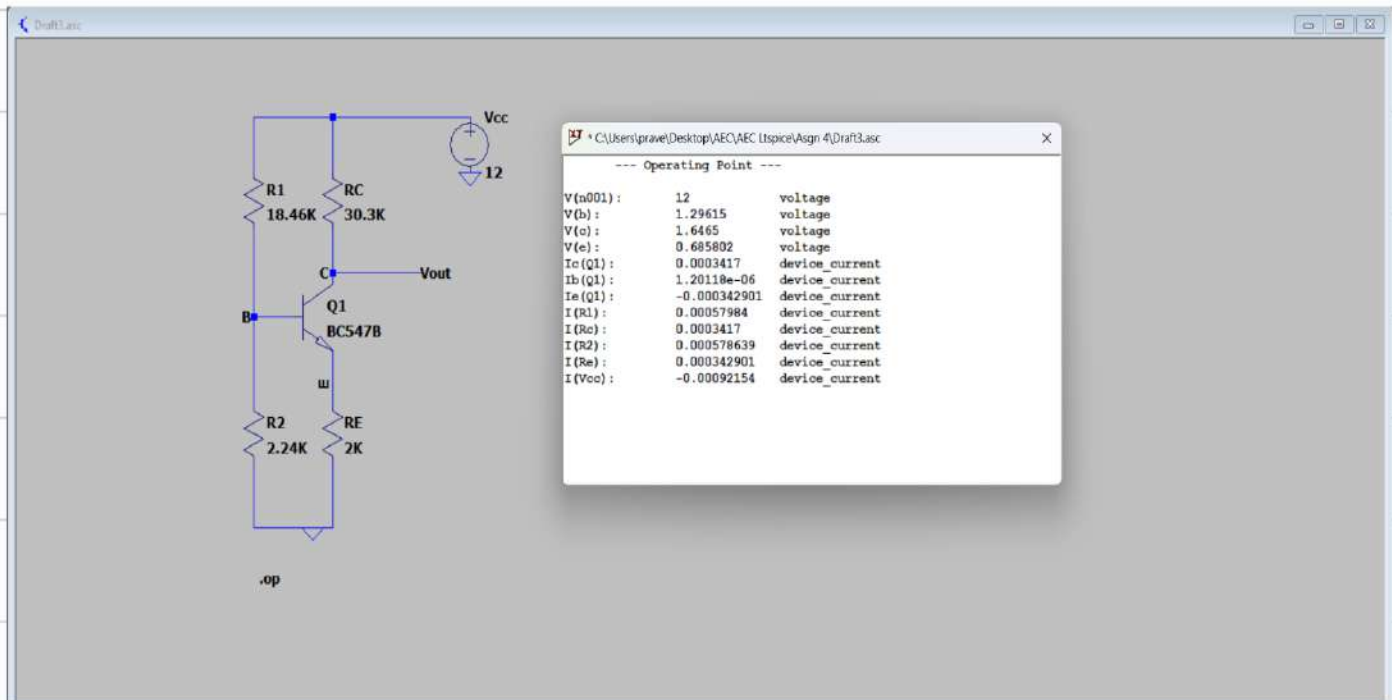

(b) Operation Point Simulation (.op)

	Theoretical Values	Simulated Values
V_b	1.2986 V	1.29615 V
V_c	2.9706 V	1.6465 V
V_e	0.5986 V	0.6858 V
I_b	1.3 μA	1.201 μA
I_c	298 μA	341.7 μA
I_e	299.3 μA	342.90 μA

(c) Calculation of small signal parameters

$$g_m = \frac{I_c}{V_T} = \frac{341.7 \times 10^{-6}}{25 \times 10^{-3}}$$

$$g_m = 0.013668$$

$$r_\pi = \frac{\beta}{g_m} = \frac{259.56}{0.013668} \quad 2k$$

$$r_\pi = 18.99 \text{ k}\Omega$$

$r_o \rightarrow$ arises due to the Early Voltage

$$r_o = \frac{V_A}{I_c} = \frac{54.67}{298 \times 10^{-6}} \quad 18.99k$$

$$r_o = 183.45 \text{ k}\Omega$$


\downarrow
Early resistance

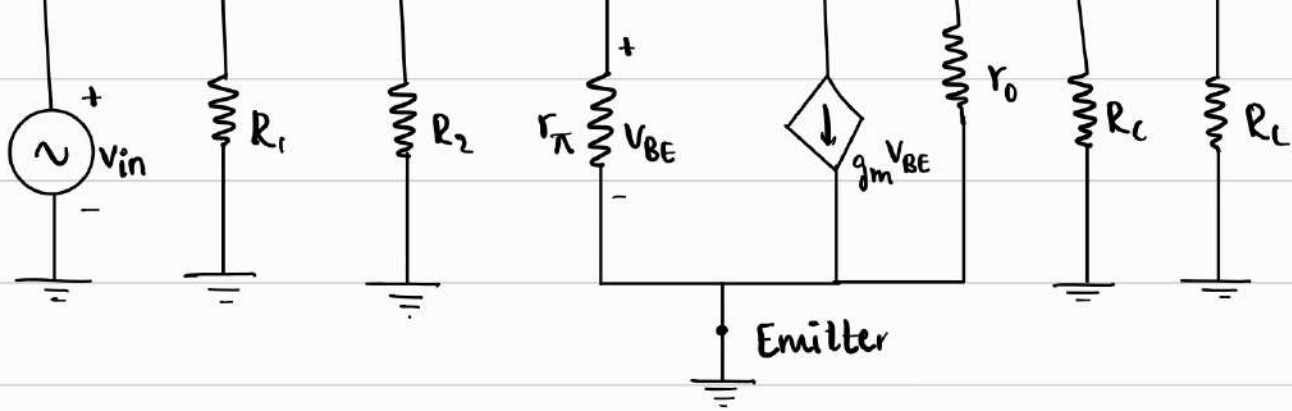(d) Small-signal Equivalent Circuit:

All the DC sources are replaced by their AC equivalents.

All the capacitors are shorted to allow the AC signal.





(e) Small Signal Voltage Gain :

$$V_{BE} = v_{in} \quad [\because R_1, R_2, r_{\pi} \text{ are all in parallel}]$$

Apply KVL at V_{out}

$$\frac{V_{out}}{R_L} + \frac{V_{out}}{R_c} + \frac{V_{out}}{r_o} + g_m V_{be} = 0$$

$$V_{out} \left[\frac{1}{R_L} + \frac{1}{R_c} + \frac{1}{r_o} \right] = -g_m V_{BE}$$

The value of r_o is very high when compared to R_L and R_c . Hence, we can neglect it.

$$\Rightarrow V_{out} = \left| \frac{-g_m v_{in}}{\left(\frac{1}{R_L} + \frac{1}{R_c} \right)} \right|$$


$$\frac{V_{out}}{V_{in}} = \left| -g_m \times \frac{R_c R_L}{(R_c + R_L)} \right|$$

$$= 0.013668 \times \left(\frac{30.3k \times 1k}{1 + 30.8k} \right)$$

$$= 0.013668 \times 968.0512$$

$$A_v = \frac{V_{out}}{V_{in}} = 13.231$$

(f) V_{in} and V_{out}

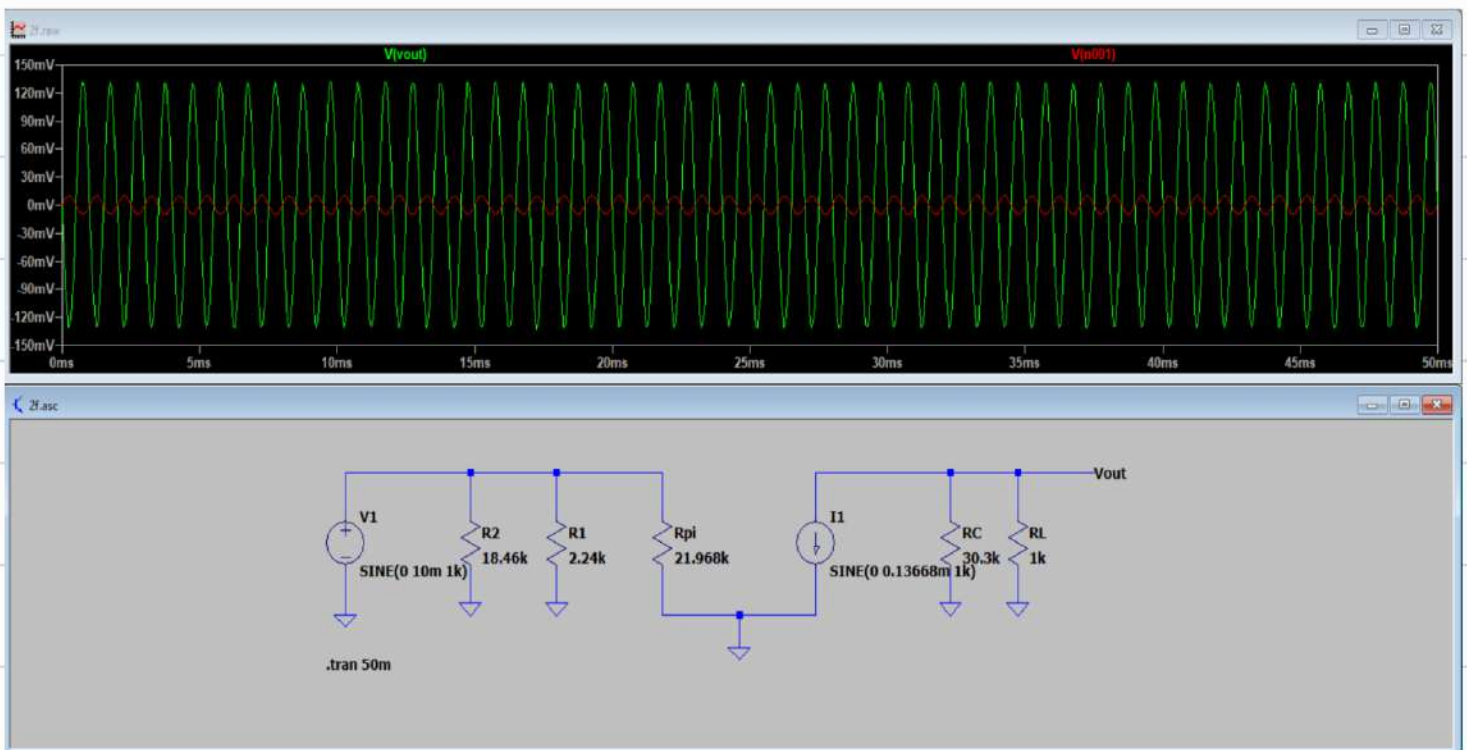

In the above plot, V_{pp} of $V_{out} = 131.580 \text{ mV}$

From the given inQ, V_{pp} of $V_{in} = 10 \text{ mV}$


$$\text{Gain} = \frac{V_{out}}{V_{in}} = \frac{131.580 \text{ m}}{10 \text{ m}}$$

$$\text{Gain} = 13.158$$


The gain calculated in the previous part = 13.231
which is almost similar.

(g) Fundamental frequency, $f_0 = 1\text{kHz}$


1st Harmonic

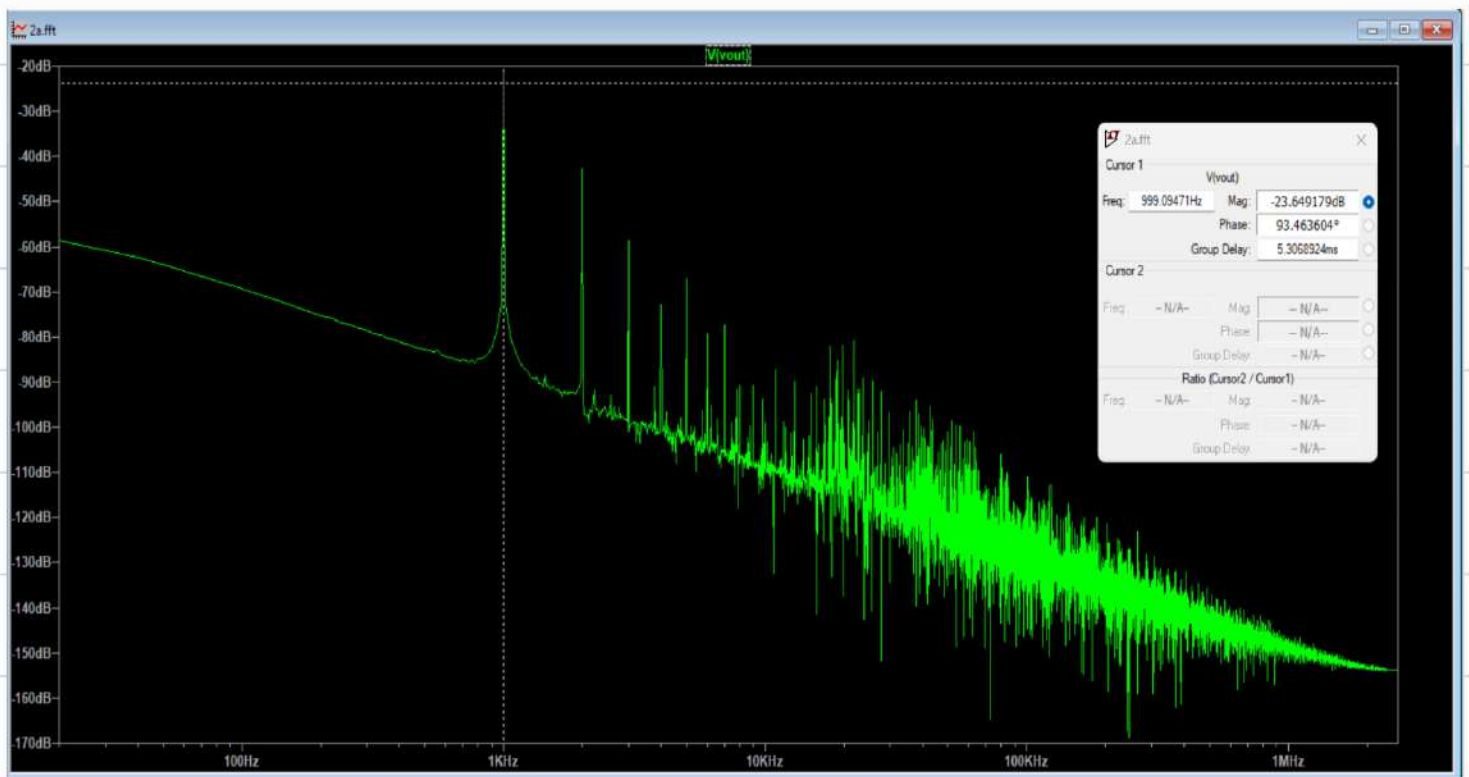


2nd Harmonic

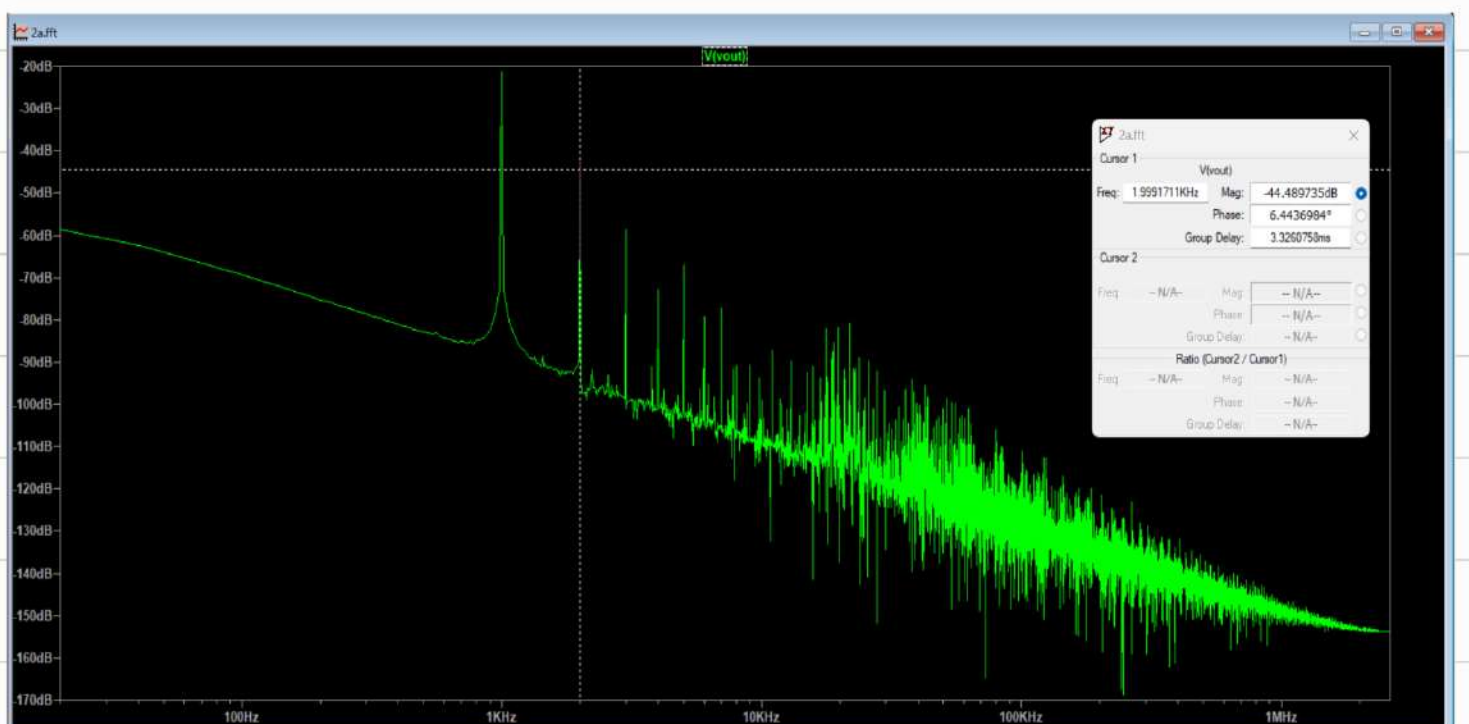

3rd Harmonic

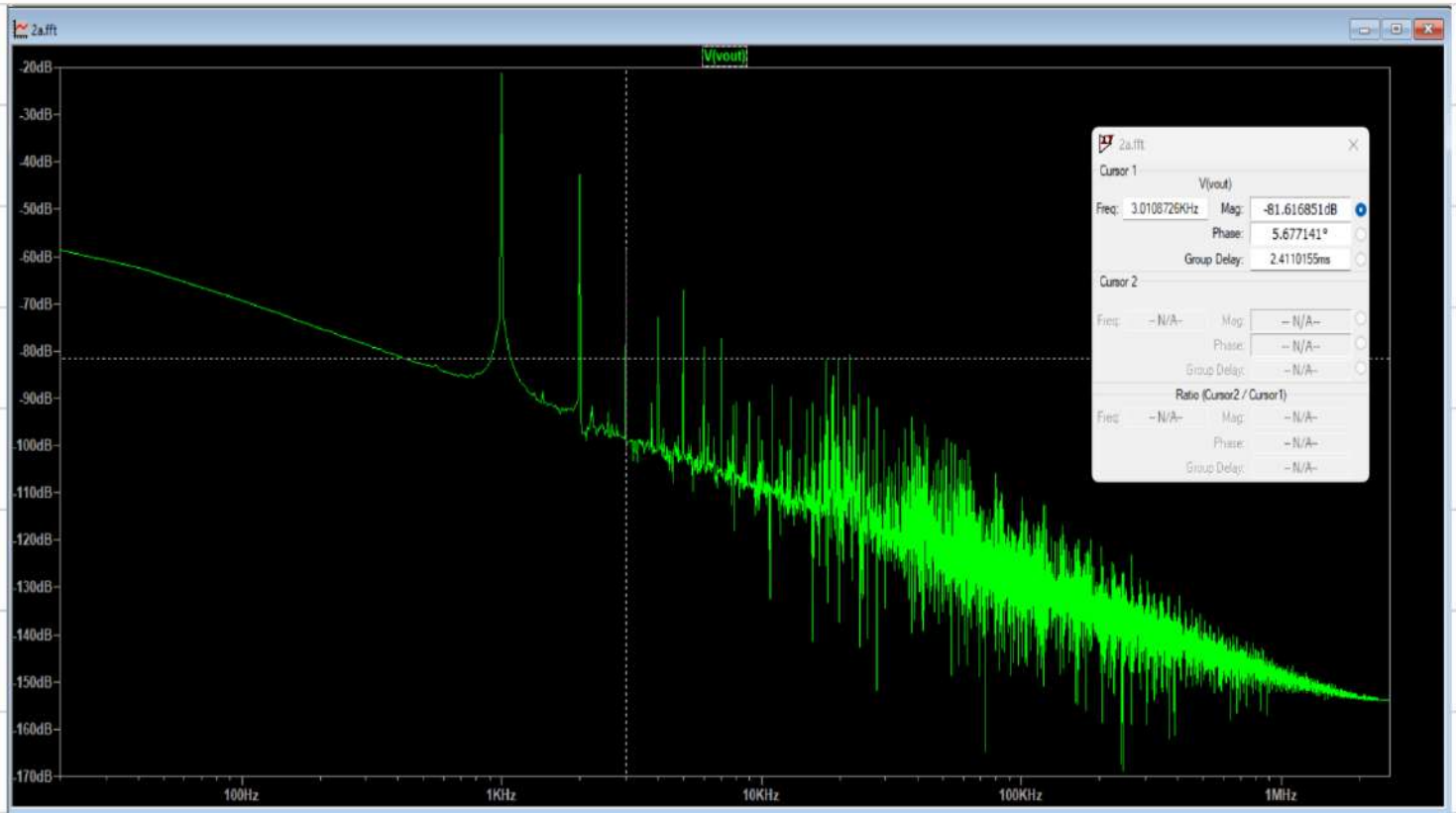

4th Harmonic

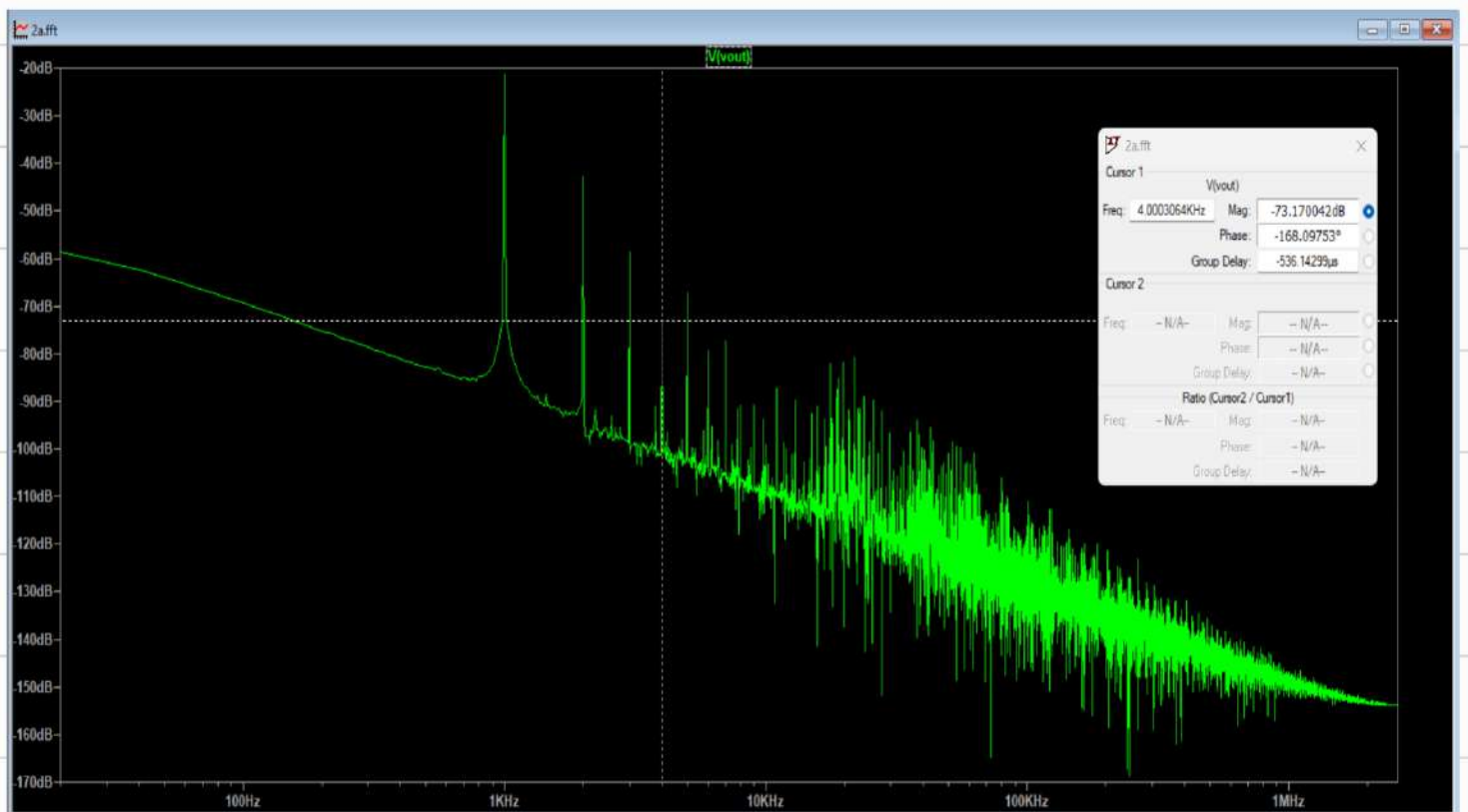



From the data in the photos,


Difference can be reported.

Magnitude of 1st Harmonic = -23.649 dB

Harmonic	Frequency	Difference
2nd	1.99 kHz	$= -44.84 - (-23.649) = -21.191$
3rd	3.01 kHz	$= -61.616 - (-23.649) = -37.967$
4th	4.00 kHz	$= -73.170 - (-23.649) = -49.521$

(h) Total Harmonic Distribution (THD)

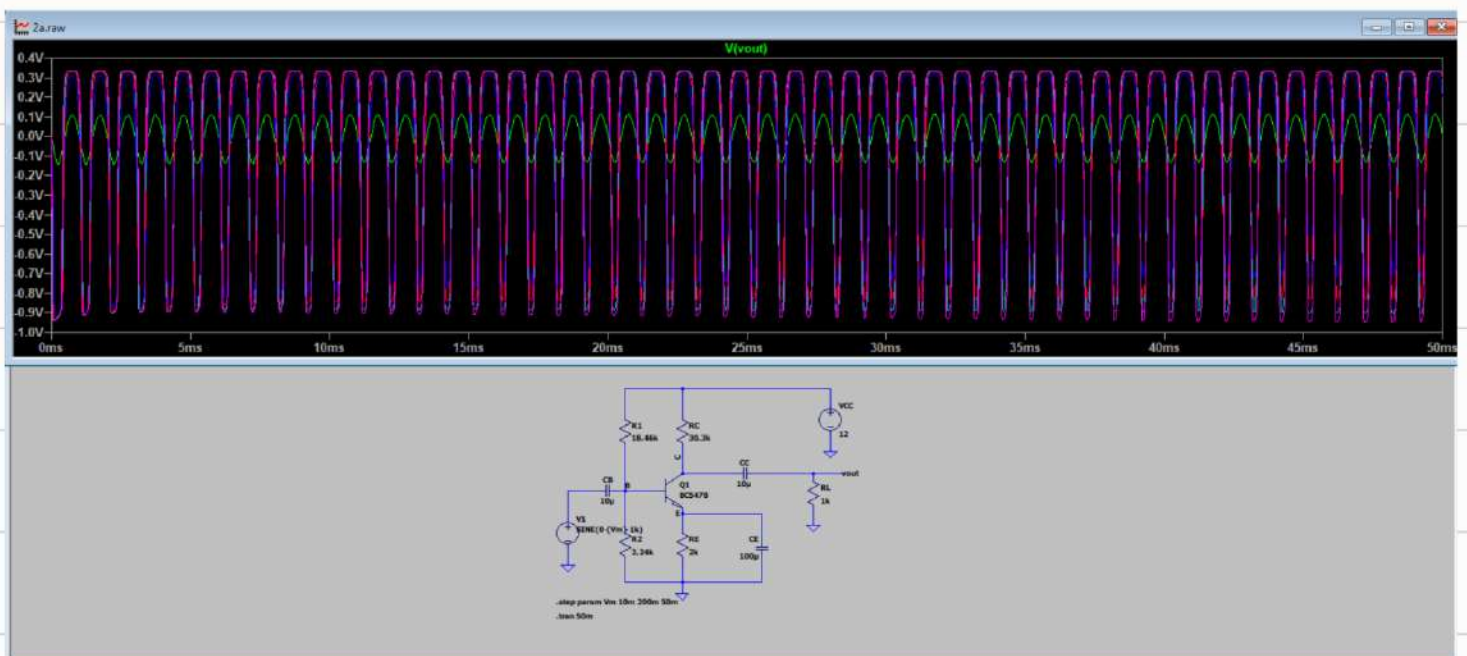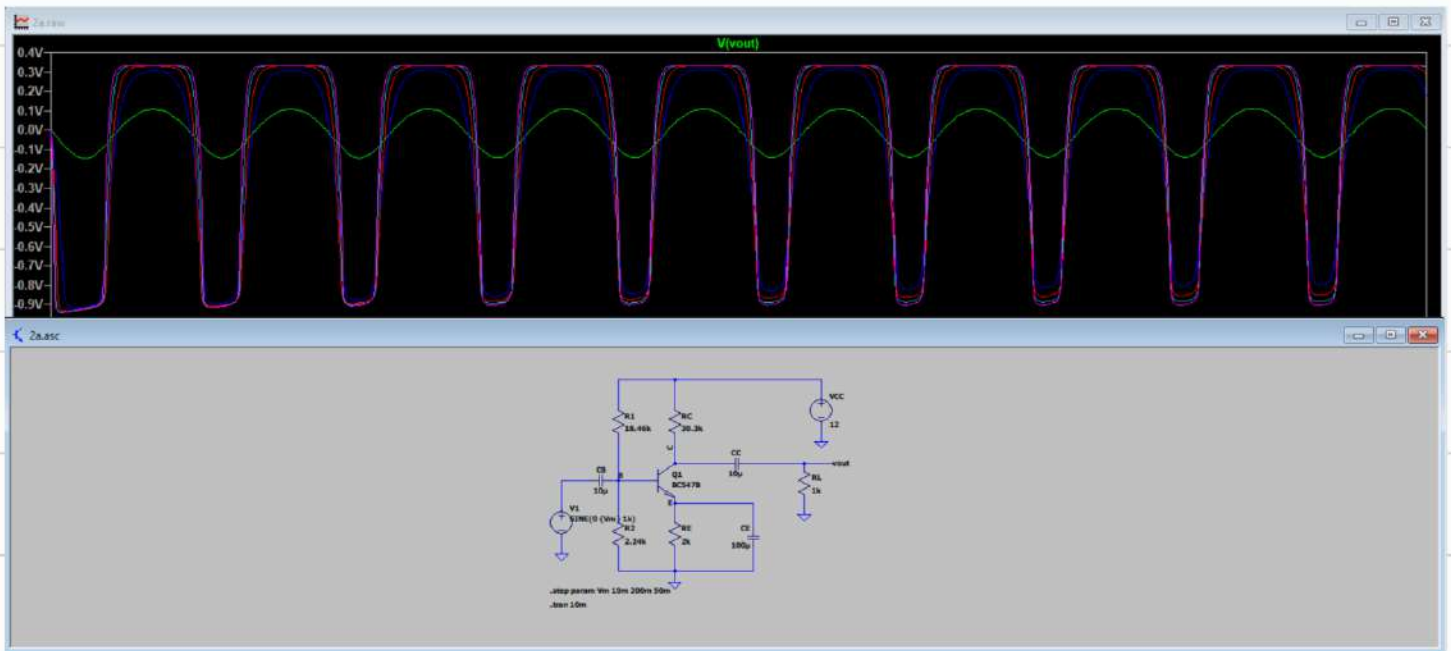

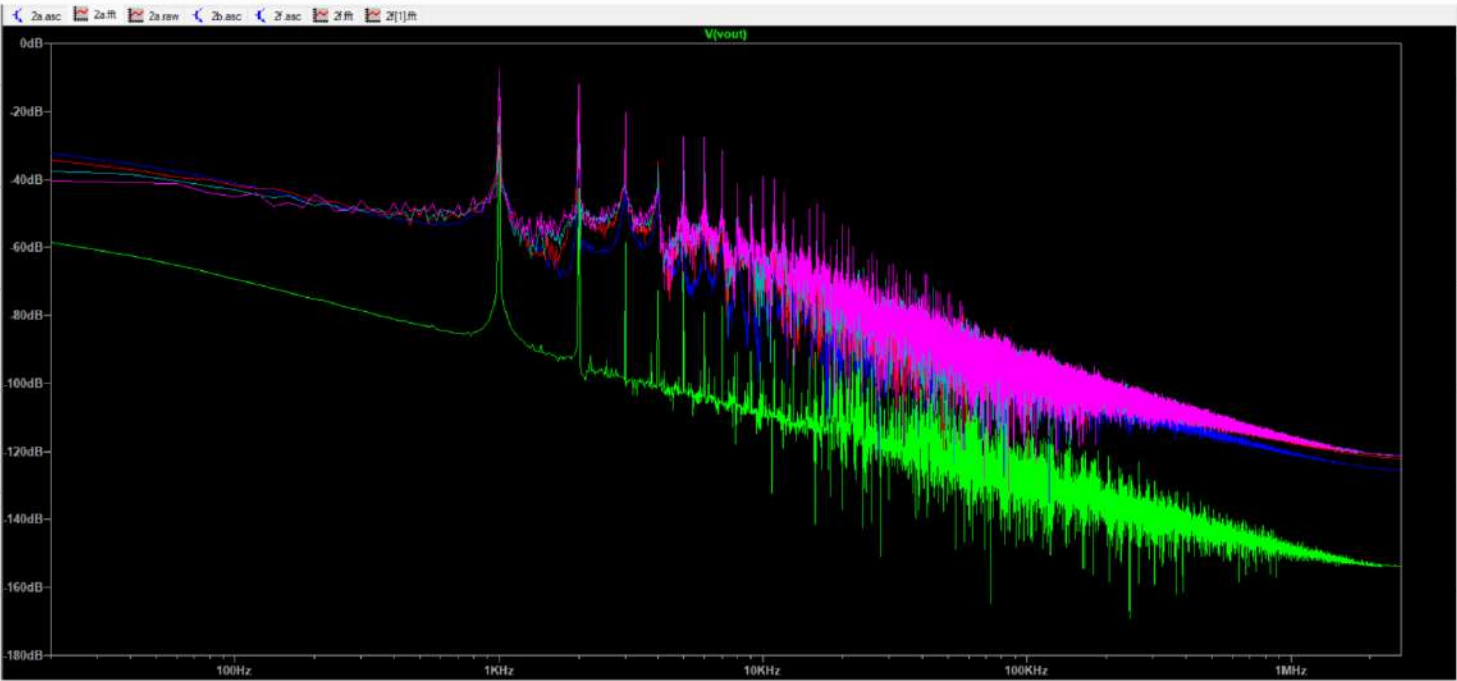

```
.step vm=0.06
N-Period=10
Fourier components of V(vout)
DC component:-0.0127641
```

Harmonic Number	Frequency [Hz]	Fourier Component	Normalized Component
1	1.000e+3	4.943e-1	1.000e+0
2	2.000e+3	2.039e-1	4.124e-1
3	3.000e+3	4.950e-2	1.001e-1
4	4.000e+3	8.030e-4	1.624e-3
5	5.000e+3	1.181e-2	2.390e-2
6	6.000e+3	1.273e-2	2.575e-2
7	7.000e+3	1.044e-2	2.112e-2
8	8.000e+3	6.900e-3	1.396e-2
9	9.000e+3	3.526e-3	7.133e-3
10	1.000e+4	1.203e-3	2.434e-3

Partial Harmonic Distortion: 42.668874%
Total Harmonic Distortion: 42.675338%

```
.step vm=0.11
N-Period=10
Fourier components of V(vout)
DC component:-0.00181328
```

Harmonic Number	Frequency [Hz]	Fourier Component	Normalized Component
1	1.000e+3	5.434e-1	1.000e+0
2	2.000e+3	2.843e-1	5.232e-1
3	3.000e+3	7.932e-2	1.460e-1
4	4.000e+3	1.350e-2	2.485e-2
5	5.000e+3	3.184e-2	5.859e-2
6	6.000e+3	2.332e-2	4.292e-2
7	7.000e+3	1.205e-2	2.217e-2
8	8.000e+3	4.514e-3	8.307e-3
9	9.000e+3	5.938e-4	1.093e-3
10	1.000e+4	1.495e-3	2.751e-3

Partial Harmonic Distortion: 54.908886%
Total Harmonic Distortion: 54.951963%

```
.step vm=0.01
N-Period=10
Fourier components of V(vout)
DC component:-0.000430312
```

Harmonic Number	Frequency [Hz]	Fourier Component	Normalized Component
1	1.000e+3	1.207e-1	1.000e+0
2	2.000e+3	1.047e-2	8.679e-2
3	3.000e+3	1.683e-3	1.395e-2
4	4.000e+3	3.284e-4	2.721e-3
5	5.000e+3	6.192e-4	5.131e-3
6	6.000e+3	1.621e-4	1.343e-3
7	7.000e+3	2.011e-4	1.666e-3
8	8.000e+3	4.755e-5	3.940e-4
9	9.000e+3	4.218e-5	3.495e-4
10	1.000e+4	1.813e-5	1.502e-4

Partial Harmonic Distortion: 8.812570%
Total Harmonic Distortion: 8.817012%

```
.step vm=0.16
N-Period=10
Fourier components of V(vout)
DC component:0.00275325
```

Harmonic Number	Frequency [Hz]	Fourier Component	Normalized Component
1	1.000e+3	5.596e-1	1.000e+0
2	2.000e+3	3.365e-1	6.014e-1
3	3.000e+3	1.215e-1	2.171e-1
4	4.000e+3	8.389e-3	1.499e-2
5	5.000e+3	5.026e-2	8.981e-2
6	6.000e+3	4.620e-2	8.256e-2
7	7.000e+3	2.731e-2	4.880e-2
8	8.000e+3	9.532e-3	1.703e-2
9	9.000e+3	4.315e-3	7.711e-3
10	1.000e+4	9.168e-3	1.638e-2

Partial Harmonic Distortion: 65.340304%

Total Harmonic Distortion: 65.649412%

```
.step vm=0.2
N-Period=10
Fourier components of V(vout)
DC component:0.00399901
```

Harmonic Number	Frequency [Hz]	Fourier Component	Normalized Component
1	1.000e+3	5.683e-1	1.000e+0
2	2.000e+3	3.672e-1	6.463e-1
3	3.000e+3	1.533e-1	2.699e-1
4	4.000e+3	7.492e-3	1.318e-2
5	5.000e+3	6.157e-2	1.084e-1
6	6.000e+3	6.791e-2	1.195e-1
7	7.000e+3	4.597e-2	8.089e-2
8	8.000e+3	1.793e-2	3.156e-2
9	9.000e+3	6.551e-3	1.153e-2
10	1.000e+4	1.809e-2	3.183e-2

Partial Harmonic Distortion: 72.482836%

Total Harmonic Distortion: 72.849067%


V_m	THD
0.01	8.817012 %
0.06	42.675338 %
0.11	54.951963 %
0.16	65.649412 %
0.2	72.849067 %

Yes, with increase in the value of V_m , there is also an increase in the THD.

There are also a few unwanted harmonics and distortions present in the signal.

→ As V_m increases, the value of output increases; that is, THD is directly proportional to the output of circuit. Thus we observed increasing values of THD's when V_m increases.


(i) AC Analysis and DC Gain

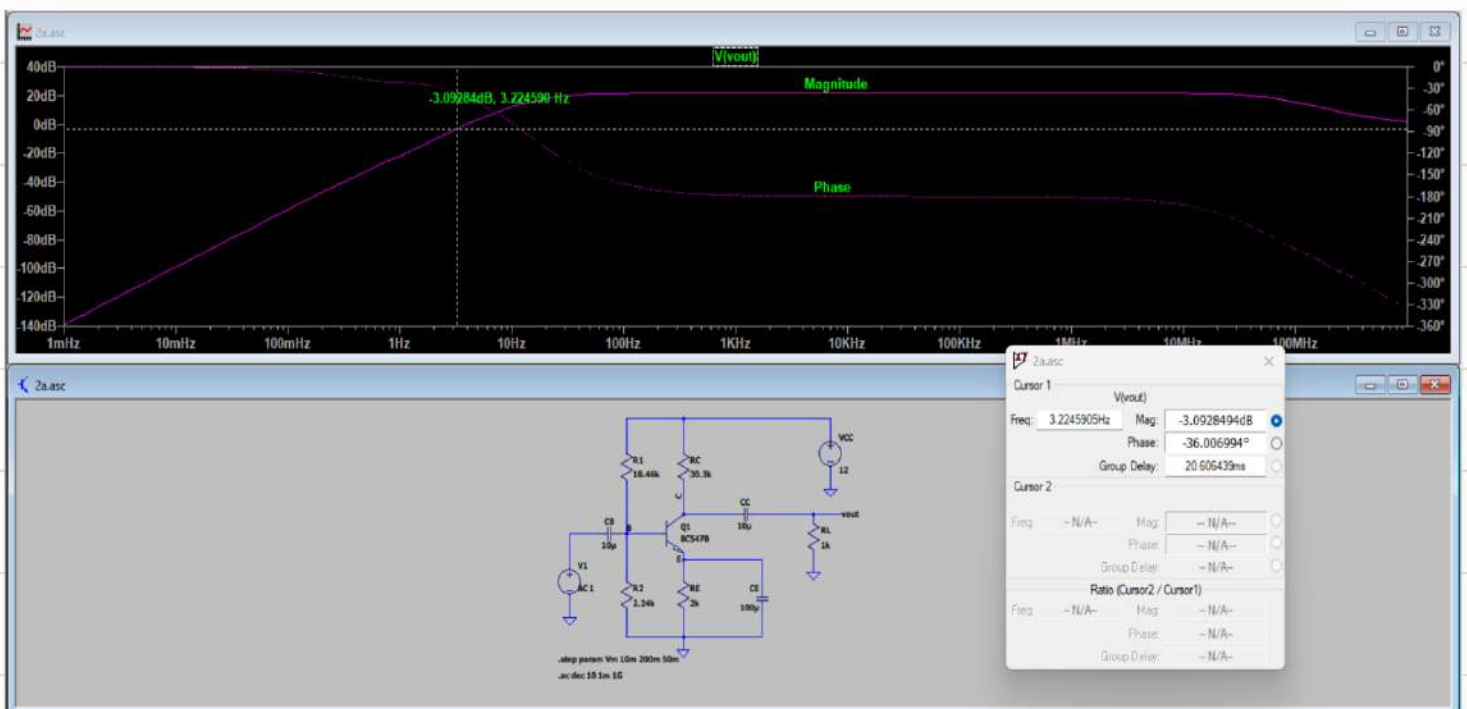

The -3dB bandwidth is obtained at
at a frequency = 3.224590 Hz

Maximum gain is obtained at 21.393612 dB

(j) DC gain for different values of R_c

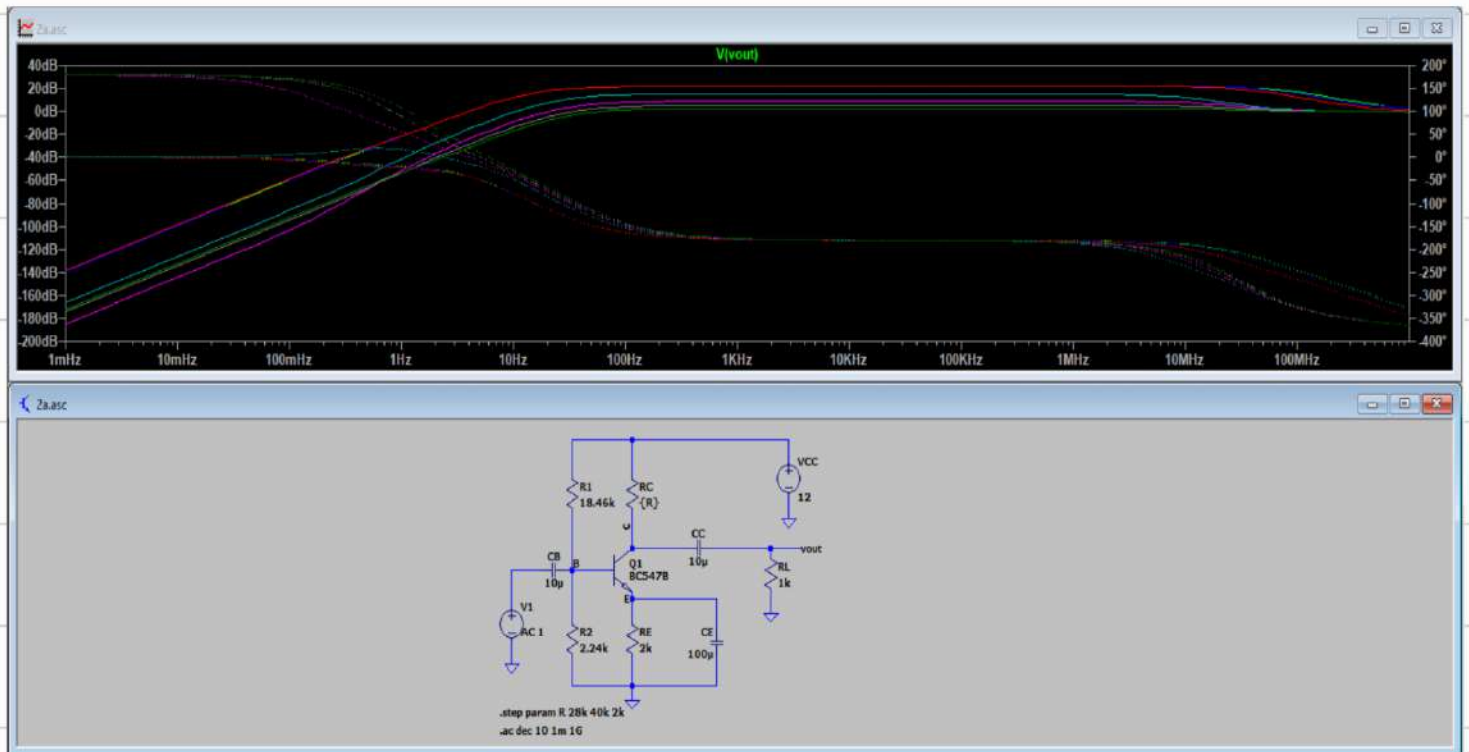

R_c	DC Gain
28 k Ω	21.913622 dB
30 k Ω	21.928602 dB
32 k Ω	21.940915 dB
34 k Ω	15.007594 dB
36 k Ω	8.7741936 dB
38 k Ω	5.0444321 dB
40 k Ω	2.3946224 dB

Comparison :

DC gain for $R = 30k\Omega$ is 21.929 dB

DC gain for $R = 40k\Omega$ is 2.394 dB

Justification:

As the value of R_c increases, then the output impedance increases accordingly.

Then the gain decreases.

Question 3 : Designing an Amplifier

Given that, $R_i = 1k\Omega$

$$V_{CC} = 5 \text{ Volts}$$


$$A_v = 12.231 \text{ (from prev Q)}$$


$$\text{Bandwidth} = 17 \text{ Hz (from previous problem)}$$

We need to find,

$$C_B, C_c, C_E, R_i, R_z, R_E, R_c, I_c, I_B$$

Large Signal Model

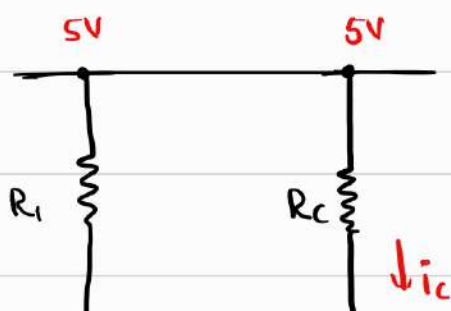

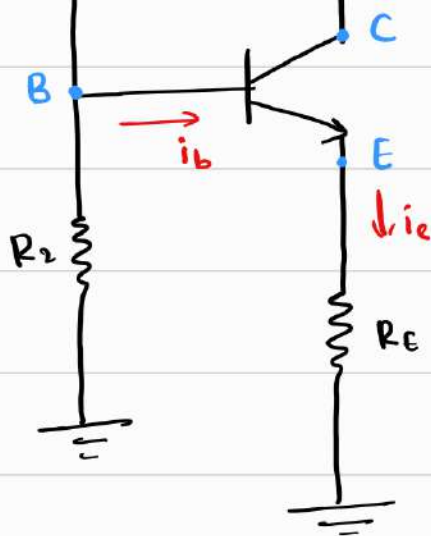

Consider the following assumptions :

Let, $I_C = 3 \text{ mA}$

$$V_{CE} = \frac{V_{CC}}{2} = 2.5 \text{ V}$$

we know that,

$$\text{gain} = A_v = 13.231$$

$$A_v = g_m (R_L || R_C) = 13.231$$

$$\frac{I_C}{V_T} \left(\frac{R_L \cdot R_C}{R_C + R_C} \right) = 13.231$$

$$\frac{1k \cdot R_C}{1000 + R_C} = \frac{13.231 \times 25 \times 10^3}{3 \times 10^3}$$

$$\frac{R_C}{1000 + R_C} = 110.25 \text{ m}$$

$$1 + \frac{1000}{R_C} = \frac{1000}{110.25}$$



$$R_c = 123.91 \, \Omega$$

$$I_B = \frac{I_c}{\beta} = \frac{3m}{259.56}$$

$$I_B = 11.55 \, \mu A$$

$$I_E = I_c + I_B$$

$$= 3mA + 11.55 \, \mu A$$

$$I_E = 3.0115 \, mA$$

Apply KVL on right half of circuit, i.e from collector to the emitter

$$5 - I_c R_c - V_{CE} - I_E R_E = 0$$

$$5 = 371.73 \times 10^{-3} + 2.5 + (3.0115 \times 10^{-3}) R_E$$

$$R_E = 706.71 \, \Omega$$

$$V_E = I_E R_E$$

$$V_E = 2.128 \, V$$

$$V_B = V_{BE} + V_E$$

$$= 0.7 + 2.128$$

$$[\because V_{BE} = 0.7V \text{ given standard}]$$

$$V_B = 2.828 \, V$$

$$V_B = 2.828 \text{ V}$$

Let us also assume

$$R_1 = 700 \, \Omega$$

$$\text{Then, } V_B = \frac{R_2}{R_1 + R_2} \times V_{CC}$$

$$2.828 = \frac{R_2}{700 + R_2} \times 5$$

$$0.768$$


$$1 + \frac{700}{R_2} = \frac{5}{2.828}$$

$$\Rightarrow R_2 = 911.458 \, \Omega$$

$$r_\pi = \frac{\beta}{g_m}$$

$$= \frac{\beta V_T}{I_C} = \frac{259.56 \times 25 \text{ mV}}{3 \text{ mA}}$$

$$r_\pi = 2.163 \text{ k}\Omega$$

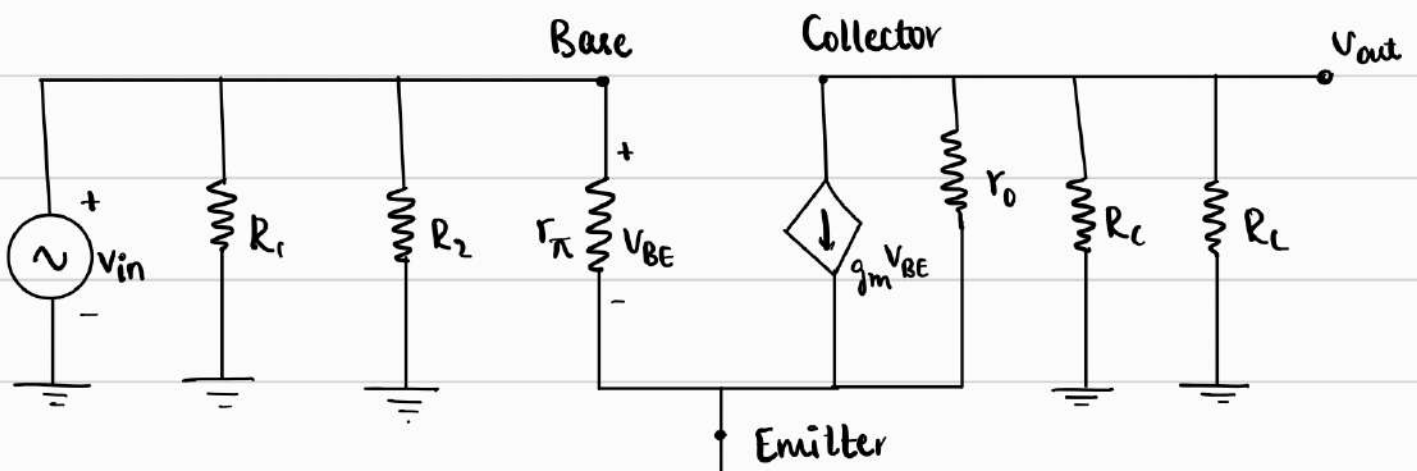

At the input,

let $z_{in} \rightarrow$ input impedance

$$z_{in} = [R_1 \parallel R_2 \parallel r_{\pi}]$$

$$z_{in} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{r_{\pi}}}$$
$$= \frac{1}{0.002556}$$

$$z_{in} = 391.236 \Omega$$

Since bandwidth in prev & new prob are the same

$$\frac{1}{2\pi z_{in} C_{new}} = \frac{1}{2\pi R_{in} C_{old}}$$

$$C_{B_{new}} = \frac{R_{in} \times C_{old}}{z_{in}}$$

$$= \frac{1803.98 \times 10 \times 10^{-6}}{391.236}$$

R_{in} - input
impedance
in prev prob

$$C_B = 46 \mu F$$

Similarly,

$Z_{out} \rightarrow$ Output Impedance
at C_c

$$Z_{out} = R_c \parallel R_L$$

$$Z_{out} = 110.24$$

$R_{out} \rightarrow$ Output
impedance
in prev

$$\frac{1}{2\pi Z_{out} C_c} = \frac{1}{2\pi R_{out} C_{old}}$$

$$Z_{out} = \frac{968.05 \times 10 \mu}{110.24}$$

$$Z_{out} = 87.80 \times \mu$$

$$C_c = 87.8 \mu F$$

At the emitter,

Let $Z_e \rightarrow$ emitter impedance

$$\frac{1}{Z_e} = \frac{1}{R_e} + \frac{\beta+1}{r_{\pi}}$$

5552.23

$$Z_E = R_E \parallel \frac{r_\pi}{\beta + 1}$$

$$= \frac{706.71 \times 8.301}{715.011}$$

$$\boxed{Z_E = 8.204}$$

$$\frac{1}{Z_E C_{new}} = \frac{1}{R_{old} C_{old}}$$

$R_{old} = \text{Impedance at emitter in c2)}$

$$= 70.375 \Omega$$

$$Z_E = \frac{100 \mu F \times 70.375}{8.204}$$

$$\boxed{C_E = 85.81 \mu F}$$

∴ The required values are

$$C_B = 46 \mu F$$

$$C_C = 87.8 \mu F$$

$$C_E = 85.81 \mu F$$

$$R_1 = 700 \Omega$$

$$R_2 = 911.452 \Omega$$

$$R_E = 706.71$$

$$I_C = 3 \text{ mA}$$

$$R_C = 123.91 \Omega$$

$$I_B = 11.55 \mu\text{A}$$

Gain in the New Circuit:

$$V_{in}(\text{max}) = 9.9823 \text{ mV}$$

$$V_{out}(\text{max}) = 131.566 \text{ mV}$$

$$\text{Gain}_{\text{new}} = \frac{131.566}{9.9823} = 13.179 \text{ — Experimental}$$

$$\text{Gain}_{\text{theoretical}} = g_m (R_C \parallel R_L) = \frac{I_C}{V_T} (R_C \parallel R_L)$$

$$= \frac{3 \text{ mA}}{25 \text{ mV}} (110.189) = 13.22 \text{ — Theoretical}$$

DC Power Consumption :

$$\text{At } V_C = 5\text{V}$$

$$I_{\text{drawn}} = 6.1986 \text{ mA}$$

$$\text{Power} = V_C \times I_{\text{drawn}}$$

$$= 30.993 \text{ mW}$$


$$\text{At } V_c = 12\text{V}$$

$$I_{\text{drawn}} = 0.9219\text{ mA}$$


$$\begin{aligned} \text{Power} &= V_c \times I_{\text{drawn}} \\ &= 11.0628\text{ mW} \end{aligned}$$


V_{cc}	I_{drawn}	P_{DC}
12V	0.9219 mA	11.0628 mW
5V	6.1986 mA	30.993 mW

V_{out}

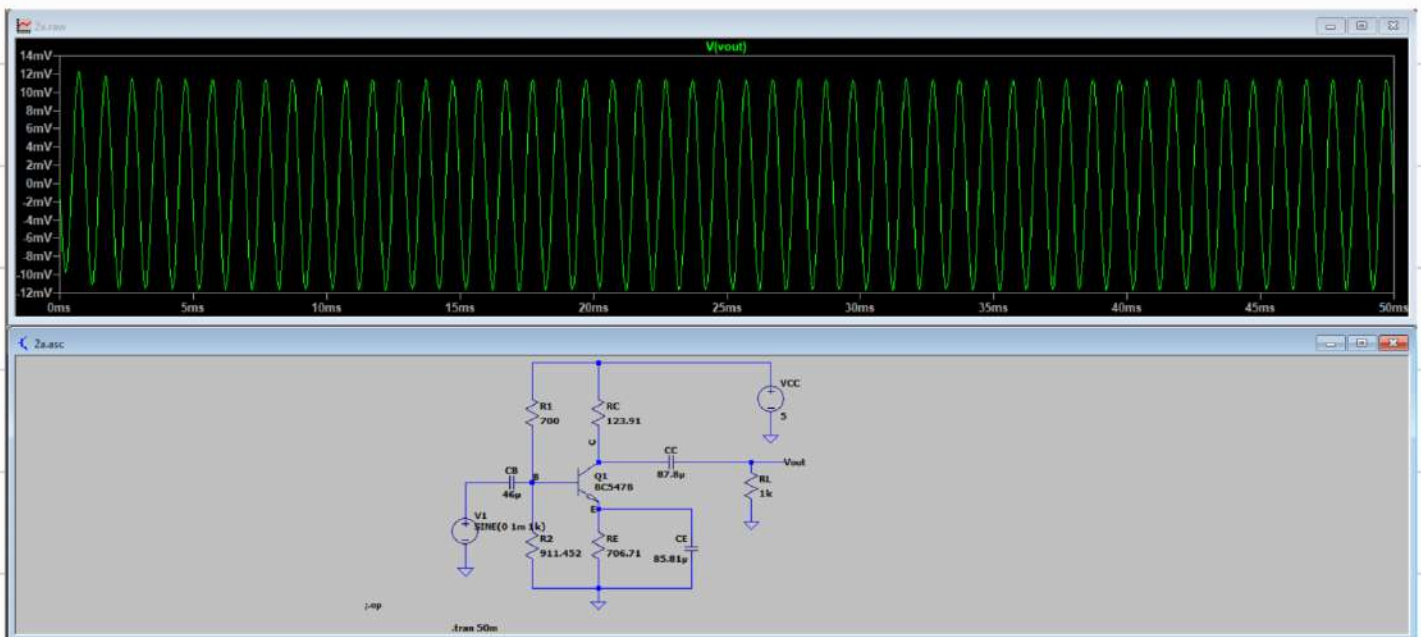


The New Designed Circuit

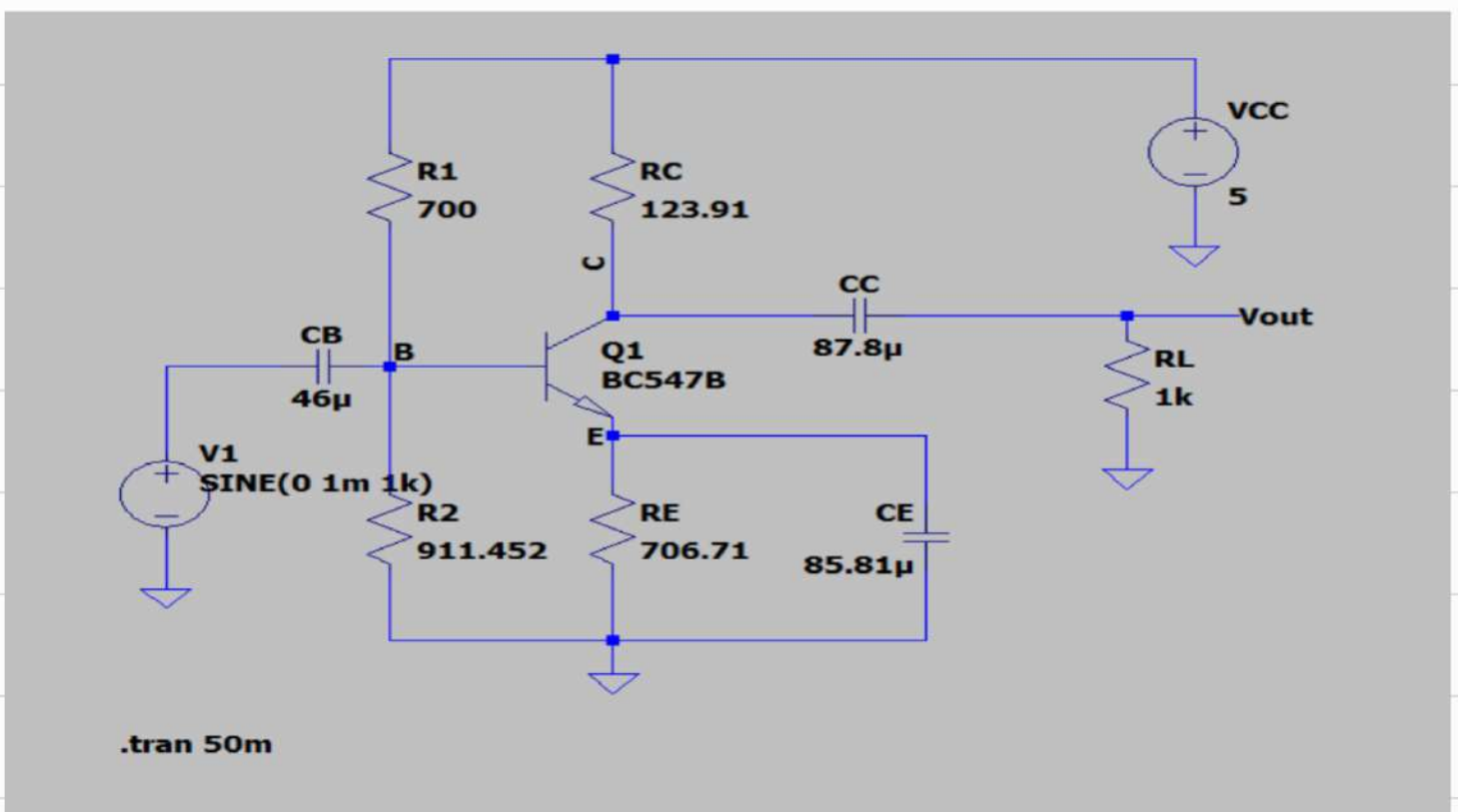


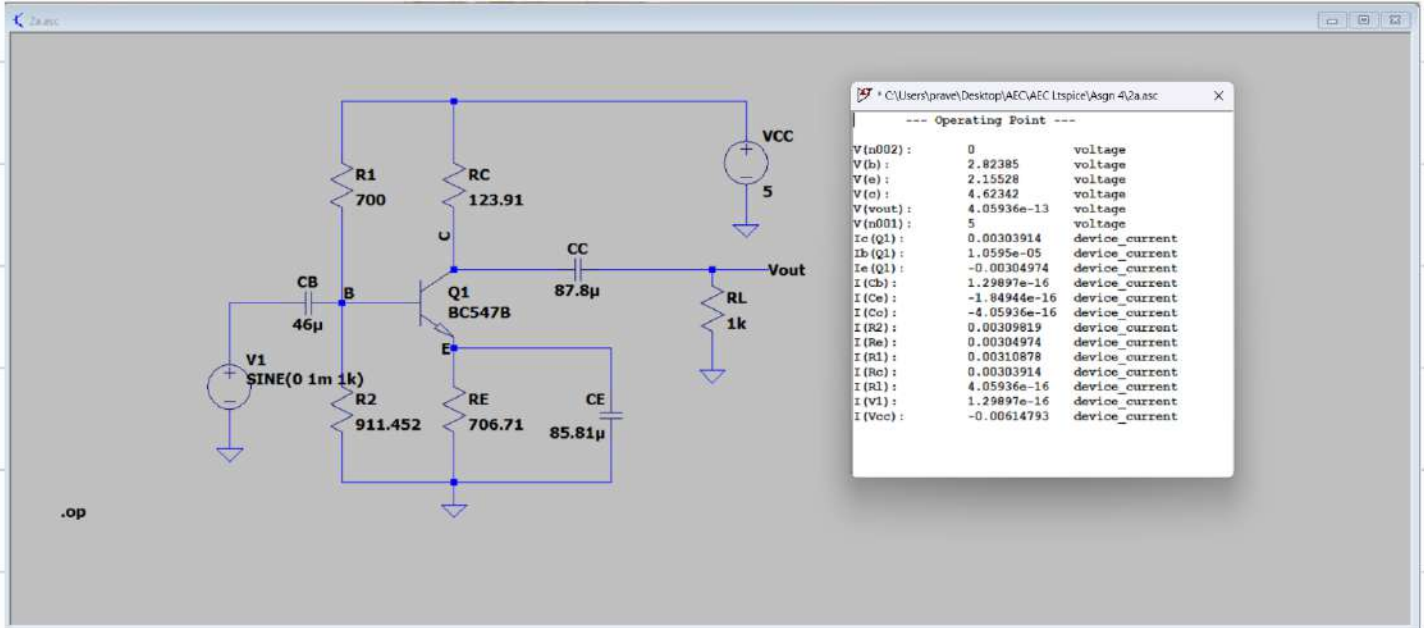


FFT :

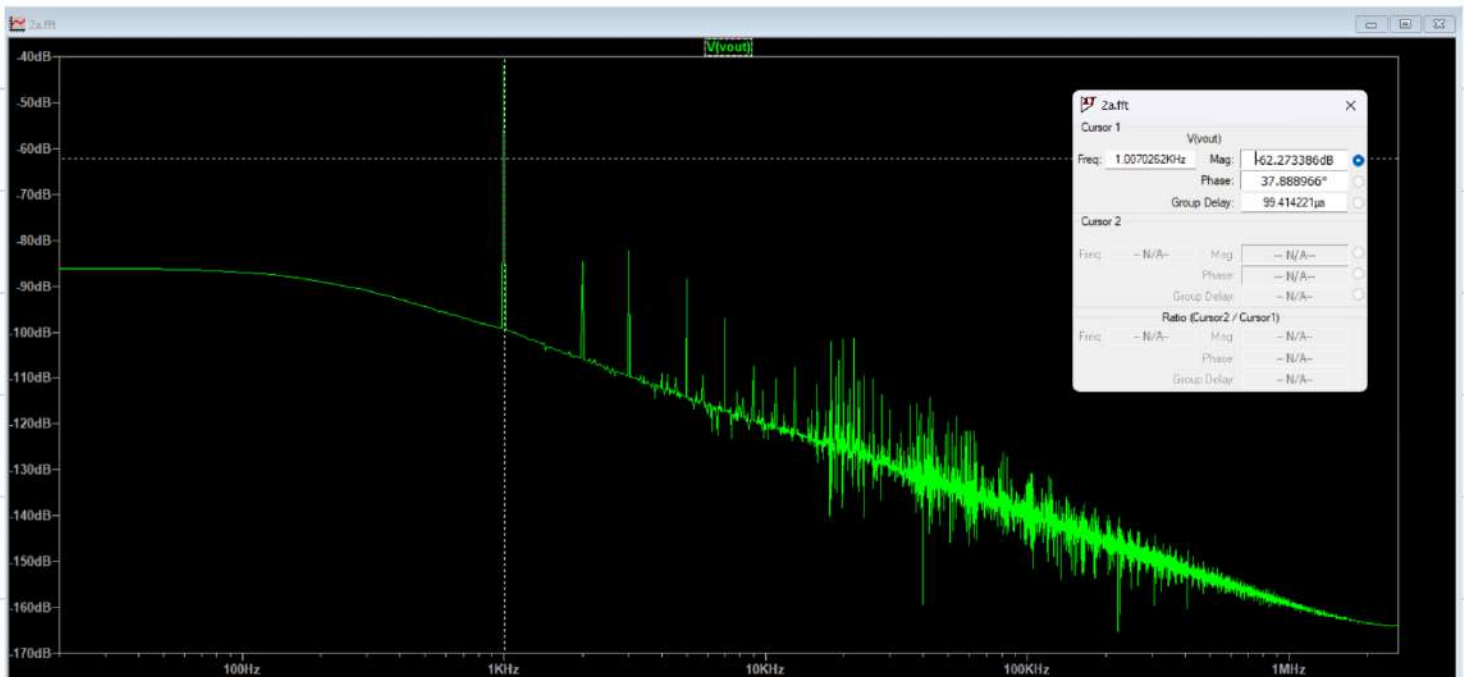

Vout and Vin

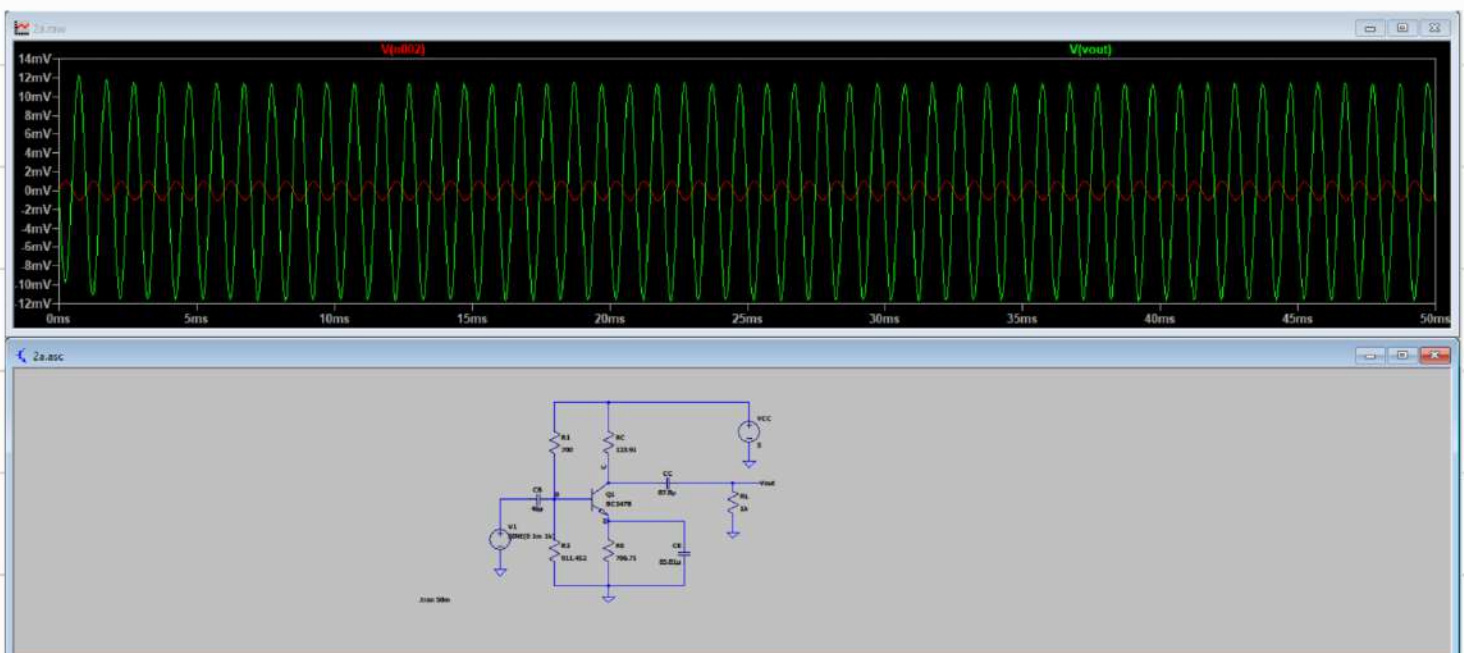

Bode Plot

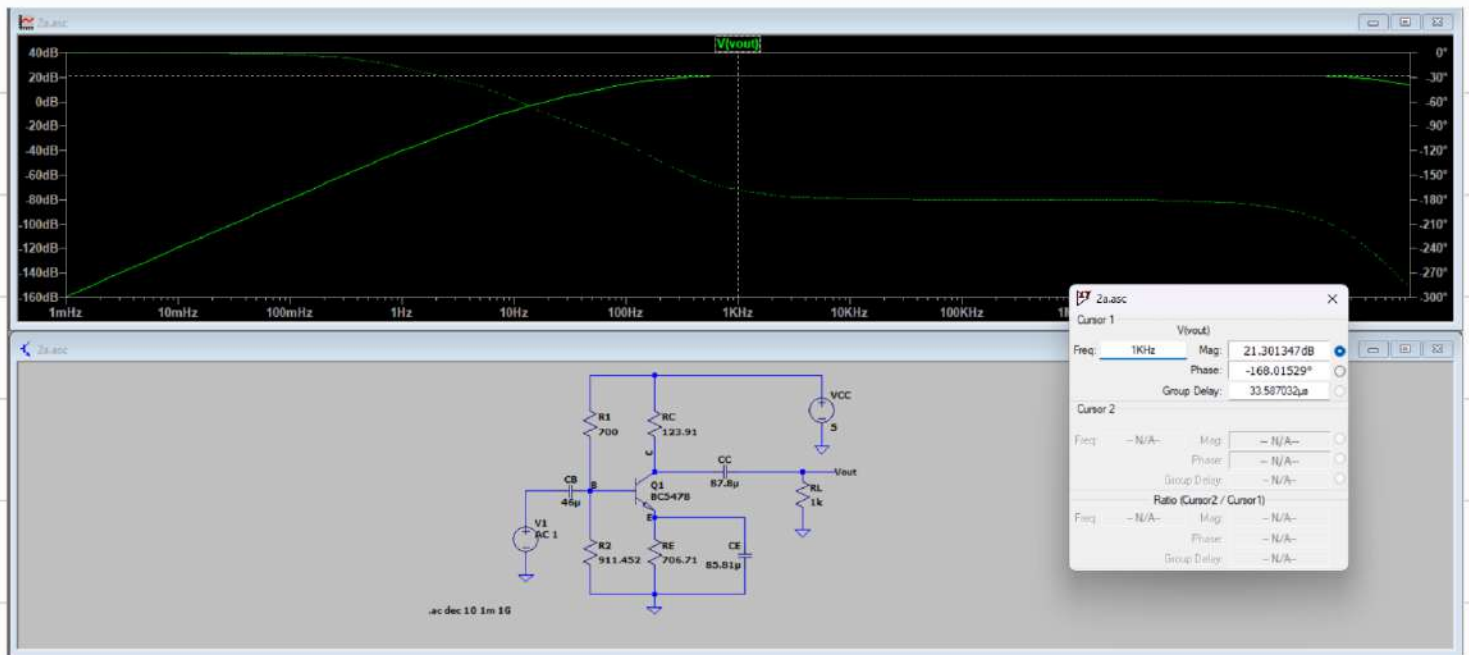

-3dB Frequency in Bode Plot.

