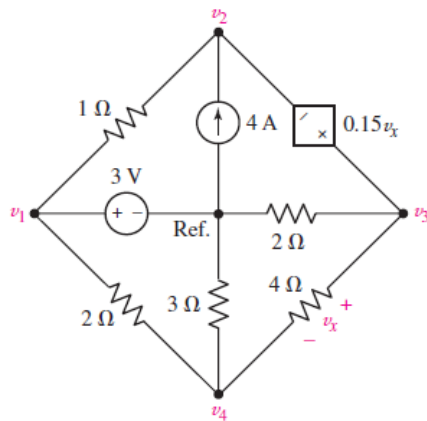



# NESS TUTORIAL

## CHAPTER 4 AND 5

- 1) Find nodal voltages assuming ref voltage is 0



- 2)

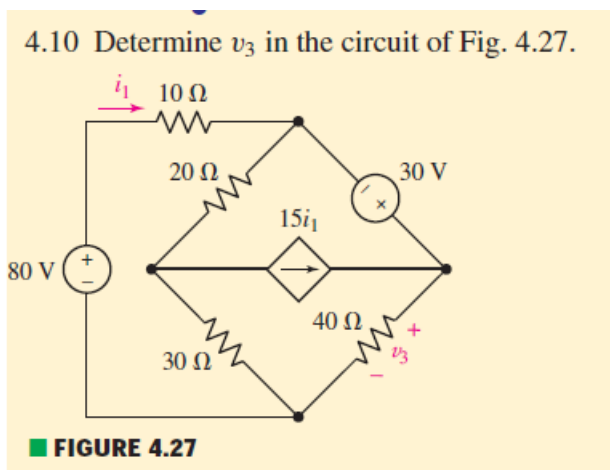

- 3) Use superposition principle to find voltage across each current source

