

---

# Analog Electronic Circuits (EC2.103) : Assignment-5

Spring 2024, IIIT Hyderabad, Due date : Fri 29 Mar, 2024 (18:00 hrs)

Instructor: Prof. Abhishek Srivastava, CVEST, IIIT Hyderabad

---

## Instructions:

1. Submit your assignment as a single pdf (Name\_RollNo.pdf) at moodle on or before the due date
  2. Hand-written/typed (latex/word/notion/others) submissions are allowed
  3. Report should be self explanatory and must carry complete solution - Answers with schematics, SPICE directives, annotated waveforms, inference/discussion on results
  4. Use the given technology file TSMC\_180nm.txt for simulations
  5. Specify MOSFET parameters W, L, AS, AD, PS, PD for all simulations
- 

1. As shown in Fig. 1, plot  $I_D$  vs  $V_{DS}$  for an NMOS transistor having  $\frac{W}{L} = \frac{1.8\mu}{0.18\mu}$  by sweeping  $V_{DS}$  from 0 to 1.8 V in a step of 0.01 V and sweeping  $V_{GS}$  0 to 1.8 V in a step of 0.3 V. Assume  $V_{BS} = 0$  V.

**(Hint:** Use NMOS4 from library, edit and change model name to CMOSN, enter W, L, drain/source area (AD/AS), drain/source perimeter (PD/PS) as follows:  $AS = \{5 * width\_N * LAMBDA\}$ ,  $PS = \{10 * LAMBDA + 2 * width\_N\}$ ,  $AD = \{5 * width\_N * LAMBDA\}$ ,  $PD = \{10 * LAMBDA + 2 * width\_N\}$ , where  $\{width\_N\} = W$ , &  $\{2 * LAMBDA\} = L$ . Use “.include TSMC\_180nm.txt” in the spice directive.)

 


Figure 1

2. Plot  $I_D$  vs  $V_{GS}$  for  $\frac{1.8\mu}{0.18\mu}$  NMOS transistor for  $V_{DS} = 50$  mV and  $V_{BS} = 0$  V.
  - (a) Estimate the technology parameter  $\mu C_{ox}$  and  $V_T$  from the graph for  $V_{DS} = 50$  mV.
  - (b) Plot  $I_D$  vs  $V_{GS}$  for  $V_{DS} = 1.8$  V and extract  $V_T$  from the graph. Compare the obtained  $V_T$  with  $V_{DS} = 50$  mV case. Do you observe any difference in  $V_T$  values for the two cases? If yes, explain why. (Hint :DIBL)
3. From the simple MOS models discussed in class, find out  $V_T$  for NMOS and PMOS devices ( $\frac{W}{L} = \frac{1.8\mu m}{0.18\mu m}$ ) with the help of  $I_D$  vs  $V_{GS}$  simulations for i) Body to source voltage ( $V_{BS}$ ) of 0 V, ii)  $V_{BS} = 900$  mV and ii)  $V_{BS} = -900$  mV. Overlay the three graphs. Do you observe any difference in  $V_T$  for the three cases? Briefly discuss.  
(Hint : $I_D$  vs  $V_{GS}$  simulation with  $V_{BS}$  list, body effect. For PMOS based simulations, use PMOS4 component and use model name : CMOSF, define AS/AD/PS/PD.)

4. Fig. 2 depicts a diode connected NMOS. Sweep  $I_D$  from  $10 \mu\text{A}$  to  $1 \text{ mA}$  in steps of  $1 \mu\text{A}$  and plot  $g_m$  vs  $I_D$  curve using  $g_m = 2I_D/(V_{GS} - V_T)$  for  $\frac{W}{L} = \frac{1\mu\text{m}}{0.18\mu\text{m}}$ . Report maximum  $g_{m_{max}}$ . How can you achieve  $4 \times g_{m_{max}}$ , show the circuit modification and simulation results. (Hint : Run DC, use  $V_T$  extracted from previous question)

 


Figure 2

5. (a) Consider the CS amplifier shown in Fig. 3. It is given that  $\frac{W}{L} = \frac{1\mu\text{m}}{0.18\mu\text{m}}$ ,  $V_{DD} = 500 \text{ mV}$  and  $R_L = 1 \text{ k}\Omega$ . Sweep  $V_{GS}$  from  $V_T$  (calculated earlier) to  $V_{DD}$  in step size of  $0.01 \text{ V}$  and plot  $g_m$  vs  $V_{GS}$  curve using  $g_m = 2I_D/(V_{GS} - V_T)$ . Clearly mark region of MOSFET operations on the curve. What is the maximum value of  $g_{m_{max}}$  and corresponding  $V_{GS}$  value.
- (b) Plot  $g_m$  vs  $V_{GS}$  for  $\frac{W}{L} = \frac{4\mu\text{m}}{0.18\mu\text{m}}$ . As compared to the previous case, which amplifier parameters (gain, swing, bandwidth) gets affected? Briefly discuss the trade-offs.

 


Figure 3

6. Design a common source amplifier (shown in Fig. 4) with a resistive load of  $10 \text{ k}\Omega$  for a voltage gain  $> 5$  and an overdrive voltage (of input transistor) of  $200 \text{ mV}$ . The minimum input signal frequency is  $100 \text{ Hz}$ . Design for the minimum power consumption. Clearly write your assumptions (if any).

 


Figure 4

- (a) Show the design procedure with calculations for sizes of transistors,  $I_{REF}$ ,  $C_b$  and  $R_b$ . What is the overall power consumed by your amplifier.
- (b) Give the transient (4-5 cycles) simulations plots showing the gain and considering  $v_{in} = 10\sin(2\pi(1000)t) \text{ mV}$ .

- (c) Show the AC response plots ( $20\log|A_v|$  vs frequency) and find unity bandwidth frequency ( $f_u$ ). Vary the frequency from 1 Hz to 1 GHz for AC simulations.
- (d) **Bonus problem: (Not mandatory to submit)** Replace the load resistor with a PMOS current source load as shown in Fig. 5 and redesign the circuit for a voltage gain  $> 15$ . Show the design procedure, transient and AC response of this amplifier also.

 


Figure 5

7. **Suggested practice problems: Single stage amplifiers (Razavi).** (No need to submit it.)

---