


Lecture 22 – Registers and Counters 2

Dr. Aftab M. Hussain,
Assistant Professor, PATRIOT Lab, CVEST

Chapter 6

Serial transfer


- The datapath of a digital system is said to operate in serial mode when information is transferred and manipulated one bit at a time
- Information is transferred one bit at a time by shifting the bits out of the source register and into the destination register
- This type of transfer is in contrast to parallel transfer, whereby all the bits of the register are transferred at the same time
- The serial transfer of information from register *A* to register *B* is done with shift registers, as shown
- The serial output (*SO*) of register *A* is connected to the serial input (*SI*) of register *B*

 

 (a) Block diagram

Serial transfer


- To prevent the loss of information stored in the source register, the information in register *A* is made to circulate by connecting the serial output to its serial input
- The initial content of register *B* is shifted out through its serial output and is lost unless it is transferred to a third shift register
- The shift control input determines when and how many times the registers are shifted
- For simplicity here, this is done with an AND gate that allows clock pulses to pass into the *CLK* terminals only when the shift control is active



 (a) Block diagram

Serial transfer


- Assume that the binary content of A before the shift is 1011 and that of B is 0010
- The serial transfer from A to B occurs in four steps
- With the first pulse, T_1 , the rightmost bit of A is shifted into the leftmost bit of B and is also circulated into the leftmost position of A
- At the same time, all bits of A and B are shifted one position to the right



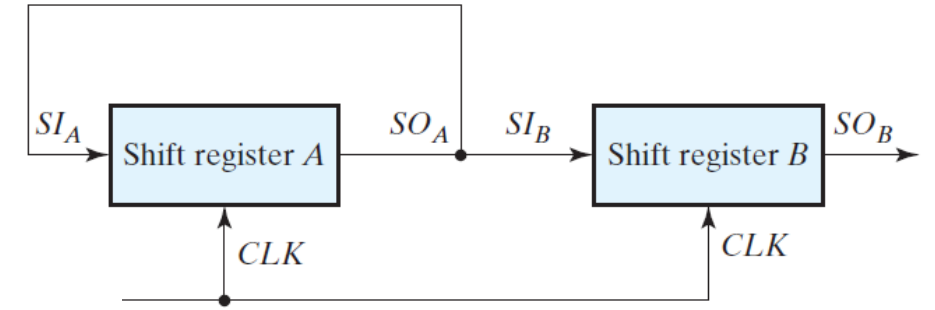(a) Block diagram

Serial transfer

- The previous serial output from B in the rightmost position is lost, and its value changes from 0 to 1
- The next three pulses perform identical operations, shifting the bits of A into B , one at a time
- After the fourth shift, the shift control goes to 0, and registers A and B both have the value 1011
- Thus, the contents of A are copied into B , so that the contents of A remain unchanged i.e., the contents of A are restored to their original value




(a) Block diagram

Timing Pulse	Shift Register A				Shift Register B			
Initial value	1	0	1	1	0	0	1	0
After T_1	1	1	0	1	1	0	0	1
After T_2	1	1	1	0	1	1	0	0
After T_3	0	1	1	1	0	1	1	0
After T_4	1	0	1	1	1	0	1	1


Serial addition

- Can we design a serial addition circuit? The two binary numbers to be added serially are stored in two shift registers
- This is similar to the algorithm we use for adding manually
- Beginning with the least significant pair of bits, the circuit adds one pair at a time through a single full-adder (FA) circuit
- The carry out of the full adder is transferred to a D flip-flop, the output of which is then used as the carry input for the next pair of significant bits
- The sum bit from the S output of the full adder could be transferred into a third shift register
- By shifting the sum into A while the bits of A are shifted out, it is possible to use one register for storing both the augend and the sum bits
- The serial input of register B can be used to transfer a new binary number while the addend bits are shifted out during the addition

 

Serial addition

- Comparing the serial adder with the parallel adder (4-bit adder), we note several differences
- The parallel adder uses registers with a parallel load, whereas the serial adder uses shift registers
- The number of full-adder circuits in the parallel adder is equal to the number of bits in the binary numbers, whereas the serial adder requires only one full-adder circuit and a carry flip-flop
- Excluding the registers, the parallel adder is a combinational circuit, whereas the serial adder is a sequential circuit which consists of a full adder and a flip-flop that stores the output carry

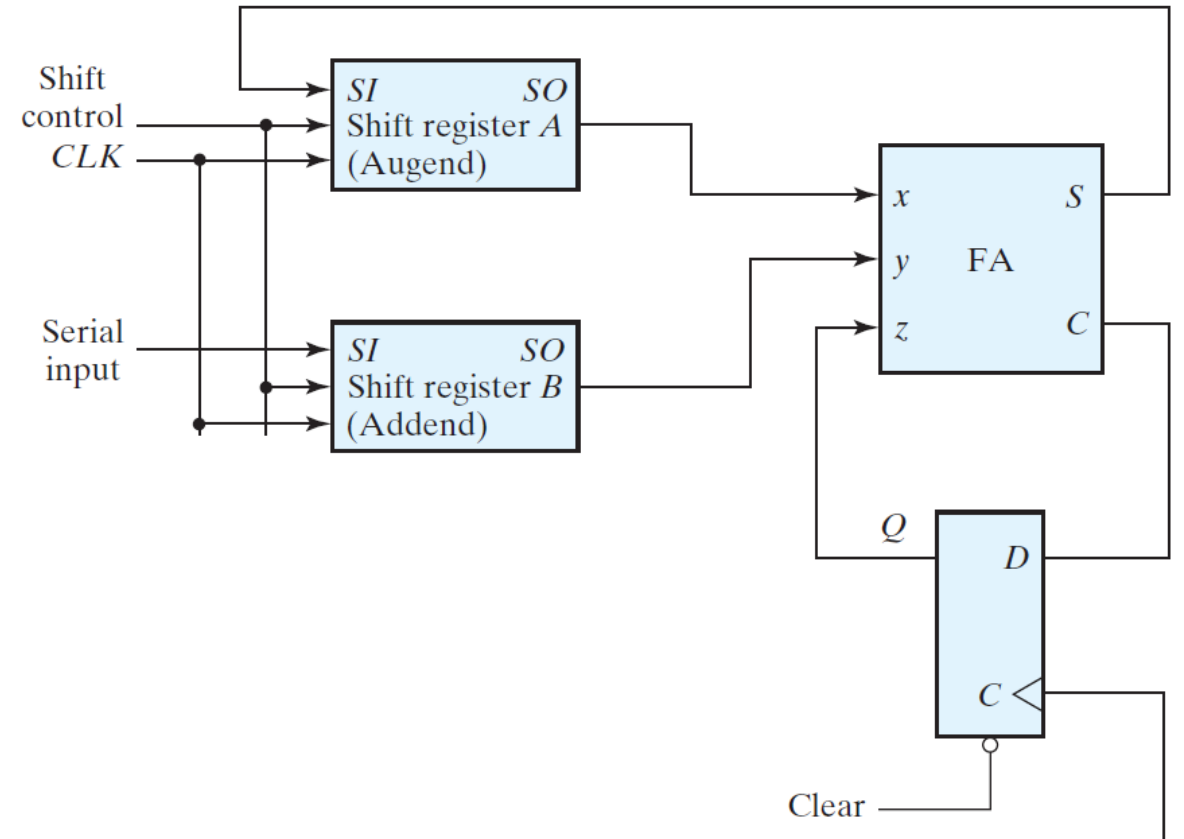


Universal register

- If the flip-flop outputs of a shift register are accessible, then information entered serially by shifting can be taken out in parallel from the outputs of the flip-flops
- If a parallel load capability is added to a shift register, then data entered in parallel can be taken out in serial fashion by shifting the data stored in the register
- Some shift registers provide the necessary input and output terminals for parallel transfer
- They may also have both shift-right and shift-left capabilities

Universal register

- The most general shift register has the following capabilities:
 1. A *clear* control to clear the register to 0
 2. A *clock* input to synchronize the operations
 3. A *shift-right* control to enable the shift-right operation and the *serial input* and *output* lines associated with the shift right
 4. A *shift-left* control to enable the shift-left operation and the *serial input* and *output* lines associated with the shift left
 5. A *parallel-load* control to enable a parallel transfer and the n input lines associated with the parallel transfer
 6. n parallel output lines
 7. A control state that leaves the information in the register unchanged in response to the clock


Universal register

 

Mode Control		
s_1	s_0	Register Operation
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load


Universal register

 - The circuit consists of four D flip-flops and four multiplexers
- The four multiplexers have two common selection inputs s_1 and s_0
- The selection inputs control the mode of operation of the register according to the function required
- The output of the MUXes are applied to the inputs of the FFs which controls the next state of the FF



Universal register

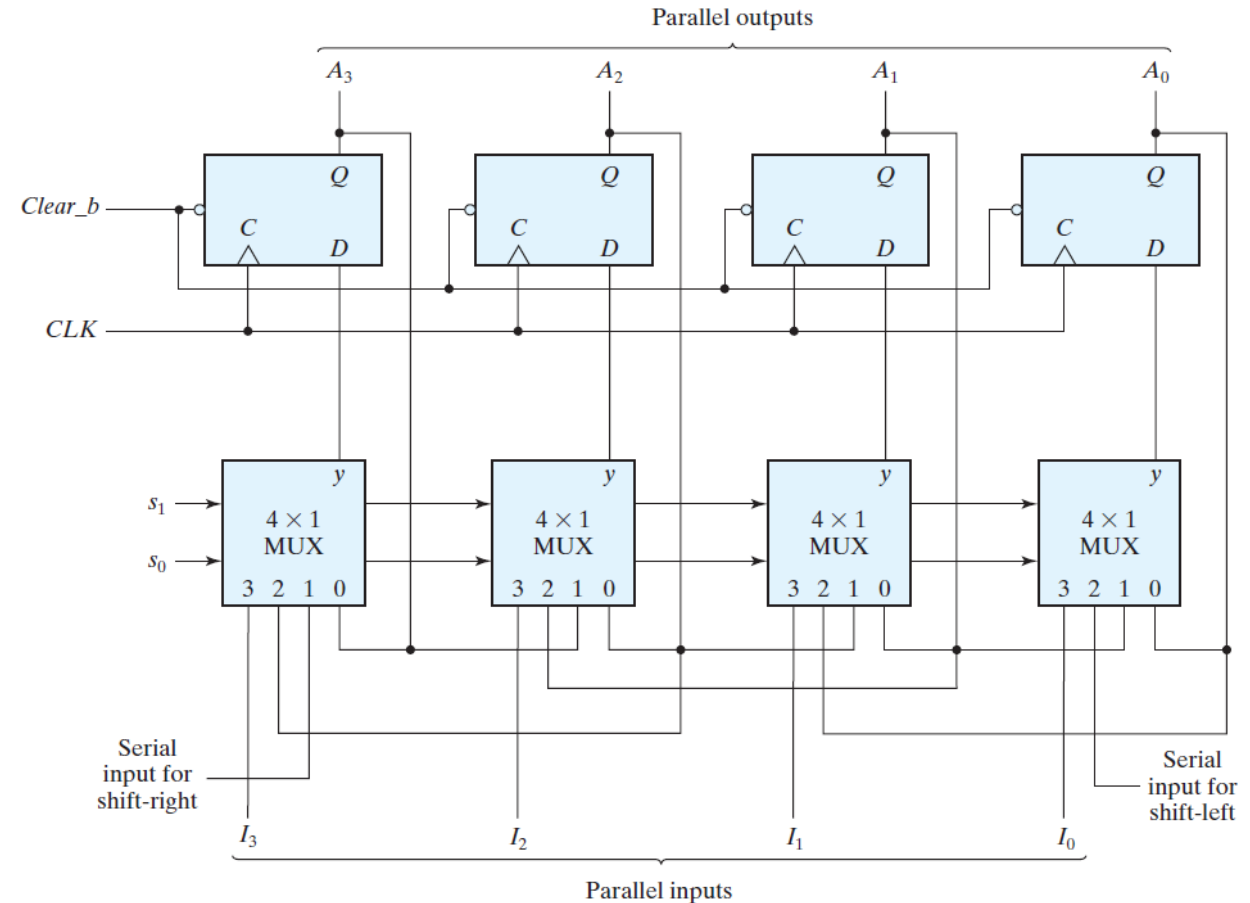- When $s_1s_0 = 00$, the present value of the register is applied to the D inputs of the flip-flops
- This condition forms a path from the output of each flip-flop into the input of the same flip-flop, so that the output recirculates to the input in this mode of operation
- The next clock edge transfers into each flip-flop the binary value it held previously, and no change of state occurs



Universal register

- When $s_1s_0 = 01$, terminal 1 of the multiplexer inputs has a path to the D inputs of the flip-flops
- This causes a shift-right operation, with the serial input transferred into flip-flop A_3
- When $s_1s_0 = 10$, a shift-left operation results, with the other serial input going into flip-flop A_0
- Finally, when $s_1s_0 = 11$, the binary information on the parallel input lines is transferred into the register simultaneously during the next clock edge

