
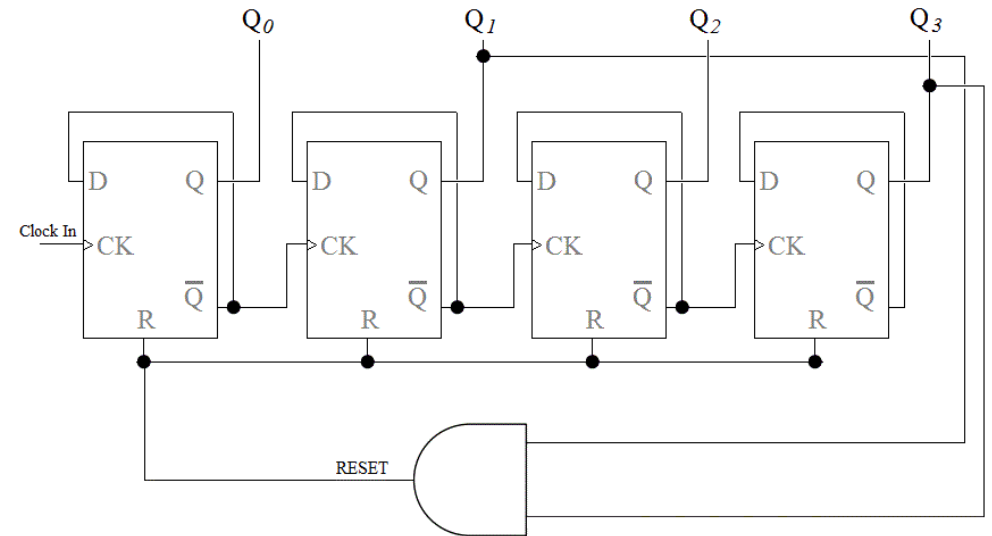


# Lecture 22 – Registers and Counters 3

## Chapter 6

 
# Ripple counter - BCD

- A decimal counter follows a sequence of 10 states and returns to 0 after the count of 9
- Such a counter must have at least four flip-flops to represent each decimal digit, since a decimal digit is represented by a binary code with at least four bits
- The sequence of states in a decimal counter is dictated by the binary code used to represent a decimal digit
- A decimal counter is similar to a binary counter, except that the state after 1001 (the code for decimal digit 9) is 0000 (the code for decimal digit 0)


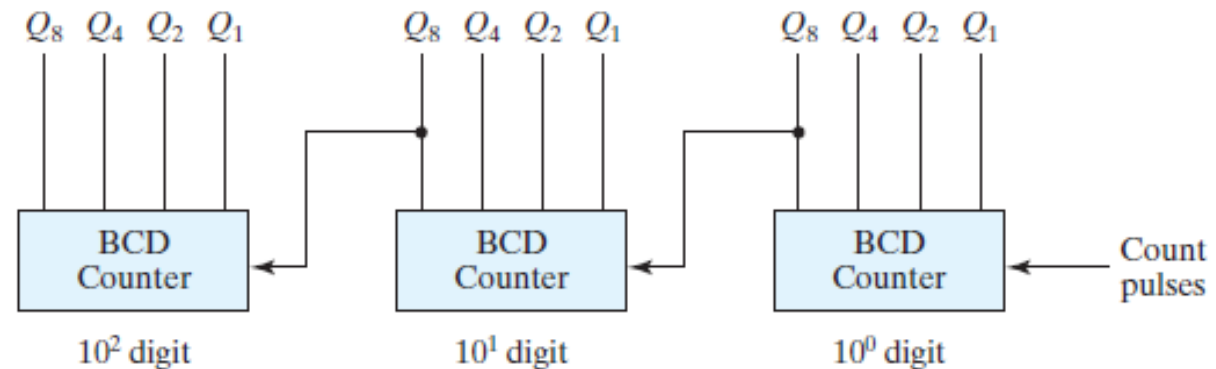
# Ripple counter - BCD

- A **decade counter** counts from 0 to 9
- To count in decimal from 0 to 99, we need a two-decade counter
- To count from 0 to 999, we need a three-decade counter
- Multiple decade counters can be constructed by connecting BCD counters in cascade, one for each decade
- The inputs to the second and third decades come from  $Q_8$  of the previous decade
- When  $Q_8$  in one decade goes from 1 to 0, it triggers the count for the next higher order decade while its own decade goes from 9 to 0





# Synchronous counter - binary

- Synchronous counters are different from ripple counters in that clock pulses are applied to the inputs of all flip-flops
- A common clock triggers all flip-flops simultaneously, rather than one at a time in succession as in a ripple counter
- The decision whether a flip-flop is to be complemented is determined from the values of the data inputs, such as  $T$  or  $J$  and  $K$  at the time of the clock edge
- If  $T = 0$  or  $J = K = 0$ , the flip-flop does not change state. If  $T = 1$  or  $J = K = 1$ , the flip-flop complements



# Synchronous counter - binary

## 2-bit synchronous binary counter

  

# Synchronous counter - binary

## 3-bit synchronous binary counter

 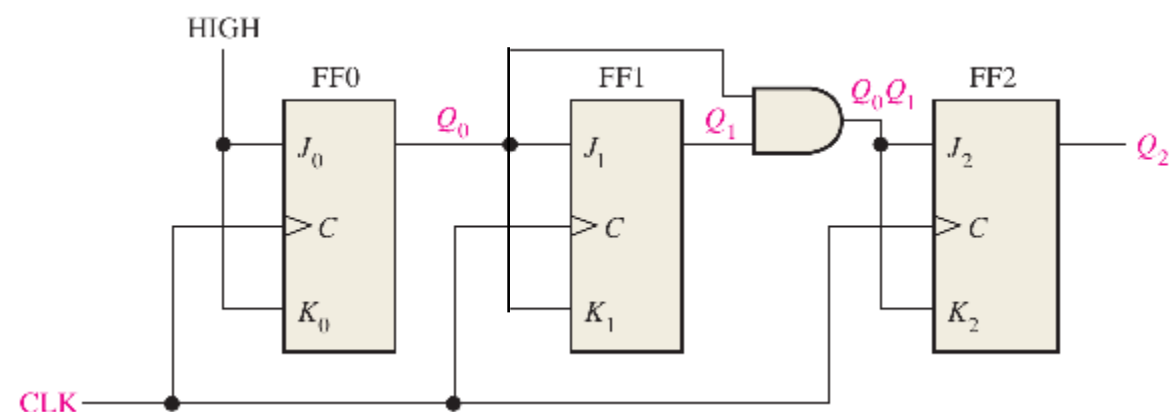


Clock Pulse	$Q_2$	$Q_1$	$Q_0$
Initially	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8 (recycles)	0	0	0

# Synchronous counter - binary

- The design of a synchronous binary counter is very simple
- In a synchronous binary counter, the flip-flop in the least significant position is complemented with every pulse
- *A flip-flop in any other position is complemented when all the bits in the lower significant positions are equal to 1*
- For example, if the present state of a four-bit counter is  $A_3A_2A_1A_0 = 0011$ , the next count is 0100
- $A_0$  is always complemented
- $A_1$  is complemented because the present state of  $A_0 = 1$
- $A_2$  is complemented because the present state of  $A_1A_0 = 11$
- However,  $A_3$  is not complemented, because the present state of  $A_2A_1A_0 = 011$ , which does not give an all-1's condition
 
# Synchronous counter - binary


- Synchronous binary counters have a regular pattern and can be constructed with complementing flip-flops and gates
- The regular pattern can be seen from the four-bit counter
- The  $C$  inputs of all flip-flops are connected to a common clock
- The counter is enabled by *Count\_enable*
- If the enable input is 0, all  $J$  and  $K$  inputs are equal to 0 and the clock does not change the state of the counter
- The first stage,  $A_0$ , has its  $J$  and  $K$  equal to 1 if the counter is enabled
- The other  $J$  and  $K$  inputs are equal to 1 if all previous least significant stages are equal to 1 and the count is enabled




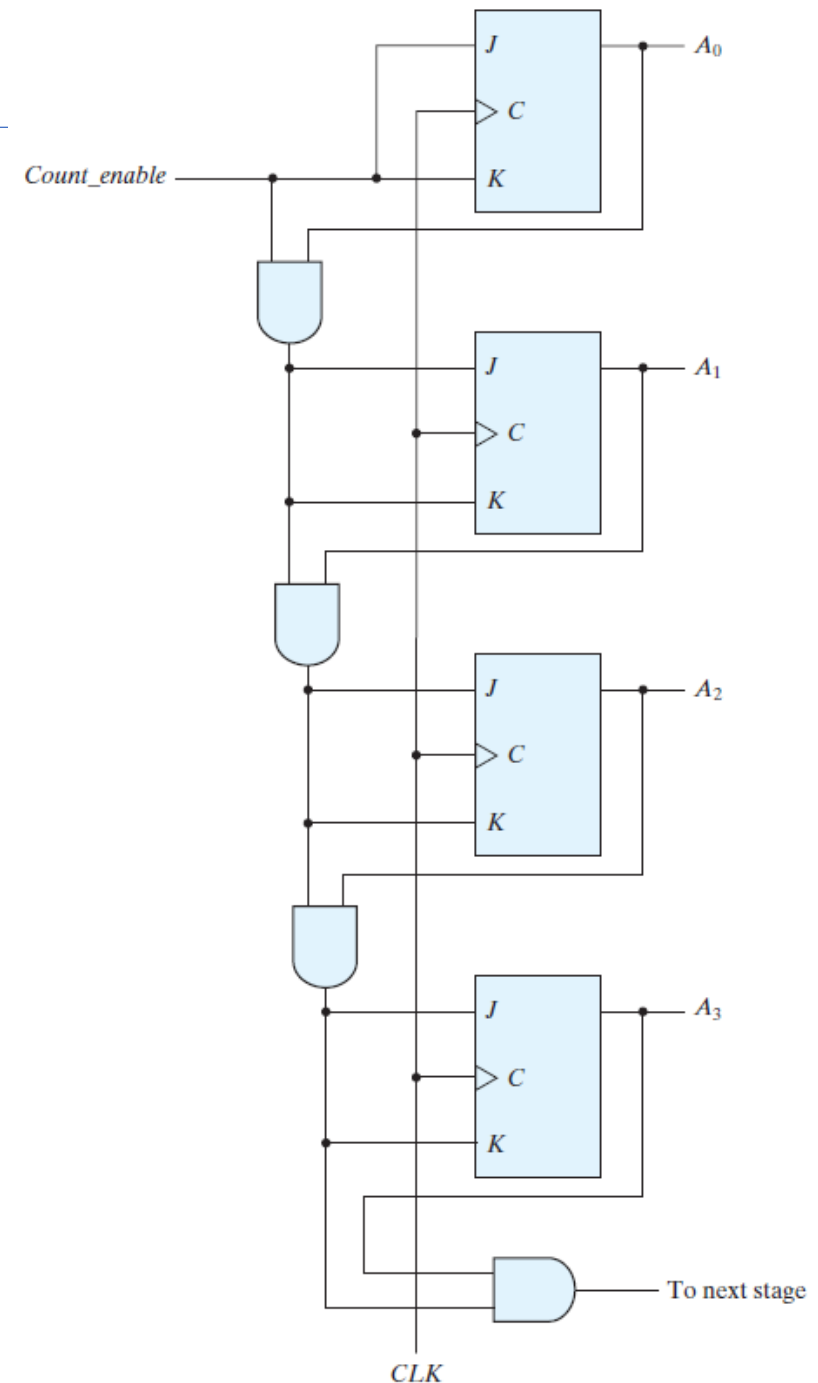
# Synchronous counter - binary

- Note that the flip-flops trigger on the positive edge of the clock
- The synchronous counter can be triggered with either the positive or the negative clock edge
- The complementing flip-flops in a binary counter can be of either the *JK* type, the *T* type, or the *D* type with XOR gates



# Synchronous counter – down counter

- A synchronous countdown binary counter goes through the binary states in reverse order, from 1111 down to 0000 and back to 1111 to repeat the count
- It is possible to design a countdown counter in the usual manner, but the result is predictable by inspection of the downward binary count
- The bit in the least significant position is complemented with each pulse
- *A bit in any other position is complemented if all lower significant bits are equal to 0*
- For example, the next state after the present state of 0100 is 0011
- The second significant bit is complemented because the first bit was 0
- The third significant bit is complemented because the first two bits were equal to 0
- But the fourth bit does not change, because not all lower significant bits are equal to 0
- A countdown binary counter can be constructed as a regular counter, except that the inputs to the AND gates must come from the complemented outputs, instead of the normal outputs, of the previous flip-flops

# Synchronous counter – up/down counter

- Let us see if we can design a counter that counts up/down based on a control input
- The counter should count up if  $U=1$ ,  $D=0$ ; down if  $U=0$ ,  $D=1$ ; no change if  $U=D=0$ ; and up if  $U=D=1$
- We can cascade this logic to make the synchronous up/down counter

# Synchronous counter – up/down counter

- Let us see if we can design a counter that counts up/down based on an input
- The counter should count up if  $U=1$ ,  $D=0$ ; down if  $U=0$ ,  $D=1$ ; no change if  $U=D=0$ ; and up if  $U=D=1$
- We can cascade this logic to make the synchronous up/down counter

